



**KOLEJ YAYASAN PELAJARAN JOHOR
ONLINE FINAL EXAMINATION**

COURSE NAME : CIRCUIT ANALYZE
COURSE CODE : DKE 2093
SESSION : DECEMBER 2021
DURATION : 2 HOURS 30 MINUTES

**INSTRUCTION TO CANDIDATES/
ARAHAN KEPADA CALON**

1. This examination paper consists of **SIX (6)** questions. /
Kertas soalan ini mengandungi ENAM (6) soalan.
2. Students are allowed to refer to resources such as lecture notes, books, internet or any other relevant resources. /
Pelajar dibenarkan merujuk kepada sumber seperti nota kuliah, buku, internet atau mana-mana sumber yang berkaitan.
3. Answer **ALL** questions in the answer sheet which is **A4** size paper (or other paper with the consent of the relevant lecturer). /
Jawab SEMUA soalan di dalam kertas jawapan iaitu kertas bersaiz A4 (atau lain-lain kertas dengan persetujuan pensyarah berkaitan).
4. Write your details as follows in the upper left conner for each answer sheet: /
Tulis butiran anda sepertimana berikut di penjuru atas kiri bagi setiap kertas jawapan:
 - i. Student Full Name / Nama Penuh Pelajar
 - ii. Identification Card (I/C) No. / No. Kad Pengenalan
 - iii. Class Section / Seksyen Kelas
 - iv. Course Code / Kod Kursus
 - v. Course Name / Nama Kursus
 - vi. Lecturer Name / Nama Pensyarah
5. Each answer sheet must have a page number written at the bottom right corner. /
Setiap helai kertas jawapan mesti ditulis nombor muka surat di penjuru bawah kanan.
6. Answers should be **neat and clear in handwritten form**. /
Jawapan hendaklah ditulis tangan, kemas dan jelas.

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIBERITAHU**

This examination paper consists of **10** printed pages including front page
Kertas soalan ini mengandungi 10 halaman bercetak termasuk muka hadapan

This examination paper consists of **SIX (6)** questions. Answer **ALL** the questions in an Answering Booklet.

*Kertas soalan ini mengandungi **ENAM (6)** soalan. Jawab **SEMUA** soalan dalam Buku Jawapan.*

QUESTION 1/ SOALAN 1

Referring to **Figure 1**. Find:

a) the value of inductor, L_1 if the equivalent inductance, L_{eq} at terminal A-B is 20mH.

(5 marks / markah)

b) the total voltage, V_T .

(2 marks / markah)

c) the total energy stored in circuit, w_T .

(2 marks / markah)

d) the voltage across inductors L_2 and L_3 .

(6 marks / markah)

Merujuk kepada **Rajah 1**. Dapatkan:

a) nilai paruh, L_1 jika kearuhan setara, L_{eq} pada terminal A-B adalah 20mH.

b) jumlah voltan, V_T .

c) jumlah tenaga yang disimpan dalam litar, w_T .

d) voltan merintang paruh L_2 dan L_3 .

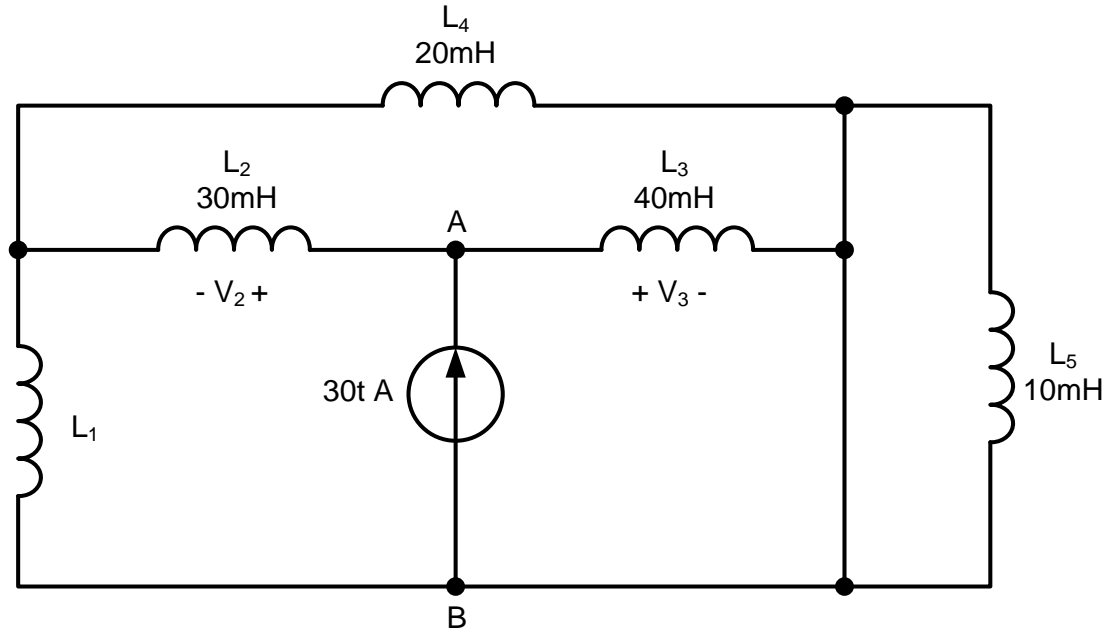


Figure 1/ *Rajah 1*

QUESTION 2/ SOALAN 2

Assume that the circuit in **Figure 2** is in its steady state condition at $t < 0$. Find $i(t)$ for $t > 0$ using transient analysis method.

(20 marks / markah)

Anggapkan bahawa litar dalam **Rajah 2** telah berada dalam keadaan mantap pada $t < 0$. Dapatkan $i(t)$ untuk $t > 0$ dengan menggunakan analisis ubahnika.

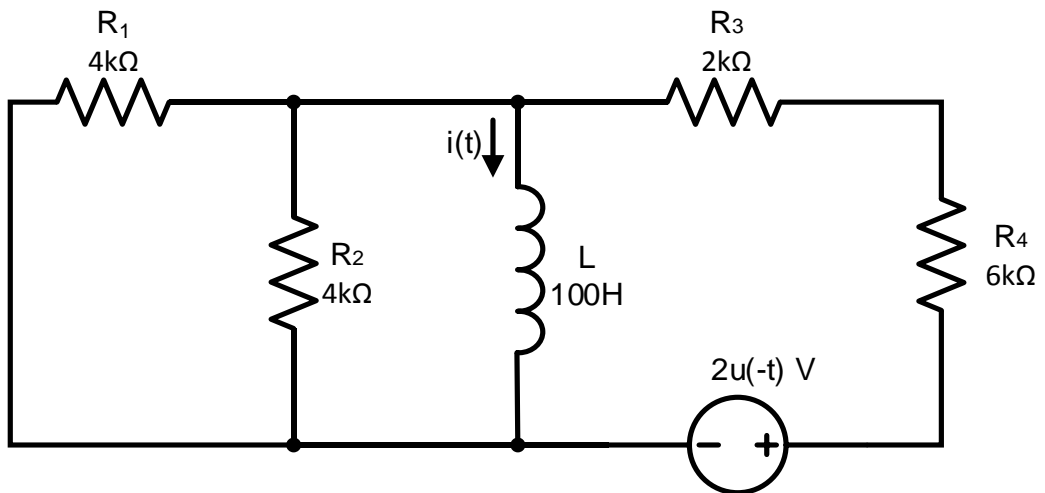


Figure 2/ *Rajah 2*

QUESTION 3/ SOALAN 3

The circuit in **Figure 3** has reached steady state at $t = 0^-$. Find $i(t)$ for $t \geq 0$ using transient analysis method.

(20 marks / markah)

Litar dalam **Rajah 3** telah mencapai keadaan mantap pada $t = 0^-$. Dapatkan $i(t)$ untuk $t \geq 0$ menggunakan kaedah analisis ubahtika.

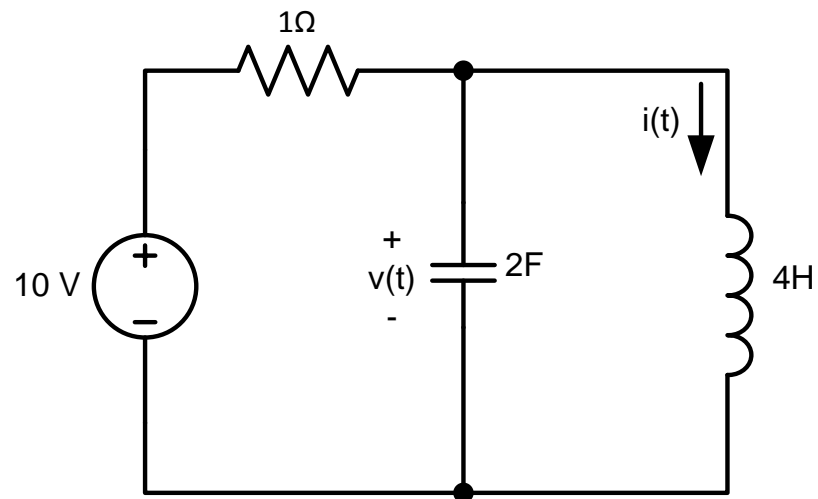


Figure 3/ Rajah 3

QUESTION 4/ SOALAN 4

The circuit in **Figure 4** is in steady state at $t < 0$. Find the Laplace function of the voltage across inductor, $V_o(s)$ for $t \geq 0$ using Laplace analysis method.

(15 marks / markah)

Litar dalam **Rajah 4** berada dalam keadaan mantap pada $t < 0$. Dapatkan fungsi Laplace bagi voltan merintang pearuh, $V_o(s)$ untuk $t \geq 0$ menggunakan kaedah analisis Laplace.

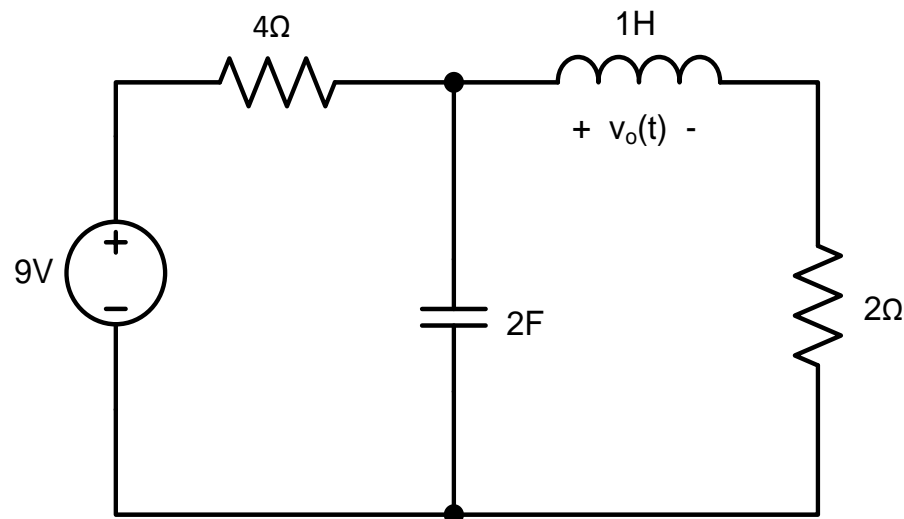


Figure 4/ Rajah 4

QUESTION 5/ SOALAN 5

Draw the magnitude Bode Plot for the following transfer function:

$$H(s) = \frac{2783s^2(s + 10000)}{(s^2 + 4.2s + 900)(s + 700)^2}$$

Use minimum frequency, $\omega = 1$ rad/s and maximum frequency,
 $\omega = 100,000$ rad/s.

(15 marks / markah)

Lukiskan magnitud Rajah Bode untuk rangkap pindah berikut:

$$H(s) = \frac{2783s^2(s + 10000)}{(s^2 + 4.2s + 900)(s + 700)^2}$$

Guna frekuensi minima, $\omega = 1$ rad/s dan frekuensi maksima, $\omega = 100,000$ rad/s.

QUESTION 6/ SOALAN 6

The two-port network is terminated as shown in **Figure Q6**. Find the output voltage, V_2 and the output current, I_2 .

$$z = \begin{pmatrix} s+2 & \frac{1}{s} \\ -2 & 2+\frac{1}{s} \end{pmatrix}$$

(15 marks / markah)

Rangkaian dua-liang ditamatkan seperti ditunjukkan dalam **Rajah Q6**. Dapatkan voltan keluaran, V_2 dan arus keluaran, I_2 .

$$z = \begin{pmatrix} s+2 & \frac{1}{s} \\ -2 & 2+\frac{1}{s} \end{pmatrix}$$

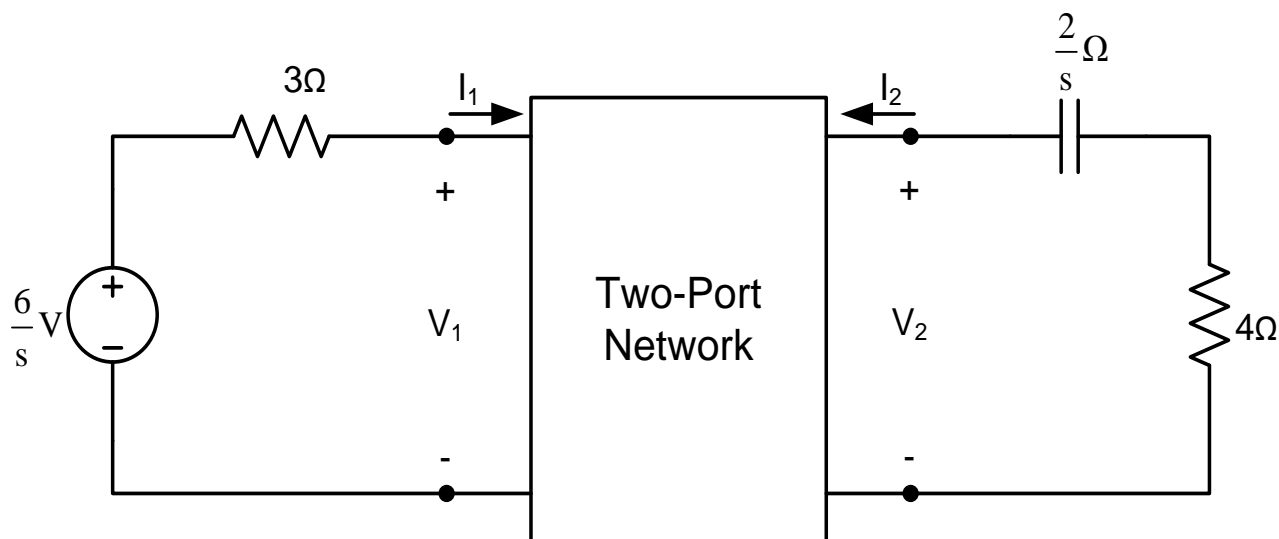


Figure Q6/ Rajah Q6

[100 MARKS/ 100 MARKAH]

END OF QUESTION PAPER/ KERTAS SOALAN TAMAT

Forcing Functions and Their Assumed Solutions
(Fungsi Berdaya dan Penyelesaian Anggapan)

Forcing function (Fungsi Berdaya)		Assumed Solution (Penyelesaian Anggapan)
Constan (Malar)		$f(t) = A$ $x_f(t) = K_2$
Exponential (Eksponen)		$f(t) = M e^{-st}$ $x_f(t) = K_2 e^{-st}$
Variable (Pembolehubah)	Ramp (Tanjak)	$f(t) = mt$ $x_f(t) = K_2 t + K_3$
	Parabolic (Parabola)	$f(t) = t^2$ $x_f(t) = K_2 t^2 + K_3 t + K_4$
Sinusoidal (Sinus)		$f(t) = M \sin(\omega t + \theta)$ $f(t) = M \cos(\omega t + \theta)$ $x_f(t) = K_2 \sin \omega t + K_3 \cos \omega t$
Exponential Sinusoidal (Sinus Eksponen)		$f(t) = M e^{-st} \sin(\omega t + \theta)$ $x_f(t) = e^{-st} (K_2 \sin \omega t + K_3 \cos \omega t)$

Table of Laplace Transform Pairs
(Jadual Penukaran Pasangan Penjelmaan Laplace)

Functions (<i>Fungsi</i>)	$f(t)$	$F(s)$
Unit Impulse (<i>Dedenyut</i>)	$\delta(t)$	1
Unit Step (<i>Unit langkah</i>) Constant (<i>Malar</i>)	$u(t)$ 1	$\frac{1}{s}$
Unit Ramp (<i>Unit Tanjak</i>) t function (<i>Rangkap t</i>)	$t u(t)$	$\frac{1}{s^2}$
Unit Parabolic (<i>Unit Parabola</i>)	$\frac{1}{2} t^2 u(t)$	$\frac{1}{s^3}$
n^{th} integral of impulse (<i>Kamiran ke-n dedenyut</i>)	$\delta^{-n}(t)$	$\frac{1}{s^n}$
n^{th} derivative of impulse (<i>Kerbezaan ke-n dedenyut</i>)	$\delta^n(t)$	s^n
Power of t (<i>Kuasa t</i>)	$\frac{t^{n-1}}{(n-1)!}$	$\frac{1}{s^n}$
Exponential (<i>Eksponen</i>)	e^{-at}	$\frac{1}{s+a}$
t -multiplication exponential (<i>Pendaraban t bagi eksponen</i>)	te^{-at}	$\frac{1}{(s+a)^2}$
Repeated t -multiplication exponential (<i>Pendaraban t berulang bagi eksponen</i>)	$\frac{1}{(n-1)!} t^{n-1} e^{-at}$	$\frac{1}{(s+a)^n}$
Sine (<i>Sinus</i>)	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
Cosine (<i>Kosinus</i>)	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
Damped sine (<i>Sinus teredam</i>)	$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
Damped cosine (<i>Kosinus teredam</i>)	$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$
t -multiplied sine (<i>Pendaraban t bagi sinus</i>)	$t \sin \omega t$	$\frac{2\omega s}{(s^2 + \omega^2)^2}$
t -multiplied cosine (<i>Pendaraban t bagi kosinus</i>)	$t \cos \omega t$	$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$

Two-Port Network Parameters
(Parameter Rangkaian Dua Liang)

Impedance parameters

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

Admittance parameters

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

Hybrid parameters

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

Transmission parameters

$$V_1 = A V_2 - B I_2$$

$$I_1 = C V_2 - D I_2$$

Jadual Penukaran Untuk Rangkaian Dua Liang
(Conversion Table for Two-Port Network Parameters)

	z		y		h		ABCD	
z	z_{11}	z_{12}	$\frac{y_{22}}{\Delta_y}$	$-\frac{y_{12}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$	$\frac{A}{C}$	$\frac{\Delta_T}{C}$
	z_{21}	z_{22}	$-\frac{y_{21}}{\Delta_y}$	$\frac{y_{11}}{\Delta_y}$	$-\frac{h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$	$\frac{1}{C}$	$\frac{D}{C}$
y	$\frac{z_{22}}{\Delta_z}$	$-\frac{z_{12}}{\Delta_z}$	y_{11}	y_{12}	$\frac{1}{h_{11}}$	$-\frac{h_{12}}{h_{11}}$	$\frac{D}{B}$	$-\frac{\Delta_T}{B}$
	$-\frac{z_{21}}{\Delta_z}$	$\frac{z_{11}}{\Delta_z}$	y_{21}	y_{22}	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$	$-\frac{1}{B}$	$\frac{A}{B}$
h	$\frac{\Delta_z}{z_{22}}$	$\frac{z_{12}}{z_{22}}$	$\frac{1}{y_{11}}$	$-\frac{y_{12}}{y_{11}}$	h_{11}	h_{12}	$\frac{B}{D}$	$\frac{\Delta_T}{D}$
	$-\frac{z_{21}}{z_{22}}$	$\frac{1}{z_{22}}$	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta_y}{y_{11}}$	h_{21}	h_{22}	$-\frac{1}{D}$	$\frac{C}{D}$
ABCD	$\frac{z_{11}}{z_{21}}$	$\frac{\Delta_z}{z_{21}}$	$-\frac{y_{22}}{y_{21}}$	$-\frac{1}{y_{21}}$	$-\frac{\Delta_h}{h_{21}}$	$-\frac{h_{11}}{h_{21}}$	A	B
	$\frac{1}{z_{21}}$	$\frac{z_{22}}{z_{21}}$	$-\frac{\Delta_y}{y_{21}}$	$-\frac{y_{11}}{y_{21}}$	$-\frac{h_{22}}{h_{21}}$	$-\frac{1}{h_{21}}$	C	D