



**KOLEJ YAYASAN PELAJARAN JOHOR
FINAL EXAMINATION**

COURSE NAME : POWER ELECTRONICS
COURSE CODE : DKE 3063
SESSION : NOVEMBER 2020
DURATION : 2 HOURS 30 MINUTES

**INSTRUCTION TO CANDIDATES /
ARAHAN KEPADA CALON**

1. This examination paper consists of **FIVE (5)** questions. Answer **ALL** questions. /
Kertas soalan ini mengandungi LIMA (5) soalan. Jawab SEMUA soalan.

2. Candidates are not allowed to bring any material/note to the examination hall/room except with the permission from the invigilator. The formula sheet is attached to the back of this question paper. /
Calon tidak dibenarkan untuk membawa sebarang bahan/nota ke dewan/bilik peperiksaan tanpa kebenaran daripada pengawas. Rumus dilampirkan dibelakang kertas soalan peperiksaan.

3. Please check to make sure that this examination pack consist of: /
Pastikan kertas soalan peperiksaan ini mengandungi:
 - i. The Question Paper /
Kertas Soalan
 - ii. An Answering Booklet /
Buku Jawapan
 - iii. Attachment 1 /
Lampiran 1

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIBERITAHU**

This examination paper consists of **9** printed pages including front page
Kertas soalan ini mengandungi 9 halaman bercetak termasuk muka hadapan

This paper contains of **FIVE (5)** questions. Answer **ALL** questions.

Answer the questions in an answering booklet.

*Kertas soalan ini mengandungi **LIMA (5)** soalan. Jawab **SEMUA** soalan.*

Sila jawab dalam buku jawapan.

QUESTION 1 / SOALAN 1

- a. Define power electronic.

Berikan definisi elektronik kuasa.

(2 marks/ 2 markah)

- b. State the function of rectifier circuit and give **two (2)** applications for the circuit.

*Nyatakan fungsi litar penerus dan berikan **dua (2)** aplikasi litar tersebut.*

(3 marks/ 3 markah)

- c. For half-wave rectifier with R-L load, $R=100\Omega$, $L=0.1H$, $\omega=377\text{rad/s}$, and $V_s=100V$. Determine:

- i. An expression for the current in this circuit.
- ii. The point where diode turns off.
- iii. The average current.
- iv. The rms current.
- v. The power absorbed by the R-L load.
- vi. The power factor.

Bagi penerus separuh gelombang dengan beban RL, $R = 100\Omega$, $L = 0.1H$, $\omega = 377\text{rad/s}$, dan $V_s = 100V$. Tentukan:

- i. Satu ungkapan untuk arus dalam litar ini.
- ii. Titik di mana diod dimatikan.
- iii. Arus purata semasa.
- iv. Arus pmkd semasa.
- v. Kuasa yang diserap oleh beban R-L.
- vi. Faktor kuasa

(15 marks/ 15 markah)

QUESTION 2 / SOALAN 2

- a. Give **two (2)** applications of controlled rectifier.

*Berikan **dua (2)** aplikasi bagi penerus terkawal.*

(2 marks/ 2 markah)

- b. Sketch and label the I-V characteristic curve for a SCR.

Lakar dan labelkan lengkung ciri I-V bagi SCR

(3 marks/ 3 markah)

- c. The full wave controlled bridge rectifier has an AC input of $120 V_{\text{rms}}$ at 60 Hz and a 20Ω load resistor. The delay angle is 40° . Draw the circuit diagram and sketch the output voltage waveform. Determine:

- i. Average and rms current in the load.
- ii. Power absorbed by load in watt.
- iii. Power source in volt-ampere.
- iv. Power factor.

Penerus terkawal titi gelombang penuh mempunyai masukan AU, $120 V_{pmkd}$ pada 60 Hz dan beban rintangan, 20Ω . Sudut lengah adalah 30° . Lukiskan gambar rajah litar dan lakarkan gelombang voltan keluaran. Tentukan:

- i. Arus purata dan pmkd beban.*
- ii. Kuasa diserap oleh beban dalam watt.*
- iii. Kuasa bekalan dalam volt-ampere.*
- iv. Faktor kuasa.*

(15 marks/ 15 markah)

QUESTION 3 / SOALAN 3

- a. Define the ac voltage controller.

Berikan definisi pengawal voltan au.

(2 marks/ 2 markah)

- b. List down **three (3)** applications of AC voltage controllers.

*Senaraikan **tiga (3)** aplikasi pengawal voltan AU.*

(3 marks/ 3 markah)

- c. Single phase AC voltage controller in **Figure Q3(c)** has a resistive load of $R = 10 \Omega$ and input voltage is $V_s = 120 V$, 60 Hz. The delay angle of thyristor T_1 is $\alpha = \pi/2$. Determine:

- i. $V_{o(rms)}$*
- ii. Input power factor*
- iii. Average input current.*

*Fasa pengawal AU voltan dalam **Rajah Q3(c)** mempunyai rintangan beban, $R = 10 \Omega$ dan voltan masukan adalah $V_s = 120 V$, 60 Hz. Sudut lengah thyristor T_1 adalah $\alpha = \pi/2$. Tentukan:*

- i. $V_o (pmkd)$*
- ii. Faktor kuasa masukan.*
- iii. Arus masukan purata.*

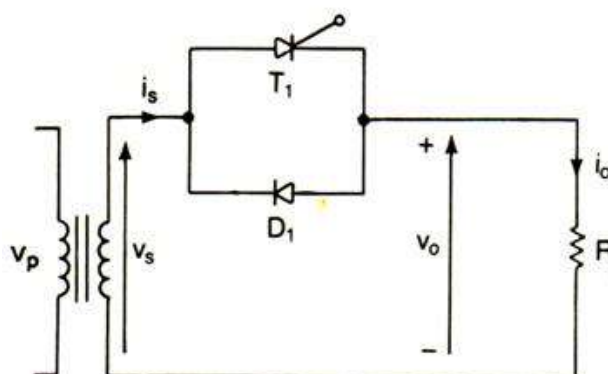


Figure Q3(c) / Rajah Q3(c)

(15 marks/ 15 markah)

QUESTION 4 / SOALAN 4

- a. State **two (2)** applications of DC chopper

*Nyatakan **dua (2)** aplikasi pemenggal AT.*

(2 marks/ 2 markah)

- b. List **three (3)** advantages of a DC chopper circuit.

*Senaraikan **tiga (3)** kelebihan litar pemenggal AT.*

(3 marks/ 3 markah)

- c. The Step-down DC Chopper in **Figure Q4(c)** has a resistive load, $R = 10 \Omega$ and input voltage, $V_s = 220 \text{ V}$. When the chopper switch (SW) remains ON, its voltage drop is $V_{ch} = 2 \text{ V}$ and chopping frequency is $f = 10 \text{ kHz}$. If the duty cycle is 50%, determine:

- i. The average output voltage, $V_{o\text{dc}}$.
- ii. The rms output voltage, $V_{o\text{rms}}$.
- iii. The chopper efficiency, η .

Sebuah pemenggal AT Langkah-turun seperti dalam **Rajah Q4(c)** berbeban perintang tulen, $R = 10 \Omega$ dan voltan masukan, $V_s = 220 \text{ V}$. Semasa suis pemenggal (SW) kekal TUTUP, voltan kejatuhannya, $V_{ch} = 2 \text{ V}$ dan frekuensi pemenggal $f = 10 \text{ kHz}$. Jika kitar kerja, adalah 80%, tentukan:

- Voltan keluaran purata, $V_{o\text{dc}}$.
- Voltan keluaran PMKD, $V_{o\text{rms}}$.
- Kecekapan pemenggal, η .

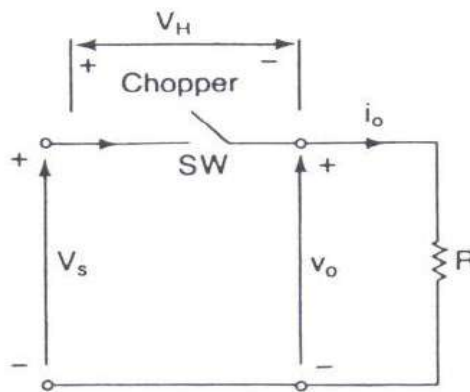


Figure Q4(c) / Rajah Q4(c)

(15 marks/ 15 markah)

QUESTION 5 / SOALAN 5

- a. Define an inverter.

Berikan definisi penyongsang.

(2 marks/ 2 markah)

- b. State **three (3)** applications of inverter in industrial application.

*Nyatakan **tiga (3)** aplikasi penyongsang dalam aplikasi industri.*

(3 marks/ 3 markah)

- c. Referring to **Figure Q5(c)**. Given $V_s = 220\text{ V}$ and $R = 10\ \Omega$, determine:
- The rms output voltage at the fundamental frequency, V_1 .
 - The output power, P_o .
 - The average current of each transistor, I_Q .
 - The rms current of each transistor, I_1 .
 - The peak current of each transistor, I_p .

Merujuk kepada **Rajah Q5(c)**. Diberi $V_s = 220\text{ V}$ and $R = 10\ \Omega$, tentukan

- Voltan keluaran pmkd pada frekuensi asas, V_1 .
- Kuasa keluaran, P_o .
- Arus purata bagi setiap transistor, I_Q .
- Arus pmkd bagi setiap transistor, I_1 .
- Arus puncak bagi setiap transistor, I_p .

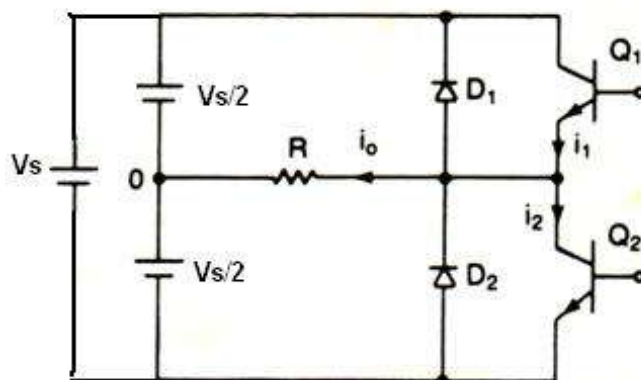


Figure Q5(c) / Rajah Q5(c)

(15 marks/ 15 markah)

[100 MARKS/ 100 MARKAH]

END OF QUESTION PAPER / KERTAS SOALAN TAMAT

Attachment 1 / Lampiran 1

Uncontrolled rectifier

$$\begin{aligned}
 V_{o(dc)} &= 0.318V_m & V_{o(rms)} &= 0.5 V_m \\
 V_{o(dc)} &= \frac{V_m}{2\pi} [1 - \cos(\beta)] & V_{o(rms)} &= \frac{V_m}{2} \sqrt{\frac{\beta}{\pi} - \frac{\sin(2\beta)}{2\pi}} \\
 V_{o(dc)} &= 0.6366V_m & V_{o(rms)} &= 0.707 V_m \\
 V_{o(dc)} &= 1.654V_m & V_{o(rms)} &= 1.6554 V_m \\
 V_{o(dc)} &= 0.827V_m & V_{o(rms)} &= 0.8407 V_m
 \end{aligned}$$

Controlled rectifier

$$\begin{aligned}
 V_{o(dc)} &= \frac{V_m}{2\pi} (1 + \cos\alpha) & V_{o(rms)} &= \frac{V_m}{2} \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2} \\
 V_{o(dc)} &= \frac{2V_m}{\pi} \cos\alpha & V_{o(rms)} &= V_m \left[\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi} \right]^{1/2}
 \end{aligned}$$

Principle of AC Voltage controller

$$\begin{aligned}
 V_s &= \sqrt{2} V_s \sin\omega t \\
 V_o &= V_s \sqrt{\frac{n}{m+n}} = V_s \sqrt{k}
 \end{aligned}$$

$$V_o(rms) = V_s \left[\frac{1}{2\pi} \left(2\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}$$

$$V_o(dc) = \frac{\sqrt{2} V_s}{2\pi} (\cos\alpha - 1)$$

AC Voltage controller : Single Phase

$$V_o(rms) = V_s \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{\alpha} \right) \right]^{1/2} \quad V_o(rms) = V_s \left[\frac{1}{\pi} \left(\beta - \alpha + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right) \right]^{1/2}$$

AC Voltage controller : Three Phase Half waveFor $0^\circ \leq \alpha < 90^\circ$:

$$V_o(\text{rms}) = \sqrt{3}V_s \left[\frac{1}{\pi} \left(\frac{\pi}{3} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{8} \right) \right]^{1/2}$$

For $90^\circ \leq \alpha < 120^\circ$:

$$V_o(\text{rms}) = \sqrt{3}V_s \left[\frac{1}{\pi} \left(\frac{11\pi}{24} - \frac{\alpha}{2} \right) \right]^{1/2}$$

For $120^\circ \leq \alpha < 210^\circ$:

$$V_o(\text{rms}) = \sqrt{3}V_s \left[\frac{1}{\pi} \left(\frac{7\pi}{24} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{16} - \frac{\sqrt{3} \cos 2\alpha}{16} \right) \right]^{1/2}$$

AC Voltage controller : Three Phase Full waveFor $0^\circ \leq \alpha < 60^\circ$:

$$V_o(\text{rms}) = \sqrt{6}V_s \left[\frac{1}{\pi} \left(\frac{\pi}{6} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{8} \right) \right]^{1/2}$$

For $60^\circ \leq \alpha < 90^\circ$:

$$V_o(\text{rms}) = \sqrt{6}V_s \left[\frac{1}{\pi} \left(\frac{\pi}{12} + \frac{3\sin 2\alpha}{16} + \frac{\sqrt{3} \cos 2\alpha}{16} \right) \right]^{1/2}$$

For $120^\circ \leq \alpha < 210^\circ$:

$$V_o(\text{rms}) = \sqrt{6}V_s \left[\frac{1}{\pi} \left(\frac{5\pi}{24} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{16} + \frac{\sqrt{3} \cos 2\alpha}{16} \right) \right]^{1/2}$$