



---

**KOLEJ YAYASAN PELAJARAN JOHOR  
FINAL EXAMINATION**

---

**COURSE NAME : SEMICONDUCTOR DEVICES**  
**COURSE CODE : DEE 1023**  
**EXAMINATION : JANUARY 2024**  
**DURATION : 2 HOURS 30 MINUTES**

---

**INSTRUCTION TO CANDIDATES/  
ARAHAN KEPADA CALON**

1. This examination paper consists of **ONE (1)** part : / PART A (100 Marks) /  
*Kertas soalan ini mengandungi **SATU (1)** bahagian:* BAHAGIAN A (100 Markah)
2. Candidates are not allowed to bring any material to examination room except with the permission from the invigilator. The formula was attached at the back question paper. /  
*Calon tidak dibenarkan untuk membawa sebarang bahan/nota ke bilik peperiksaan tanpa arahan/kebenaran daripada pengawas.*
3. Please check to make sure that this examination pack consists of: /  
Pastikan kertas soalan peperiksaan ini mengandungi:
  - i. Question Paper /  
Kertas Soalan.
  - ii. Answering Booklet /  
Buku Jawapan.

---

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /  
JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIBERITAHU**

---

This examination paper consists of 7 printed pages including front page  
*Kertas soalan ini mengandungi 7 halaman bercetak termasuk muka hadapan*



This examination paper consists of **FOUR (4)** questions. Answer **ALL** the questions in the **Answering Booklet**.

*Kertas soalan ini mengandungi **FOUR (4)** soalan. Jawab **SEMUA** soalan dalam **Buku Jawapan**.*

### QUESTION 1/ SOALAN 1

- a) Briefly explain the difference between conductor, insulator, and semiconductor in terms of the number of valence electrons in the valence shell of each material.

**(6 marks/ markah)**

- b) With the aid of an appropriate diagram, describe a PN junction that is

- i) forward bias.
- ii) reverse bias.

**(8 marks/ markah)**

- c) i) Draw and label completely the IV characteristics of a diode which is forward biased.

- ii) Explain its characteristics.

**(5 marks/ markah)**

- d) There are **two (2)** types of biasing in a diode. By using a LED, construct the schematic diagram and explain each of them accordingly.

**(6 marks/ markah)**

- a) *Terangkan secara ringkas perbezaan di antara pengalir, penebat, dan separuh pengalir dari segi bilangan elektron valens di dalam orbit luar setiap bahan.*

- b) *Dengan bantuan gambar rajah yang sesuai, jelaskan simpang PN.*

- i) pincang hadapan.  
ii) pincang balikan.
- c) i) Lukis dan label dengan lengkap ciri IV bagi sebuah diod pincang hadapan.  
ii) Terangkan ciri tersebut.
- d) Terdapat **dua (2)** jenis pincangan bagi sebuah diod. Dengan menggunakan LED, bina gambar rajah skematik yang sesuai dan terangkan.

**QUESTION 2/ SOALAN 2**

- a) Referring to **Figure 2 (a)**, calculate  $I$  and  $V_o$ .  
(5 marks/ *markah*)
- b) Determine  $I_1$ ,  $I_2$ ,  $I_3$ ,  $V_{o1}$  and  $V_{o2}$  for the circuit in **Figure 2 (b)**.  
(12 marks/ *markah*)
- c) Referring to **Figure 2 (c)**, sketch the output waveform,  $v_o$  with reference to input waveform,  $v_i$ . Show your analysis in detail.  
(8 marks/ *markah*)
- a) Berdasarkan **Rajah 2 (a)**, kira  $I$  dan  $V_o$ .
- b) Tentukan  $I_1$ ,  $I_2$ ,  $I_3$ ,  $V_{o1}$  dan  $V_{o2}$  untuk litar dalam **Rajah 2 (b)**.
- c) Berdasarkan **Rajah 2 (c)**, lakarkan gelombang keluaran,  $V_o$  dengan merujuk kepada gelombang masukan,  $V_i$ . Tunjukkan analisis anda dengan jelas.

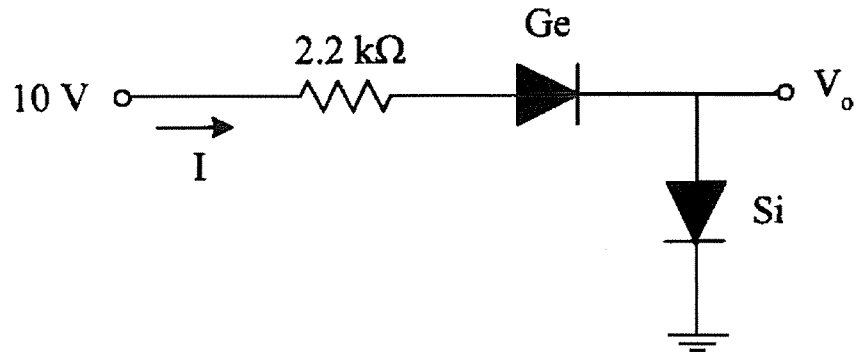


Figure 2 (a) /Rajah 2 (a)

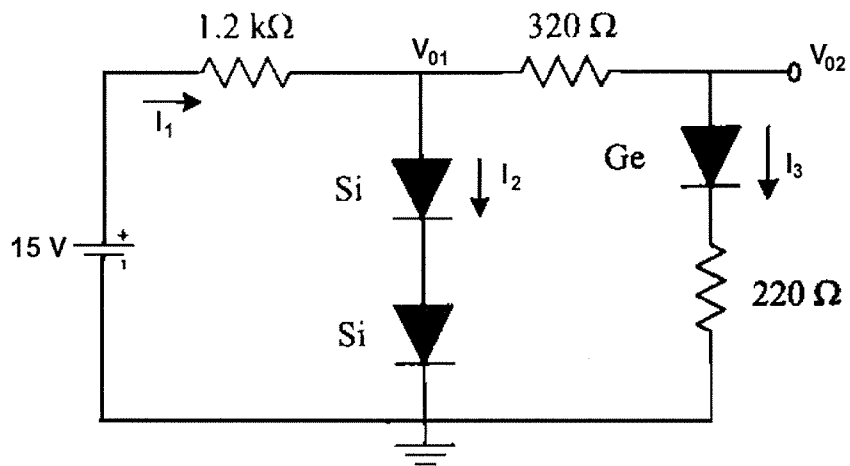


Figure 2 (b) /Rajah 2 (b)

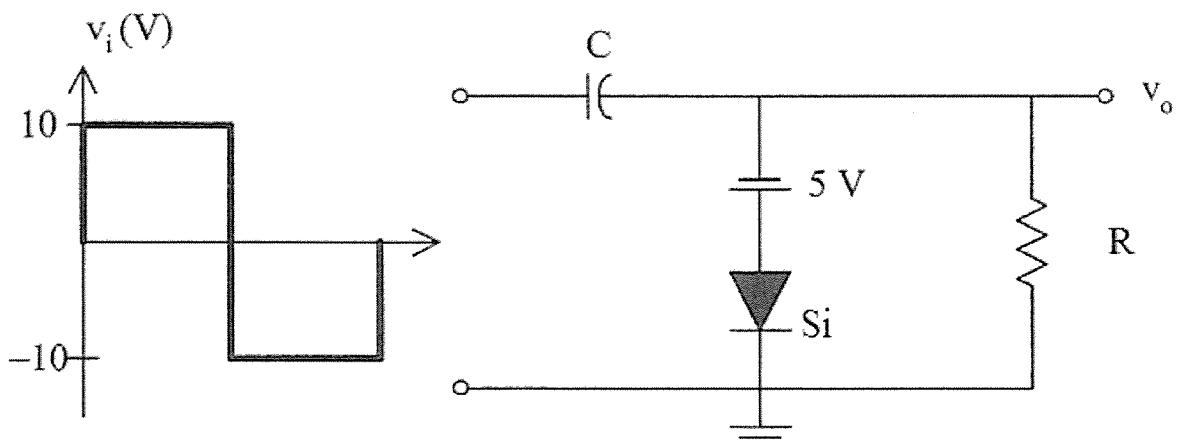


Figure 2 (c) /Rajah 2 (c)

**QUESTION 3/ SOALAN 3**

a) Referring to **Figure 3 (a)**, determine:

- i) base current,  $I_B$ .
- ii) collector current,  $I_C$ .
- iii) collector-emitter voltage,  $V_{CE}$ .
- iv) collector voltage,  $V_C$ .
- v) base voltage,  $V_B$ .

**(11 marks/ markah)**

b) Referring to **Figure 3 (b)**, determine:

- i) base current,  $I_B$ .
- ii) base resistor,  $R_B$ .
- iii) collector voltage,  $V_C$ .
- iv) emitter voltage,  $V_E$ .
- v) collector-emitter voltage,  $V_{CE}$ .
- vi) base voltage,  $V_B$ .

**(14 marks/ markah)**

a) Merujuk pada **Rajah 3 (a)**, tentukan:

- i) arus tapak,  $I_B$ .
- ii) arus pemungut,  $I_C$ .
- iii) voltan pemungut-pemancar,  $V_{CE}$ .
- iv) voltan pemungutr,  $V_C$ .
- v) voltan tapak,  $V_B$ .

b) Merujuk pada **Rajah 3 (b)**, tentukan:

- i) arus tapak,  $I_B$ .
- ii) rintangan tapak,  $R_B$ .
- iii) voltan pemungut,  $V_C$ .
- iv) voltan pemancar,  $V_E$ .
- v) voltan pemungut-pemancar,  $V_{CE}$ .
- vi) voltan tapak,  $V_B$ .

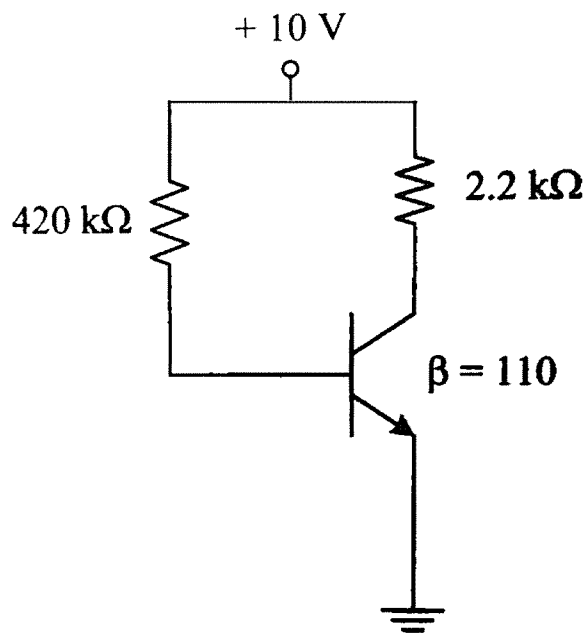


Figure 3 (a) /Rajah 3 (a)

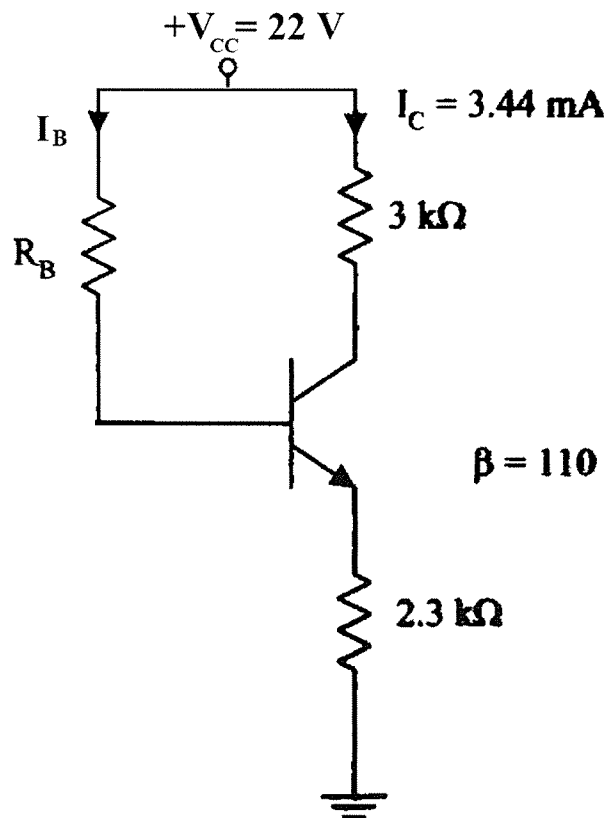


Figure 3 (b) /Rajah 3 (b)

## QUESTION 4/ SOALAN 4

Based on **Figure 4**:

- i) sketch AC equivalent circuit using re model.
- ii) determine input impedance,  $Z_i$ .
- iii) determine output impedance,  $Z_o$ .
- iv) determine voltage gain,  $A_v$ .
- v) determine current gain,  $A_i$ .
- vi) given  $v_i = 10 \sin \omega t$  mV, sketch  $v_o$  with reference to  $v_i$ .

(25 marks/ markah)

Berdasarkan **Rajah 4**:

- i) lakarkan litar setara AU dengan menggunakan model re.
- ii) tentukan galangan masukan,  $Z_i$ .
- iii) tentukan galangan keluaran,  $Z_o$ .
- iv) tentukan gandaan voltan,  $A_v$ .
- v) tentukan gandaan arus,  $A_i$ .
- vi) diberi  $v_i = 10 \sin \omega t$  mV, lakarkan  $v_o$  dengan merujuk kepada  $v_i$ .

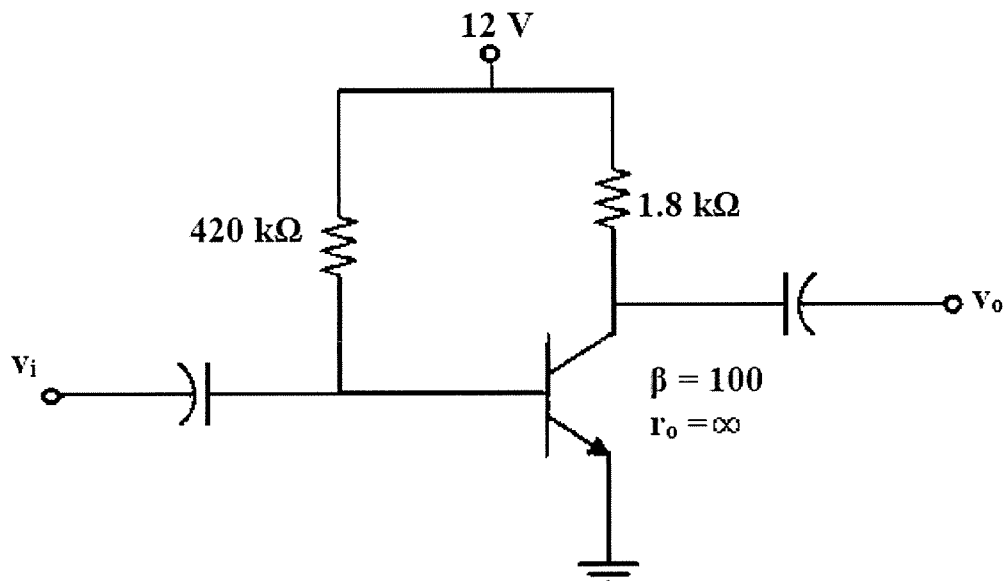


Figure 4 /Rajah 4

[100 MARKS/ MARKAH]

END OF QUESTION PAPER/ KERTAS SOALAN TAMAT



