



---

**KOLEJ YAYASAN PELAJARAN JOHOR  
ONLINE FINAL EXAMINATION**

---

**COURSE NAME : INDUSTRIAL ELECTRONICS**  
**COURSE CODE : DKE 3043**  
**SESSION : DECEMBER 2021**  
**DURATION : 2 HOURS 30 MINUTES**

---

**INSTRUCTION TO CANDIDATES /  
ARAHAN KEPADA CALON**

1. This examination paper consists of **TWO (2)** part: /  
*Kertas soalan ini mengandungi **DUA (2)** bahagian:*  
PART A (20 Marks) /  
PART B (80 Marks) /  
BAHAGIAN A (20 Markah)  
BAHAGIAN B (80 Markah)
2. Students are allowed to refer to resources such as lecture notes, books, internet or any other relevant resources. /  
*Pelajar dibenarkan merujuk kepada sumber seperti nota kuliah, buku, internet atau mana-mana sumber yang berkaitan.*
3. Answer **ALL** questions in the answer sheet which is **A4** size paper (or other paper with the consent of the relevant lecturer). /  
*Jawab **SEMUA** soalan di dalam kertas jawapan iaitu kertas bersaiz **A4** (atau lain-lain kertas dengan persetujuan pensyarah berkaitan).*
4. Write your details as follows in the upper left corner for each answer sheet: /  
*Tulis butiran anda sepetimana berikut di penjuru atas kiri bagi setiap kertas jawapan:*
  - i. Student Full Name / Nama Penuh Pelajar
  - ii. Identification Card (I/C) No. / No. Kad Pengenalan
  - iii. Class Section / Seksyen Kelas
  - iv. Course Code / Kod Kursus
  - v. Course Name / Nama Kursus
  - vi. Lecturer Name / Nama Pensyarah
5. Each answer sheet must have a page number written at the bottom right corner. /  
*Setiap helai kertas jawapan mesti ditulis nombor muka surat di penjuru bawah kanan.*
6. Answers should be handwritten, neat and clear. /  
*Jawapan hendaklah ditulis tangan, kemas dan jelas.*

---

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /  
JANGAN BUKA KERTAS SOALANINI SEHINGGA DIBERITAHU**

---

This examination paper consists of **10** printed pages including front page  
*Kertas soalan ini mengandungi **10** halaman bercetak termasuk muka hadapa*

**PART A / BAHAGIAN A**

This part consists of **FOUR (4)** questions. Answer **ALL** the questions in an answering booklet.


*Bahagian ini mengandungi **EMPAT (4)** soalan. Jawab **SEMUA** soalan dalam buku jawapan.*

**QUESTION 1 / SOALAN 1**

Referring to **Figure 1** shows a block diagram of a series voltage regulator of a transistor with a feedback signal. Explain the function of each block in the given diagram.

(5 marks / markah)

*Merujuk pada **Rajah 1** menunjukkan satu rajah blok pengatur voltan siri transistor dengan isyarat suapbalik. Terangkan fungsi setiap blok di dalam rajah yang diberikan tersebut.*

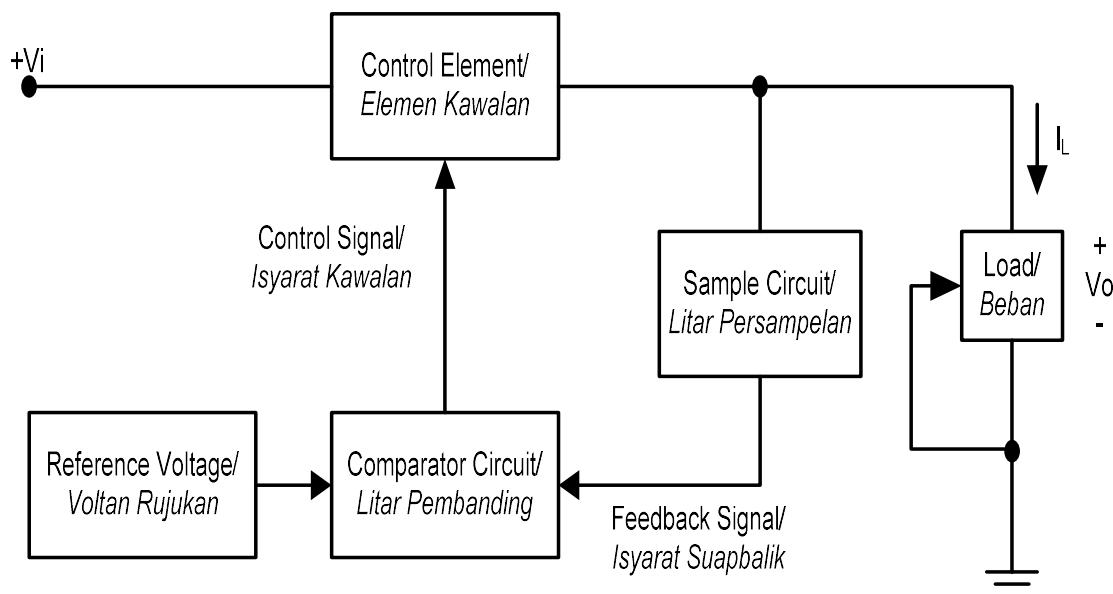


**Figure 1 / Rajah 1**

**QUESTION 2 / SOALAN 2**

**Figure 2** shows the internal build of 555 timers. Explain the **five (5)** functions of the pins on the timer.

(5 marks / markah)

**Rajah 2** menunjukkan binaan dalaman sebuah pemasa 555. Terangkan lima (5) fungsi pin yang terdapat pada pemasa tersebut.

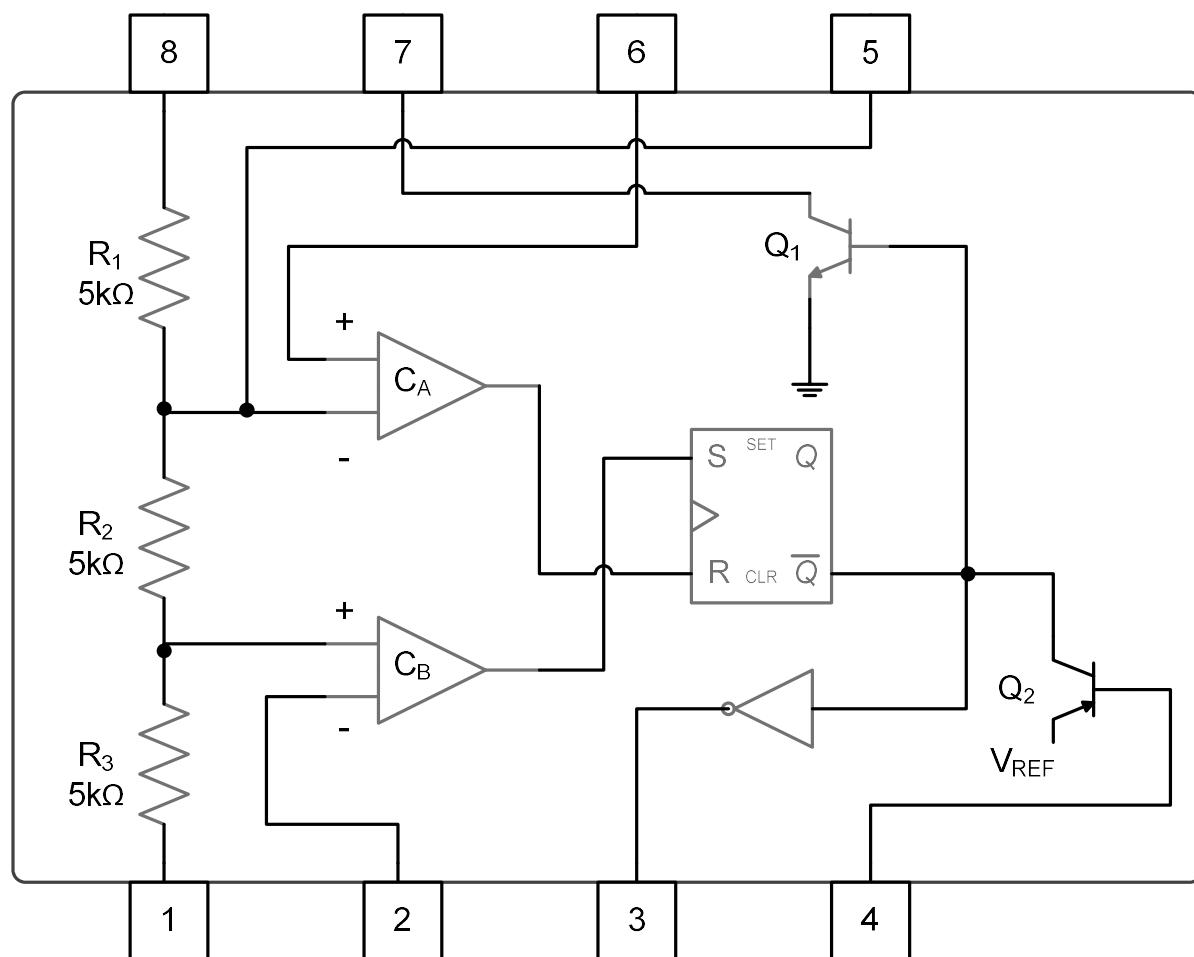

**Figure 2 / Rajah 2**

**QUESTION 3 / SOALAN 3**

Express completely I-V characteristic curve of silicon controlled rectifier, SCR.

**(5 marks / markah)**

*Nyatakan dengan lengkap lengkung cirian I-V bagi penerus terkawal silikon, SCR.*

**QUESTION 4 / SOALAN 4**

List **four (4)** important parameters for an optocoupler and describe **one (1)** of those parameters.

**(5 marks / markah)**

*Senaraikan **empat (4)** parameter penting bagi sesebuah pengganding opto danuraikan **satu (1)** daripada parameter tersebut.*

**PART B / BAHAGIAN B**

This part consists of **FOUR (4)** questions. Answer **ALL** the questions in an answering booklet.

*Bahagian ini mengandungi **EMPAT (4)** soalan. Jawab **SEMUA** soalan dalam buku jawapan.*

**QUESTION 5 / SOALAN 5**

Referring to **Figure 5** shows a regulator. Given  $\beta_1 = 100$ ,  $\beta_2 = 200$ ,  $V_{BE1} = V_{BE2} = 0.7 \text{ V}$ ,  $V_Z = 6.3 \text{ V}$  and  $V_i = 25 \text{ V}$ . Find:

- a. the value of regulated output voltage,  $V_O$  for the regulator circuit.

(6 marks / markah)

- b. the values of currents  $I_{R4}$ ,  $I_{B1}$ ,  $I_{E1}$  and  $I_{C1}$

(8 marks / markah)

- c. the maximum power rating for transistor,  $Q_1$ .


(6 marks / markah)

*Merujuk kepada **Rajah 5** menunjukkan sebuah pengatur. Diberi  $\beta_1 = 100$ ,  $\beta_2 = 200$ ,  $V_{BE1} = V_{BE2} = 0.7 \text{ V}$ ,  $V_Z = 6.3 \text{ V}$  dan  $V_i = 25 \text{ V}$ . Dapatkan:*

- a. nilai voltan keluaran teratur,  $V_O$  bagi litar pengatur tersebut.

- b. nilai arus  $I_{R4}$ ,  $I_{B1}$ ,  $I_{E1}$  dan  $I_{C1}$

- c. kadaran kuasa maksimum bagi transistor,  $Q_1$ .

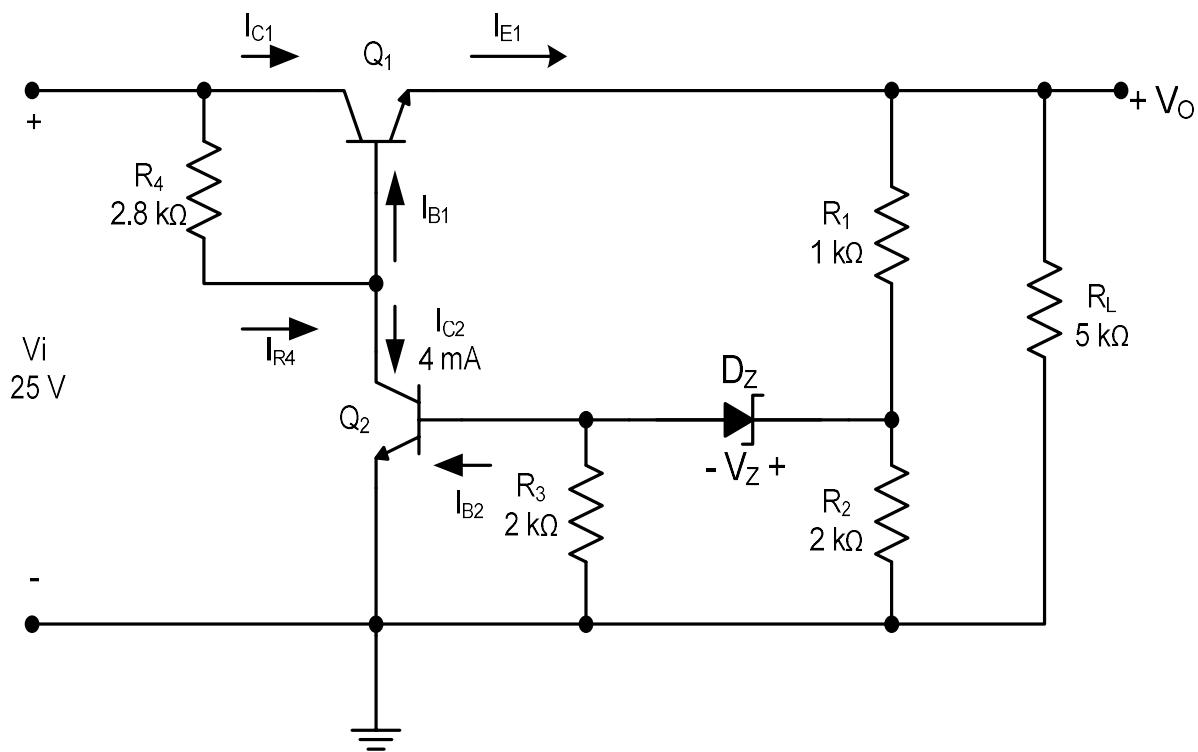**Figure 5 / Rajah 5****QUESTION 6 / SOALAN 6**

Referring to **Figure 6** is unstable multivibrator circuit using 555 timers which generates a square wave frequency,  $f = 1\text{kHz}$  and the duty cycle is 60%. Given the supply voltage,  $+V_{CC} = +12\text{V}$  and  $I_{C(\min)} = 1\text{mA}$ . Find:

- a. period, T, high duration,  $T_H$ , low duration,  $T_L$  and pulse width,  $P_W$ .

**(8 marks / markah)**

- b. capacitor value,  $C_A$ .

**(6 marks / markah)**

- c. resistors value,  $R_A$  and  $R_B$ .


**(6 marks / markah)**

Merujuk pada **Rajah 6** iaitu litar pemberbilang getar tak stabil dengan menggunakan pemasa 555 yang menghasilkan gelombang segiempat yang berfrekuensi,  $f = 1\text{kHz}$  dan kitar tugas adalah 60%. Diberi voltan bekalan,  $+V_{CC} = +12\text{V}$  dan  $I_{C(min)} = 1\text{mA}$ . Dapatkan:

a. tempoh,  $T$ , tempoh tinggi,  $T_H$ , tempoh rendah,  $T_L$  dan lebar denyut,  $P_W$ .

b. nilai pemuat,  $C_A$ .

c. nilai perintang,  $R_A$  dan  $R_B$ .

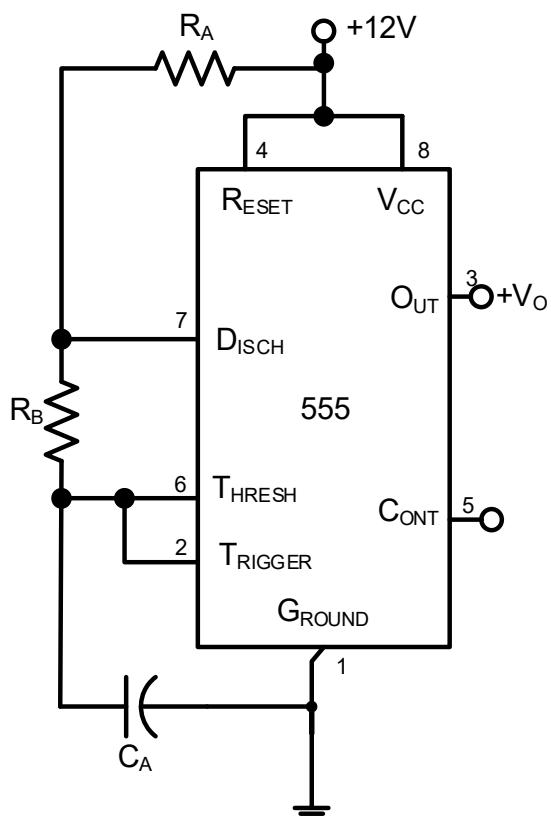

**Figure 6 / Rajah 6**

**QUESTION 7 / SOALAN 7**

Referring to **Figure 7**, given peak input voltage,  $V_{i(\text{peak})} = 100 \text{ V}$ , load resistance,  $R_L = 10 \Omega$ , resistance,  $R_1 = R_2 = 4.7 \text{ k}\Omega$ , gate trigger current,  $I_{GT} = 50 \mu\text{A}$ , gate trigger voltage,  $V_{GT} = 1 \text{ V}$  and breakdown voltage for device P = 20 V. Find:

- a. the firing angle.

(6 marks / markah)

- b. the maximum power of an alternating current across the load,  $R_L$ .

(4 marks / markah)

- c. the percentage of the maximum power supplied to the load at the firing angle in (a).

(10 marks / markah)

Merujuk pada **Rajah Q7**, diberi voltan masukan puncak,  $V_{i(\text{puncak})} = 100 \text{ V}$ , rentangan beban,  $R_L = 10 \Omega$ , rentangan,  $R_1 = R_2 = 4.7 \text{ k}\Omega$ , arus picuan get,  $I_{GT} = 50 \mu\text{A}$ , voltan picuan get,  $V_{GT} = 1 \text{ V}$  dan voltan pecah lampau bagi peranti P = 20 V. Dapatkan:

- a. sudut picuan.

- b. kuasa maksimum arus ulang alik yang terbina merentasi beban,  $R_L$ .

- c. peratusan kuasa maksimum yang dibekalkan ke beban pada sudut picuan dalam (a).

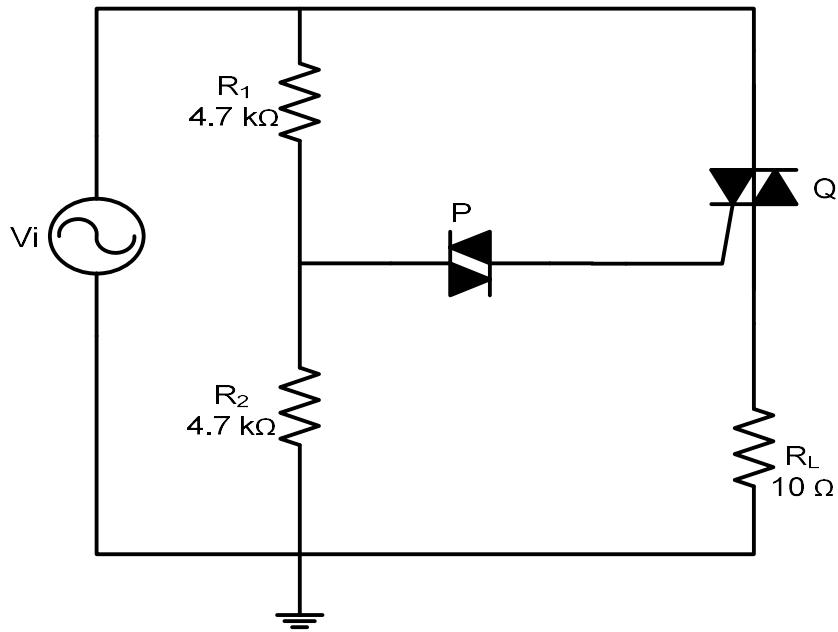


Figure 7 / Rajah 7

**QUESTION 8 / SOALAN 8**

The circuit at **Figure 8** shows the light detector circuit. If the diode,  $D_1$  is germanium and the opto coupling circuit has a current transfer ratio, CTR of 50%. Determine:

- the resistance value of the light dependent resistor,  $R_{LDR}$  when the LED starts to malfunction.

(8 marks / markah)

- base current,  $I_B$  when the LED starts to malfunction.

(12 marks / markah)

*Litar pada **Rajah 8** menunjukkan litar pengesan cahaya. Jika diod,  $D_1$  adalah germanium dan litar gandingan opto mempunyai nisbah arus pindah, CTR sebanyak 50%. Tentukan:*

- nilai rintangan perintang peka cahaya,  $R_{LDR}$  ketika LED mula tidak berfungsi.
- arus tapak,  $I_B$  ketika LED mula tidak berfungsi.

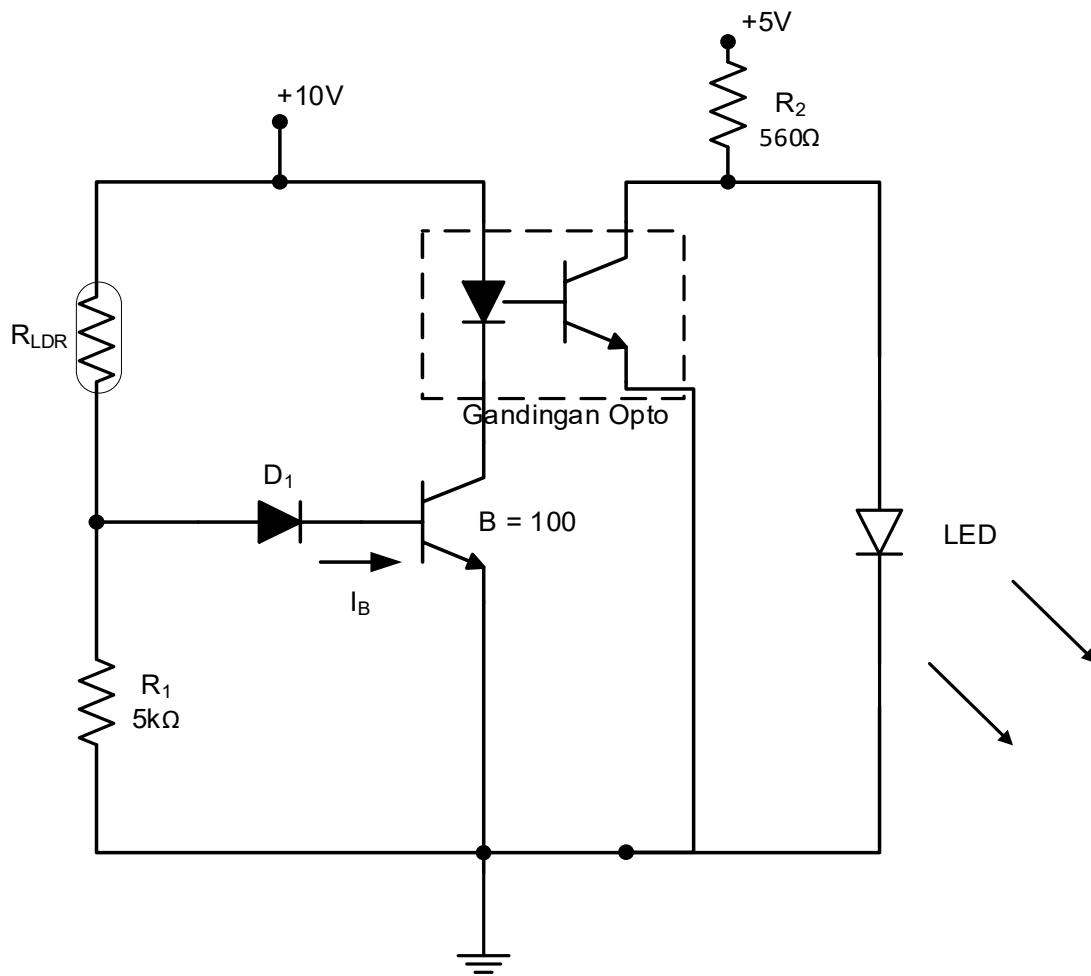


Figure 8 / Rajah 8

[100 MARKS / 100 MARKAH]

END OF QUESTION PAPER / KERTAS SOALAN TAMAT