



**FINAL EXAMINATION / PEPERIKSAAN AKHIR
SEMESTER 1 – SESSION 2016 / 2017
PROGRAM KERJASAMA**

COURSE CODE : DDPE 1142
KOD KURSUS

COURSE NAME : INSTRUMENTATION / INSTRUMENTASI
NAMA KURSUS

YEAR / PROGRAMME : 1DDPE / K / P
TAHUN / PROGRAM

DURATION : 2 HOURS / 2 JAM
TEMPOH

DATE : OCT 2016
TARIKH

INSTRUCTION :
ARAHAN

1. This question paper consist of **FIVE (5)** questions.
Kertas soalan ini mengandungi LIMA (5) soalan.
2. Answer **ALL** questions.
Jawab SEMUA soalan.

(You are required to write your name and your lecturer's name on your answer script)
(Pelajar dikehendaki tuliskan nama dan nama pensyarah pada skrip jawapan)

| | | |
|-----------------------------------|---|-------|
| STUDENT'S NAME / NAMA PELAJAR | : | |
| I.C NO. / NO. K/PENGENALAN | : | |
| YEAR / COURSE TAHUN / KURSUS | : | |
| LECTURER'S NAME NAMA PENSYARAH | : | |
| COLLEGE'S NAME NAMA KOLEJ | : | |

This examination paper consists of **10** pages including the cover
Kertas soalan ini mengandungi 10 muka surat termasuk kulit hadapan

- Q1 (a) Transducers are normally classified according to three characteristics. Explain briefly these three (3) characteristics.

Transduser lazimnya dikelaskan mengikut tiga ciri. Terangkan dengan ringkas tiga (3) ciri tersebut.

(6 marks/markah)

- (b) Figure Q1(b) shows a circuit utilizing a resistance temperature detector (RTD) R_t . The RTD has a temperature coefficient of $\alpha = 0.0038K^{-1}$ and a resistance of 120Ω at the reference temperature of $0^\circ C$. The battery voltage $E = 9.0 V$.
- Explain briefly the functions of RTD.
 - R_1 is set so that the output voltage V_o is $4.5 V$ at the reference temperature. Calculate R_1 .
 - Calculate V_o when the temperature rises to $50^\circ C$.
 - A change in temperature causes the output voltage to change to $4.23 V$. Calculate the new temperature.

Rajah Q1(b) menunjukkan litar yang menggunakan pengesan suhu rintangan (RTD) R_t . RTD tersebut mempunyai pekali suhu $\alpha = 0.0038 K^{-1}$ dan rintangan 120Ω pada suhu rujukan $0^\circ C$. Voltan bateri $E = 9.0 V$.

- Terangkan dengan ringkas bagaimana RTD berfungsi.
- R_1 diset supaya voltan keluaran V_o ialah $4.5 V$ pada suhu rujukan. Kirakan R_1 .
- Kirakan V_o apabila suhu naik ke $50^\circ C$.
- Perubahan suhu menyebabkan voltan keluaran berubah ke $4.23 V$. Kirakan suhu yang baru.

$$V_o = R_o (1 + \alpha \Delta T)$$

$$R_1 = R_o (1 + \alpha \Delta T)$$

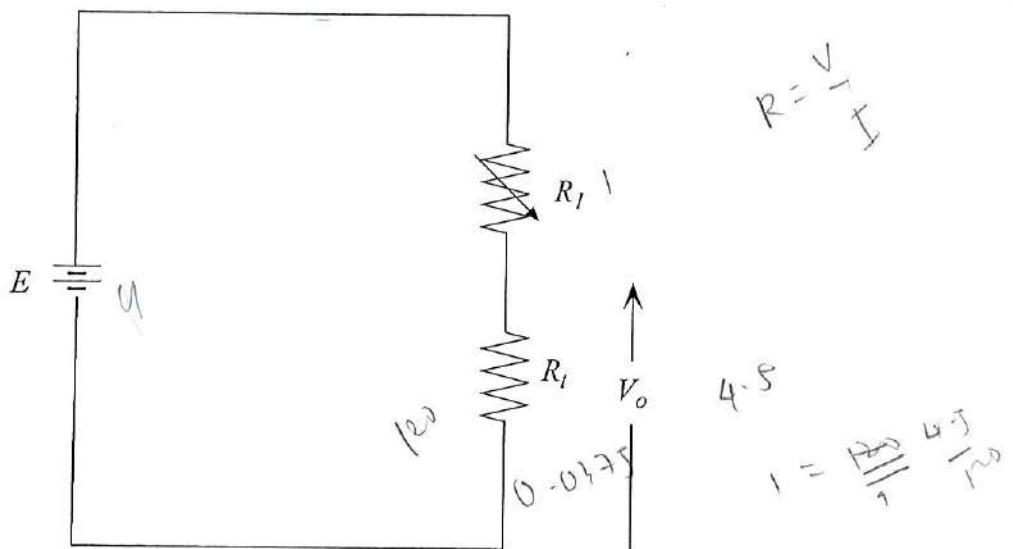


Figure Q1(b) / Rajah Q1(b)

(14 marks/markah)

- Q2. (a) Describe the principle operation of one (1) of the following transducers. Illustrate your answer with appropriate diagrams.
- Linear variable differential transformer (LVDT)
 - Resistance temperature detector (RTD)
 - Photovoltaic cell

Huraikan prinsip pengendalian satu (1) daripada transduser berikut. Sertakan gambar rajah yang sesuai.


- Pengubah kebezaan bolehubah lelurus (LVDT)
- Pengesan suhu berintangan (RTD)
- Sel fotovolta. ~ aktif

(8 marks/markah)

- (b) Appendix A shows the table for type S thermocouple.
- (i) List two (2) advantages and two (2) disadvantages of the thermocouple as compared to other temperature transducers.
- (ii) Type S thermocouple produces an output voltage of 10.949 mV. Determine the temperature at the hot junction when given the temperature of the cold junction is 20 °C.
- (iii) The temperature of the cold junction is adjusted to 10 °C. Determine the output voltage if the temperature of the hot junction does not change.

Lampiran A menunjukkan jadual pengganding suhu jenis S.

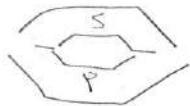- (i) Senaraikan dua (2) kelebihan dan dua (2) kekurangan pengganding suhu berbanding dengan transduser suhu lain.
- (ii) Pengganding suhu jenis S menghasilkan voltan keluaran 10.949 mV. Tentukan suhu pada simpang panas jika suhu simpang sejuk ialah 20 °C.
- (iii) Suhu simpang sejuk dilaraskan ke 10 °C. Tentukan voltan keluaran jika suhu simpang panas tidak berubah.



(12 marks/markah)

- Q3. (a) (i) Explain briefly the role of signal conditioners in instrumentation systems.
(ii) Give a brief explanation of the Wheatstone bridge.
- (i) Terangkan dengan ringkas peranan penyesuaian isyarat dalam sistem instrumentasi.
(ii) Berikan penerangan ringkas tentang tili Wheatstone.


(6 marks/markah)

peranti elektronik yg menyumbang
isynopsis kuantiti yg sama syn upm

- (b) Figure Q3(b) shows the circuit of a half Wheatstone bridge.
- (i) Explain the difference between the half Wheatstone bridge and the full Wheatstone bridge.
- (ii) Show that the Thevenin parameters for the half Wheatstone bridge between terminals c-d is given by

$$V_{TH} = \frac{\Delta R}{2R} E$$

$$R_{TH} \approx R$$

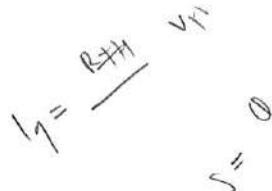

with the assumption that $\Delta R \ll R$.

- (iii) Sketch the Thevenin equivalent circuit.
- (iv) A galvanometer with internal resistance 100Ω is used as a detector between terminals c-d. Calculate the current through the meter given that $E = 2 V$, $R = 200 \Omega$ and the resistance change is 2%.

Rajah Q3(b) menunjukkan litar titi separuh Wheatstone.

- (i) Terangkan perbezaan titi separuh Wheatstone berbanding dengan titi penuh Wheatstone.
- (ii) Tunjukkan bahawa parameter Thevenin bagi tetimbang tersebut antara terminal c-d diberikan oleh

$$V_{TH} = \frac{\Delta R}{2R} E$$

$$R_{TH} \approx R$$

dengan andaian bahawa $\Delta R \ll R$.

- (iii) Lakarkan litar setara Thevenin.
- (iv) Meter galvani dengan rintangan dalam 100Ω digunakan sebagai pengesan antara terminal c-d. Kirakan arus yang mengalir melalui meter tersebut jika $E = 2 V$, $R = 200 \Omega$, dan perubahan rintangan ialah 2%.

$I_2 =$

-7-

DDPE 1142

$$\frac{R^2}{2R} + \frac{R^2}{2R}$$

$$2R^2$$

$$V = \frac{R_{TH}}{R_{TH} + R_2} \times V_{TH}$$

$$\Delta R = 4$$

$$R = 200$$

$$E = 2$$

$$R_{TH} = (199.96)$$


$$V_{TH} = 0.02$$

$$R_{TH} = 199.96$$

$$199.96$$

$$V = 13.33 \text{ mV}$$

$$S = V_R =$$

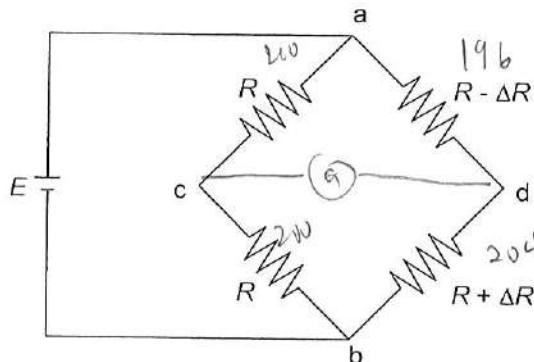

$$R \Delta R$$

Figure Q3(b)/Rajah Q3(b)

(14 marks/markah)

$$S = \frac{\theta}{\pi}$$

- Q4. (a) Figure Q4 (a) shows a Wein bridge circuit . Given $R_1 = 5 \text{ k}\Omega$, $R_2 = 3 \text{ k}\Omega$, $R_3 = 4 \text{ k}\Omega$, $C_1 = C_3 = 2 \mu\text{F}$.

- (i) State the application of the Wein bridge.
- (ii) Show that in the null condition, the frequency is given by

$$f = \frac{1}{2\pi\sqrt{C_1 C_3 R_1 R_3}}$$

$$f = 2\pi\omega$$

$$\omega = 2\pi f$$

$$f = \frac{\omega}{2\pi}$$

- (iii) Calculate the frequency.

Rajah Q4(a) menunjukkan litar titi Wein. Diberi $R_1 = 5 \text{ k}\Omega$, $R_2 = 3 \text{ k}\Omega$, $R_3 = 4 \text{ k}\Omega$, $C_1 = C_3 = 2 \mu\text{F}$.

- (i) Nyatakan kegunaan titi Wein
- (ii) Tunjukkan bahawa pada keadaan nol, frekuensi diberikan oleh,

$$f = \frac{1}{2\pi\sqrt{C_1 C_3 R_1 R_3}}$$

- (iii) Kirakan frekuensi tersebut.

$$2\pi f = \frac{1}{\sqrt{C_1 C_3 R_1 R_3}}$$

$$\omega = \frac{1}{\sqrt{C_1 C_3 R_1 R_3}}$$

$$C_1 C_3 R_1 R_3 \omega^2 = \frac{1}{C_1 C_3 R_1 R_3}$$

$$Z_1 Z_2 = Z_3 Z_4$$

$$\frac{Z_1}{Z_3} Z_2 = Z_4$$

Z₃

$$\left(R_1 + \frac{1}{j\omega C_1} \right) \left(\frac{1}{R_3} + j\omega L_4 \right) (R_2) = R_4$$

$$\left(R_1 + \frac{1}{j\omega C_1} \right) \left(\frac{1}{R_3} + j\omega L_4 \right) = \frac{R_4}{R_2}$$

E

$$\frac{R_1}{R_2}$$

-8-

DDPE 1142

$$Z_1 = R_1 + \frac{1}{j\omega C_1}$$

$$Z_2 = R_2$$

$$Z_3 = \frac{1}{R_3} + j\omega L_4$$

$$Z_4 = R_4$$

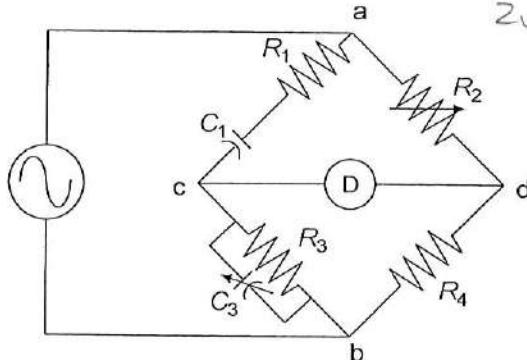


Figure Q4(a)/Rajah Q4(a)

(8 marks/markah)

- (b) (i) Give four (4) examples of signal conditioners in an instrumentation system.
 (ii) State the main application of a filter in an instrumentation system.
 (iii) Name the four (4) types of filters used in signal conditioning and sketch their respective frequency responses.
 (iv) In a measurement process, the signal frequency used is below 1 kHz, but the noise is at 1 MHz. Propose a suitable filter for the process. Determine the value of the cut-off frequency (f_c) if the voltage gain (V_o / V_{in}) is 1% at the maximum measurement frequency of 1 kHz.

$$f = 1 \text{ kHz}$$

$$V_o / V_{in} = 1$$

- (i) Berikan empat (4) contoh penyesuaian isyarat dalam sebuah sistem instrumentasi.
 (ii) Nyatakan kegunaan utama penapis dalam sistem instrumentasi.
 (iii) Namakan empat (4) jenis penapis yang digunakan untuk penyesuaian isyarat dan lakarkan sambutan frekuensi masing-masing.
 (iv) Dalam suatu proses pengukuran, frekuensi isyarat yang digunakan di bawah 1 kHz, tetapi isyarat hingar berada pada 1 MHz. Cadangkan penapis yang sesuai digunakan untuk proses tersebut. Dapatkan nilai frekuensi potong (f_c) jika gandaan voltan (V_o / V_{in}) ialah 1% pada frekuensi isyarat pengukuran maksimum 1 kHz.

(12 marks/markah)

- Q5. (a) Give the main reason why the use of data acquisition systems based on digital systems are widely used in instrumentation as compared to analogue systems.

Berikan sebab utama mengapa sistem perolehan data yang berdasarkan sistem digit semakin banyak digunakan dalam pengalatan berbanding dengan sistem analog.

(6 marks/markah)

- (b) The IEEE 488 bus is widely used in data communications. Explain the terms talker, listener and controller within the context of the IEEE 488 bus.

Bas IEEE 488 digunakan dengan meluas dalam perhubungan data. Terangkan istilah penutur, pendengar dan pengawal dalam konteks bas IEEE 488.

(6 marks/markah)

- (c) The RS232 bus is also an interface used in digital systems. Explain briefly the difference between the RS232 bus and the IEEE 488 bus.




Bas RS232 juga merupakan antaramuka yang digunakan dalam sistem digit. Terangkan dengan ringkas perbezaan diantara bas RS232 dan bas IEEE 488.

(8 marks/markah)

penyelesaian isyarat

penapis

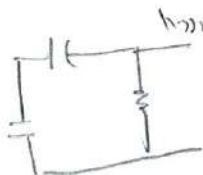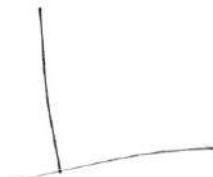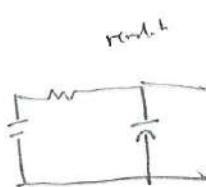- penapis tulus hingga rendah
- penapis tulus rendah



APPENDIX A / LAMPIRAN A
TYPE S THERMOCOUPLE TABLE

JADUAL PENGGANDING SUHU JENIS S

Appendix 3 Thermocouple Tables

537

Type S: Platinum-Platinum/10% Rhodium

| | 0 | 5 | 10 | 15 | 20 | 25 | 30 | 35 | 40 | 45 |
|-------|--------|--------|--------|--------|--------|--------|--------|--------|--------|--------|
| - 150 | | | | | | | | | | |
| - 100 | | | | | | | | | | |
| - 50 | | | | | | | | | | |
| - 0 | | | | | | | | | | |
| + 0 | 0.000 | 0.028 | 0.056 | 0.084 | 0.113 | 0.143 | 0.173 | 0.204 | 0.235 | 0.266 |
| 50 | 0.299 | 0.331 | 0.364 | 0.397 | 0.431 | 0.466 | 0.500 | 0.535 | 0.571 | 0.607 |
| 100 | 0.643 | 0.680 | 0.717 | 0.754 | 0.792 | 0.830 | 0.869 | 0.907 | 0.946 | 0.986 |
| 150 | 1.025 | 1.065 | 1.166 | 1.146 | 1.187 | 1.228 | 1.269 | 1.311 | 1.352 | 1.394 |
| 200 | 1.436 | 1.479 | 1.521 | 1.564 | 1.607 | 1.650 | 1.693 | 1.736 | 1.780 | 1.824 |
| 250 | 1.868 | 1.912 | 1.956 | 2.001 | 2.045 | 2.090 | 2.135 | 2.180 | 2.225 | 2.271 |
| 300 | 2.316 | 2.362 | 2.408 | 2.453 | 2.499 | 2.546 | 2.592 | 2.638 | 2.685 | 2.731 |
| 350 | 2.778 | 2.825 | 2.872 | 2.919 | 2.966 | 3.014 | 3.061 | 3.108 | 3.156 | 3.203 |
| 400 | 3.251 | 3.299 | 3.347 | 3.394 | 3.442 | 3.490 | 3.539 | 3.587 | 3.635 | 3.683 |
| 450 | 3.732 | 3.780 | 3.829 | 3.878 | 3.926 | 3.975 | 4.024 | 4.073 | 4.122 | 4.171 |
| 500 | 4.221 | 4.270 | 4.319 | 4.369 | 4.419 | 4.468 | 4.518 | 4.568 | 4.618 | 4.668 |
| 550 | 4.718 | 4.768 | 4.818 | 4.869 | 4.919 | 4.970 | 5.020 | 5.071 | 5.122 | 5.173 |
| 600 | 5.224 | 5.275 | 5.326 | 5.377 | 5.429 | 5.480 | 5.532 | 5.583 | 5.635 | 5.686 |
| 650 | 5.738 | 5.790 | 5.842 | 5.894 | 5.946 | 5.998 | 6.050 | 6.102 | 6.155 | 6.207 |
| 700 | 6.260 | 6.312 | 6.365 | 6.418 | 6.471 | 6.524 | 6.577 | 6.630 | 6.683 | 6.737 |
| 750 | 6.790 | 6.844 | 6.897 | 6.951 | 7.005 | 7.058 | 7.112 | 7.166 | 7.220 | 7.275 |
| 800 | 7.329 | 7.383 | 7.438 | 7.492 | 7.547 | 7.602 | 7.656 | 7.711 | 7.766 | 7.821 |
| 850 | 7.876 | 7.932 | 7.987 | 8.042 | 8.098 | 8.153 | 8.209 | 8.265 | 8.320 | 8.376 |
| 900 | 8.432 | 8.488 | 8.545 | 8.601 | 8.657 | 8.714 | 8.770 | 8.827 | 8.883 | 8.940 |
| 950 | 8.997 | 9.054 | 9.111 | 9.168 | 9.225 | 9.282 | 9.340 | 9.397 | 9.455 | 9.512 |
| 1000 | 9.570 | 9.628 | 9.686 | 9.744 | 9.802 | 9.860 | 9.918 | 9.976 | 10.035 | 10.093 |
| 1050 | 10.152 | 10.210 | 10.269 | 10.328 | 10.387 | 10.446 | 10.505 | 10.564 | 10.623 | 10.682 |
| 1100 | 10.741 | 10.801 | 10.860 | 10.919 | 10.979 | 11.038 | 11.098 | 11.157 | 11.217 | 11.277 |
| 1150 | 11.336 | 11.396 | 11.456 | 11.516 | 11.575 | 11.635 | 11.695 | 11.755 | 11.815 | 11.875 |
| 1200 | 11.935 | 11.995 | 12.055 | 12.115 | 12.175 | 12.236 | 12.296 | 12.356 | 12.416 | 12.476 |
| 1250 | 12.536 | 12.597 | 12.657 | 12.717 | 12.777 | 12.837 | 12.897 | 12.957 | 13.018 | 13.078 |
| 1300 | 13.138 | 13.198 | 13.258 | 13.318 | 13.378 | 13.438 | 13.498 | 13.558 | 13.618 | 13.678 |
| 1350 | 13.738 | 13.798 | 13.858 | 13.918 | 13.978 | 14.038 | 14.098 | 14.157 | 14.217 | 14.277 |
| 1400 | 14.337 | 14.397 | 14.457 | 14.516 | 14.576 | 14.636 | 14.696 | 14.755 | 14.815 | 14.875 |
| 1450 | 14.935 | 14.994 | 15.054 | 15.113 | 15.173 | 15.233 | 15.292 | 15.352 | 15.411 | 15.471 |
| 1500 | 15.530 | 15.590 | 15.649 | 15.709 | 15.768 | 15.827 | 15.887 | 15.946 | 16.006 | 16.065 |
| 1550 | 16.124 | 16.183 | 16.243 | 16.302 | 16.361 | 16.420 | 16.479 | 16.538 | 16.597 | 16.657 |
| 1600 | 16.716 | 16.775 | 16.834 | 16.893 | 16.952 | 17.010 | 17.069 | 17.128 | 17.187 | 17.246 |
| 1650 | 17.305 | 17.363 | 17.422 | 17.481 | 17.539 | 17.598 | 17.657 | 17.715 | 17.774 | 17.832 |
| 1700 | 17.891 | 17.949 | 18.008 | 18.066 | 18.124 | 18.183 | 18.241 | 18.299 | 18.358 | 18.416 |
| 1750 | 18.474 | 18.532 | 18.590 | 18.648 | | | | | | |

Mukasurat ini sengaja dibiarkan kosong

[This page is purposely left blank]