



**KOLEJ YAYASAN PELAJARAN JOHOR
FINAL EXAMINATION**

COURSE NAME : ELECTRONIC CIRCUIT
COURSE CODE : DEE 1073
EXAMINATION : JUNE 2023
DURATION : 2 HOURS 30 MINUTES

**INSTRUCTION TO CANDIDATES/
ARAHAN KEPADA CALON**

1. This examination paper consists of **FOUR (4)** questions. /
*Kertas soalan ini mengandungi **EMPAT (4)** soalan.*
2. Candidates are not allowed to bring any material to examination room except with the permission from the invigilator. The formula was attached at the back question paper. /
Calon tidak dibenarkan untuk membawa sebarang bahan/nota ke bilik peperiksaan tanpa arahan/kebenaran daripada pengawas. Rumus dilampirkan di belakang kertas soalan peperiksaan.
3. Please check to make sure that this examination pack consists of: /
Pastikan kertas soalan peperiksaan ini mengandungi:
 - i. Question Paper /
Kertas Soalan
 - ii. Answering Booklet /
Buku Jawapan
 - iii. Attachment 1 /
Lampiran 1
 - iv. Attachment 2 /
Lampiran 2
 - v. Attachment 3 /
Lampiran 3

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIBERITAHU**

This examination paper consists of **13** printed pages including front page
*Kertas soalan ini mengandungi **13** halaman bercetak termasuk muka hadapan*

This examination paper consists of **FOUR (4)** questions. Answer **ALL** the questions in the answer sheet.

*Kertas soalan ini mengandungi **EMPAT (4)** soalan. Jawab **SEMUA** soalan dalam buku jawapan.*

QUESTION 1/ SOALAN 1

The point of operation for transistor is known as quiescent point (Q-point). All three basic configuration for field effect transistor (FET) need Q-point to obtain the drain current and gate-to-source voltage.

- a) Referring to **Figure 1(a)**, draw the transfer curve using shorthand method. The graph is given in the **Attachment 1**.

(10 marks/ markah)

- b) Using the universal curve given in the **Attachment 2**, identify the values :

- i) drain current, I_D
- ii) gate-to-source voltage, V_{GS}

(5 marks/ markah)

- c) Calculate :

- i) drain-to-source voltage, V_{DS}
- ii) source voltage, V_S
- iii) drain voltage, V_D
- iv) drain-to-gate voltage, V_{DG}

(9 marks/ markah)

- b) If the value of R_S increased, what happen to Q-point?

(1 marks/ markah)

Titik operasi bagi transistor dikenali sebagai titik senyap (Q-point). Semua 3 konfigurasi asas bagi field effect transistor (FET) memerlukan Q-point untuk mendapatkan arus salir dan voltan get-sumber.

- a) Merujuk kepada **Rajah 1(a)**, lukiskan lengkung pindah menggunakan kaedah shorthand. Graf diberi di **Lampiran 1**.

b) Dengan menggunakan lengkuk universal yang diberi di Lampiran 2, tetapkan jumlah :

- i) arus salir, I_D
- ii) voltan get-sumber, V_{GS}

c) Kirakan :

- i) voltan salir-sumber, V_{DS}
- ii) voltan sumber, V_S
- iii) voltan salir, V_D
- iv) voltan salir-get, V_{DG}

d) Jika jumlah R_S meningkat, apa akan terjadi terhadap Q-point?

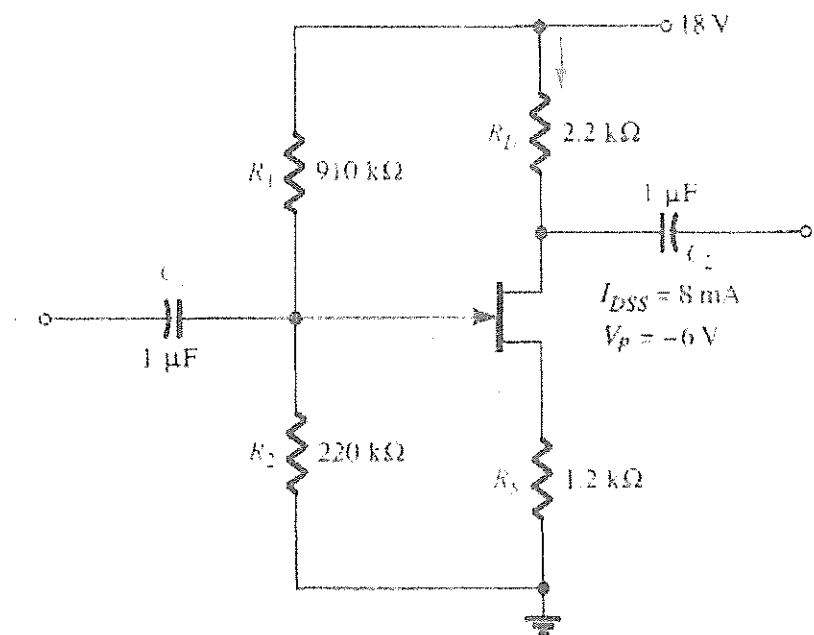


Figure 1(a) / Rajah 1(a)

QUESTION 2/ SOALAN 2

- a) Calculate transconductance, g_m , at $V_{GS} = 0V$ for a JFET having device parameters $I_{DSS} = 8mA$ and $V_p = -5V$.

(5 marks/ markah)

- b) Given $I_{DSS} = 6 mA$, $V_p = -6 V$, $g_{cs} = 40 \mu S$ and $V_{DSO} = -2 V$. Referring to Figure 2(b), determine .

- i) input impedance, Z_i
- ii) output impedance, Z_o .
- iii) voltage gain, A_v

(20 marks/ markah)

- a) Kirakan kealiran pindah, g_m pada $V_{GS} = 0V$ untuk JFET yang mempunyai parameter $I_{DSS} = 8 mA$ dan $V_p = -5 V$.

- b) Diberi $I_{DSS} = 6 mA$, $V_p = -6 V$, $g_{cs} = 40 \mu S$ dan $V_{DSO} = -2 V$. Merujuk kepada Rajah 2(b), tentukan :

- i) input impedance, Z_i
- ii) output impedance, Z_o
- iii) voltage gain, A_v .

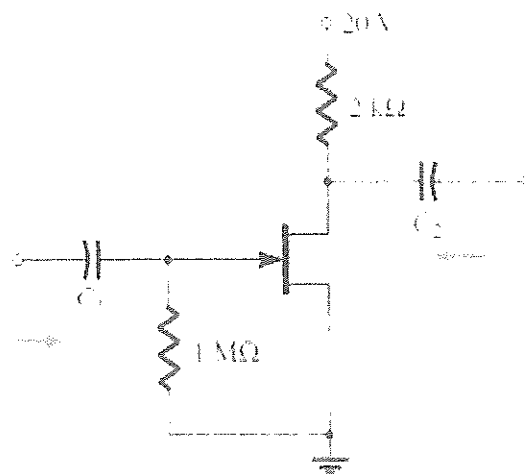


Figure 2(b) / Rajah 2(b)

QUESTION 3/ SOALAN 3

Differential operation involves the use of opposite-polarity inputs. Common-mode operation involves the use of the same-polarity inputs. Common-mode rejection ratio (CMRR) compares the gain for differential inputs to that for common inputs

- a) Calculate the common-mode rejection ratio, CMRR (in dB) for the circuit measurements of $V_1 = 200\mu\text{V}$, $V_2 = 140\mu\text{V}$, $V_o = 120\text{mV}$, $V_c = 1\text{mV}$ and $V_d = 20\mu\text{V}$.

(8 marks/ markah)

- b) Calculate the output voltage for Figure 3(b) below. Given V_1 (rms) = 40mV and V_2 (rms) = 20mV.

(5 marks/ markah)

- c) Referring to the operational amplifier circuit in Figure 3(c), calculate the output voltages V_2 and V_3 . Given $V_1 = 0.2\text{V}$.

(12 marks/ markah)

Operasi pembezaan melibatkan penggunaan masukan bertlainan kekutuban. Operasi mod biasa melibatkan penggunaan masukan kekutuban sama. Nisbah penolakan mod biasa (CMRR) membandingkan gandaan untuk masukan pembezaan terhadap masukan biasa.

- a) Kirakan CMRR (dalam dB) bagi ukuran litar $V_{11} = 200 \mu\text{V}$, $V_{12} = 140 \mu\text{V}$, $V_o = 120 \text{mV}$, $V_c = 1 \text{mV}$, dan $V_d = 20 \mu\text{V}$.

- b) Kirakan voltan keluaran bagi Rajah 3(b) di bawah. Diberi V_1 (rms) = 40 mV dan V_2 (rms) = 20 mV.

- c) Merujuk kepada litar penguat kendalian dalam Rajah 3(c), kirakan voltan keluaran V_2 dan V_3 . Diberi $V_1 = 0.2 \text{V}$.

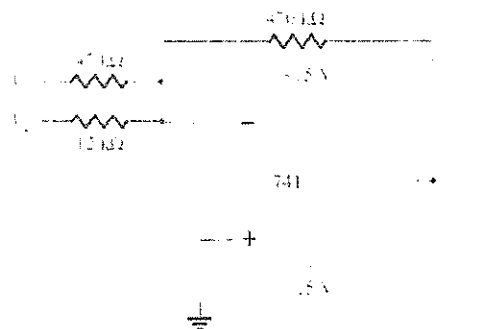


Figure 3(b) / Rajah 3(b)

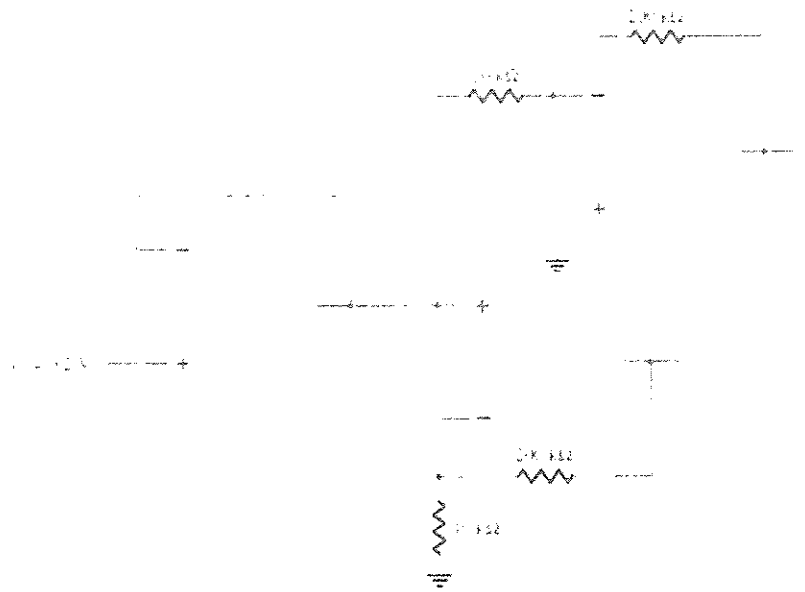


Figure 3(c) / Rajah 3(c)

QUESTION 4/ SOALAN 4

Power Amplifier can be categorized into several classes. Each class will be different in their operating cycle and efficiency. Based on Class B Power Amplifier circuit in Figure 4, calculate:

- the peak input voltage, $V_{i(p)}$.
- the peak voltage across the load, $V_{L(p)}$.
- the peak load current, $I_{L(p)}$.
- the direct current, I_{DC} .
- the input power, $P_{in(dc)}$.
- the output power, $P_{o(ac)}$.
- the power dissipated by each output transistor, P_D .
- the circuit efficiency, $\% \eta$.
- the maximum input power, $P_{in(max)}$.
- the maximum output power, $P_{o(max)}$.

(25 marks/ markah)

Penguat Kuasa boleh dikategorikan kepada beberapa kelas. Setiap kelas akan berbeza dari segi kitaran operasi dan kecekapan. Berdasarkan litar Penguat Kuasa Kelas B dalam Rajah 4, kirakan

- voltan puncak merentasi masukan, $V_{i(p)}$.
- voltan puncak merentasi beban, $V_{L(p)}$.
- arus puncak pada beban, $I_{L(p)}$.
- arus terus, I_{DC} .
- kuasa masukan, $P_{in(dc)}$.
- kuasa keluaran, $P_{o(ac)}$.
- kuasa yang dilesapkan oleh setiap keluaran transistor, P_D .
- kecekapan litar, $\% \eta$.
- kuasa masukan maksimum $P_{in(max)}$.
- kuasa keluaran maksimum $P_{o(max)}$.

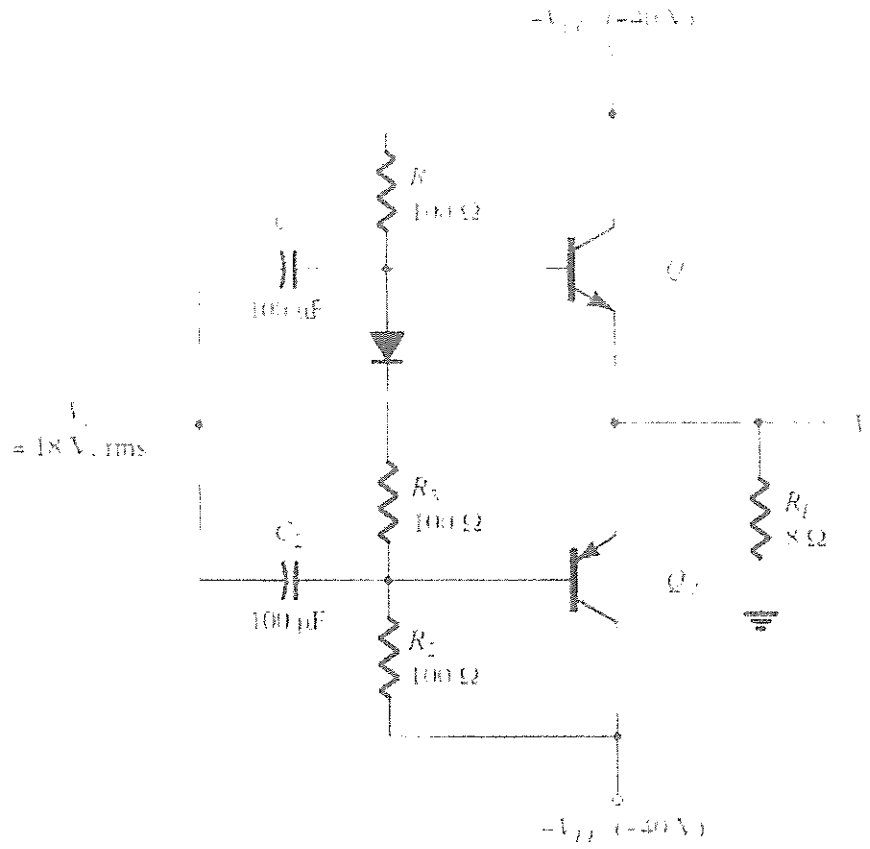


Figure 4 / Rajah 4

[100 MARKS/ MARKAH]

END OF QUESTION PAPER/ KERTAS SOALAN TAMAT

Attachment 1 / *Lampiran 1*


Name / *Nama* :

Lecturer / *Pensyarah* :

Attachment 2 / Lampiran 2

Name / Nama :

Lecturer / Pensyarah :

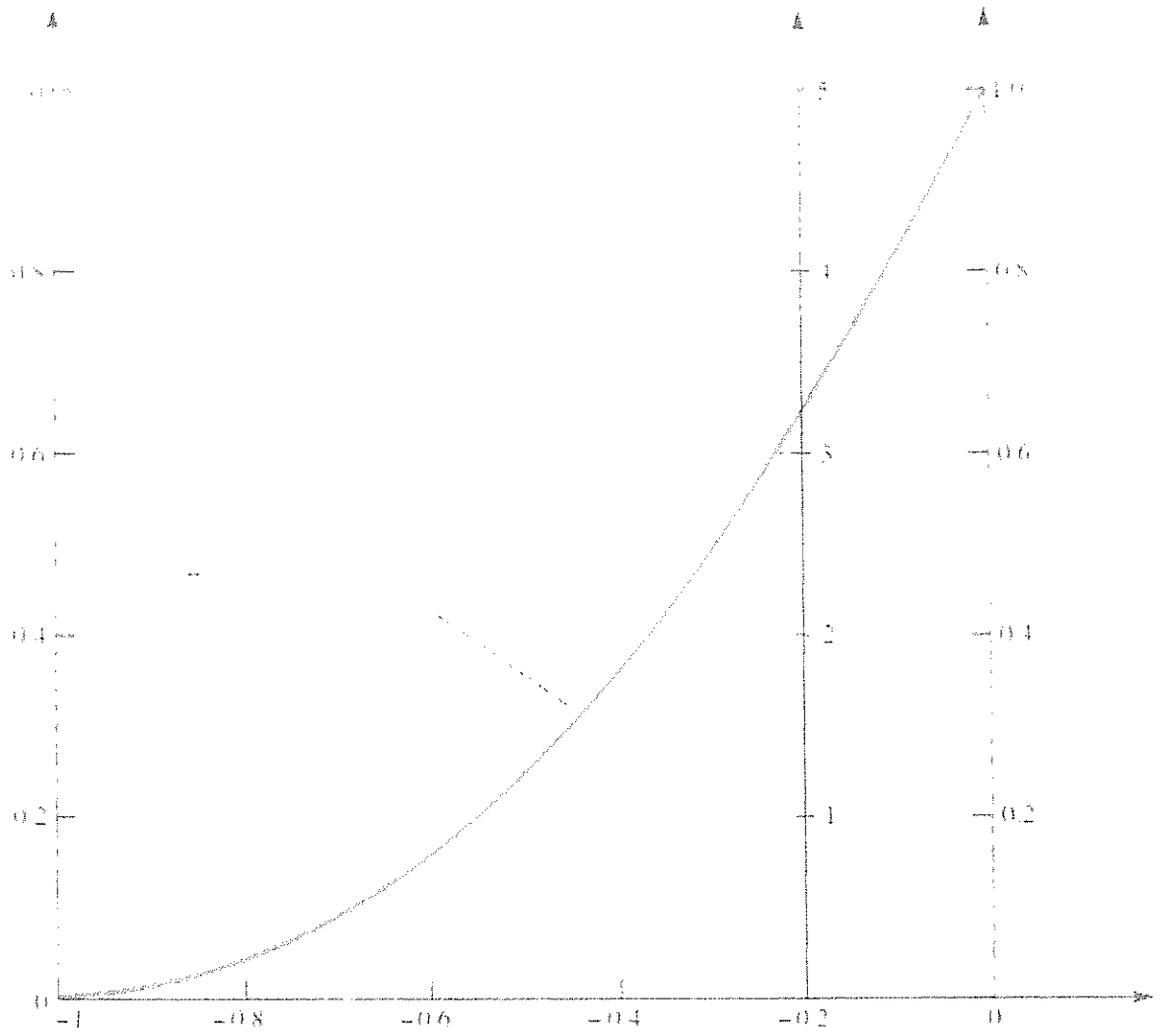

Attachment 3 / Lampiran 3

Formula / Rumus

JFET

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 \Rightarrow \sqrt{\frac{I_D}{I_{DSS}}} = 1 - \frac{V_{GS}}{V_{GS(off)}} \Rightarrow \frac{V_{GS}}{V_{GS(off)}} = 1 - \sqrt{\frac{I_D}{I_{DSS}}}$$

$$V_{GS} = V_{GS(off)} \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right)$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

$$= \frac{I_{DSS}}{4} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

MOSFET enhancement

$$I_D = k(V_{GS} - V_T)^2$$

$$I_D = \frac{k_{n0}}{2} (V_{GS} - V_T)^2$$

JFETs/depletion-type MOSFETs

$$\text{Fixed-bias configuration: } V_{GS} = -V_{GS(off)} = V_{GS}$$

$$\text{Self-bias configuration: } V_{GS} = -I_D R_S$$

$$\text{Voltage-divider biasing: } V_{GS} = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$V_{GS} = V_{GS} - I_D R_S$$

Enhancement-type MOSFETs

$$\text{Feedback biasing: } V_{DS} = V_{GS}$$

$$V_{GS} = V_{DD} - I_D R_D$$

$$\text{Voltage-divider biasing: } V_{GS} = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$V_{GS} = V_{GS} - I_D R_S$$

$$g_m = \mu_f = \frac{\Delta I_D}{\Delta V_{GS}}$$

$$g_{m0} = \frac{\Delta I_{DSS}}{V_T}$$

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_T} \right]$$

$$g_m = g_{m0} \sqrt{\frac{I_D}{I_{DSS}}}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{\Delta V_{DS}}{\Delta I_D} \Big|_{V_{GS} = \text{constant}}$$

$$\text{Slew rate (SR)} = \frac{\Delta V_o}{\Delta t} = \frac{1}{R_1 C}$$

Inverting amplifier:

$$V_o = -\frac{R_2}{R_1} V_i$$

Voltage summing amplifier:

$$V_o = -\left(\frac{R_2}{R_1} V_1 + \frac{R_2}{R_3} V_2 \right)$$

Current summing:

$$V_o = -V_i$$

Summing amplifier:

$$V_o = -\left(\frac{R_2}{R_1} V_1 + \frac{R_2}{R_2} V_2 + \frac{R_2}{R_3} V_3 \right)$$

Integrator amplifier:

$$V_o(t) = -\frac{1}{R_1 C} \int V_i(t) dt$$

$$\text{Slew rate (SR)} = \frac{\Delta V_o}{\Delta t} = V_{\text{max}}$$

Constant-gain multiplier:

$$V_o = -\frac{R_2}{R_1} V_i$$

Non-inverting constant-gain multiplier:

$$V_o = \left(1 + \frac{R_2}{R_1} \right) V_i$$

Voltage summing amplifier:

$$V_o = -\frac{R_2}{R_1} V_1 + \frac{R_2}{R_2} V_2 + \frac{R_2}{R_3} V_3$$

Voltage buffer:

$$V_o = V_i$$

Low-pass active filter cutoff frequency:

$$f_{\text{cut}} = \frac{1}{2\pi R C}$$

High-pass active filter cutoff frequency:

$$f_{\text{cut}} = \frac{1}{2\pi R C}$$

$$\begin{aligned}
 I_{\text{rms}} &= \frac{1}{\sqrt{2}} I_m \\
 P_{\text{avg}} &= I_{\text{rms}}^2 R = \left(\frac{1}{\sqrt{2}} I_m\right)^2 R \\
 &= \frac{1}{2} I_m^2 R \\
 &= \frac{1}{2} \left(\frac{V_m}{Z}\right)^2 R \\
 I_{\text{avg}} &= \frac{V_{\text{eff}} I_{\text{eff}} \cos \theta}{S} \\
 &= \frac{V_{\text{eff}}^2 \cos \theta}{S} \\
 &= \frac{V_{\text{eff}}^2 \cos \theta}{V_{\text{eff}} I_{\text{eff}}} \\
 \cos \theta &= \frac{P_{\text{avg}}}{P_{\text{eff}}} = 100\%
 \end{aligned}$$

Transformer action

$$\begin{aligned}
 \frac{V_2}{V_1} &= \frac{N_2}{N_1} \\
 \frac{I_2}{I_1} &= \frac{N_1}{N_2}
 \end{aligned}$$

$$I_{\text{dc}} = \frac{2}{\pi} I_p$$

$$P_{\text{avg}} = V_{\text{eff}} \left(\frac{2}{\pi} I_p \right)$$

$$P_{\text{avg}} = \frac{V_{\text{eff}} I_p}{R_1}$$

$$\text{maximum } P_{\text{avg}} = \frac{V_{\text{eff}}^2}{2R_1}$$

$$\text{maximum } P_{\text{avg}} = V_{\text{eff}} (\text{maximum } I_{\text{dc}}) = V_{\text{eff}} \left(\frac{2V_{\text{eff}}}{\pi R_1} \right) = \frac{2V_{\text{eff}}^2}{\pi R_1}$$

$$\text{maximum } P_{\text{avg}} = \frac{2V_{\text{eff}}^2}{\pi^2 R_1}$$

Harmonic distortion

$$\% \text{ harmonic distortion} = \% D_n = \frac{|A_n|}{|A_1|} \times 100\%$$

Heat sink

$$P_{\text{total}} = P_{\text{dc}} + P_{\text{ac}} + P_{\text{loss}}$$

·
·
·

⌋

⌋

