



---

**KOLEJ YAYASAN PELAJARAN JOHOR  
FINAL EXAMINATION**

---

**COURSE NAME : ELECTRONICS 2**  
**COURSE CODE : DKE 2073**  
**EXAMINATION : OCTOBER 2019**  
**DURATION : 2 HOURS 30 MINUTES**

---

**INSTRUCTION TO CANDIDATES /  
ARAHAN KEPADA CALON**

1. This examination paper consists of **ONE (1)** part : / PART A (100 Marks) /  
*Kertas soalan ini mengandungi **SATU (1)** bahagian: BAHAGIAN A (100 Markah)*
  
2. Candidates are not allowed to bring any material to examination room except with the permission from the invigilator. The graph paper was attached at the back question paper. /  
*Calon tidak dibenarkan untuk membawa sebarang bahan/nota ke bilik peperiksaan tanpa arahan/kebenaran daripada pengawas. Kertas graf dilampirkan di belakang kertas soalan peperiksaan.*
  
3. Please check to make sure that this examination pack consist of: /  
Pastikan kertas soalan peperiksaan ini mengandungi:
  - i. Question paper /  
Kertas soalan
  
  - ii. Answer booklet /  
Buku jawapan

---

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /  
JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIBERITAHU**

---

This examination paper consists of **8** printed pages including front page  
*Kertas soalan ini mengandungi **8** muka surat termasuk kulit hadapan*




This part contains of **FOUR(4)** questions. Answer **ALL** questions in Answer Booklet.  
*Bahagian ini mengandungi EMPAT (4) soalan. Jawab SEMUA soalan di dalam buku jawapan yang disediakan.*

**QUESTION 1/ SOALAN 1**

- a. Determine the  $I_{DQ}$  and  $V_{GSQ}$  for **Figure Q1 (a)** below using transfer curve technique. The graph is given in the Attachment 1.

*Tentukan  $I_{DQ}$  dan  $V_{GSQ}$  untuk **Rajah Q1 (a)** di bawah menggunakan teknik lengkung pindah. Graf diberi di Lampiran 1.*

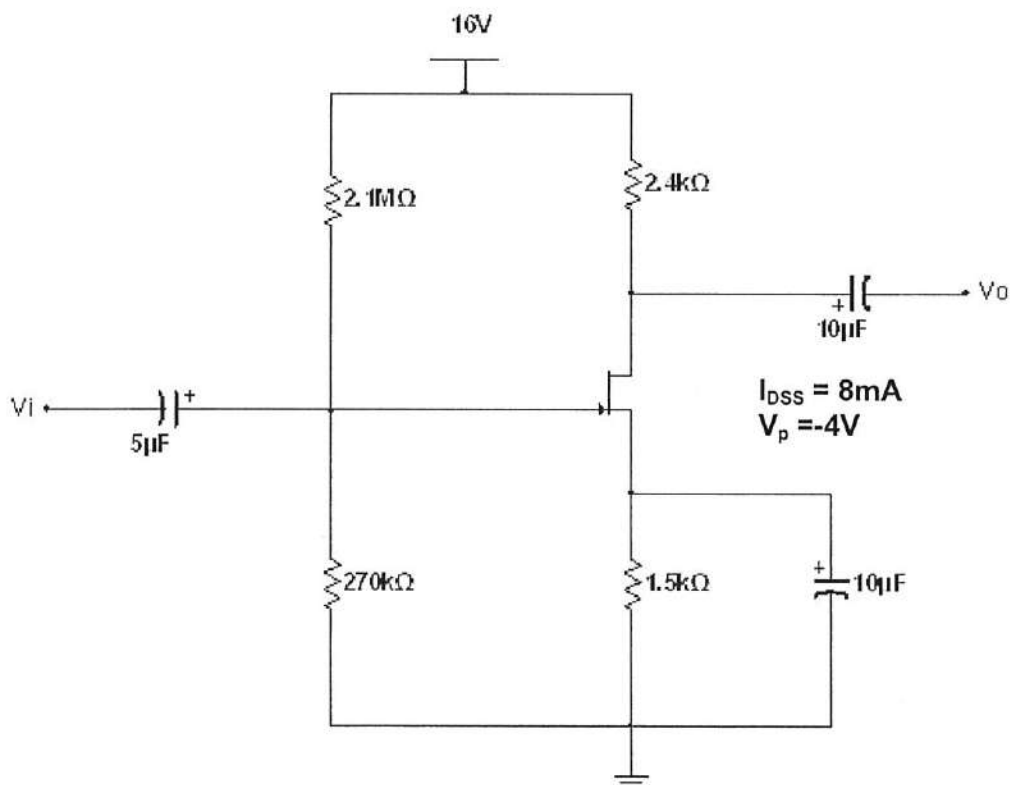

**Figure Q1 (a)/ Rajah Q1 (a)**

**(15 marks/markah)**

- b. Referring to **Figure Q1 (a)**, calculate the values of  $V_D$ ,  $V_S$ , and  $V_{DS}$ .

*Merujuk pada **Rajah Q1 (a)**, kirakan nilai bagi  $V_D$ ,  $V_S$ , dan  $V_{DS}$ .*

**(10 marks/markah)**

QUESTION 2/ SOALAN 2

- a. Referring to **Figure Q2 (a)**, determine  $g_m$ ,  $r_d$ ,  $z_i$ ,  $z_o$ , and  $A_v$ .  
 Given  $I_{DSS} = 10\text{mA}$ ,  $V_p = -8\text{V}$ ,  $V_{GSQ} = -2\text{V}$ ,  $I_{DQ} = 5.625\text{mA}$ ,  $y_{os} = 40\mu\text{S}$ .

Merujuk pada **Rajah Q2 (a)**, tentukan nilai bagi  $g_m$ ,  $r_d$ ,  $z_i$ ,  $z_o$ , dan  $A_v$ .  
 Diberi  $I_{DSS} = 10\text{mA}$ ,  $V_p = -8\text{V}$ ,  $V_{GSQ} = -2\text{V}$ ,  $I_{DQ} = 5.625\text{mA}$ ,  $y_{os} = 40\mu\text{S}$ .


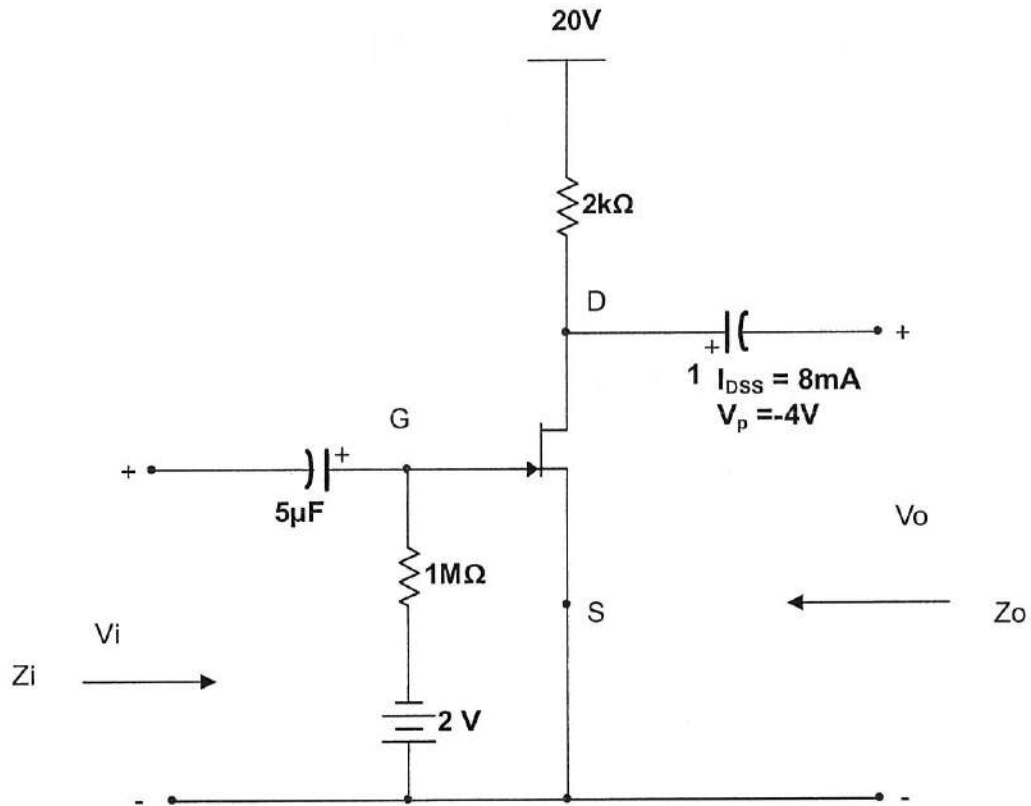


Figure Q2 (a)/ Rajah Q2 (a)

(18 marks/markah)

- b. Determine  $V_{DS}$  value for the network of **Figure Q2 (b)** below.

*Tentukan nilai  $V_{DS}$  bagi **Rajah Q2 (b)** di bawah.*

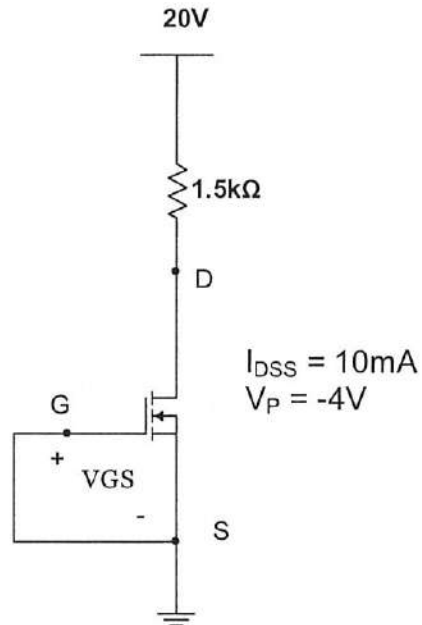

**Figure Q2 (b)/ Rajah Q2 (b)**

**(7 marks/markah)**

**QUESTION 3/ SOALAN 3**

- a. Calculate the CMRR (in dB) for the circuit measurements of  $V_d = 1\text{mV}$ ,  $V_o = 12\text{mV}$  and  $V_c = 1\text{mV}$ ,  $V_o = 20\mu\text{V}$ .

*Kirakan CMRR (dalam dB) bagi litar pengukuran  $V_d = 1\text{mV}$ ,  $V_o = 12\text{mV}$  and  $V_c = 1\text{mV}$ ,  $V_o = 20\mu\text{V}$ .*

**(8 marks/markah)**

- b. Calculate the output voltage for **Figure Q3 (b)** below.  
Given  $V_1 = 0.05 \sin 1000t$  V and  $V_2 = 0.01 \sin 3000t$  V.

*Kirakan voltan keluaran bagi Rajah Q3 (b) di bawah.*

*Diberi  $V_1 = 0.05 \sin 1000t$  V dan  $V_2 = 0.01 \sin 3000t$  V.*

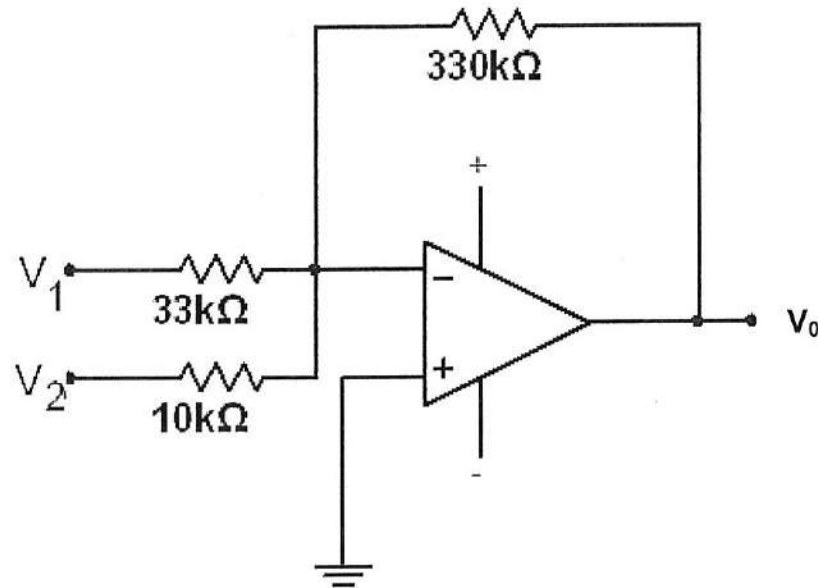


Figure Q3 (b)/ Rajah Q3 (b)

(5 marks/markah)

- c. Referring to the op-amp circuit in **Figure Q3 (c)** below, calculate the value of  $V_{o1}$ ,  $V_{o2}$  and  $V_{o3}$ . Given  $V_1 = 1$  V,  $V_2 = 2$  V and  $V_3 = -2.4$  V.

*Merujuk kepada litar penguat kendalian dalam **Rajah Q3 (c)** di bawah, kirakan nilai bagi  $V_{o1}$ ,  $V_{o2}$  and  $V_{o3}$ . Diberi  $V_1 = 1$  V,  $V_2 = 2$  V dan  $V_3 = -2.4$  V.*

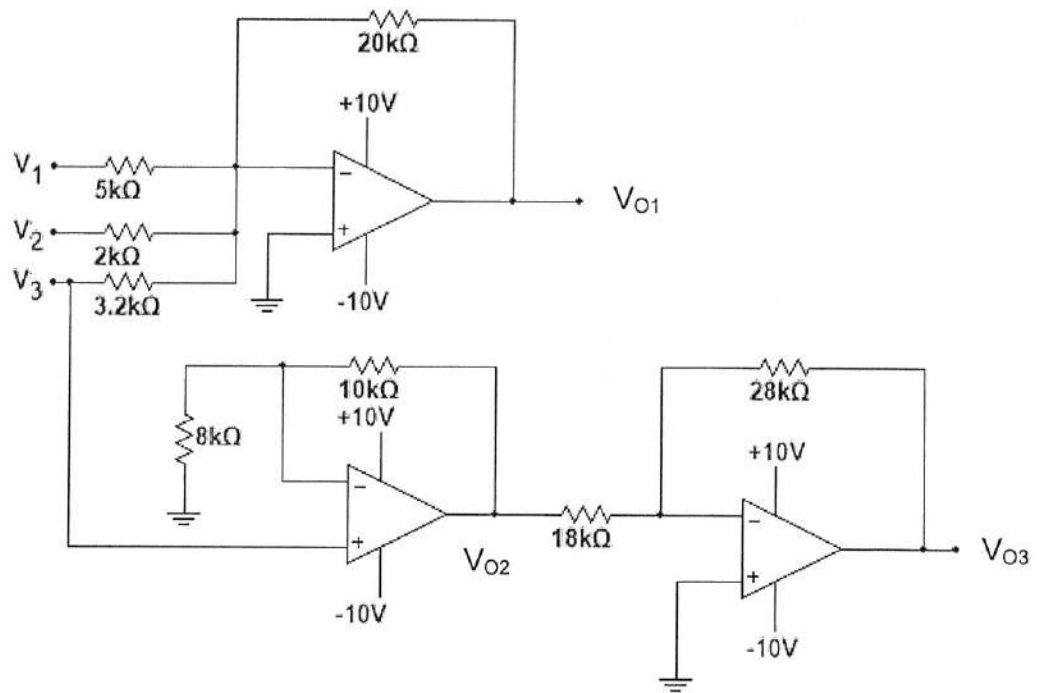


Figure Q3 (c)/ Rajah Q3 (c)

(12 marks/markah)

## QUESTION 4/ SOALAN 4

Figure Q4 (a) is Class B Power Amplifier. Calculate:

- i. the peak input voltage,  $V_i(p)$
- ii. the peak voltage across the load,  $V_L(p)$
- iii. the peak load current,  $I_L(p)$
- iv. the direct current,  $I_{DC}$
- v. the input power,  $P_{in(dc)}$
- vi. the output power,  $P_{o(ac)}$
- vii. the power dissipated by each output transistor,  $P_Q$ ,
- viii. the circuit efficiency,  $\% \eta$
- ix. the maximum input power,  $P_{in(max)}$  and
- x. the maximum output power,  $P_{o(max)}$

**Rajah Q4 (a)** ialah Penguat Kuasa Kelas B. Kirakan:-

- i. voltan puncak pada masukan,  $V_i(p)$
- ii. voltan puncak pada beban,  $V_L(p)$
- iii. arus puncak pada beban,  $I_L(p)$
- iv. arus terus,  $I_{DC}$
- v. kuasa masukan,  $P_{in(dc)}$
- vi. kuasa keluaran,  $P_{o(ac)}$
- vii. kuasa yang dilesapkan oleh transistor pada keluaran,  $P_Q$
- viii. kecekapan litar,  $\% \eta$
- ix. kuasa masukan maksimum  $P_{in(max)}$  dan
- x. kuasa keluaran maksimum,  $P_{o(max)}$

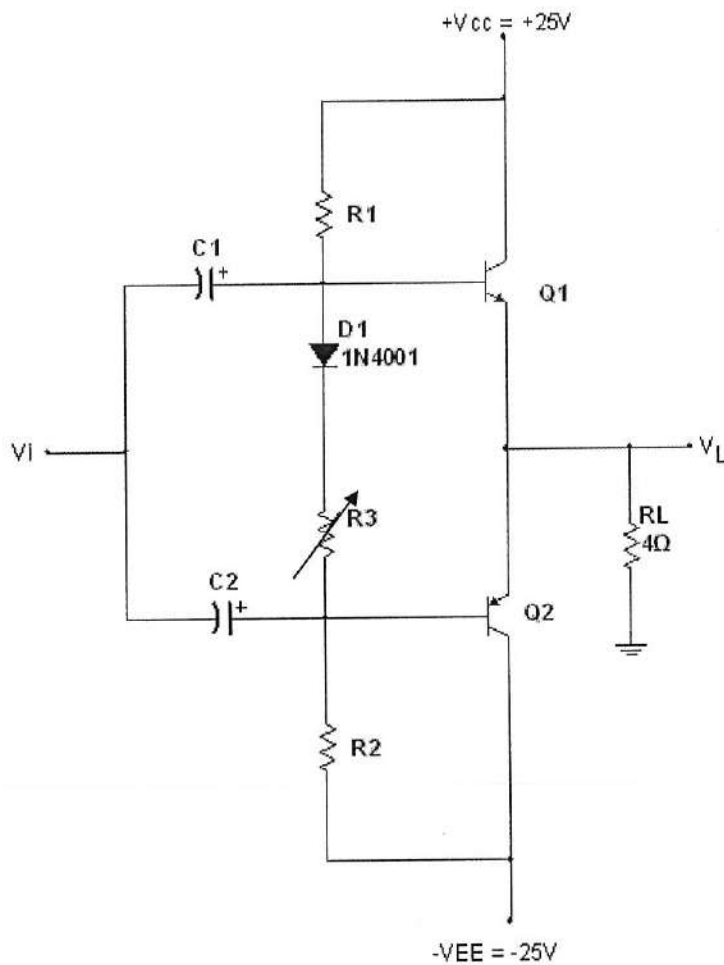


Figure Q4 (a)/ Rajah Q4 (a)

(25 marks/markah)

[100 MARKS / MARKAH]

END OF QUESTION PAPER/KERTAS SOALAN TAMAT





