



**KOLEJ YAYASAN PELAJARAN JOHOR
FINAL EXAMINATION**

COURSE NAME : INDUSTRIAL ELECTRONICS
COURSE CODE : DEE 2203
EXAMINATION : JUNE 2024
DURATION : 2 HOURS 30 MINUTES

**INSTRUCTION TO CANDIDATES /
ARAHAN KEPADA CALON**

1. This examination paper consists of **ONE (1)** part: / **Kertas soalan ini mengandungi SATU (1) bahagian:** PART A (100 Marks) / **BAHAGIAN A (100 Markah)**
2. Candidates are not allowed to bring any material to examination room except with the permission from the invigilator. The formula was attached at the back question paper. / **Calon tidak dibenarkan untuk membawa sebarang bahan/nota ke bilik peperiksaan tanpa kebenaran daripada pengawas. Rumus dilampirkan di belakang kertas soalan peperiksaan.**
3. Please check to make sure that this examination pack consists of: / **Pastikan kertas soalan peperiksaan ini mengandungi:**
 - i. Question Paper / **Kertas Soalan.**
 - ii. Answering Booklet / **Buku Jawapan.**
 - iii. Attachment / **Lampiran.**

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALANINI SEHINGGA DIBERITAHU**

This examination paper consists of **14** printed pages including front page
Kertas soalan ini mengandungi 14 halaman bercetak termasuk kulit hadapan

PART A/ BAHAGIAN A

This part consists of **FIVE (5)** questions. Answer **ALL** the questions in an answering booklet.

Bahagian ini mengandungi LIMA (5) soalan. Jawab SEMUA soalan dalam buku jawapan.

QUESTION 1/ SOALAN 1

Referring to the circuit in **Figure Q1**. Given $P_{z\max}=0.5W$ and $I_{z\min}=2mA$. Calculate:

- a. the output voltage, V_o range by changing the value of resistor, R_1 .

(8 marks/ markah)

- b. the maximum power dissipated by the transistor, Q_1 if resistor, R_1 is set at maximum value.

(6 marks/ markah)

- c. the range of allowable resistor, R_S to ensure the Zener diode is always in the breakdown region.

(6 marks/ markah)

Berdasarkan litar dalam Rajah Q1. Diberi $P_{z\max}=0.5W$ dan $I_{z\min}=2mA$. Kirakan:

- a. julat voltan keluaran, V_o dengan menukar nilai perintang, R_1 .

- b. kuasa maksimum yang dilesapkan oleh transistor, Q_1 jika perintang, R_1 ditetapkan pada nilai maksimum.

- c. julat perintang, R_S yang dibenarkan untuk memastikan diod Zener sentiasa berada dalam kawasan pecah tebat.

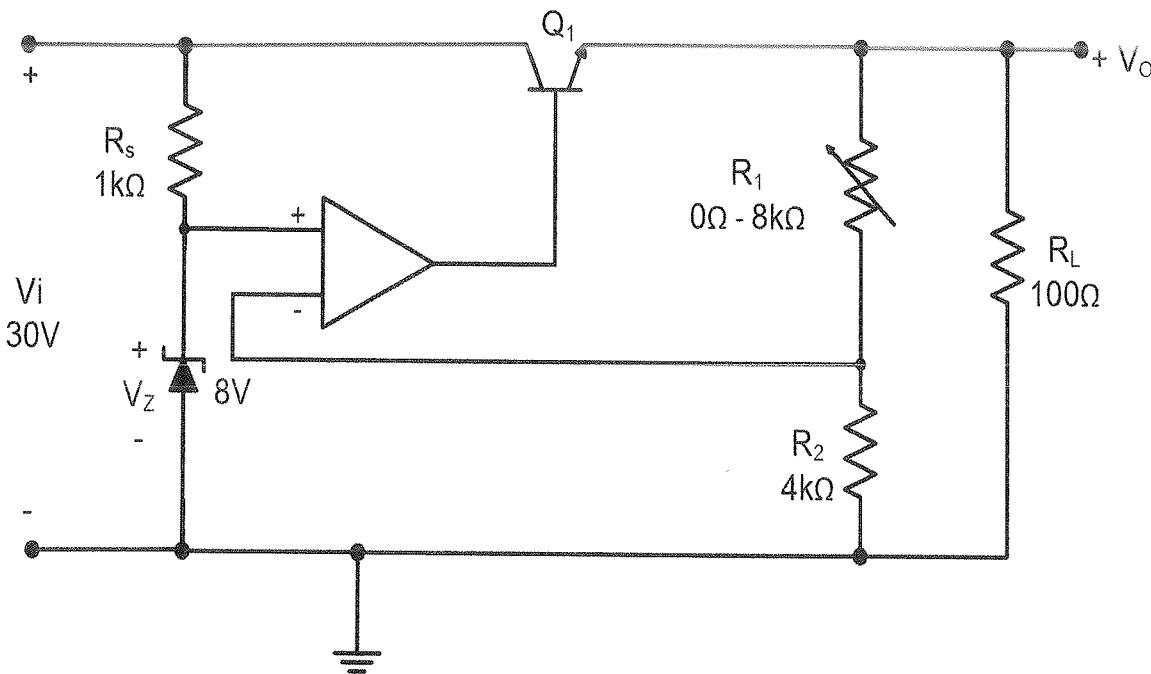


Figure Q1/ Rajah Q1

QUESTION 2/ SOALAN 2

Referring to the voltage-shunt feedback connection in Figure Q2.

- a. Prove that closed loop gain with feedback, A_f is equal to:

$$A_f = \frac{V_o}{I_s} = \frac{A}{(1 + A\beta)}$$

(8 marks/ markah)

- b. Determine the gain value, A_f

(2 marks/ markah)

- c. Calculate the value of input impedance, Z_{iF} and the value of output impedance, Z_{oF} .

(10 marks/ markah)

Given the gain value, $A=100$ and the feedback network, $\beta=0.1$.

Merujuk sambungan suapbalik voltan-pirau dalam **Rajah Q2**.

- a. Buktikan bahawa gandaan gelung tertutup dengan suapbalik, A_f adalah sama dengan:

$$A_f = \frac{V_o}{I_s} = \frac{A}{(1 + A\beta)}$$

- b. Tentukan nilai gandaan, A_f .

- c. Kira nilai galangan masukan, Z_{iF} dan nilai galangan keluaran, Z_{oF} .

Diberi nilai gandaan, $A=100$ dan rangkaian suapbalik, $\beta=0.1$.

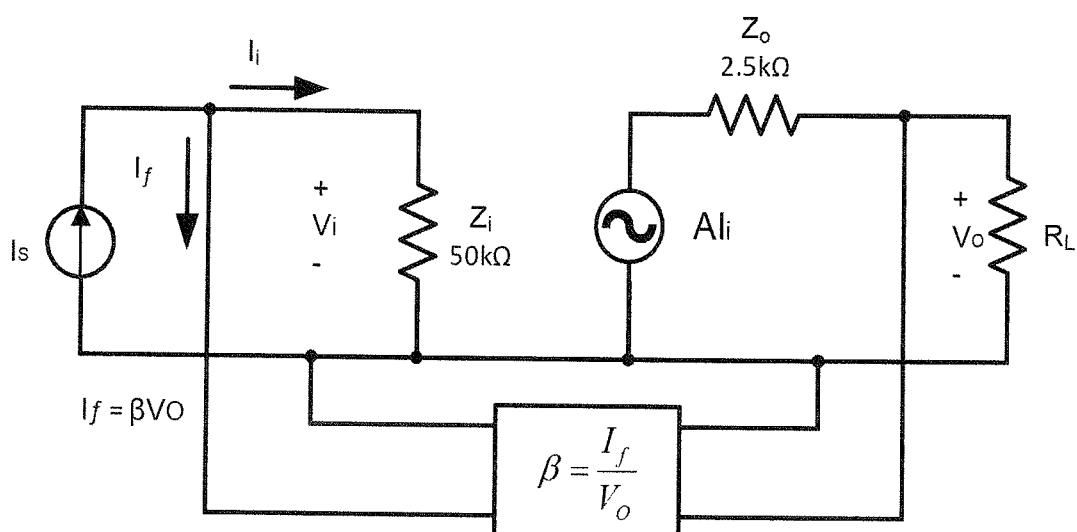


Figure Q2/ Rajah Q2

QUESTION 3 / SOALAN 3

Referring to Figure Q3.

- a. Show that oscillation frequency for oscillator is:

$$f_o = \frac{1}{2\pi \sqrt{L(\frac{C_1 C_2}{C_1 + C_2})}}$$

(8 marks / markah)

- b. Prove the equation of an amplifier gain is:

$$A = \frac{V_o}{V_f} = -\frac{C_1}{C_2}$$

when oscillation occurs.

(6 marks / markah)

- c. Calculate the oscillation frequency, f_o , the amplifier gain, A and the feedback gain, β while the oscillation is maintained.

(6 marks / markah)

Merujuk pada Rajah Q3.

- a. Tunjukkan bahawa frekuensi ayunan bagi pengayun adalah:

$$f_o = \frac{1}{2\pi \sqrt{L(\frac{C_1 C_2}{C_1 + C_2})}}$$

- b. Buktikan persamaan gandaan penguat adalah:

$$A = \frac{V_o}{V_f} = -\frac{C_1}{C_2}$$

ketika ayunan berlaku.

c. Kira frekuensi ayunan, f_0 , gandaan penguat, A dan gandaan suapbalik, β semasa pengayunan dikelaskan.

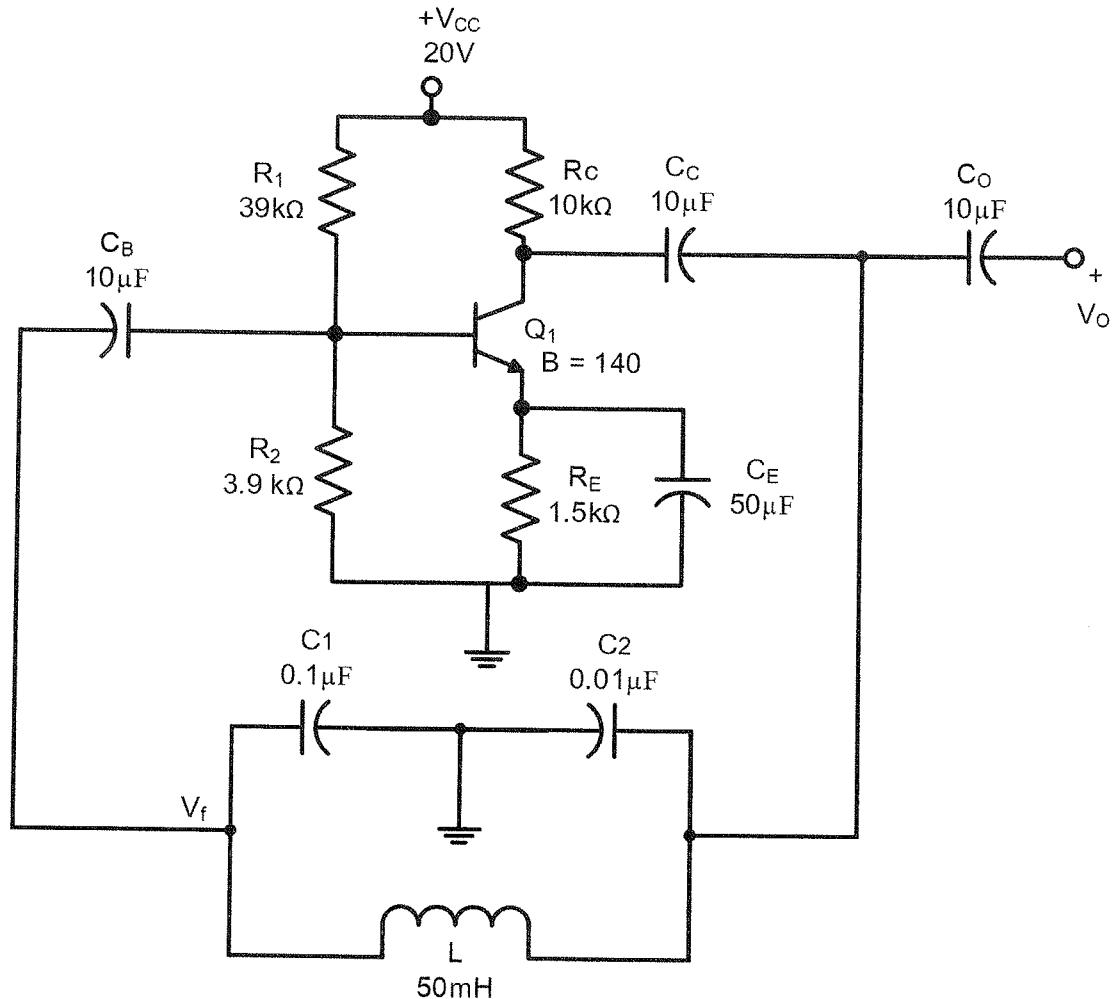


Figure Q3/ Rajah Q3

QUESTION 4/ SOALAN 4

Referring to Figure Q4 is astable multivibrator circuit using 555 timers which generates a square wave frequency, $f = 2\text{kHz}$ and the duty cycle is 66%. Given the supply voltage, $+V_{CC} = +18V$ and $I_{C(\min)} = 1\text{mA}$. Determine:

- a. period T, high duration, T_H , low duration, T_L and pulse width, Pw .

(8 marks/ markah)

b. capacitor value, C_A .

(6 marks/ markah)

c. resistor value, R_A and R_B .

(6 marks/ markah)

Berdasarkan **Rajah Q4** ialah litar pemberbilang getar tak stabil dengan menggunakan pemasa 555 yang menghasilkan gelombang segiempat yang berfrekuensi, $f = 2\text{kHz}$ dan kitar tugas ialah 66%. Diberi voltan bekalan, $+V_{CC} = +18\text{V}$ dan $I_C(\text{min}) = 1\text{mA}$. Tentukan:

a. tempoh, T , tempoh tinggi, T_H , tempoh rendah, T_L dan lebar denyut, P_W .

b. nilai pemuat, C_A .

c. nilai perintang, R_A dan R_B .

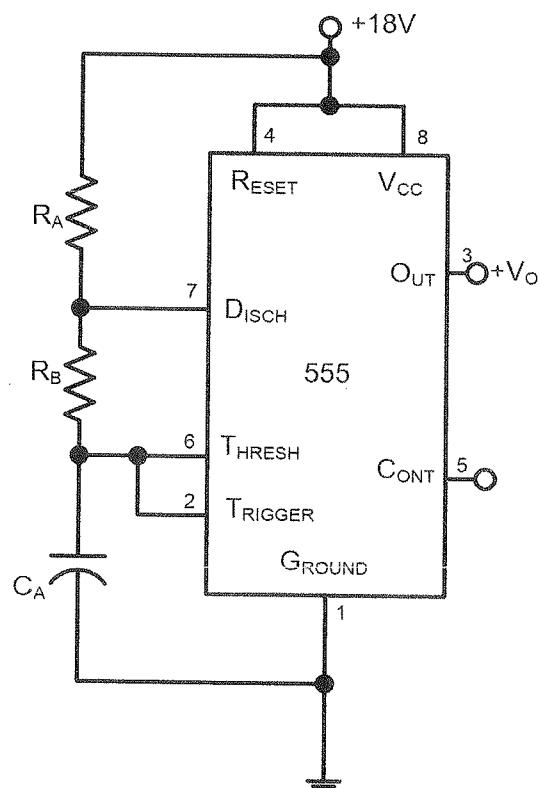


Figure Q4/ Rajah Q4

QUESTION 5/ SOALAN 5

Referring to **Figure Q5**, determine the following values:

- a. current I_1 , I_2 and I_{LED} .

(12 marks/ markah)

- b. voltage, V_{CE} .

(3 marks/ markah)

- c. power dissipated by the transistor, Q.

(5 marks/ markah)

Merujuk kepada **Rajah Q5**, tentukan nilai berikut:

- a. arus, I_1 , I_2 dan I_{LED} .

- b. voltan, V_{CE} .

- c. Kuasa yang dilesapkan oleh transistor, Q.

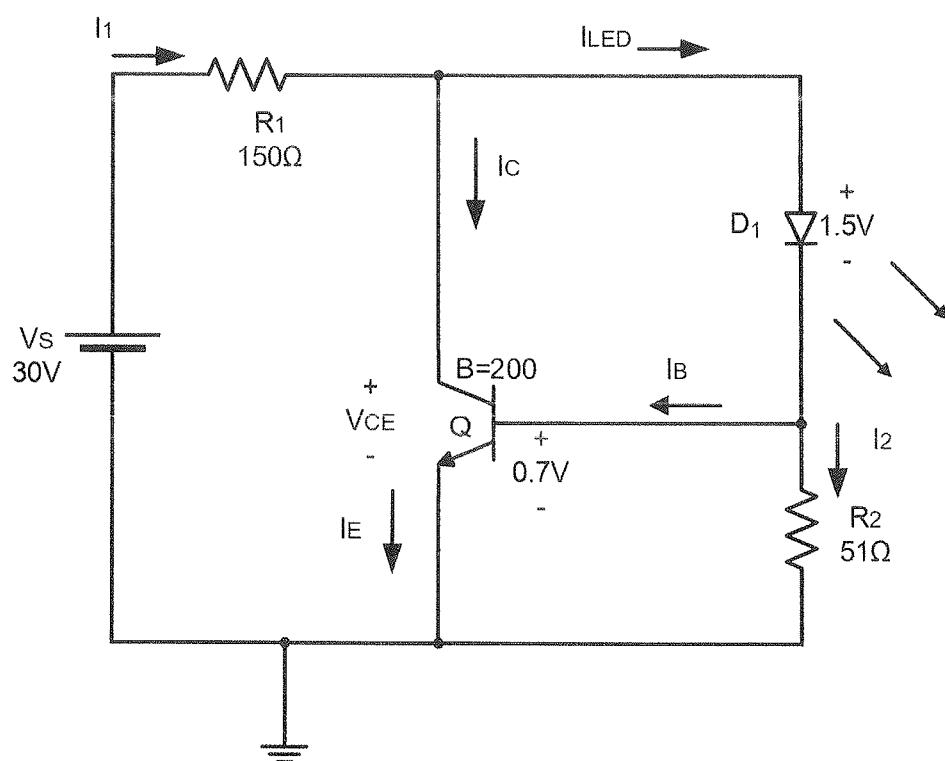


Figure Q5/ Rajah Q5

[100 MARKS/ 100 MARKAH]

END OF QUESTION PAPER/ KERTAS SOALAN TAMAT

Attachment/ Lampiran

Ripple factor of rectifier.

$$r = \frac{\text{rms value of ac component of signal}}{\text{average value of signal}}$$

$$r = \frac{V_r(\text{rms})}{V_{dc}}$$

Root mean square (rms) value of the total voltage rectified signal.

$$V_r(\text{rms}) = 0.385V_m \text{ (half-wave)}$$

$$V_r(\text{rms}) = 0.308V_m \text{ (full-wave)}$$

Ripple voltage of capacitor filter section.

$$V_{dc} = V_m - \frac{V_r(p-p)}{2}$$

Ripple factor of filter section.

$$r = \frac{1}{2\sqrt{3}R_L fC} \text{ (half-wave)}$$

$$r = \frac{1}{4\sqrt{3}R_L fC} \text{ (full-wave)}$$

DC operation of RC filter section.

$$V'_{dc} = \frac{R_L}{R+R_L} V_{dc}$$

AC operation of RC filter section.

$$V'_r(\text{rms}) = \frac{X_{c2}}{R+X_{c2}} V_r(\text{rms})$$

Load regulation.

$$\%L.R = \frac{\frac{V_{o(NL)} - V_{o(FL)}}{V_{o(FL)}} \times 100\%}{I_{L(FL)} - I_{L(NL)}}$$

Line regulation.

$$\%L.R = \frac{\frac{V_{o(ORIGINAL)} - V_{o(NEW)}}{V_{o(ORIGINAL)}} \times 100\%}{V_{i(ORIGINAL)} - V_{i(NEW)}}$$

Percent efficiency of the power supply.

$$\% \eta = \frac{P_L}{P_i} \times 100\%$$

Ideal op-amp.

$$V^+ = V^-$$

$$I^+ = I^- = 0A$$

Upper trigger point of square wave signal generator.

$$V_{UTP} = \frac{R_3}{(R_2 + R_3)} \times (+V_{cc})$$

Lower trigger point of square wave signal generator.

$$V_{LTP} = \frac{R_3}{(R_2 + R_3)} \times (-V_{cc})$$

The time period of square wave signal generator.

$$T_H = R_1 C \ell_n \left(\frac{V_{cc} - V_{LTP}}{V_{cc} - V_{UTP}} \right)$$

$$T_L = R_1 C \ell_n \left(\frac{-V_{cc} - V_{UTP}}{-V_{cc} - V_{LTP}} \right)$$

Output wave frequency of square wave signal generator.

$$f_o = \frac{1}{T_H + T_L}$$

Pulse width of monostable multivibrator.

$$PW = RC \ell_n \left(\frac{V_{cc} - 0}{V_{cc} - \frac{2}{3}V_{cc}} \right)$$

$$PW = 1.1RC$$

The period of the astable multivibrator.

$$T_H = \tau_1 \ell_n \left(\frac{V_{cc} - \frac{1}{3}V_{cc}}{V_{cc} - \frac{2}{3}V_{cc}} \right)$$

$$T_H = 0.693(R_A + R_B)C_1$$

$$T_L = \tau_2 \ell_n \left(\frac{0 - \frac{2}{3}V_{cc}}{0 - \frac{1}{3}V_{cc}} \right)$$

$$T_L = 0.693(R_B)C_1$$

$$T = 0.693(R_A + 2R_B)C_1$$

The oscillation frequency of square wave astable multivibrator.

$$f_o = \frac{1}{0.693(R_A + 2R_B)C_1}$$

Duty cycle.

$$D = \frac{T_H}{T_H + T_L} \times 100\%$$

$$D = \frac{R_A + R_B}{R_A + 2R_B} \times 100\%$$

Barkhausen criterion of oscillation.

$$A\beta = 1 \text{ and } A_f = \infty$$

The voltage gain of the amplifier with positive feedback.

$$A_f = \frac{A}{1 - A\beta}$$

Frequency of oscillation of RC Phase Shift Oscillator.

$$f_o = \frac{1}{2\pi RC\sqrt{6}}$$

The feedback factor of Phase Shift Oscillator.

$$\beta = \frac{1}{29}$$

Frequency of oscillation of Wien-bridge Oscillator.

$$f_o = \frac{1}{2\pi \sqrt{(R_1 C_1 R_2 C_2)}}$$

The feedback factor of Wien-bridge Oscillator.

$$\beta = \frac{1}{3}$$

Frequency of oscillation of Colpitts Oscillator.

$$f_o = \frac{1}{2\pi \sqrt{(LC_{eq})}} \quad \text{where;} \quad C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

The feedback factor of Colpitts Oscillator.

$$\beta = \frac{C_2}{C_1}$$

Frequency of oscillation of Hartley Oscillator.

$$f_o = \frac{1}{2\pi\sqrt{(L_{eq}C)}} \text{ where; } L_{eq} = L_1 + L_2$$

The feedback factor of Hartley Oscillator.

$$\beta = \frac{L_1}{L_2}$$

Frequency of oscillation of Crystal Oscillator.

$$f_o = \frac{1}{2\pi\sqrt{LC_{eq}}} \text{ where; } C_{eq} = C + C_M$$

Relation between frequency and wave length.

$$f = \frac{c}{\lambda} \text{ where } c = 3 \times 10^8$$

Relation between flux luminous and power per meter square.

$$1lm = 1.464 \frac{mW}{m^2}$$

