



KOLEJ YAYASAN PELAJARAN JOHOR
FINAL EXAMINATION

COURSE NAME : INDUSTRIAL ELECTRONICS
COURSE CODE : DKE 3043
SESSION : JANUARY 2024
DURATION : 2 HOURS 30 MINUTES

INSTRUCTION TO CANDIDATES /
ARAHAH KEPADA CALON

1. This examination paper consists of **TWO (2)** parts: /
*Kertas soalan ini mengandungi **DUA (2)** bahagian:* PART A (20 Marks) /
PART B (80 Marks) /
BAHAGIAN A (20 Markah)
BAHAGIAN B (80 Markah)
2. Candidates are not allowed to bring any material to examination room except with the permission from the invigilator. /
Calon tidak dibenarkan untuk membawa sebarang bahan/nota ke bilik peperiksaan tanpa kebenaran daripada pengawas.
3. Please check to make sure that this examination pack consists of: /
Pastikan kertas soalan peperiksaan ini mengandungi:
 - i. Question Paper /
Kertas Soalan.
 - ii. Answering Booklet /
Buku Jawapan.
 - iii. Attachment /
Lampiran.

DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALANINI SEHINGGA DIBERITAHU

This examination paper consists of 15 printed pages including front page
Kertas soalan ini mengandungi 15 halaman bercetak termasuk kulit hadapan



PART A/ BAHAGIAN A

This part consists of **FOUR (4)** questions. Answer **ALL** the questions in an answering booklet.

*Bahagian ini mengandungi **EMPAT (4)** soalan. Jawab **SEMUA** soalan dalam buku jawapan.*

QUESTION 1/ SOALAN 1

Figure Q1 shows a block diagram of a direct current power supply. Illustrate the output waveform of each block in the diagram.

(5 marks/ markah)

Rajah Q1 menunjukkan satu rajah blok bekalan kuasa arus terus. Ilustrasikan bentuk gelombang keluaran bagi setiap blok dalam rajah itu.

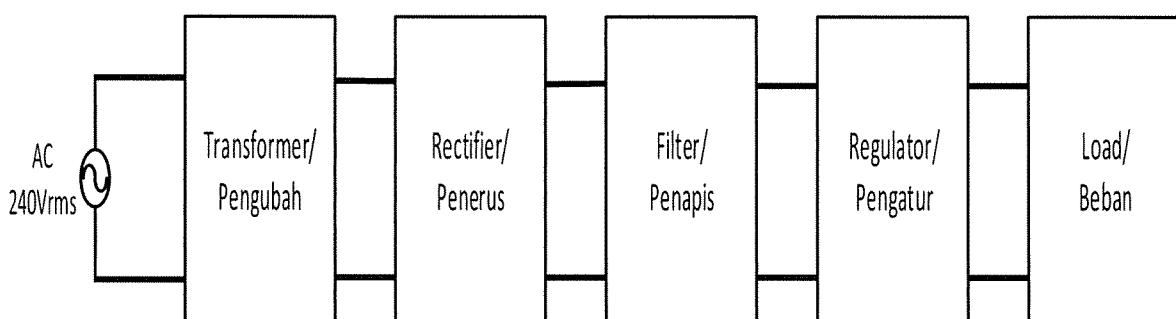


Figure Q1/ Rajah Q1

QUESTION 2/ SOALAN 2

Compare between a monostable multivibrator and an astable multivibrator.

(5 marks/ markah)

Bandingkan antara pemberbilang getar monostabil dengan pemberbilang getar tak stabil.

QUESTION 3/ SOALAN 3

Express completely I-V characteristic curve of triac.

(5 marks/ markah)

Nyatakan dengan lengkap lengkung cirian I-V bagi triak.

QUESTION 4/ SOALAN 4

Based on the circuit in **Figure Q4**, find the value of resistor, R_c if the maximum current, I_c (max) flowing through the light emitted diode (LED) is 40mA.

(5 marks/ markah)

*Berdasarkan litar dalam **Rajah Q4**, cari nilai perintang, R_c jika arus maksimum, I_c (maks) yang mengalir melalui diod pemancar cahaya (LED) ialah 40mA.*

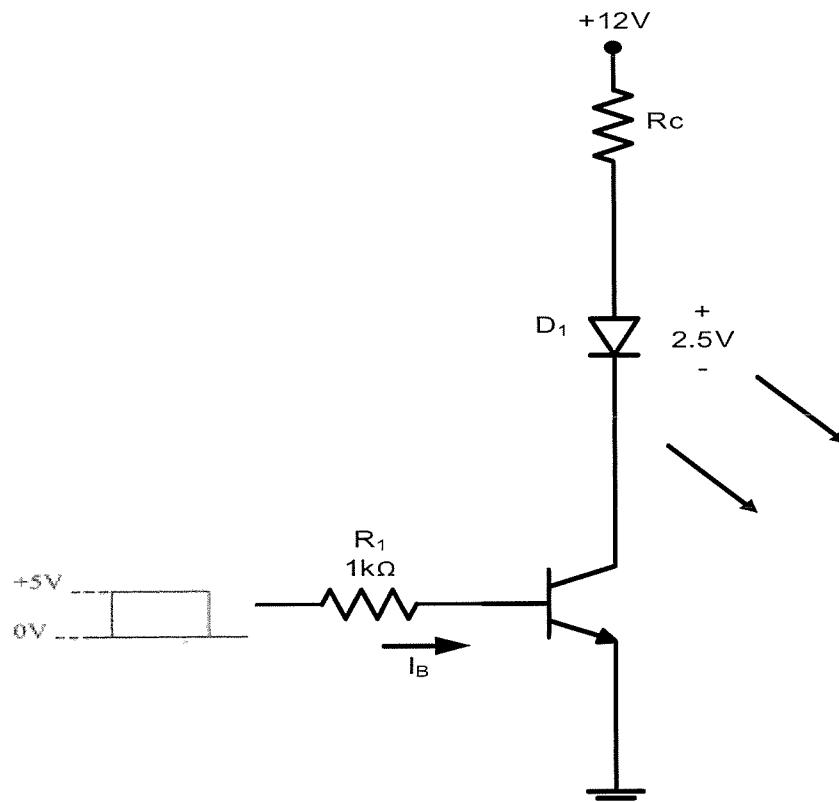


Figure Q4/ Rajah Q4

PART B / BAHAGIAN B

This part consists of **FOUR (4)** questions. Answer **ALL** the questions in an answering booklet.

*Bahagian ini mengandungi **EMPAT (4)** soalan. Jawab **SEMUA** soalan dalam buku jawapan.*

QUESTION 5/ SOALAN 5

Referring to the circuit in **Figure Q5**. Given $P_{z\max}=0.5W$ and $I_{z\min}=2mA$. Calculate:

- a. the output voltage, V_o range by changing the value of resistor, R_1 .

(8 marks/ markah)

- b. the maximum power dissipated by the transistor, Q_1 if resistor, R_1 is set at maximum value.

(6 marks/ markah)

- c. the range of allowable resistor, R_s to ensure the Zener diode is always in the breakdown region.

(6 marks/ markah)

*Berdasarkan litar dalam **Rajah Q5**. Diberi $P_{z\max}=0.5W$ dan $I_{z\min}=2mA$. Kirakan:*

- a. julat voltan keluaran, V_o dengan menukar nilai perintang, R_1 .

- b. kuasa maksimum yang dilesapkan oleh transistor, Q_1 jika perintang, R_1 ditetapkan pada nilai maksimum.

- c. julat perintang, R_s yang dibenarkan untuk memastikan diod Zener sentiasa berada dalam kawasan pecah tebat.

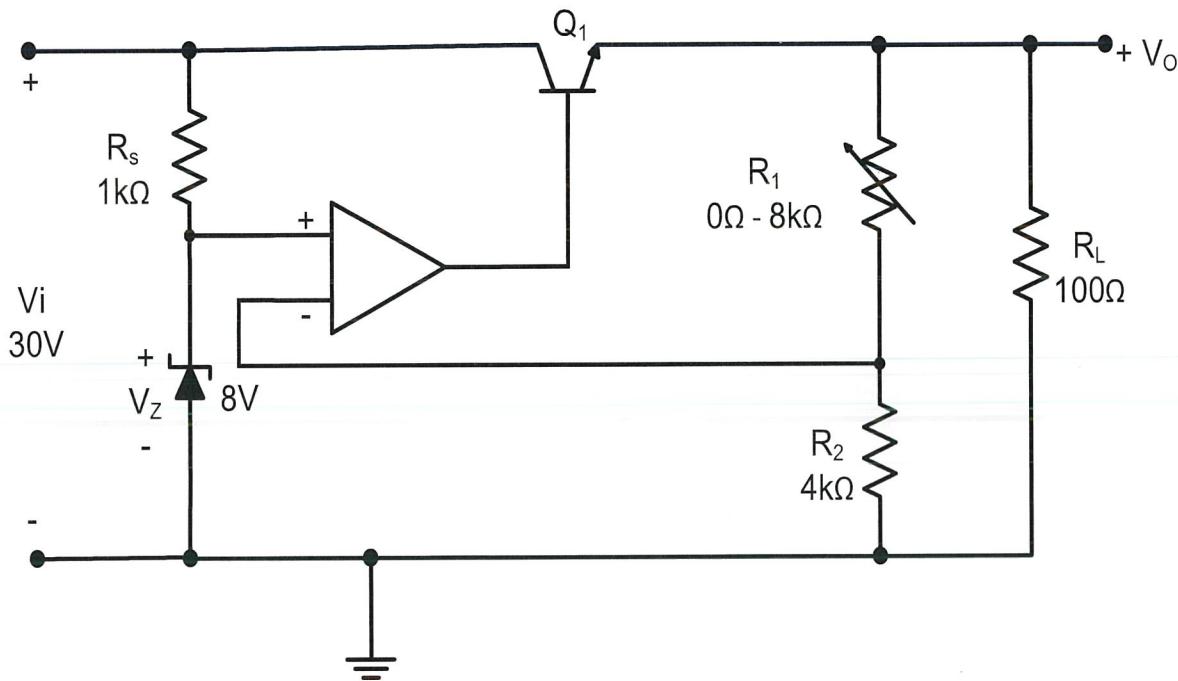


Figure Q5/ Rajah Q5

QUESTION 6/ SOALAN 6

Referring to **Figure Q6** is astable multivibrator circuit using 555 timers that operates at 5kHz. Calculate:

- a. the capacitor value, C if resistor, $R_A=1\text{k}\Omega$ and resistor, $R_B=3.3\text{k}\Omega$.

(6 marks/ markah)

- b. the duty cycle of the timer circuit.

(6 marks/ markah)

- c. the high period, T_{high} and low period, T_{low} of the generated output waveform.

(8 marks/ markah)

Berdasarkan **Rajah Q6** yang menunjukkan litar jenis pemberbilang getar tak stabil dengan menggunakan pemasa 555 yang beroperasi pada 5kHz. Kirakan:

- nilai pemuat, C jika perintang, $R_A=1k\Omega$ dan perintang, $R_B=3.3k\Omega$.
- kitaran tugas litar pemasa.
- tempoh tinggi, T_{tinggi} dan tempoh rendah, T_{rendah} bagi gelombang keluaran yang dijana.

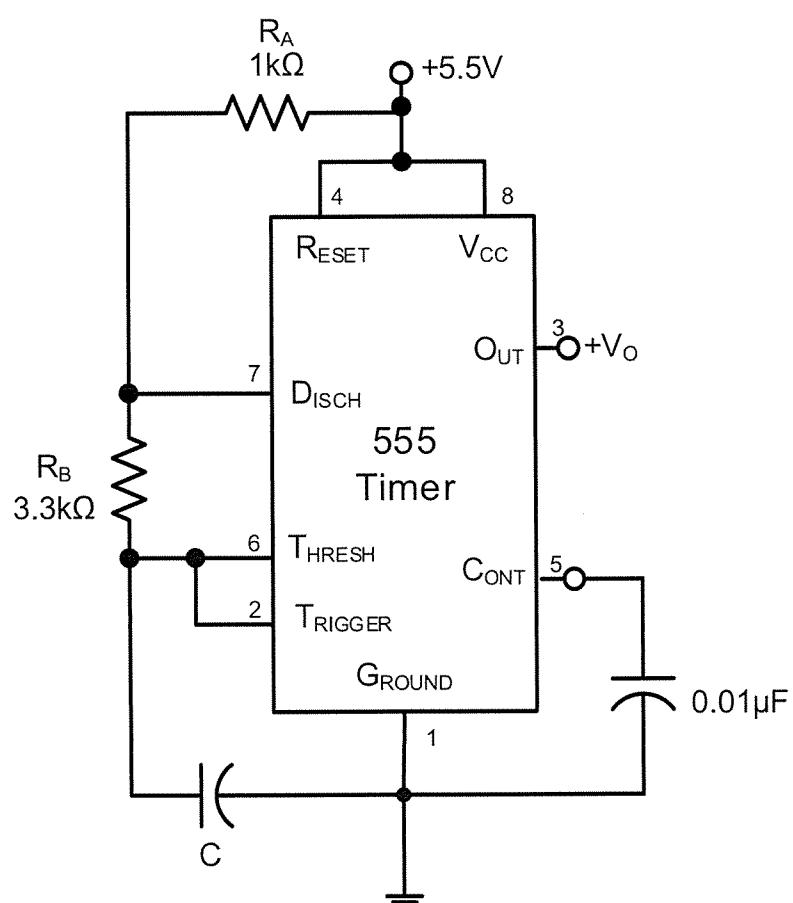


Figure Q6/ Rajah Q6

QUESTION 7/ SOALAN 7

Referring to **Figure Q7**, given peak input voltage, $V_{i(\text{peak})}=60V$, load resistance, $R_L=10\Omega$, resistance, $R_1=47k\Omega$, $R_2=10k\Omega$, $R_3=4.7k\Omega$, gate trigger current, $I_{GT}=15\mu A$ and gate trigger voltage, $V_{GT}=1V$. Calculate:

- a. the trigger voltage enters the gate, V_T .

(4 marks/ markah)

- b. the maximum firing angles, Θ_{\max} .

(8 marks/ markah)

- c. the minimum firing angles, Θ_{\min} .

(8 marks/ markah)

Berdasarkan **Rajah Q7**, diberi voltan masukan puncak, $V_{i(\text{puncak})}=60V$, rintangan beban, $R_L=10\Omega$, rintangan, $R_1=47k\Omega$, $R_2=10k\Omega$, $R_3=4.7k\Omega$, arus picuan get, $I_{GT}=15\mu A$ dan voltan picuan get, $V_{GT}=1V$. Kirakan:

- a. voltan picuan masuk ke get, V_T .

- b. sudut tembak maksimum, Θ_{\max} .

- c. sudut tembak minimum, Θ_{\min} .

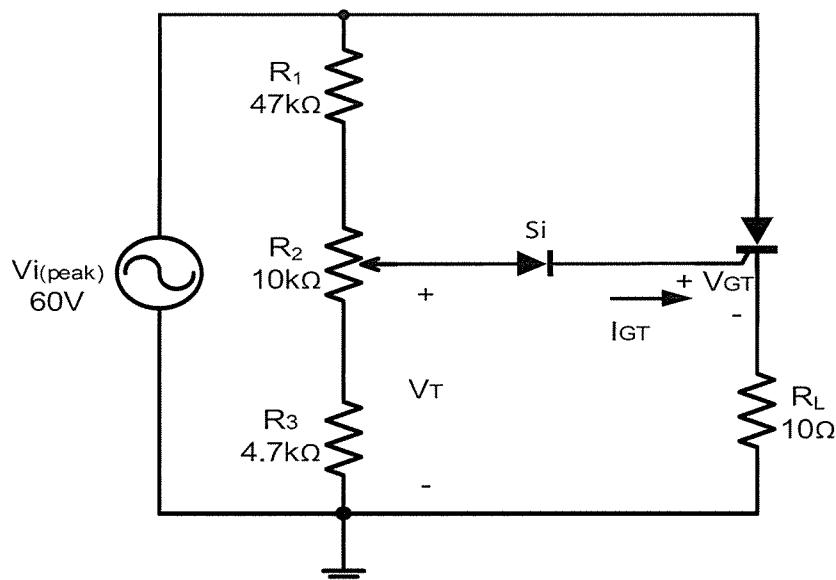


Figure Q7/ Rajah Q7

QUESTION 8/ SOALAN 8

Referring to **Figure Q8**, determine the following values:

- a. current I_1 , I_2 and I_{LED} .

(12 marks/ markah)

- b. voltage, V_{CE} .

(3 marks/ markah)

- c. power dissipated by the transistor, Q.

(5 marks/ markah)

Merujuk kepada **Rajah Q8**, tentukan nilai berikut:

- a. arus, I_1 , I_2 dan I_{LED} .

- b. voltan, V_{CE} .

- c. Kuasa yang dilesapkan oleh transistor, Q.

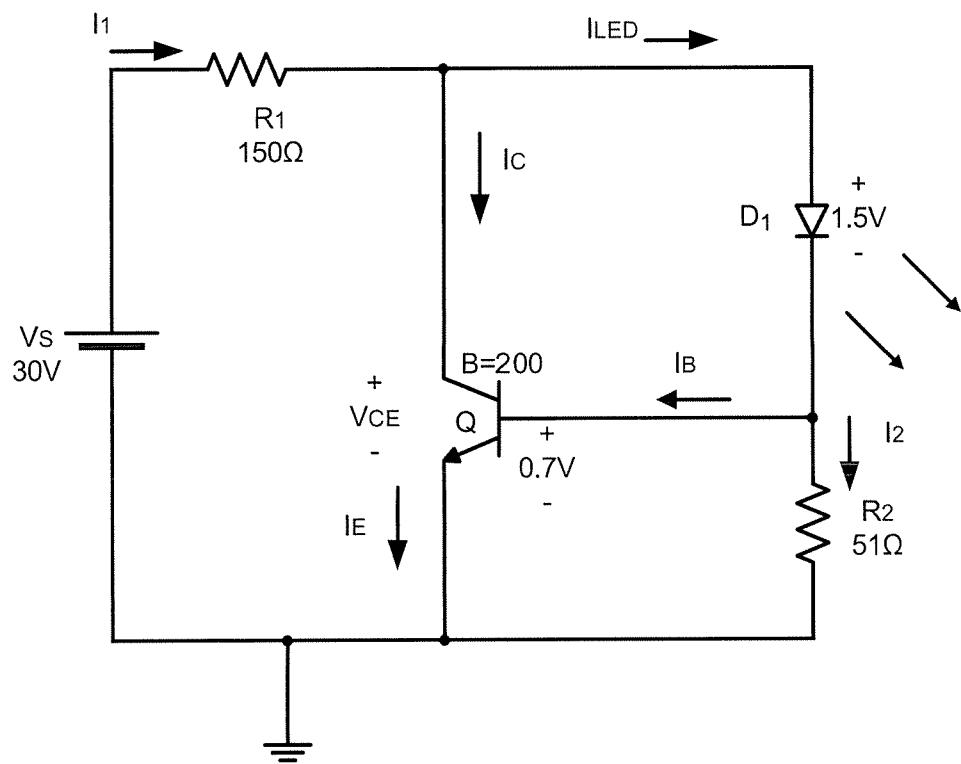


Figure Q8/ Rajah Q8

[100 MARKS/ 100 MARKAH]

END OF QUESTION PAPER/ KERTAS SOALAN TAMAT

Attachment/ *Lampiran*

Ripple factor of rectifier.

$$r = \frac{\text{rms value of ac component of signal}}{\text{average value of signal}}$$

$$r = \frac{V_r(\text{rms})}{V_{dc}}$$

Root mean square (rms) value of the total voltage rectified signal.

$$V_r(\text{rms}) = 0.385V_m(\text{half-wave})$$

$$V_r(\text{rms}) = 0.308V_m(\text{full-wave})$$

Ripple voltage of capacitor filter section.

$$V_{dc} = V_m - \frac{V_r(p-p)}{2}$$

Ripple factor of filter section.

$$r = \frac{1}{2\sqrt{3}R_LfC}(\text{half-wave})$$

$$r = \frac{1}{4\sqrt{3}R_LfC}(\text{full-wave})$$

DC operation of RC filter section.

$$V'_{dc} = \frac{R_L}{R+R_L}V_{dc}$$

AC operation of RC filter section.

$$V'_r(\text{rms}) = \frac{X_{c2}}{R+X_{c2}}V_r(\text{rms})$$

Load regulation.

$$\%L.R = \frac{\frac{V_{o(NL)} - V_{o(FL)}}{V_{o(FL)}} \times 100\%}{I_{L(FL)} - I_{L(NL)}}$$

Line regulation.

$$\%L.R = \frac{\frac{V_{o(ORIGINAL)} - V_{o(NEW)}}{V_{o(ORIGINAL)}} \times 100\%}{V_{i(ORIGINAL)} - V_{i(NEW)}}$$

Percent efficiency of the power supply.

$$\% \eta = \frac{P_L}{P_i} \times 100\%$$

Ideal op-amp.

$$V^+ = V^-$$

$$I^+ = I^- = 0A$$

Upper trigger point of square wave signal generator.

$$V_{UTP} = \frac{R_3}{(R_2 + R_3)} \times (+V_{cc})$$

Lower trigger point of square wave signal generator.

$$V_{LTP} = \frac{R_3}{(R_2 + R_3)} \times (-V_{cc})$$

The time period of square wave signal generator.

$$T_H = R_l C \ell_n \left(\frac{V_{cc} - V_{LTP}}{V_{cc} - V_{UTP}} \right)$$

$$T_L = R_l C \ell_n \left(\frac{-V_{cc} - V_{UTP}}{-V_{cc} - V_{LTP}} \right)$$

Output wave frequency of square wave signal generator.

$$f_o = \frac{1}{T_H + T_L}$$

Pulse width of monostable multivibrator.

$$PW = RC\ell_n \left(\frac{V_{CC} - 0}{V_{CC} - \frac{2}{3}V_{CC}} \right)$$

$$PW = 1.1RC$$

The period of the astable multivibrator.

$$T_H = \tau_1 \ell_n \left(\frac{V_{CC} - \frac{1}{3}V_{CC}}{V_{CC} - \frac{2}{3}V_{CC}} \right)$$

$$T_H = 0.693(R_A + R_B)C_1$$

$$T_L = \tau_2 \ell_n \left(\frac{0 - \frac{2}{3}V_{CC}}{0 - \frac{1}{3}V_{CC}} \right)$$

$$T_L = 0.693(R_B)C_1$$

$$T = 0.693(R_A + 2R_B)C_1$$

The oscillation frequency of square wave astable multivibrator.

$$f_o = \frac{1}{0.693(R_A + 2R_B)C_1}$$

Duty cycle.

$$D = \frac{T_H}{T_H + T_L} \times 100\%$$

$$D = \frac{R_A + R_B}{R_A + 2R_B} \times 100\%$$

Barkhausen criterion of oscillation.

$$A\beta = 1 \text{ and } A_f = \infty$$

The voltage gain of the amplifier with positive feedback.

$$A_f = \frac{A}{1 - A\beta}$$

Frequency of oscillation of RC Phase Shift Oscillator.

$$f_o = \frac{1}{2\pi RC\sqrt{6}}$$

The feedback factor of Phase Shift Oscillator.

$$\beta = \frac{1}{29}$$

Frequency of oscillation of Wien-bridge Oscillator.

$$f_o = \frac{1}{2\pi\sqrt{(R_1C_1R_2C_2)}}$$

The feedback factor of Wien-bridge Oscillator.

$$\beta = \frac{1}{3}$$

Frequency of oscillation of Colpitts Oscillator.

$$f_o = \frac{1}{2\pi\sqrt{(LC_{eq})}} \quad \text{where;} \quad C_{eq} = \frac{C_1C_2}{C_1 + C_2}$$

The feedback factor of Colpitts Oscillator.

$$\beta = \frac{C_2}{C_1}$$

Frequency of oscillation of Hartley Oscillator.

$$f_o = \frac{1}{2\pi\sqrt{(L_{eq}C)}} \quad \text{where; } L_{eq} = L_1 + L_2$$

The feedback factor of Hartley Oscillator.

$$\beta = \frac{L_1}{L_2}$$

Frequency of oscillation of Crystal Oscillator.

$$f_o = \frac{1}{2\pi\sqrt{LC_{eq}}} \quad \text{where; } C_{eq} = C + C_M$$

Firing angle of SCR.

$$\theta_f = \alpha$$

Conducting angle of SCR.

$$\theta_c = \beta$$

Total angle of SCR

$$\theta_f + \theta_c = 180^\circ$$

$$\alpha + \beta = 180^\circ$$

Stand-off ratio of UJT

$$\eta = \left(\frac{R_{B1}}{R_{BB}} \right) \quad \text{where } R_{BB} = R_{B1} + R_{B2}$$

Relation between V_{RB1} and V_{BB} of UJT

$$V_{RB1} = \left(\frac{R_{B1}}{R_{BB}} \right) V_{BB}$$

$$V_{RB1} = \eta V_{BB}$$

Relation between frequency and wave length.

$$f = \frac{c}{\lambda} \text{ where } c = 3 \times 10^8$$

Relation between flux luminous and power per meter square.

$$1Im = 1.464 \frac{mW}{m^2}$$



