



**FINAL EXAMINATION / PEPERIKSAAN AKHIR
SEMESTER 2 – SESSION 2015 / 2016
PROGRAM KERJASAMA**

COURSE CODE : DDPE 2173
KOD KURSUS

COURSE NAME : CIRCUIT THEORY / TEORI LITAR
NAMA KURSUS

YEAR / PROGRAMME : 2 DDPB / E / K / P
TAHUN / PROGRAM

DURATION : 2 HOURS 30 MINUTES / 2 JAM 30 MINIT
TEMPOH

DATE : APRIL 2016
TARIKH

INSTRUCTION : ANSWER ALL QUESTIONS / JAWAB SEMUA SOALAN
ARAHAH

(You are required to write your name and your lecturer's name on your answer script)

(Pelajar dikehendaki tuliskan nama dan nama pensyarah pada skrip jawapan)

NAME / NAMA PELAJAR	:
I.C NO. / NO. K/PENGENALAN	:
YEAR / PROGRAMME TAHUN / PROGRAM	:
COLLEGE'S NAME NAMA KOLEJ	:
LECTURER'S NAME NAMA PENSYARAH	:

This examination paper consists of 7 pages including the cover
Kertas soalan ini mengandungi 7 muka surat termasuk kulit hadapan

- Q1. Calculate the current, I_o in the circuit of Figure Q1 using nodal analysis.

Kira nilai arus, I_o dalam litar Rajah Q1 menggunakan analisis nod.

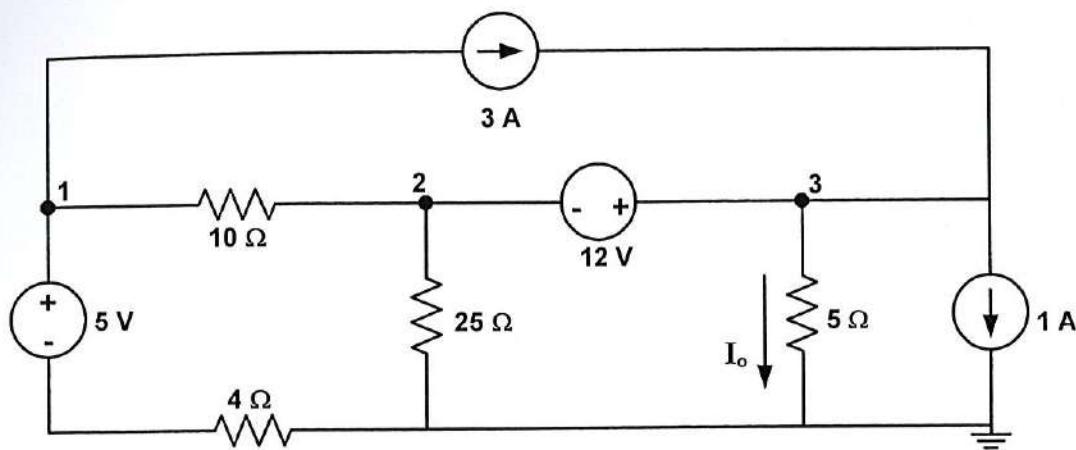


Figure Q1 / Rajah Q1

(13 marks/ markah)

- Q2. Determine the voltage, V_o in the circuit of Figure Q2 using Norton's theorem. Solve for Norton current, I_N using mesh analysis.

Tentukan voltan, V_o dalam litar Rajah Q2 menggunakan teorem Norton. Gunakan analisis jejaring untuk mendapatkan arus Norton, I_N .

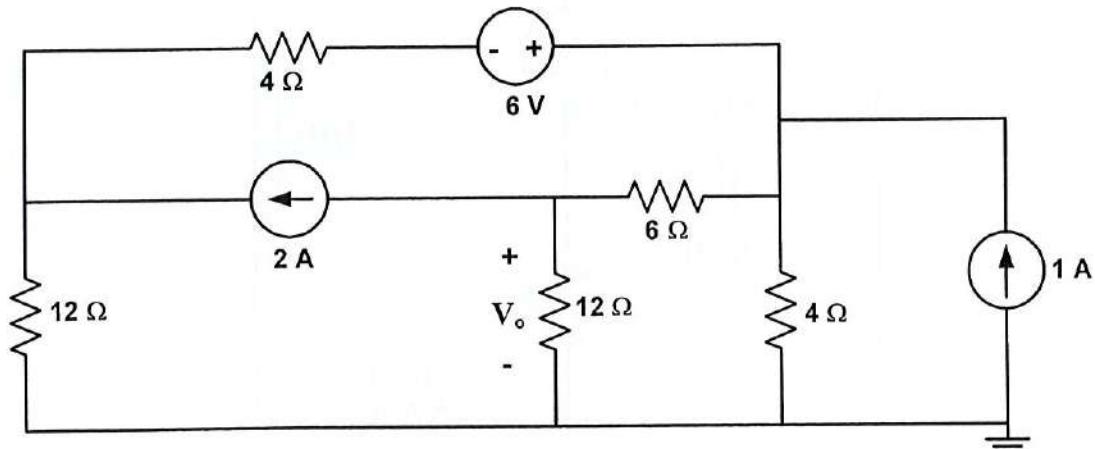


Figure Q2 / Rajah Q2

(15 marks/ markah)

Q3. Referring to Figure Q3, given that the current, $i_1(t) = 5 \sin(500t + 100^\circ) A$.

- (a) Draw the phasor circuit.
- (b) Find the total impedance, Z_T .
- (c) Draw the impedance triangle.
- (d) Determine the voltage source, V_s .
- (e) Find the current, $i_2(t)$.
- (f) Find the voltage, V_C .

Merujuk kepada Rajah Q3, diberi arus, $i_1(t) = 5 \sin(500t + 100^\circ) A$.

- (a) Lukiskan litar pemfasa.
- (b) Dapatkan jumlah galangan, Z_T .
- (c) Lukiskan segitiga galangan.
- (d) Tentukan sumber voltan, V_s .
- (e) Dapatkan arus, $i_2(t)$.
- (f) Dapatkan voltan, V_C .

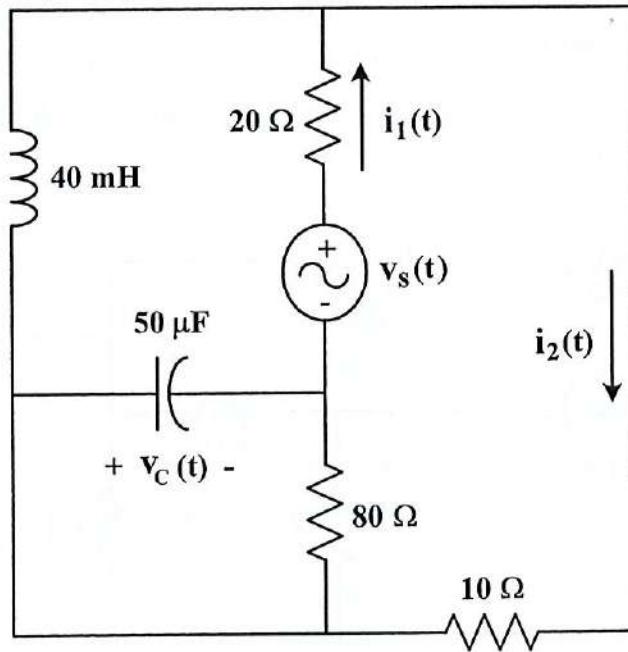


Figure Q3 / Rajah Q

(18 marks/ markah)

- Q4. Referring to Figure Q5, find the voltage, V_o using superposition theorem.

Merujuk Rajah Q5, dapatkan voltan, V_o menggunakan teorem tindihan.

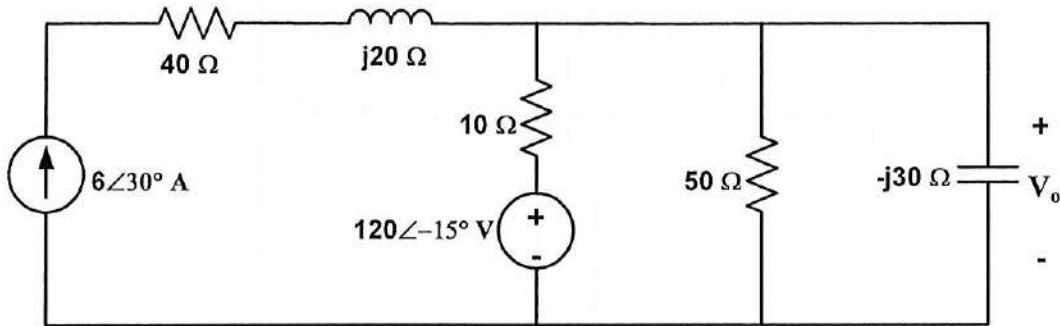


Figure Q4 / Rajah Q4

(13 marks/ markah)

- Q5. Referring to the circuit in Figure Q5,

- Determine the Thevenin's equivalent circuit looking from terminal ab.
- The value of the load impedance, Z_L for maximum power to be transferred to the load.
- Calculate the maximum power.

Merujuk kepada litar dalam Rajah Q5,

- Tentukan litar setara Thevenin yang dilihat dari terminal ab.
- Nilai galangan beban, Z_L untuk kuasa maksima dipindahkan kepada beban.
- Kirakan nilai kuasa maksima tersebut.

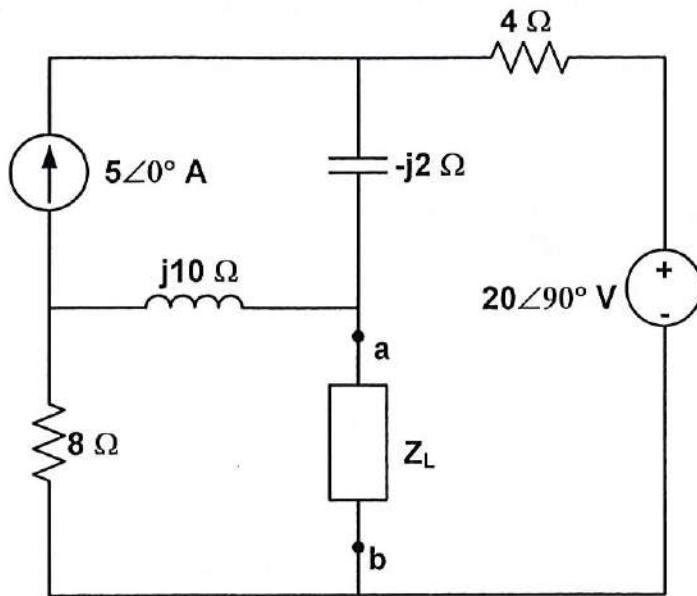


Figure Q5/Rajah Q5

(17 marks/ markah)

- Q6. a) State the components of the complete response for a first order circuit.

Nyatakan komponen sambutan lengkap bagi satu litar tertib pertama.

(2 marks/ markah)

- b) The circuit in Figure Q6(b) is in steady state for $t < 0$. Find:

- the initial value for the current flowing through the inductor, $i(0^-)$
- the complete solution for the current flowing through the inductor, $i(t)$ for $t \geq 0$.

Litar dalam Rajah Q6(b) berada dalam keadaan mantap untuk $t < 0$. Dapatkan:

- nilai awal arus melalui induktor, $i(0^-)$
- penyelesaian lengkap bagi arus melalui induktor $i(t)$ untuk $t \geq 0$.

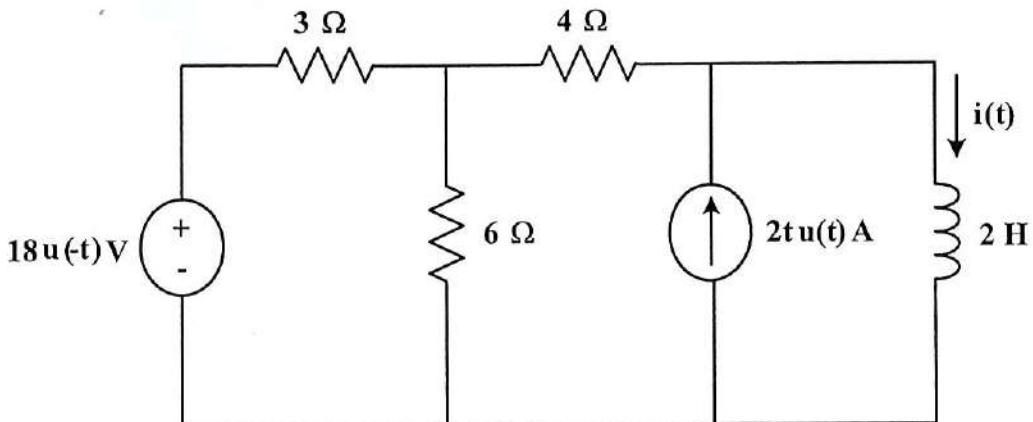


Figure Q6(b) / Rajah Q6(b)

(22 marks/ markah)

Forcing functions and their assumed solutions

Forcing function		Assumed solution
Constant	$f(t) = A$	$x_f(t) = K_2$
Exponential	$f(t) = M e^{-st}$	$x_f(t) = K_2 e^{-st}$
Variable	Ramp	$x_f(t) = K_2 t + K_3$
	Parabolic	$x_f(t) = K_2 t^2 + K_3 t + K_4$
Sinusoidal		$x_f(t) = K_2 \sin \omega t + K_3 \cos \omega t$
$f(t) = M \cos(\omega t + \theta)$		
$f(t) = M e^{-st} \sin(\omega t + \theta)$		$x_f(t) = e^{-st} (K_2 \sin \omega t + K_3 \cos \omega t)$