



**KOLEJ YAYASAN PELAJARAN JOHOR
FINAL EXAMINATION**

COURSE NAME : POWER ELECTRONICS
COURSE CODE : DKE 3063
SESSION : DECEMBER 2022
DURATION : 2 HOURS 30 MINUTES

**INSTRUCTION TO CANDIDATES /
ARAHAN KEPADA CALON**

1. This examination paper consists of **FIVE (5)** questions. Answer **ALL** questions. /
*Kertas soalan ini mengandungi **LIMA (5)** soalan. Jawab **SEMUA** soalan.*

2. Candidates are not allowed to bring any material/note to the examination hall/room except with the permission from the invigilator. The formula sheet is attached to the back of this question paper. /
Calon tidak dibenarkan untuk membawa sebarang bahan/nota ke dewan/bilik peperiksaan tanpa kebenaran daripada pengawas. Rumus dilampirkan dibelakang kertas soalan peperiksaan.

3. Please check to make sure that this examination pack consist of: /
Pastikan kertas soalan peperiksaan ini mengandungi:
 - i. The Question Paper /
Kertas Soalan
 - ii. An Answering Booklet /
Buku Jawapan
 - iii. Attachment 1 /
Lampiran 1

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALANINI SEHINGGA DIBERITAHU**

This examination paper consists of **8** printed pages including front page
*Kertas soalan ini mengandungi **8** halaman bercetak termasuk muka hadapan*

This paper contains of **FIVE (5)** questions. Answer **ALL** questions in the answering booklet.

*Kertas soalan ini mengandungi **LIMA (5)** soalan. Jawab **SEMUA** soalan dalam buku jawapan.*

QUESTION 1 / SOALAN 1

- a. Name two (2) different kinds of circuit converters.
(2 marks/ markah)

- b. Explain three (3) advantages of a three-phase rectifier over a single-phase rectifier.
(3 marks/ markah)

- c. If the full wave center tapped rectifier has a purely resistive load of R , determine:
 - i. the efficiency.
 - ii. form factor.
 - iii. the ripple factor.
 - iv. transformer utilization factor.
 - v. peak inverse voltage current.
 - vi. crest factor for input current.
(15 marks/ markah)

- a. *Namakan dua (2) jenis perbezaan litar penukar.*

- b. *Terangkan tiga (3) kelebihan litar penerus tiga-fasa berbanding satu-fasa.*

- c. *Sekiranya penerus ketuk pembahagi gelombang penuh mempunyai beban tulen R , tentukan:*
 - i. kecekapan.
 - ii. faktor bentuk.
 - iii. faktor riak.
 - iv. faktor penggunaan pengubah.
 - v. arus voltan puncak balikan.
 - vi. faktor puncak arus masukan.

QUESTION 2 / SOALAN 2

- a. Identify one (1) difference between Silicon Controlled Rectifier and Diode Rectifier in power electronics.

(2 marks/ markah)

- b. Sketch the SCR equivalent circuit (PNP-NPN).

(3 marks/ markah)

- c. If the half wave controlled rectifier has a purely resistive load of R and the delay is $\alpha = \pi/2$, determine:

- i. rectification efficiency.
- ii. form factor.
- iii. ripple factor.
- iv. TUF.
- v. PIV.

(15 marks/ markah)

- a. Kenalpasti satu (1) perbezaan antara Penerus Terkawal Silikon dan Diod Penerus dalam elektronik kuasa.

- b. Lakarkan litar setara SCR(PNP-NPN).

- c. Jika penerus terkawal gelombang separuh mempunyai beban resistif tulen R dan kelewatannya adalah $\alpha = \pi/2$, tentukan:

- i. kecekapan pembetulan.
- ii. faktor bentuk.
- iii. faktor riak.
- iv. TUF.
- v. PIV.

QUESTION 3 / SOALAN 3

- a. List two (2) methods of controlling an AC voltage controllers.
(2 marks/ markah)
- b. List three (3) disadvantages of having a low power factor.
(3 marks/ markah)
- c. An AC voltage controller in Figure 1 has a resistive load of $R = 10 \Omega$ and the rms phase input voltage is $V_s = 120 \text{ V}$, 60 Hz. The thyristors switch is on for $n = 25$ cycles and is off for $m = 75$ cycles. Determine:
 i. rms output voltage.
 ii. input power factor.
 iii. average and rms current of thyristors.
 iv. output waveform for the circuit.
(15 marks/ markah)

- a. Senaraikan dua (2) kaedah kawalan bagi voltan pengawal AU.
- b. Senaraikan tiga (3) keburukan mempunyai faktor kuasa rendah.
- c. Pengawal voltan AU pada Rajah 1 mempunyai beban $R = 10 \Omega$ dan voltan masukan fasa pmkd adalah $V_s = 120 \text{ V}$, 60 Hz. Suis thyristor dihidupkan untuk kitaran $n = 25$ dan dimatikan untuk kitaran $m = 75$. Tentukan:
 i. voltan keluaran pmkd.
 ii. faktor kuasa masukan.
 iii. purata dan pmkd arus thyristor.
 iv. gelombang keluaran bagi litar.

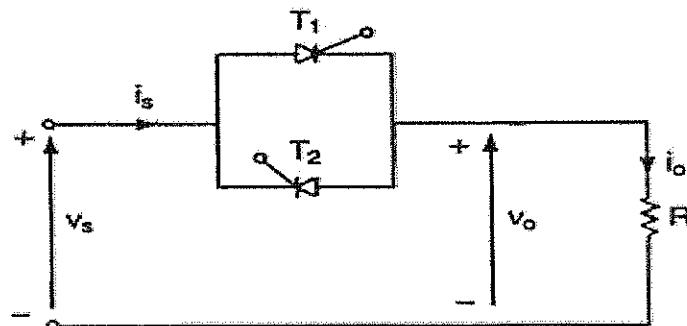


Figure 1 / Rajah 1

QUESTION 4 / SOALAN 4

- a. Define a DC to DC converter. (2 marks/ markah)
- b. Name three (3) basic types of switching-mode regulators. (3 marks/markah)
- c. A boost regulator has an input voltage of $V_s = 5$ V. The average output voltage $V_a = 15$ V and the average load current $I_a = 0.5$ A. The switching frequency is 25 kHz. If $L = 150 \mu\text{H}$ and $C = 220 \mu\text{F}$. Determine:
i. the duty cycle, k .
ii. the ripple current of inductor ΔI .
iii. the peak current of inductor I_2 .
iv. the ripple voltage of filter capacitor ΔV_c . (15 marks/ markah)

- a. Definisikan penukar AT ke AT.
- b. Namakan tiga (3) jenis asas bagi pengatur mod-pensuisan.
- c. Pengawal selia mempunyai masukan voltan $V_s = 5$ V. Purata voltan keluaran $V_a = 15$ V dan purata beban purata arus $I_a = 0.5$ A. Frekuensi pensuisan ialah 25 kHz. Jika $L = 150 \mu\text{H}$ dan $C = 220 \mu\text{F}$. Tentukan:
i. kitar tugas, k .
ii. arus riak daripada pearuh ΔI .
iii. arus puncak pearuh I_2 .
iv. voltan riak penapis pemuat ΔV_c .

QUESTION 5 / SOALAN 5

- a. Define an inverter gain.
(2 marks/ markah)
- b. Name three (3) different types of power electronics devices that are commonly used in controller inverter converters.
(3 marks/ markah)
- c. This question based on the single phase bridge inverters.
- Sketch the circuit diagram for single phase bridge inverters.
 - Show the operation of the circuit based the circuit diagram.
 - Sketch the output waveform, V_o .
- (15 marks/ markah)**
- a. *Definisikan gandaan penyongsang.*
- b. *Namakan tiga (3) jenis peranti elektronik kuasa yang biasa digunakan dalam penukar penyongsang terkawal.*
- c. *Soalan ini berdasarkan penyongsang titi fasa tunggal.*
- Lukiskan litar bagi penyongsang jambatan fasa tunggal.*
 - Tunjukkan kendalian litar tersebut berdasarkan rajah litar.*
 - Lakarkan gelombang keluaran, V_o .*
- (15 marks/ 15 markah)**

[100 MARKS/ 100 MARKAH]

END OF QUESTION PAPER / KERTAS SOALAN TAMAT

Attachment 1 / Lampiran 1

Uncontrolled rectifier

$$V_{o(\text{dc})} = 0.318V_m \quad V_{o(\text{rms})} = 0.5V_m$$

$$V_{o(\text{dc})} = \frac{V_m}{2\pi}[1 - \cos(\beta)] \quad V_{o(\text{rms})} = \frac{V_m}{2} \sqrt{\frac{\beta}{\pi} - \frac{\sin(2\beta)}{2\pi}}$$

$$V_{o(\text{dc})} = 0.6366V_m \quad V_{o(\text{rms})} = 0.707 V_m$$

$$V_{o(\text{dc})} = 1.654V_m \quad V_{o(\text{rms})} = 1.6554 V_m$$

$$V_{o(\text{dc})} = 0.827V_m \quad V_{o(\text{rms})} = 0.8407 V_m$$

Controlled rectifier

$$V_{o(\text{dc})} = \frac{V_m}{2\pi}(1 + \cos\alpha) \quad V_{o(\text{rms})} = \frac{V_m}{2} \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}$$

$$V_{o(\text{dc})} = \frac{2V_m}{\pi} \cos\alpha \quad V_{o(\text{rms})} = V_m \left[\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi} \right]^{1/2}$$

Principle of AC Voltage controller

$$Vs = \sqrt{2}Vs \sin\alpha t \quad Vo = Vs \sqrt{\frac{n}{m+n}} = Vs \sqrt{k}$$

$$Vo(\text{rms}) = Vs \left[\frac{1}{2\pi} \left(2\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}$$

$$Vo(\text{dc}) = \frac{\sqrt{2}Vs}{2\pi} (\cos\alpha - 1)$$

AC Voltage controller : Single Phase

$$Vo(\text{rms}) = Vs \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{\alpha} \right) \right]^{1/2} \quad Vo(\text{rms}) = Vs \left[\frac{1}{\pi} \left(\beta - \alpha + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right) \right]^{1/2}$$

AC Voltage controller : Three Phase Half wave

For $0^\circ \leq \alpha < 90^\circ$:

$$V_o(\text{rms}) = \sqrt{3}Vs \left[\frac{1}{\pi} \left(\frac{\pi}{3} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{8} \right) \right]^{1/2}$$

For $90^\circ \leq \alpha < 120^\circ$:

$$V_o(\text{rms}) = \sqrt{3}Vs \left[\frac{1}{\pi} \left(\frac{11\pi}{24} - \frac{\alpha}{2} \right) \right]^{1/2}$$

For $120^\circ \leq \alpha < 210^\circ$:

$$V_o(\text{rms}) = \sqrt{3}Vs \left[\frac{1}{\pi} \left(\frac{7\pi}{24} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{16} - \frac{\sqrt{3} \cos 2\alpha}{16} \right) \right]^{1/2}$$

AC Voltage controller : Three Phase Full wave

For $0^\circ \leq \alpha < 60^\circ$:

$$V_o(\text{rms}) = \sqrt{6}Vs \left[\frac{1}{\pi} \left(\frac{\pi}{6} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{8} \right) \right]^{1/2}$$

For $60^\circ \leq \alpha < 90^\circ$:

$$V_o(\text{rms}) = \sqrt{6}Vs \left[\frac{1}{\pi} \left(\frac{\pi}{12} + \frac{3 \sin 2\alpha}{16} + \frac{\sqrt{3} \cos 2\alpha}{16} \right) \right]^{1/2}$$

For $120^\circ \leq \alpha < 210^\circ$:

$$V_o(\text{rms}) = \sqrt{6}Vs \left[\frac{1}{\pi} \left(\frac{5\pi}{24} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{16} + \frac{\sqrt{3} \cos 2\alpha}{16} \right) \right]^{1/2}$$