



**KOLEJ YAYASAN PELAJARAN JOHOR
FINAL EXAMINATION**

COURSE NAME : INSTRUMENTATION
COURSE CODE : DKE 1033
EXAMINATION : OCTOBER 2019
DURATION : 2 HOURS 30 MINUTES

INSTRUCTION TO CANDIDATES

1. This examination paper consists of **FIVE (5)** questions. Answer **ALL** questions in the answer booklet provided.
*Kertas soalan ini mengandungi **LIMA (5)** soalan. Jawab **SEMUA** soalan di dalam buku jawapan yang disediakan.*
2. Candidates are not allowed to bring any material to examination room except with the permission from the invigilator.
Calon tidak dibenarkan membawa sebarang bahan/nota ke dalam bilik peperiksaan tanpa arahan/kebenaran daripada pengawas peperiksaan.
3. Please check to make sure that this examination pack consist of:
Pastikan kertas soalan peperiksaan ini mengandungi:
 - i. Question Paper/
Kertas soalan
 - ii. Answer Booklet/
Buku jawapan

DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO

*This examination paper consists of **8** printed pages including front page*



This paper contains of **FIVE(5)** questions. Answer **ALL** questions in the Answer Booklet.

*Kertas soalan ini mengandungi **LIMA (5)** soalan. Jawab **SEMUA** soalan di dalam buku jawapan yang disediakan.*

QUESTION 1 / SOALAN 1

- a. Systematic error is one of the types that frequently occur in any measurement. Explain briefly **two (2)** types of errors that are categorized as systematic error.

*Ralat sistematik merupakan salah satu jenis ralat yang sering berlaku di dalam sesuatu pengukuran. Terangkan dengan ringkas **dua (2)** jenis ralat yang dikategorikan sebagai ralat sistematik.*

(3 marks/ markah)

- b. Refer to Table Q1 (b), calculate:
- the average value of the readings.
 - the standard deviation.
 - the precision for all the readings.
 - the worst precision from all the readings.

Merujuk pada Jadual Q1 (b), kirakan :

- nilai purata bacaan.*
- sisihan piawaian.*
- kepersisan semua bacaan.*
- kepersisan terburuk dari semua bacaan.*

Data/ Data	1	2	3	4	5
Readings/ Bacaan	4.5	4.7	5.0	5.2	4.6

Table Q1 (b) / Jadual Q1 (b)

(17 marks/ markah)

QUESTION 2 / SOALAN 2

- a. A 1 mA full scale deflection current meter movement is used in an ohmmeter circuit. The meter movement has an internal resistance, $R_m = 100 \Omega$ and a 3 V battery is used in the circuit. Determine:
- the ohmmeter basic circuit.
 - the value of the variable resistance, R_z .
 - the value of R_x at 20%, 50% and 70% full-scale reflection.

Gerakan meter arus pesongan skala penuh 1 mA digunakan dalam litar meter ohm. Gerakan meter tersebut mempunyai rintangan dalam, $R_m = 100 \Omega$ dan sebuah bateri 3 V digunakan dalam litar tersebut. Tentukan :

- litar asas meter ohm.*
- nilai rintangan bolehubah, R_z .*
- nilai R_x pada 20%, 50% dan 70% pesongan skala penuh.*

(8 marks/ markah)

- b. Figure Q2 (b) shows a half-wave rectifier type AC meter with a range of 50 V. The diodes have a forward resistance of 100Ω while the parameters of the d'Arsonval movement are $50 \mu\text{A}$, 200Ω . It is required that $I_{sh} = I_m$.
- Calculate the shunt resistor R_{sh} .
 - Calculate the multiplier resistor R_s .
 - Calculate the DC sensitivity of the meter.
 - Calculate the AC sensitivity of the meter.

Gambar rajah Q2 (b) menunjukkan meter AU jenis penerus separuh-gelombang berjulat 50 V. Diod mempunyai rintangan ke depan 100Ω sementara parameter gerakan d'Arsonval ialah $50 \mu\text{A}$, 200Ω .

Dikehendaki supaya $I_{sh} = I_m$.

- Kirakan rintangan pirau R_{sh} .*
- Kirakan rintangan pendarab R_s .*
- Kirakan kepekaan AT meter.*
- Kirakan kepekaan AU meter.*

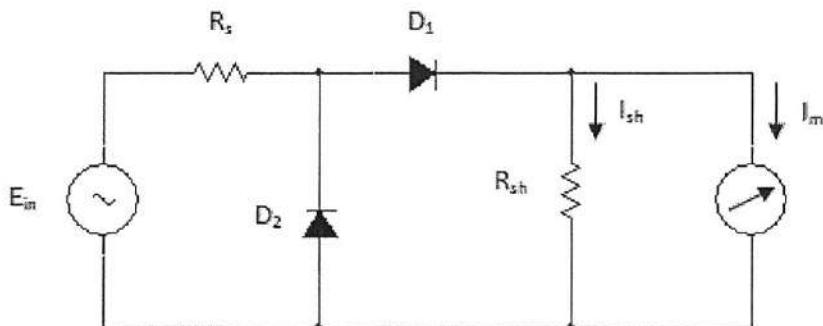


Figure Q2 (b) / Gambar rajah Q2 (b)

(12 marks/ markah)

QUESTION 3 / SOALAN 3

- a. Briefly explain **three (3)** differences between a digital instrument and a digital display instrument.

*Terangkan dengan ringkas **tiga (3)** perbezaan di antara alatan digital dan alatan paparan digital.*

(6 marks/ markah)

- b. A digital multimeter with $3\frac{1}{2}$ digit display and accuracy $\pm (1\% + 10d)$, was used to measure the current in a circuit. Calculate the error and percentage error when measuring 25 A current.

Satu meter pelbagai digit dengan paparan $3\frac{1}{2}$ digit dan kejituuan $\pm (1\% + 10d)$, telah digunakan untuk mengukur arus di dalam satu litar. Kirakan ralat dan peratus ralat ketika mengukur arus 25 A.

(6 marks/ markah)

- c. A digital voltmeter as shown in Figure Q3 (c) utilizes a voltage-to-frequency converter as its analogue-to-digital converter. The relationship between the input V_i and the output frequency f is given as:

$$V_i = \frac{f}{100}$$

If 130 pulses are sent to the AND gate in 0.5 seconds, calculate the amplitude of the input voltage V_i .

Sebuah meter volt digit seperti dalam Rajah Q3 (c) menggunakan penukar voltan-ke-frekuensi sebagai penukar analog-ke-digit. Hubungan antara V_i dan frekuensi keluaran f diberikan sebagai:

$$V_i = \frac{f}{100}$$

Jika 130 denyutan dihantar ke get DAN dalam masa 0.5 saat, kirakan amplitud voltan masukan V_i .

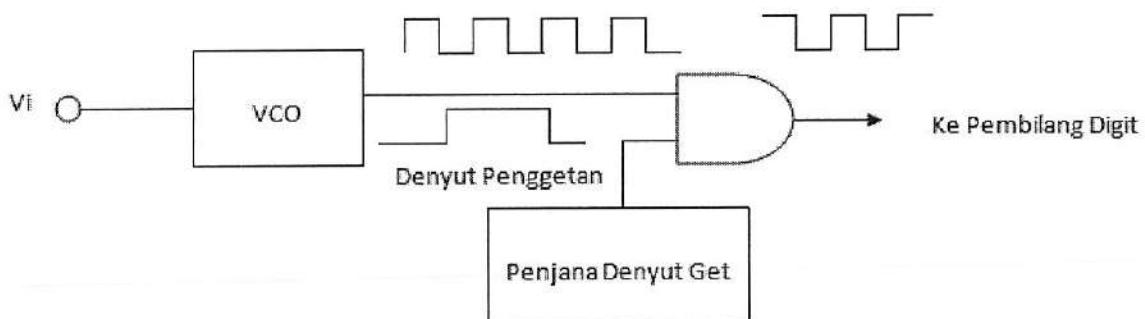


Figure Q3 (c) / Rajah Q3 (c)

(8 marks/ markah)

QUESTION 4 / SOALAN 4

- a. Prepare **three (3)** main factors to be considered in choosing a suitable transducer for an instrumentation system.

Sediakan tiga (3) faktor utama yang perlu dipertimbangkan ketika memilih transduser yang sesuai dalam sistem pengalatan.

(3 marks/ markah)

- b. A strain gauge with gauge factor 10 and unstrained resistance 100Ω is attached to a steel beam with Young's modulus $E = 2.0 \times 10^6 \text{ N/m}^2$. The beam changes in length from 100 mm to 100.4 mm.

- Calculate the strain G experienced by the beam.
- Calculate the resistance of the gauge after the strain has been applied.
- State the type of stress applied to the beam.
- Calculate the magnitude of the stress.

Sebuah tolak terikan dengan faktor tolok 10 dan rintangan tak terterik 100Ω dilekatkan pada alur keluli dengan modulus Young $E = 2.0 \times 10^6 \text{ N/m}^2$. Alur tersebut berubah panjang dari 100 mm ke 100.4 mm.

- Kirakan terikan G yang dialami oleh alur tersebut.*
- Kirakan rintangan tolok setelah terikan dikenakan.*
- Nyatakan jenis tegasan yang dikenakan pada alur tersebut.*
- Kirakan jumlah magnitud bagi tegasan.*

(17 marks/ markah)

QUESTION 5 / SOALAN 5

- a. Determine **four (4)** characteristics of the operational amplifier.

Tentukan empat (4) ciri penguat kendalian.

(3 marks/ markah)

- b. The Wheatstone bridge in Figure Q5 (b) is used as quarter-bridge where R_4 is connected to a strain gauge. Given that $R_1 = R_2 = R_3 = R$ where R is the initial resistance of the strain gauge. The strain gauge with gauge factor $K = 2.0$ and initial resistance 350Ω is used. The voltage supply $10 V$. The gauge experiences a strain of $1450 \mu\text{m/m}$.

- i. Show that the output of the bridge is

$$V_o = \frac{\Delta R}{4R} E$$

- ii. Find the change in resistance of the strain gauge, ΔR .

- iii. Calculate the output voltage.

Titi Wheatstone dalam gambar rajah Q5 (b) digunakan sebagai titi suku di mana R_4 disambungkan kepada tolok terikan. Diberi bahawa $R_1 = R_2 = R_3 = R$ dimana R ialah rintangan awal tolok terikan. Tolok terikan dengan faktor $K = 2.0$ dan rintangan awal 350Ω digunakan. Voltan bekalan ialah $10 V$. Tolok tersebut mengalami terikan $1450 \mu\text{m/m}$.

- i. Tunjukkan bahawa keluaran titi tersebut ialah

$$V_o = \frac{\Delta R}{4R} E$$

- ii. Dapatkan perubahan rintangan tolok terikan, ΔR .

- iii. Kirakan voltan keluaran.

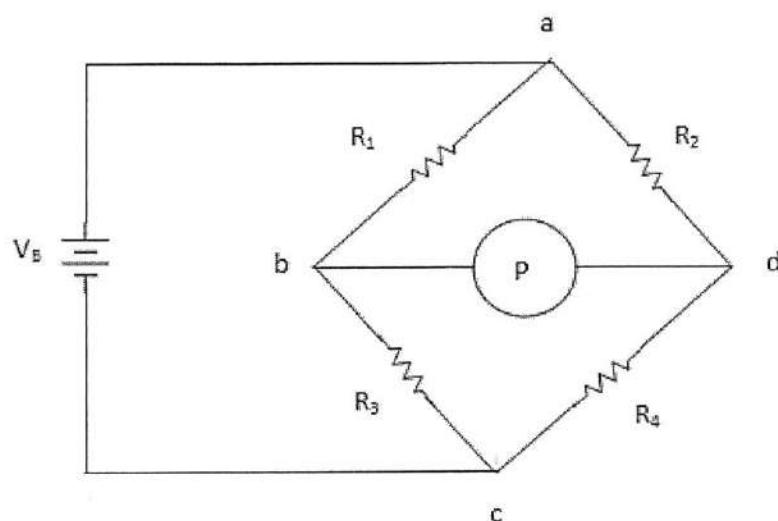


Figure Q5 (b) / Gambar rajah Q5 (b)

(14 marks/ markah)

- c. List down **three (3)** advantages IEEE488 compared to RS232.

Senaraikan tiga (3) kebaikan IEEE488 berbanding dengan RS232.

(3 marks/ markah)

[100 MARKS / 100 MARKAH]

END OF QUESTION PAPER / KERTAS SOALAN TAMAT

