



**UTM**  
UNIVERSITI TEKNOLOGI MALAYSIA

Sekolah Pendidikan Profesional dan  
Pendidikan Berterusan  
(UTMSPACE)

---

**FINAL EXAMINATION / PEPERIKSAAN AKHIR  
SEMESTER 2 – SESSION 2017 / 2018  
PROGRAM KERJASAMA**

COURSE CODE : DDWE 2163  
KOD KURSUS

COURSE NAME : ELECTRONICS II / ELEKTRONIK II  
NAMA KURSUS

YEAR / PROGRAMME : 2 DDWB / DDWE / DDWK  
TAHUN / PROGRAM

DURATION : 2 HOURS 30 MINUTES / 2 JAM 30 MINIT  
TEMPOH

DATE : APRIL 2018  
TARIKH

---

INSTRUCTION : ANSWER ALL QUESTION  
ARAHAN : JAWAB SEMUA SOALAN.







PART A (30 MARKS) / BAHAGIAN A (30 MARKAH)

- Q1 Given a voltage gain of BJT amplifier,  $A_v = -300$ . Sketch the frequency response on the  $|A_v| \text{ dB}$  scale. Label the mid band frequency gain (in dB), the low and the high cut-off frequency.

Diberi gandaan voltan penguat BJT,  $A_v = -300$ . Lakarkan sambutan frekuensi pada skala  $|A_v| \text{ dB}$ . Labelkan gandaan frekuensi pertengahan (dalam dB), frekuensi potong rendah dan frekuensi potong tinggi.

(5 marks / markah)

- Q2. State 1 (one) advantage and 1(one) disadvantage of FET as amplifier.

Nyatakan 1 (satu) kelebihan dan 1(satu) keburukan FET sebagai penguat.

(2 marks / markah)

- Q3. Referring to Figure Q3,

- sketch and label the output waveform,  $V_o$  with reference to input,  $V_i$ .
- calculate the total voltage gain in decibel (dB).

Merujuk kepada Rajah Q3,

- lakar dan label gelombang keluaran,  $V_o$  dengan merujuk kepada masukan,  $V_i$ .
- kirakan jumlah gandaan voltan dalam desibel (dB).

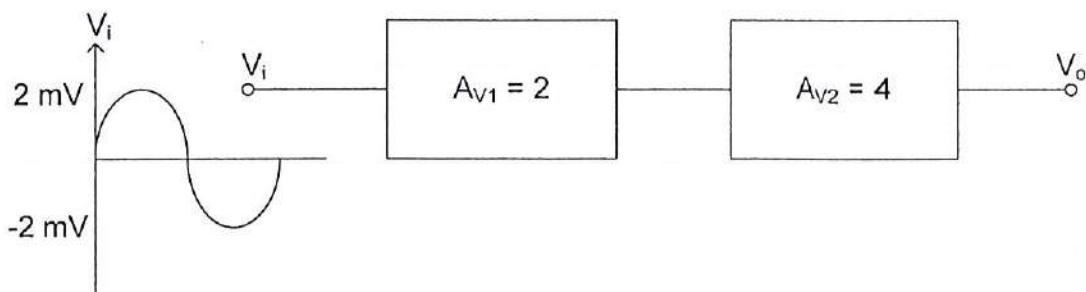


Figure Q3/Rajah Q3

(8 marks / markah)



- Q4 a) With an aid of a simple diagram, formulate the gain of the following Op-Amps:
- i) Inverting amplifier.
  - ii) Non-inverting amplifier.
  - iii) Voltage follower .

Dengan bantuan gamba rajah mudah, terbitkan gandaan Op-Amp berikut:

- i) Penguat songsang
- ii) Penguat tak songsang
- iii) Pengikut voltan.

- b) Determine the output voltage of an Op-amp for input voltages of  $V_{i1}=150\mu V$  and  $V_{i2}= 140\mu V$ . The amplifier has a differential gain  $A_d = 4000$  and the CMRR is:
- i) 100
  - ii)  $10^5$

Tentukan voltan keluaran sebuah Op-Amp untuk voltan masukkan  $V_{i1}=150\mu V$  dan  $V_{i2}= 140\mu V$ . Gandaan beza penguat  $A_d = 4000$  dan nilai CMRR ialah:

- i) 100
- ii)  $10^5$

(8 marks / markah)

- Q5 a) With aid of diagram, explain the differences between negative feedback and positive feedback.  
*Berpandukan gamba rajah, terangkan perbezaan antara suapbalik negatif dan suapbalik positif.*
- b) State four (4) advantages of negative feedback.  
*Nyatakan empat (4) kelebihan suapbalik negatif.*

(7 marks / markah)



**PART B ( 70 MARKS ) / BAHAGIAN B ( 70 MARKAH )**

Q6 Refer to Figure Q6.

- (a) Sketch and label ac equivalent circuit using  $r_e$  model.
- (b) Derive the voltage gain  $A_v$  as the function of  $R_C$ ,  $r_o$  and  $r_e$ .
- (c) Given  $V_{CC} = 20 \text{ V}$ ,  $R_B = 420 \text{ k}\Omega$ ,  $R_C = 1.5 \text{ k}\Omega$ ,  $R_E = 0.56 \text{ k}\Omega$ ,  $\beta = 100$ ,  $r_o = \infty$ . Determine :
  - i) Voltage gain,  $A_v$ .
  - ii) Input impedance,  $Z_i$ ,
  - iii) Output impedance,  $Z_o$ ,
  - iv) Current gain,  $A_i$ .
- (d) Given  $v_i = 10 \sin \omega t \text{ mV}$ , sketch and label  $v_o$  with reference to  $v_i$ .

*Rujuk pada Rajah Q6.*

- (a) Lakar dan labelkan litar setara au model  $r_e$ .
- (b) Dapatkan gandaan voltan,  $A_v$  dalam sebutan  $R_C$ ,  $r_o$  dan  $r_e$ .
- (c) Diberi  $V_{CC} = 20 \text{ V}$ ,  $R_B = 420 \text{ k}\Omega$ ,  $R_C = 1.5 \text{ k}\Omega$ ,  $R_E = 0.56 \text{ k}\Omega$ ,  $\beta = 100$ ,  $r_o = \infty$ . Tentukan :
  - i) Gandaan voltan,  $A_v$ .
  - ii) Galangan masukan,  $Z_i$ ,
  - iii) Galangan keluaran,  $Z_o$ ,
  - iv) Gandaan arus,  $A_i$ .
- (d) Diberi  $v_i = 10 \sin \omega t \text{ mV}$ , lakar dan labelkan  $v_o$  merujuk kepada  $v_i$ .


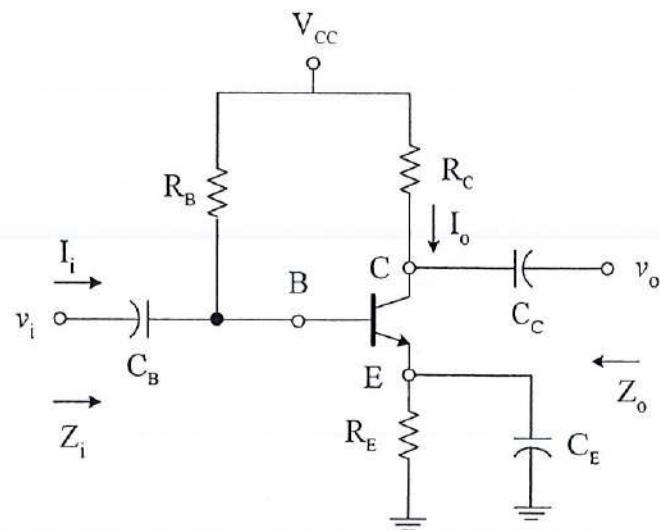


Figure Q6 / Rajah Q6

(15 marks / markah)

 






Q8. Refer to Figure Q8.

- Draw and label the ac equivalent circuit.
- Calculate  $I_D$ ,  $V_{GSQ}$ ,  $g_m$ ,  $Z_i$ ,  $Z_o$ ,  $A_{V1}$ ,  $A_{V2}$ , and  $A_V$ .
- Sketch and label the output voltage,  $V_o$  with reference to the input voltage,  $V_i$ . Given  $V_i = 1mV_{rms}$  sine wave.

Rujuk pada Rajah Q8.

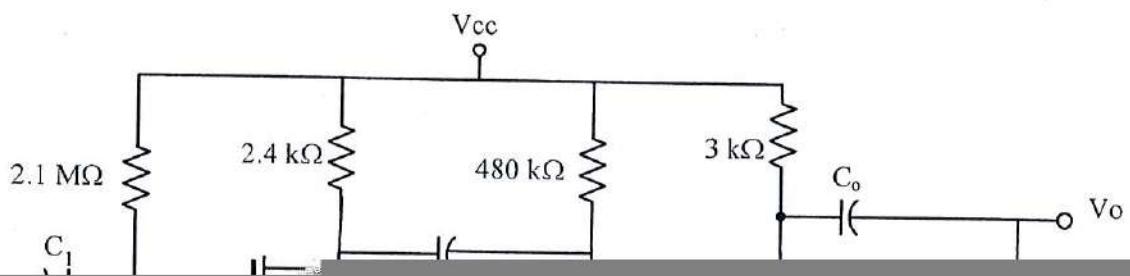- Lukis dan labelkan litar setara au.
- Kirakan  $I_D$ ,  $V_{GSQ}$ ,  $g_m$ ,  $Z_i$ ,  $Z_o$ ,  $A_{V1}$ ,  $A_{V2}$  dan  $A_V$ .
- Lakar dan labelkan voltan keluaran,  $V_o$  dengan merujuk pada voltan masukan,  $V_i$ . Diberi  $V_i = 1mV_{rms}$  gelombang sinus.





Q9 a) Referring to the Op-Amp circuit in Figure Q9(a),

- i) named each of amplifier used in this multistage Op-Amp.
- ii) calculate the output voltage  $V_{o1}$ ,  $V_{o2}$  and  $V_o$ .

Merujuk pada litar Op-Amp dalam Rajah Q9(a),

- i) namakan setiap penguat dalam Op Amp berbilang tahap.
- ii) tentukan voltan keluaran  $V_{o1}$ ,  $V_{o2}$  dan  $V_o$ .

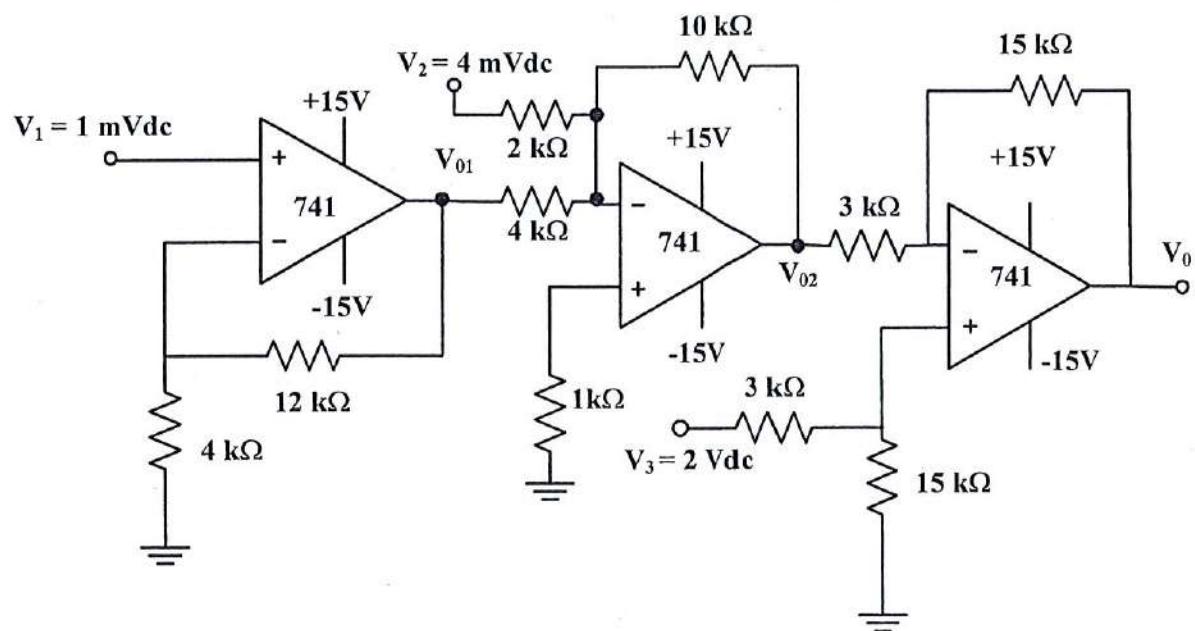


Figure Q9 (a) / Rajah Q9 (a)



- b) Referring to Figure Q9(b),
- state the application of the operational amplifier,
  - sketch the output voltage,  $V_o$ .

*Merujuk pada Rajah Q9(b)*

- nyatakan kegunaan penguat kendalian tersebut,
- lakarkan voltan keluaran,  $V_o$ .

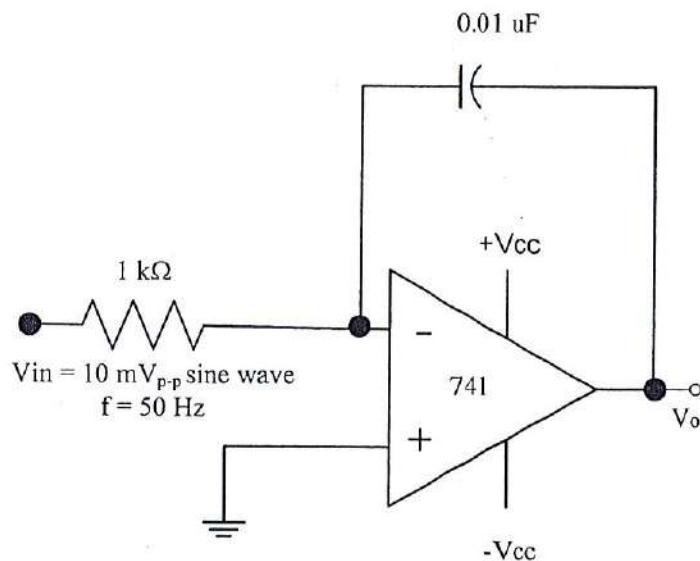


Figure Q9 (b) / Rajah Q9(b)

(20 marks / markah)

