



**KOLEJ YAYASAN PELAJARAN JOHOR
ONLINE FINAL EXAMINATION**

COURSE NAME : POWER ELECTRONICS
COURSE CODE : DKE 3063
SESSION : DECEMBER 2021
DURATION : 2 HOURS 30 MINUTES

**INSTRUCTION TO CANDIDATES /
ARAHAN KEPADA CALON**

1. This examination paper consists of **FIVE (5)** questions. Answer **ALL** questions. /
*Kertas soalan ini mengandungi **LIMA (5)** soalan. Jawab **SEMUA** soalan.*
2. Students are allowed to refer to resources such as lecture notes, books, internet or any other relevant resources. /
Pelajar dibenarkan merujuk kepada sumber seperti nota kuliah, buku, internet atau mana - mana sumber yang berkaitan.
3. Answer ALL questions in the answer sheet which is A4 size paper (or other paper with the consent of the relevant lecturer). /
*Jawab **SEMUA** soalan di dalam kertas jawapan iaitu kertas bersaiz A4 (atau lain-lain kertas dengan persetujuan pensyarah berkaitan).*
4. Write your details as follows in the upper left corner for each answer sheet: /
Tulis butiran anda sepertimana berikut di penjuru atas kiri bagi setiap kertas jawapan:
 - i. Student Full Name / *Nama Penuh Pelajar*
 - ii. Identification Card (I/C) No. / *No. Kad Pengenalan*
 - iii. Class Section / *Seksyen Kelas*
 - iv. Course Code / *Kod Kursus*
 - v. Course Name / *Nama Kursus*
 - vi. Lecturer Name / *Nama Pensyarah*
5. Each answer sheet must have a page number written at the bottom right corner. /
Setiap helai kertas jawapan mesti ditulis nombor muka surat di penjuru bawah kanan.
6. Answers should be handwritten, neat and clear. /
Jawapan hendaklah ditulis tangan, kemas dan jelas.

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIBERITAHU**

This examination paper consists of **9** printed pages including front page
*Kertas soalan ini mengandungi **9** halaman bercetak termasuk muka hadapan*

This paper contains of **FIVE (5)** questions. Answer **ALL** questions.

Answer the questions in an answer sheet.

*Kertas soalan ini mengandungi **LIMA (5)** soalan. Jawab **SEMUA** soalan.*

Sila jawab dalam kertas jawapan.

QUESTION 1 / SOALAN 1

- a) Name **two (2)** types of circuit converter. .
(2 marks / markah)
- b) State **three (3)** advantages of a three phase rectifier over a single phase rectifier.
(3 marks / markah)
- c) If the full wave center tapped rectifier has a purely resistive load of R , determine:
- The efficiency.
 - Form factor.
 - The ripple factor.
 - Transformer utilization factor.
 - Peak inverse voltage current.
 - Creast factor for input current.
- (15 marks / markah)**
- a) *Namakan **dua (2)** jenis litar penukar.*
- b) *Nyatakan **tiga (3)** kelebihan litar penerus tiga fasa berbanding satu fasa.*
- c) *Sekiranya penerus ketuk pembahagi gelombang penuh mempunyai beban tulen R , tentukan:*
- Kecekapan.*
 - Faktor bentuk.*
 - Faktor riak.*
 - Faktor penggunaan pengubah.*
 - Arus voltan puncak balikan.*
 - Faktor puncak arus masukan.*

QUESTION 2 / SOALAN 2

- a) Give **one (1)** difference between Silicon Controlled Rectifier and Diode Rectifier in power electronics.
(2 marks / markah)
- b) Sketch and label the SCR equivalent circuit (PNP-NPN).
(3 marks / markah)
- c) If the half wave controlled rectifier has a purely resistive load of R and the delay is $\alpha = \pi/2$, determine:
- Rectification efficiency.
 - Form factor
 - Ripple factor
 - TUF
 - PIV

(15 marks / markah)

- a) Berikan **satu (1)** perbezaan antara Penerus Terkawal Silikon dan Diod Penerus dalam elektronik kuasa.
- b) Lakar dan labelkan litar setara SCR(PNP-NPN).
- c) Jika penerus terkawal gelombang separuh mempunyai beban resistif tulen R dan kelewatannya adalah $= \pi/2$, tentukan:
- Kecekapan pembedulan.
 - Faktor bentuk.
 - Faktor riak.
 - TUF
 - PIV

QUESTION 3 / SOALAN 3

- a) State **two (2)** methods of controlling an AC voltage controllers.
(2 marks / markah)
- b) State **three (3)** disadvantages of having a low power factor.
(3 marks / markah)
- c) An AC voltage controller in **Figure Q3(c)** has a resistive load of $R = 10 \Omega$ and the rms phase input voltage is $V_s = 120 \text{ V}$, 60 Hz. The thyristors switch is on for $n = 25$ cycles and is off for $m = 75$ cycles. Determine:
- Rms output voltage.
 - Input power factor.
 - Average and rms current of thyristors.
 - Output waveform for the circuit.
- (15 marks / markah)

- a) Nyatakan **dua (2)** kaedah kawalan bagi voltan pengawal AU.
- b) Nyatakan **tiga (3)** keburukan mempunyai faktor kuasa rendah.
- c) Pengawal voltan AU pada **Rajah Q3(c)** mempunyai beban tulen $R = 10 \Omega$ dan voltan masukan fasa pmkd adalah $V_s = 120 \text{ V}$, 60 Hz. Suis thyristor dihidupkan untuk $n = 25$ kitaran dan dimatikan untuk $m = 75$ kitaran. Tentukan:
- Voltan keluaran pmkd.
 - Faktor kuasa masukan.
 - Arus purata dan pmkd untuk thyristor.
 - Gelombang keluaran bagi litar.

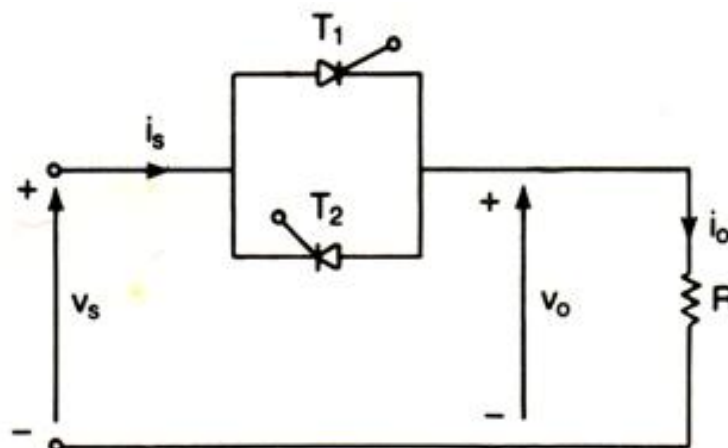


Figure Q3(c) / Rajah Q3(c)

QUESTION 4 / SOALAN 4

- a) Define a DC to DC converter. (2 marks / markah)
- b) Name **three (3)** basic types of switching-mode regulators. (3 marks / markah)
- c) A boost regulator has an input voltage of $V_s = 5$ V. The average output voltage $V_a = 15$ V and the average load current $I_a = 0.5$ A. The switching frequency is 25 kHz. If $L = 150$ μ H and $C = 220$ μ F. Determine:
- i. The duty cycle, k .
 - ii. The ripple current of inductor ΔI .
 - iii. The peak current of inductor I_2 .
 - iv. The ripple voltage of filter capacitor ΔV_C .

(15 marks / markah)

- a) *Definisikan penukar AT ke AT.*
- b) *Namakan **tiga (3)** jenis asas bagi pengatur mod-pensuisan.*
- c) *Pengawal selia mempunyai masukan voltan $V_s = 5\text{ V}$. Purata voltan keluaran $V_a = 15\text{ V}$ dan purata beban purata arus $I_a = 0.5\text{ A}$. Frekuensi pensuisan ialah 25 kHz . Jika $L = 150\ \mu\text{H}$ dan $C = 220\ \mu\text{F}$. Tentukan:*
- Kitar tugas, k .*
 - Arus riak daripada pearly ΔI .*
 - Arus puncak pearly I_2 .*
 - Voltan riak penapis pearly ΔV_C .*

QUESTION 5 / SOALAN 5

- a) State the definition of inverter gain. **(2 marks / markah)**
- b) State **three (3)** types of common power electronics devices commonly used in controller inverter converter. **(3 marks / markah)**
- c) Refer to **Figure Q5(c)**.
- Name the circuit configuration.
 - Briefly explain the circuit operation.
 - Sketch the output waveform, V_o .
- (15 marks / markah)**

- a) Nyatakan definisi gandaan penyongsang.
- b) Nyatakan **tiga (3)** jenis peranti elektronik kuasa yang umum digunakan dalam penukar songsang terkawal.
- c) Rujuk kepada **Rajah Q5(c)**.
- Namakan konfigurasi litar tersebut.
 - Terangkan secara ringkas kendalian litar tersebut.
 - Lakarkan gelombang keluaran, V_o .

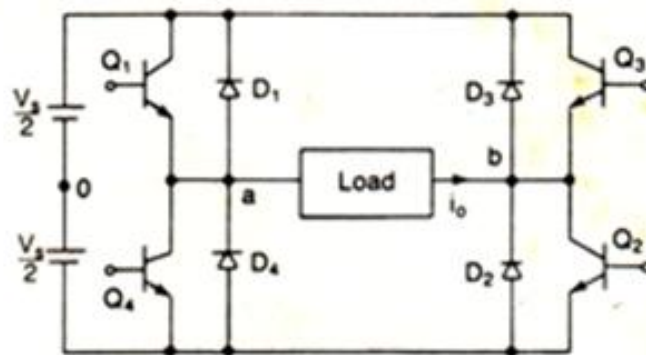


Figure Q5(c) / Rajah Q5(c)

[100 MARKS / MARKAH]

END OF QUESTION PAPER / KERTAS SOALAN TAMAT

Attachment 1 / Lampiran 1

Uncontrolled rectifier

$$\begin{aligned}
 V_{o(\text{dc})} &= 0.318V_m & V_{o(\text{rms})} &= 0.5 V_m \\
 V_{o(\text{dc})} &= \frac{V_m}{2\pi} [1 - \cos(\beta)] & V_{o(\text{rms})} &= \frac{V_m}{2} \sqrt{\frac{\beta}{\pi} - \frac{\sin(2\beta)}{2\pi}} \\
 V_{o(\text{dc})} &= 0.6366 V_m & V_{o(\text{rms})} &= 0.707 V_m \\
 V_{o(\text{dc})} &= 1.654V_m & V_{o(\text{rms})} &= 1.6554 V_m \\
 V_{o(\text{dc})} &= 0.827V_m & V_{o(\text{rms})} &= 0.8407 V_m
 \end{aligned}$$

Controlled rectifier

$$\begin{aligned}
 V_{o(\text{dc})} &= \frac{V_m}{2\pi} (1 + \cos \alpha) & V_{o(\text{rms})} &= \frac{V_m}{2} \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2} \\
 V_{o(\text{dc})} &= \frac{2V_m}{\pi} \cos \alpha & V_{o(\text{rms})} &= V_m \left[\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi} \right]^{1/2}
 \end{aligned}$$

Principle of AC Voltage controller

$$\begin{aligned}
 V_s &= \sqrt{2}V_s \sin \omega t \\
 V_o &= V_s \sqrt{\frac{n}{m+n}} = V_s \sqrt{k}
 \end{aligned}$$

$$V_o(\text{rms}) = V_s \left[\frac{1}{2\pi} \left(2\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}$$

$$V_o(\text{dc}) = \frac{\sqrt{2}V_s}{2\pi} (\cos \alpha - 1)$$

AC Voltage controller : Single Phase

$$V_o(\text{rms}) = V_s \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{\alpha} \right) \right]^{1/2} \quad V_o(\text{rms}) = V_s \left[\frac{1}{\pi} \left(\beta - \alpha + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right) \right]^{1/2}$$

AC Voltage controller : Three Phase Half waveFor $0^\circ \leq \alpha < 90^\circ$:

$$V_o(\text{rms}) = \sqrt{3}V_s \left[\frac{1}{\pi} \left(\frac{\pi}{3} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{8} \right) \right]^{1/2}$$

For $90^\circ \leq \alpha < 120^\circ$:

$$V_o(\text{rms}) = \sqrt{3}V_s \left[\frac{1}{\pi} \left(\frac{11\pi}{24} - \frac{\alpha}{2} \right) \right]^{1/2}$$

For $120^\circ \leq \alpha < 210^\circ$:

$$V_o(\text{rms}) = \sqrt{3}V_s \left[\frac{1}{\pi} \left(\frac{7\pi}{24} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{16} - \frac{\sqrt{3} \cos 2\alpha}{16} \right) \right]^{1/2}$$

AC Voltage controller : Three Phase Full waveFor $0^\circ \leq \alpha < 60^\circ$:

$$V_o(\text{rms}) = \sqrt{6}V_s \left[\frac{1}{\pi} \left(\frac{\pi}{6} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{8} \right) \right]^{1/2}$$

For $60^\circ \leq \alpha < 90^\circ$:

$$V_o(\text{rms}) = \sqrt{6}V_s \left[\frac{1}{\pi} \left(\frac{\pi}{12} + \frac{3\sin 2\alpha}{16} + \frac{\sqrt{3} \cos 2\alpha}{16} \right) \right]^{1/2}$$

For $120^\circ \leq \alpha < 210^\circ$:

$$V_o(\text{rms}) = \sqrt{6}V_s \left[\frac{1}{\pi} \left(\frac{5\pi}{24} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{16} + \frac{\sqrt{3} \cos 2\alpha}{16} \right) \right]^{1/2}$$