



**KOLEJ YAYASAN PELAJARAN JOHOR
FINAL EXAMINATION**


COURSE NAME : INSTRUMENTATION AND MEASUREMENT
COURSE CODE : DEE 1053
EXAMINATION : JUNE 2024
DURATION : 2 HOURS 30 MINUTES

**INSTRUCTION TO CANDIDATES /
ARAHAN KEPADA CALON**

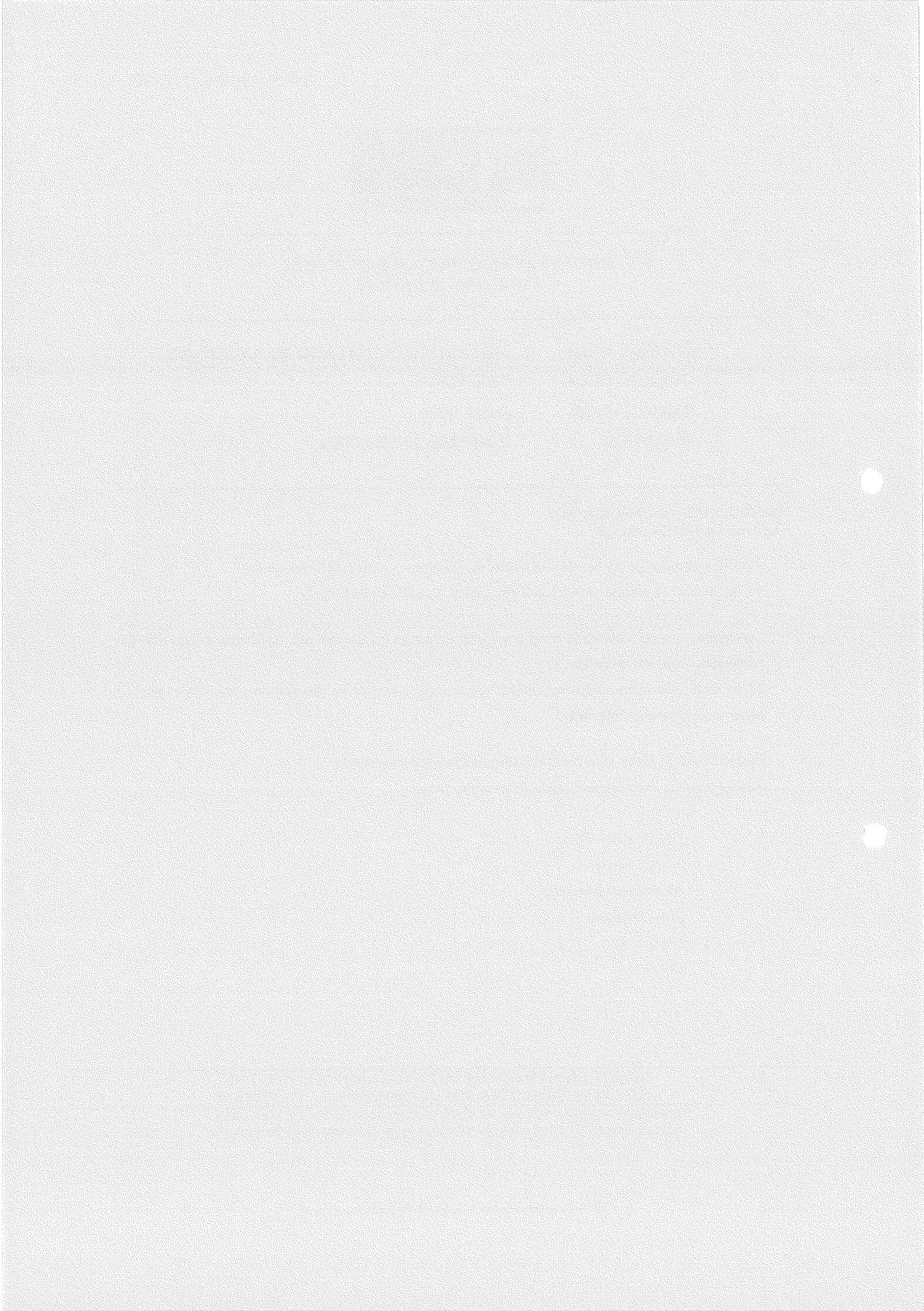1. This examination paper consists of **FIVE (5)** questions. Answer **ALL** questions. /
*Kertas soalan ini mengandungi **LIMA (5)** soalan. Jawab **SEMUA** soalan.*
2. Candidates are not allowed to bring any material/note to the examination hall/room except with the permission from the invigilator. /
Calon tidak dibenarkan untuk membawa sebarang bahan/nota ke dewan/bilik peperiksaan tanpa kebenaran daripada pengawas.
3. Please check to make sure that this examination pack consist of: /
Pastikan kertas soalan peperiksaan ini mengandungi:
 - i. The Question Paper /
Kertas Soalan
 - ii. An Answering Booklet /
Buku Jawapan
 - iii. Attachment 1 /
Lampiran 1

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALANINI SEHINGGA DIBERITAHU**

This examination paper consists of **10** printed pages including front page
*Kertas soalan ini mengandungi **10** muka surat termasuk kulit hadapan*



This part contains **FIVE (5)** questions. Answer **ALL** questions in the Answering Booklet.

*Kertas soalan ini mengandungi **LIMA (5)** soalan. Jawab **SEMUA** soalan di dalam Kertas Jawapan.*

QUESTION 1 / SOALAN 1

- a) Calibration is the process of comparing and correcting the output of an instrument using standard instrument values. Explain two (2) advantages of calibration.

(4 marks/ markah)

- b) Explain two (2) types of errors that exist in a measurement.

(4 marks/ markah)

- c) Refer to **Figure 1**, calculate the power dissipated and the limiting error, if current $2.0 \pm 0.01\text{A}$ flows through a $100 \pm 0.2\Omega$ resistor.

(12 marks/ markah)

- a) *Tentukuran ialah proses membandingkan dan membetulkan keluaran sesuatu alatan menggunakan nilai alatan yang piawai. Terangkan dua (2) kebaikan tentukuran.*

- b) *Terangkan dua (2) jenis ralat yang wujud dalam sesuatu pengukuran.*

- c) *Merujuk Rajah 1, kirakan kuasa terlesap dan ralat mengehad, jika arus bernilai $2.0 \pm 0.01\text{A}$ mengalir melalui perintang $100 \pm 0.2\Omega$.*

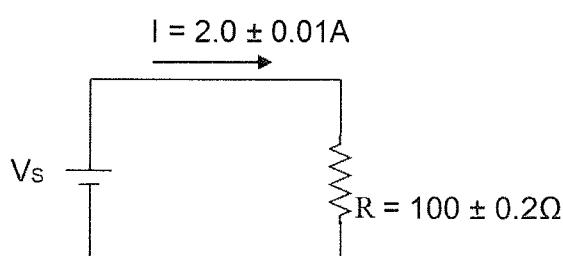


Figure 1 / Rajah 1

QUESTION 2 / SOALAN 2

- a) A $100 \mu\text{A}$ full scale deflection current meter movement is used in an Ayrton multi-range ampere meter circuit. The meter movement has an internal resistance, $R_m = 2 \text{ k}\Omega$. Determine the value of the shunt resistance, if the meter has a range of 25 mA , 65 mA and 100 mA .

(10 marks/ markah)

- b) Figure 2 shows a full-wave rectifier type AC meter with a range of 1 V . The diodes have a forward resistance each of 100Ω while the parameters of the d'Arsonval movement are $50 \mu\text{A}$, 200Ω . It is required that $I_{sh} = I_m$.


- i. Calculate the shunt resistor, R_{sh} .
- ii. Calculate the multiplier resistor, R_s .
- iii. Calculate the AC sensitivity of the meter, S_{ac} .

(10 marks/ markah)

- a) Gerakan meter arus pesongan skala penuh $100 \mu\text{A}$ digunakan dalam litar meter ampere berbilang julat pirau Ayrton. Gerakan meter tersebut mempunyai rintangan dalam, $R_m = 2 \text{ k}\Omega$. Tentukan nilai rintangan pirau, jika meter tersebut mempunyai julat 25 mA , 65 mA dan 100 mA .

- b) Rajah 2 menunjukkan meter AU jenis penerus penuh-gelombang berjulat 1 V . Setiap diod mempunyai rintangan ke depan 100Ω sementara parameter gerakan d'Arsonval ialah $50 \mu\text{A}$, 200Ω . Dikehendaki supaya $I_{sh} = I_m$.

- i. Kirakan rintangan pirau, R_{sh} .
- ii. Kirakan rintangan pendarab, R_s .
- iii. Kirakan kepekaan AU meter, S_{au} .

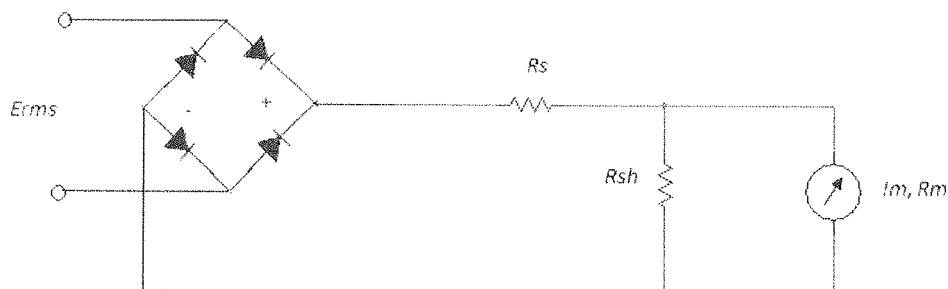**Figure 2 / Rajah 2**

QUESTION 3 / SOALAN 3

- a) Briefly explain four (4) advantages of a digital voltmeter as compared to an analogue voltmeter.

(12 marks/ markah)

- b) An analogue-to-digital converter uses an integrator in its input part.
- Sketch an integrator circuit with a resistor $10 \text{ k}\Omega$ and a capacitor $10 \mu\text{F}$.
 - If the integrator input voltage is 1 V, calculate the integrator output voltage after 0.1 second.
 - Sketch the form of the integrator output voltage.

(8 marks/ markah)

- a) Terangkan dengan ringkas empat (4) kelebihan meter volt digital berbanding dengan meter volt analog.
- b) Penukar analog-ke-digit menggunakan pengamir pada bahagian masukan litar.
- Lakarkan litar pengamir dengan nilai perintang $10 \text{ k}\Omega$ dan pemuat $10 \mu\text{F}$.
 - Jika voltan masukan pengamir ialah 1 V, kirakan voltan keluaran pengamir tersebut selepas 0.1 saat.
 - Lakarkan bentuk voltan keluaran pengamir.

QUESTION 4 / SOALAN 4

- a) With the aid of diagrams, explain two (2) transducer functions.

(6 marks/ markah)

- b) Figure 3 shows the LVDT and its specification.


- Explain briefly the operation of the LVDT.
- Calculate the displacement if the output voltage is 2.5 mV.
- Sketch the graph of the output voltage versus displacement if the output of the LVDT is at the range of -4 mV to +2.5 mV.

(14 marks/ markah)

- a) Dengan bantuan gambar rajah, terangkan dua (2) fungsi transduser.

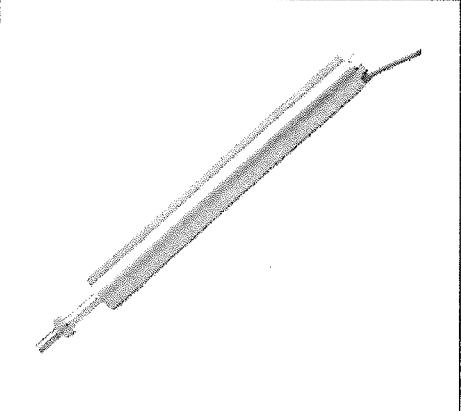- b) Rajah 3 menunjukkan LVDT dan spesifikasinya.

- Terangkan dengan ringkas prinsip pengendalian LVDT.
- Kirakan anjakan jika voltan keluaran ialah 2.5 mV.
- Lakarkan graf voltan keluaran melawan anjakan jika keluaran LVDT pada julat -4 mV hingga +2.5 mV.



The specification of LVDT is as follow: Spesifikasi LVDT ialah seperti berikut :	
Input voltage / Voltan masukan	: 10 V
Output voltage / Voltan keluaran	: ± 5 mV
Displacement range / Julat anjakan	: ± 5 inch

Figure 3 / Rajah 3

QUESTION 5 / SOALAN 5

- a) This question is related to Wien bridge circuit.
- Sketch the circuit of Wien bridge circuit.
 - Prove that when the bridge is balanced:

$$\frac{R_1}{R_3} + \frac{C_3}{C_1} = \frac{R_2}{R_4}$$

$$f = \frac{1}{2\pi \sqrt{C_1 C_3 R_1 R_3}}$$

- The frequency calculated using the Wien AC bridge is 40 Hz. If $R_1 = 400 \Omega$, $C_1 = 5.5 \mu F$ and $R_3 = R_4 = 1 k\Omega$. Calculate C_3 and R_2 .

(14 marks/ markah)

- b) List down **three (3)** features of RS232.

(6 marks/ markah)

- a) *Soalan ini berkaitan dengan litar titi Wien.*

- Lukiskan litar bagi titi Wien.*
- Buktikan bahawa titi seimbang apabila:*

$$\frac{R_1}{R_3} + \frac{C_3}{C_1} = \frac{R_2}{R_4}$$

$$f = \frac{1}{2\pi \sqrt{C_1 C_3 R_1 R_3}}$$

- Frekuensi yang dikira dengan menggunakan titi Wien adalah 40 Hz. Jika $R_1 = 400 \Omega$, $C_1 = 5.5 \mu F$ dan $R_3 = R_4 = 1 k\Omega$. Kirakan C_3 and R_2 .*

- b) *Senaraikan tiga (3) ciri RS232.*

[100 MARKS / MARKAH]**END OF QUESTION PAPER / KERTAS SOALAN TAMAT**

Attachment 1 / Lampiran 1

Measurement and Error / Ralat dan Pengukuran

Absolute Error, e <i>Ralat Mutlak, e</i>	$Y_n - X_n$	Standard Deviation <i>Sisihan Piawaian</i>	$\sigma = \sqrt{\frac{\sum_{k=1}^n d_k^2}{n-1}}$										
Percent Error, %e <i>Peratus Ralat, %e</i>	$\frac{e}{Y_n} \times 100\%$	Deviation Sisihan	$d_1 = x_1 - \bar{x}$ $d_2 = x_2 - \bar{x}$ $d_3 = x_3 - \bar{x}$ $d_n = x_n - \bar{x}$										
Accuracy, a <i>Kejituuan, a</i>	100% – Peratus ralat	Average deviation <i>Sisihan purata</i>	$D = \frac{\sum_{k=1}^n d_k }{n}$										
Precision <i>Kepersisan</i>	$1 - \left \frac{X_n - \bar{X}}{\bar{X}} \right $	Arithmetic mean / average <i>Purata / min aritmetik</i>	$\bar{X} = \frac{\sum_{k=1}^n x_k}{n}$										
Combined Measurement Error <i>Gabungan ralat pengukuran</i>		<table border="1"> <thead> <tr> <th>Operasi matematik</th> <th>Ralat gabungan</th> </tr> </thead> <tbody> <tr> <td>$C = A + B$</td> <td>$\Delta C = \pm(\Delta A + \Delta B)$</td> </tr> <tr> <td>$C = A - B$</td> <td>$\Delta C = \pm(\Delta A + \Delta B)$</td> </tr> <tr> <td>$C = A \times B$</td> <td>$\% C = \pm(\% A + \% B)$</td> </tr> <tr> <td>$C = A/B$</td> <td>$\% C = \pm(\% A + \% B)$</td> </tr> </tbody> </table>		Operasi matematik	Ralat gabungan	$C = A + B$	$\Delta C = \pm(\Delta A + \Delta B)$	$C = A - B$	$\Delta C = \pm(\Delta A + \Delta B)$	$C = A \times B$	$\% C = \pm(\% A + \% B)$	$C = A/B$	$\% C = \pm(\% A + \% B)$
Operasi matematik	Ralat gabungan												
$C = A + B$	$\Delta C = \pm(\Delta A + \Delta B)$												
$C = A - B$	$\Delta C = \pm(\Delta A + \Delta B)$												
$C = A \times B$	$\% C = \pm(\% A + \% B)$												
$C = A/B$	$\% C = \pm(\% A + \% B)$												

Analog Meter / Meter Analog

Shunt Resistance Rintangan Pirau	$R_{sh} = \frac{V_{sh}}{I_{sh}} = \frac{I_m R_m}{I_{sh}} = \frac{I_m}{I_{sh}} R_m = \frac{I_m}{I - I_m} \times R_m$ <p>Where : $I = nI_m$ Dimana</p>
Aryton Shunt Ampere Meter Meter Ampere Pirau Aryton	$R_b + R_c = \frac{I_m (R_{sh} + R_m)}{I_2}$ $R_a = R_{sh} - (R_b + R_c)$ $R_c = \frac{I_m (R_{sh} + R_m)}{I_3}$
Sensitivity Kepekaan	$\text{Kepekaan} = \frac{1}{I_{sp}} (\Omega/V)$
Aryton Shunt Voltage Meter Meter Voltan Pirau Aryton	$R_o = S \times \text{Julat} - R_m$ $R_b = S \times \text{Julat} - (R_o + R_m)$ $R_c = S \times \text{Julat} - (R_o + R_b + R_m)$
Half-wave Rectifier and Full-wave Rectifier Penerus Separuh Gelombang dan Penerus Gelombang Penuh	$S_{au} = 0.45 S_{at} \quad \text{or} \quad S_{au} = 0.9 S_{at}$ <p>Where: Dimana</p> $S_{at} = \frac{1}{I_T} \quad S_{au} = \frac{R_T}{\text{Julat}}$ $R_s = R_T - R_d - \frac{R_m R_{sh}}{R_m + R_{sh}}$ $R_s = R_T - 2 R_d - \frac{R_m R_{sh}}{R_m + R_{sh}}$ <p>Where : Dimana</p> $I_{sh} = \frac{E_m}{R_{sh}} \quad I_T = I_{sh} + I_m$ $E_{at} = 0.45 V_{pmkd} \text{ or } 0.9 \times V_{pmkd}$ $R_T = \frac{E_{at}}{I_T}$

Digital Instruments / Alatan Digital

Single Slope Converter Techniques Teknik Penukar Satu Cerun	$V_x = V_{ref} \times \frac{t_1}{t_1 + t_2}$ Bilangan denyut = $t \times f$
Dual Slope Converter Techniques Teknik Penukar Dua Cerun	Capasitor Charging Pemuat Mengecas $V_A = V_i \frac{t_2 - t_1}{RC}$ Capasitor Charging Pemuat Mengecas $V_A = V_{ref} \frac{t_3 - t_2}{RC}$
Voltage to Frequency Converter Techniques Teknik Penukar Voltan ke Frekuensi	$V_i = \frac{f}{50} \quad f = \frac{\text{Bilangan denyut}}{\text{Masa denyutan}}$

Transducers / Tranduser

Strain Gauge Tolok Terikan	$K = \frac{\Delta R/R}{\Delta l/l} \quad G = \frac{\Delta l}{l} \quad F = SA$ $\Delta R = KRG \quad S = GE$
Linear Variable Displacement Transducer (LVDT) Pengubah Kebezaan Boleh Ubah Lelurus (LVDT)	$v_o = v_1 - v_2$ $V_o = \text{Kepekaan} \times V_{in} \times \text{Anjakan}$
Thermocouple Pengganding Suhu	$V_m = V_o + V_r$ $V_o = AT^2 + BT^2$
Resistance Temperature Detector (RTD) Pengesan Suhu Rintangan (RTD)	$R = R_o (1 + \alpha \Delta T)$
Termistor Suhu Rintangan	$R = R_o e^{\beta \left(\frac{1}{T} - \frac{1}{T_o} \right)}$

Signal Conditioning / Penyesuaian Isyarat

Direct Current Bridge <i>Titi Arus Terus</i>		
Wheatstone Quarter Bridge <i>Titi Suku Wheatstone</i>	Wheatstone Half Bridge <i>Titi Separuh Wheatstone</i>	Wheatstone Full Bridge <i>Titi Penuh Wheatstone</i>
$\frac{\Delta R}{4R} E$	$\frac{\Delta R}{2R} E$	$\frac{\Delta R}{R} E$
Alternatif Current Bridge <i>Titi Arus Ulang Alik</i>		
Maxwell Bridge <i>Titi Maxwell</i>	Hay Bridge <i>Titi Hay</i>	
$\frac{1}{Z_1} = \frac{1}{R_1} + j\omega C_1$	$Z_1 = R_1 + \frac{1}{j\omega C_1}$	
$Z_2 = R_2$	$Z_2 = R_2$	
$Z_3 = R_3$	$Z_3 = R_3$	
$Z_x = R_x + j\omega L_x$	$Z_x = R_x + j\omega L_x$	
Schering Bridge <i>Titi Schering</i>	Wien Bridge <i>Titi Wien</i>	
$\frac{1}{Z_1} = \frac{1}{R_1} + j\omega C_1$	$Z_1 = R_1 + \frac{1}{j\omega C_1}$	
$Z_2 = R_2$	$Z_2 = R_2$	
$Z_3 = \frac{1}{j\omega C_3}$	$\frac{1}{Z_3} = \frac{1}{R_3} + j\omega C_3$	
$Z_x = R_x + \frac{1}{j\omega C_x}$	$Z_4 = R_4$	

