



**KOLEJ YAYASAN PELAJARAN JOHOR
ONLINE FINAL EXAMINATION**

COURSE NAME : INSTRUMENTATION
COURSE CODE : DKE 1033
EXAMINATION : DECEMBER 2021
DURATION : 2 HOURS 30 MINUTES

**INSTRUCTION TO CANDIDATES /
ARAHAN KEPADA CALON**

1. This examination paper consists of **ONE (1)** part.
Kertas soalan ini mengandungi SATU (1) bahagian: PART A (100 Markah)
BAHAGIAN A (100 Markah)
2. Answer ALL questions in the answer sheet which is A4 size paper (or other paper with the consent of the relevant lecturer). /
Jawab SEMUA soalan di dalam kertas jawapan iaitu kertas bersaiz A4 (atau lain-lain kertas dengan persetujuan pensyarah berkaitan).
3. Write your details as follows in the upper left corner for each answer sheet: /
Tulis butiran anda seperti mana berikut di penjuru atas kiri bagi setiap kertas jawapan:
 - i. Student Full Name / Nama Penuh Pelajar
 - ii. Identification Card (I/C) No. / No. Kad Pengenalan
 - iii. Class Section / Seksyen Kelas
 - iv. Course Code / Kod Kursus
 - v. Course Name / Nama Kursus
 - vi. Lecturer Name / Nama Pensyarah
4. Each answer sheet must have a page number written at the bottom right corner. /
Setiap helai kertas jawapan mesti ditulis nombor muka surat di penjuru bawah kanan.
5. Answers should be **neat and clear in handwritten form**. /
Jawapan hendaklah ditulis tangan, kemas dan jelas.

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALANINI SEHINGGA DIBERITAHU**

This examination paper consists of 7 printed pages including front page
Kertas soalan ini mengandungi 7 muka surat termasuk kulit hadapan

This part contains of **FIVE (5)** questions. Answer **ALL** questions in the answer sheet.
*Kertas soalan ini mengandungi **LIMA (5)** soalan. Jawab **SEMUA** soalan di dalam kertas jawapan.*

QUESTION 1 / SOALAN 1

- a) Explain **two (2)** suitable times to calibrate the equipment.

*Terangkan **dua (2)** masa yang sesuai bagi menentu-ukur sesuatu peralatan.*

(4 marks/ markah)

- b) Systematic error is one of the types that frequently occur in any measurement. Briefly explain **two (2)** types of errors that are categorized as systematic error.

*Ralat sistematik merupakan salah satu jenis ralat yang sering berlaku di dalam sesuatu pengukuran. Terangkan dengan ringkas **dua (2)** jenis ralat yang dikategorikan sebagai ralat sistematik.*

(4 marks/ markah)

- c) Refer to **Table Q1 (c)**, calculate:

- i. The average value of the readings.
- ii. The deviation.
- iii. Algebraic sum of all deviations.
- iv. The standard deviation.

*Merujuk pada **Jadual Q1 (c)**, kirakan:*

- i. *Nilai purata bacaan.*
- ii. *Sisihan.*
- iii. *Hasil tambah aljabar kesemua sisihan.*
- iv. *Sisihan piawaian.*

Data/ Data	1	2	3	4	5
Readings/ Bacaan	4.5	4.7	5.0	5.2	4.6

Table Q1 (c) / Jadual Q1 (c)**(12 marks/ markah)****QUESTION 2 / SOALAN 2**

- a) Briefly explain the operating principle of the d'Arsonval movement with its diagram.

Terangkan dengan ringkas prinsip pengendalian gerakan d'Arsonval berserta gambar rajahnya.

(4 marks/ markah)

- b) A 1 mA full scale deflection current meter movement is used in an ohmmeter circuit. The meter movement has an internal resistance, $R_m = 100 \Omega$ and a 3 V battery is used in the circuit. Determine:

- The ohmmeter basic circuit.
- The value of the variable resistance, R_z .
- The value of R_x at 20%, 50% and 70% full-scale reflection.

Gerakan meter arus pesongan skala penuh 1 mA digunakan dalam litar meter ohm. Gerakan meter tersebut mempunyai rintangan dalam, $R_m = 100 \Omega$ dan sebuah bateri 3 V digunakan dalam litar tersebut. Tentukan:

- Litar asas meter ohm.
- Nilai rintangan bolehubah, R_z .
- Nilai R_x pada 20%, 50% dan 70% pesongan skala penuh.

(8 marks/ markah)

- c) **Figure Q2 (c)** shows a half-wave rectifier type AC meter with a range of 50 V. The diodes have a forward resistance of $100\ \Omega$ while the parameters of the d'Arsonval movement are $50\ \mu A$, $200\ \Omega$. It is required that $I_{sh} = I_m$.
- Calculate the shunt resistor, R_{sh} .
 - Calculate the multiplier resistor, R_s .
 - Calculate the DC sensitivity of the meter, S_{dc} .

Rajah Q2 (c) menunjukkan meter AU jenis penerus separuh-gelombang berjulat 50 V. Diod mempunyai rintangan ke depan $100\ \Omega$ sementara parameter gerakan d'Arsonval ialah $50\ \mu A$, $200\ \Omega$. Dikehendaki supaya $I_{sh} = I_m$.

- Kirakan rintangan pirau, R_{sh} .
- Kirakan rintangan pendarab, R_s .
- Kirakan kepekaan AT meter, S_{at} .

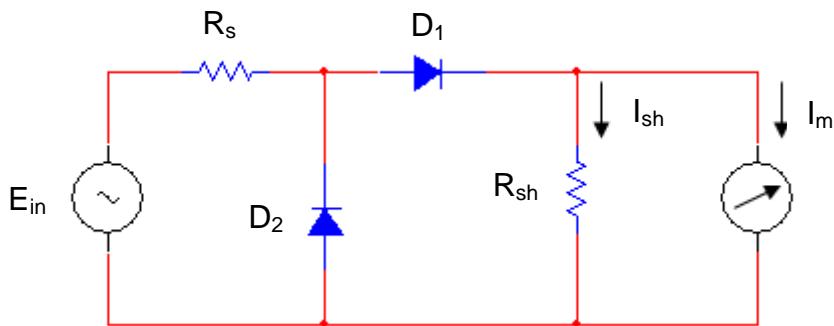


Figure Q2 (c) / Rajah Q2 (c)

(8 marks/ markah)

QUESTION 3 / SOALAN 3

- a) With the aid of diagrams, explain **three (3)** differences between a digital instrument and a digital display instrument.

Dengan bantuan gambar rajah, terangkan **tiga (3)** perbezaan di antara alatan digital dan alatan paparan digital.

(12 marks/ markah)

- b) A digital voltmeter as shown in **Figure Q3 (b)** utilizes a voltage-to-frequency converter as its analogue-to-digital converter. The relationship between the input voltage V_i and the output frequency f is given as:

$$V_i = \frac{f}{100}$$

If 130 pulses are sent to the AND gate in 0.5 seconds, calculate the amplitude of the input voltage V_i .

*Sebuah meter volt digital seperti dalam **Rajah Q3 (b)** menggunakan penukar voltan-ke-frekuensi sebagai penukar analog-ke-digital. Hubungan antara voltan masukan V_i dan frekuensi keluaran f diberikan sebagai:*

$$V_i = \frac{f}{100}$$

Jika 130 denyutan dihantar ke get DAN dalam masa 0.5 saat, kirakan amplitud voltan masukan V_i .

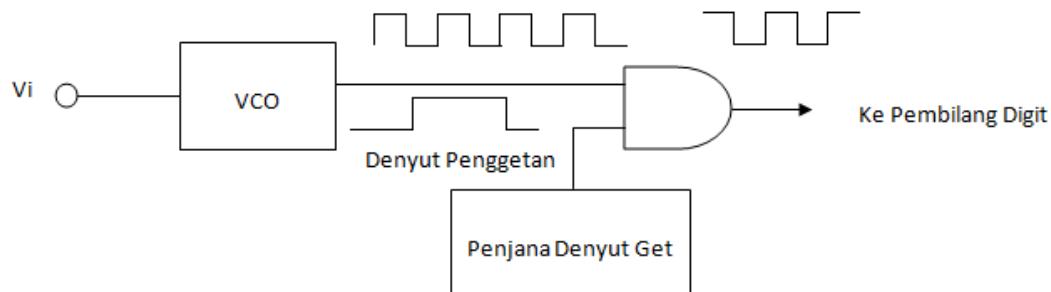


Figure Q3 (b) / Rajah Q3 (b)
(8 marks/ markah)

QUESTION 4 / SOALAN 4

- a) There are eight (8) main factors to be considered when choosing a suitable transducer. Clarify any **three (3)** of these factors.

*Terdapat lapan (8) faktor utama yang perlu dipertimbangkan ketika memilih transduser yang sesuai. Jelaskan mana-mana **tiga (3)** dari faktor tersebut.*

(6 marks/ markah)

- b) A strain gauge with gauge factor 10 and unstrained resistance 100Ω is attached to a steel beam with Young's modulus $E = 2.0 \times 10^6 \text{ N/m}^2$. The beam changes in length from 100 mm to 100.4 mm.
- Give the relationship between the strain and the resistance of the strain gauge.
 - Calculate the strain G experienced by the beam.
 - Calculate the resistance of the gauge after the strain has been applied.
 - Calculate the magnitude of the stress.
 - State **two (2)** main problems in the use of strain gauge.

Sebuah tolak terikan dengan faktor tolok 10 dan rintangan tak terterik 100Ω dilekatkan pada alur keluli dengan modulus Young $E = 2.0 \times 10^6 \text{ N/m}^2$. Alur tersebut berubah panjang dari 100 mm ke 100.4 mm.

- Berikan hubungan antara terikan dan rintangan bagi tolak terikan.*
- Kirakan terikan G yang dialami oleh alur tersebut.*
- Kirakan rintangan tolak setelah terikan dikenakan.*
- Kirakan jumlah magnitud bagi tegasan.*
- Nyatakan **dua (2)** masalah utama di dalam penggunaan tolak terikan.*

(14 marks/ markah)

QUESTION 5 / SOALAN 5

- a) State **three (3)** characteristics of the operational amplifier.

*Nyatakan **tiga (3)** ciri penguat kendalian.*

(3 marks/ markah)

- b) The Wheatstone Bridge in **Figure Q5 (b)** is used as quarter-bridge where R_4 is connected to a strain gauge. Given that $R_1 = R_2 = R_3 = R$ where R is the initial resistance of the strain gauge. The strain gauge with gauge factor $K = 2.0$ and initial resistance 350Ω is used. The voltage supply 10 V . The gauge experiences a strain of $1450 \mu\text{m/m}$.

- i. Prove that the output of the bridge is

$$V_o = \frac{\Delta R}{4R} E$$

- ii. Find the change in resistance of the strain gauge, ΔR .
 iii. Calculate the output voltage.

Titi Wheatstone dalam **Rajah Q5 (b)** digunakan sebagai titi suku di mana R_4 disambungkan kepada tolak terikan. Diberi bahawa $R_1 = R_2 = R_3 = R$ dimana R ialah rintangan awal tolak terikan. Tolok terikan dengan faktor $K = 2.0$ dan rintangan awal 350Ω digunakan. Voltan bekalan ialah $10 V$. Tolok tersebut mengalami terikan $1450 \mu\text{m}/\text{m}$.

- i. Buktiikan bahawa keluaran titi tersebut ialah

$$V_o = \frac{\Delta R}{4R} E$$

- ii. Dapatkan perubahan rintangan tolak terikan, ΔR .
 iii. Kirakan voltan keluaran.

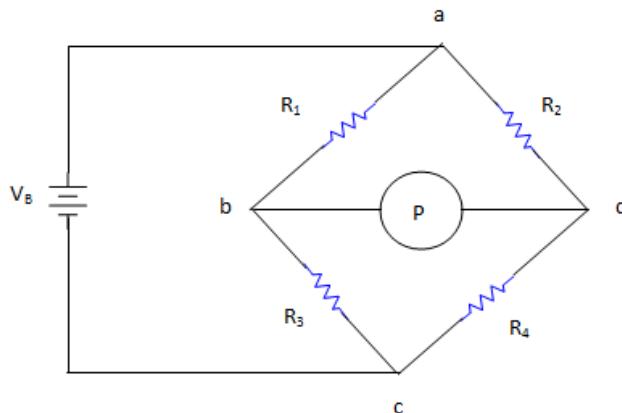


Figure Q5 (b) / Rajah Q5 (b)

(14 marks/ markah)

- c) List down **three (3)** advantages of IEEE488 compared to RS232.

Senaraikan **tiga (3)** kebaikan IEEE488 berbanding dengan RS232.

(3 marks/ markah)

[100 MARKS / 100 MARKAH]

END OF QUESTION PAPER / KERTAS SOALAN TAMAT