



**KOLEJ YAYASAN PELAJARAN JOHOR
ONLINE FINAL EXAMINATION**

COURSE NAME : DIGITAL ELECTRONICS
COURSE CODE : DKE 1083
EXAMINATION : NOVEMBER 2020
DURATION : 6 HOURS

**INSTRUCTION TO CANDIDATES /
ARAHAN KEPADA CALON**

1. This examination paper consists of **FIVE (5)** Questions. Answer **ALL** Questions. /
*Kertas soalan ini mengandungi **LIMA (5)** Soalan. Jawab **SEMUA** Soalan.*
2. Students are allowed to refer to resources such as lecture notes, books, internet or any other relevant resources. /
Pelajar dibenarkan merujuk kepada sumber seperti nota kuliah, buku, internet atau mana - mana sumber yang berkaitan.
3. Answer ALL questions in the answer sheet which is A4 size paper (or other paper with the consent of the relevant lecturer). /
*Jawab **SEMUA** soalan di dalam kertas jawapan iaitu kertas bersaiz A4 (atau lain-lain kertas dengan persetujuan pensyarah berkaitan).*
4. Write your details as follows in the upper left corner for each answer sheet: /
Tulis butiran anda sepertimana berikut di penjuru atas kiri bagi setiap kertas jawapan:
 - i. Student Full Name / *Nama Penuh Pelajar*
 - ii. Identification Card (I/C) No. / *No. Kad Pengenalan*
 - iii. Class Section / *Seksyen Kelas*
 - iv. Course Code / *Kod Kursus*
 - v. Course Name / *Nama Kursus*
 - vi. Lecturer Name / *Nama Pensyarah*
5. Each answer sheet must have a page number written at the bottom right corner. /
Setiap helai kertas jawapan mesti ditulis nombor muka surat di penjuru bawah kanan.
6. Answers should be handwritten, neat and clear. /
Jawapan hendaklah ditulis tangan, kemas dan jelas.

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIBERITAHU**

This examination paper consists of **8** printed pages including front page
*Kertas soalan ini mengandungi **8** muka surat termasuk kulit hadapan*

This paper contains of **FIVE(5)** questions. Answer **ALL** questions.

Answer the questions in Answer Booklet.

*Kertas soalan ini mengandungi **LIMA (5)** soalan. Jawab **SEMUA** soalan.*

Sila jawab dalam buku jawapan.

QUESTION 1 / SOALAN 1

- a. Define a digital system in integrated circuit technology.

Definisikan sistem digital dalam teknologi litar bersepadu.

(2 marks/ markah)

- b. Solve the hexadecimal number $E5_{16}$ to the following numbers or codes.

- i. Decimal number
- ii. Binary number
- iii. Octal number
- iv. Gray code
- v. BCD 8421
- vi. Excess-3

Selesaikan nombor perenambelasan $E5_{16}$ kepada sistem nombor atau kod berikut.

- i. Nombor perpuluhan (desimal)*
- ii. Nombor perduaan (binari)*
- iii. Nombor perlapanan (oktal)*
- iv. Kod gray*
- v. BCD 8421*
- vi. Lebihan-3*

(18 marks/ markah)

QUESTION 2 / SOALAN 2

- a. Summarize the following expression using DeMorgan's theorem and Boolean Algebra.

Ringkaskan persamaan-persamaan berikut menggunakan teorem DeMorgan's dan Aljabar Boolean.

- i. $X = (A + B)' B' + ABC' + [(AB)' (C' + A)']'$
- ii. $Y = AB + A(C' + AB)' + BC(A + AC)'$
- iii. $Z = (ABC)' (A + B + C)'$

(9 marks/ markah)

- b.

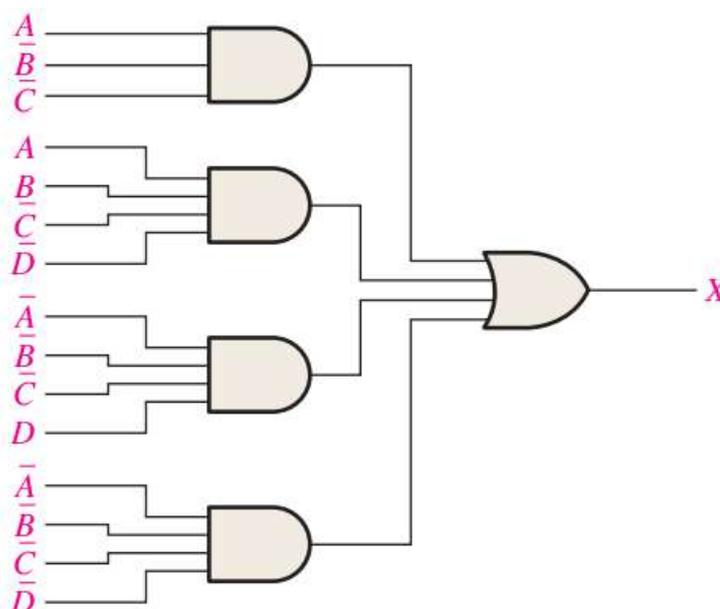


Figure Q2 (b) / Rajah Q2(b)

A combination circuit in **Figure Q2 (b)** has four binary inputs A, B ,C and D, and one output X.

- i. Find Boolean expression for output X
- ii. Express a truth table for answer in Q2(b)(i) and
- iii. Produce the answer in Q2(b)(ii) by using a Karnaugh map method

*Sebuah litar gabungan pada **Rajah Q2 (b)** mempunyai tiga masukan binari A, B, C dan D, dan satu keluaran X.*

- i. Cari persamaan Boolean untuk keluaran X
- ii. Nyatakan jadual kebenaran untuk jawapan Q2(b)(i) dan
- iii. Hasilkan jawapan Q2(b)(ii) dengan menggunakan kaedah peta Karnaugh

(11 marks/ markah)

QUESTION 3 / SOALAN 3

- a. **Figure Q3 (a)** shows the logic symbol for the half-adder.
 - i. Give the truth table.
 - ii. Define the logic expression for Σ and Cout by refer the truth table in Q3 (a) (i).
 - iii. Identify Σ and Cout using multiplexer (MUX).

Rajah Q3 (a) menunjukkan simbol logik bagi satu penambah separuh.

- i. Berikan jadual kebenaran.
- ii. Tuliskan ungkapan logik untuk Σ dan Cout dengan merujuk jadual kebenaran di Q3 (a) (i).
- iii. Illustrasikan Σ dan Cout dengan menggunakan pemultipleks (MUX).

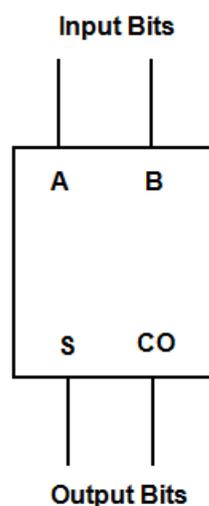


Figure Q3 (a) / Rajah Q3 (a)

(11 marks/ markah)

- b. Convert each pair of decimal numbers to binary and add using the 2's complement form:

- i. 33_{10} and 15_{10}
- ii. 56_{10} and -27_{10}
- iii. -46_{10} and 25_{10}

Tukarkan setiap pasangan nombor berikut kepada sistem binari dan gunakan kaedah pelengkap 2 bagi setiap nombor tersebut:

- i. 33_{10} dan 15_{10}
- ii. 56_{10} dan -27_{10}
- iii. -46_{10} dan 25_{10}

(9 marks/ markah)

QUESTION 4 / SOALAN 4

- a. Construct the logic circuit for SR flip flop using NOR gates and compare the differences between the circuits using NAND gates.

Binakan litar logik bagi flip flop SR menggunakan get TAK-ATAU dan bandingkan perbezaan bagi litar yang menggunakan get TAK-DAN.

(6 marks/ markah)

- b. i. Classify **two (2)** differences between synchronous and asynchronous counters by using a table.

*Klasifikasikan **dua (2)** perbezaan di antara pembilang segerak dan pembilang tak segerak dengan menggunakan jadual.*

(4 marks/ markah)

- ii. Refer to **Figure Q4 (b)**, illustrate the output waveform at **ATTACHMENT 1** for the counter circuit given. Assume the initial condition is LOW.

Rujuk **Rajah Q4 (b)**, ilustrasikan gelombang keluaran pada **LAMPIRAN 1** bagi litar pembilang yang diberikan. Anggap keluaran awal adalah **RENDAH**.

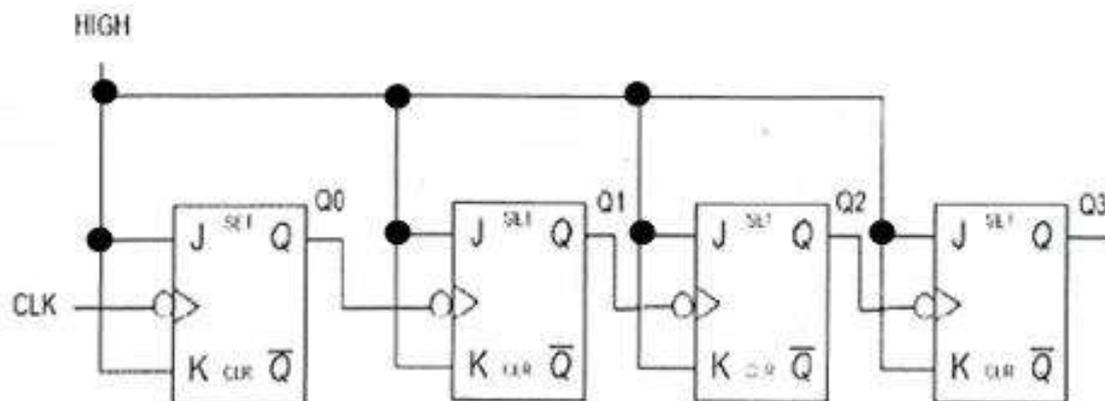


Figure Q4 (b) / Rajah Q4 (b)

(10 marks/ markah)

QUESTION 5 / SOALAN 5

- a. Describe **three (3)** main differences between TTL and CMOS circuitry.

Huraikan **tiga (3)** perbezaan utama di antara litar TTL dan CMOS.

(6 marks/ markah)

- b. Give the speed-power product of Gate A.

Berikan hasil darab halaju-kuasa bagi Get A.

Parameter	Gate A/Get A
V_{supply} (V)	5
t_{PLH} (ns)	10
T_{PHL} (ns)	8
I_{CCL} (A)	18m
I_{CCH} (A)	6m

Table Q5 (b) / Jadual Q5 (b)

(6 marks/ markah)


- c. Explain the following term in TTL characteristics.

Terangkan istilah berikut mengikut ciri-ciri bagi TTL.

- i. Fan-Out / *Rebak keluar*
- ii. Fan-In / *Rebak masuk*
- iii. Voltage transfer curve / *Lengkuk pemindahan voltan*
- iv. Noise immunity / *Imuniti hingar*

(8 marks/ markah)

ATTACHMENT 1 / LAMPIRAN 1

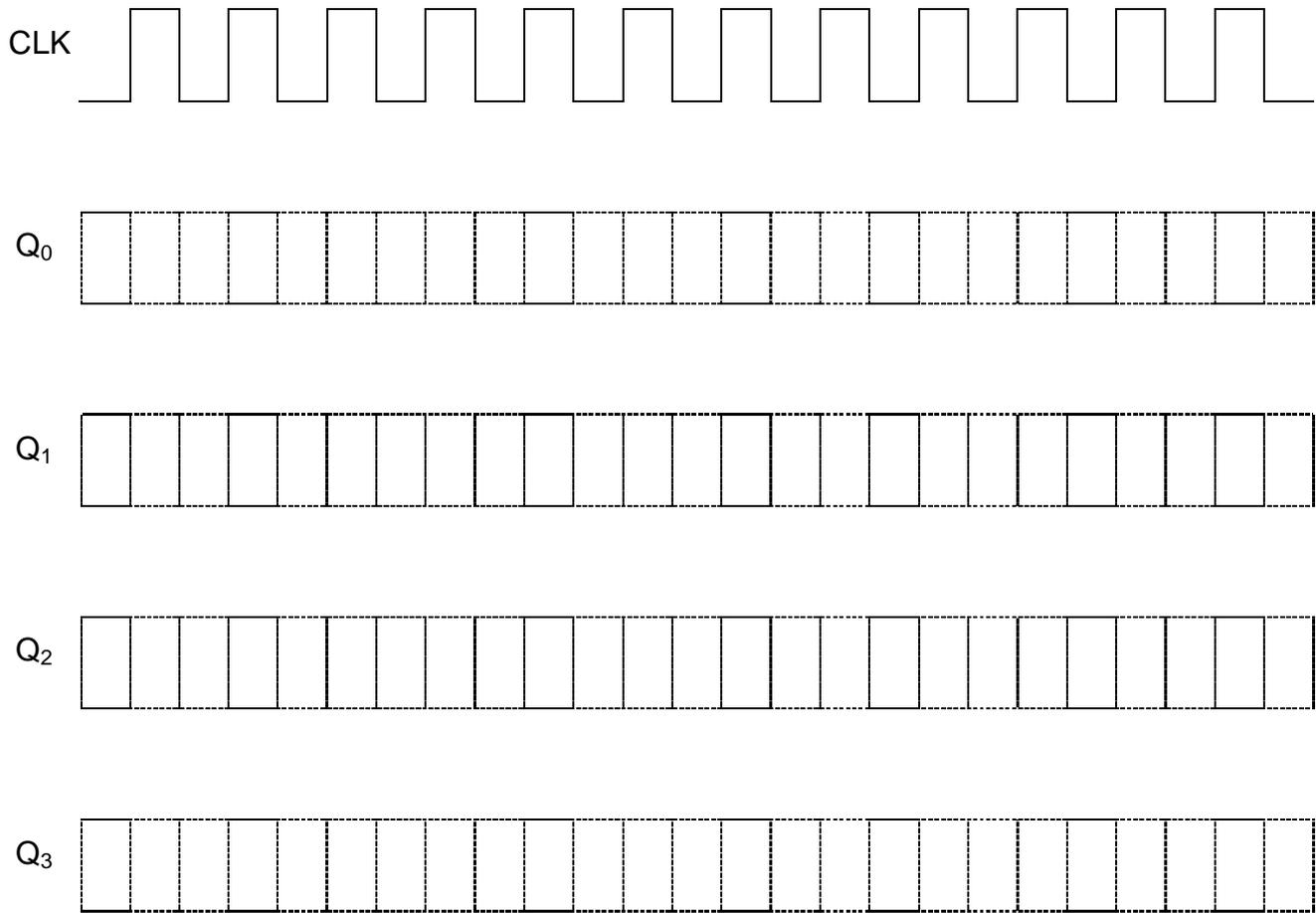

[100 MARKS / 100 MARKAH]

END OF QUESTION PAPER / KERTAS SOALAN TAMAT