



---

**KOLEJ YAYASAN PELAJARAN JOHOR  
FINAL EXAMINATION**

---

**COURSE NAME : ELECTRONIC CIRCUIT**  
**COURSE CODE : DEE 1073**  
**EXAMINATION : JANUARY 2024**  
**DURATION : 2 HOURS 30 MINUTES**

---

**INSTRUCTION TO CANDIDATES/  
ARAHAN KEPADA CALON**


1. This examination paper consists of **FOUR (4)** questions. /  
*Kertas soalan ini mengandungi EMPAT (4) soalan.*
2. Candidates are not allowed to bring any material to examination room except with the permission from the invigilator. The formula was attached at the back of the question paper. /  
*Calon tidak dibenarkan untuk membawa sebarang bahan/nota ke bilik peperiksaan tanpa arahan/kebenaran daripada pengawas. Rumus dilampirkan di belakang kertas soalan peperiksaan.*
3. Please check to make sure that this examination pack consists of: /  
*Pastikan kertas soalan peperiksaan ini mengandungi:*
  - i. Question Paper /  
*Kertas Soalan*
  - ii. Answering Booklet /  
*Buku Jawapan*
  - iii. Attachment 1 /  
*Lampiran 1*
  - iv. Attachment 2 /  
*Lampiran 2*
  - v. Attachment 3 /  
*Lampiran 3*

---

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /  
JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIBERITAHU**

---

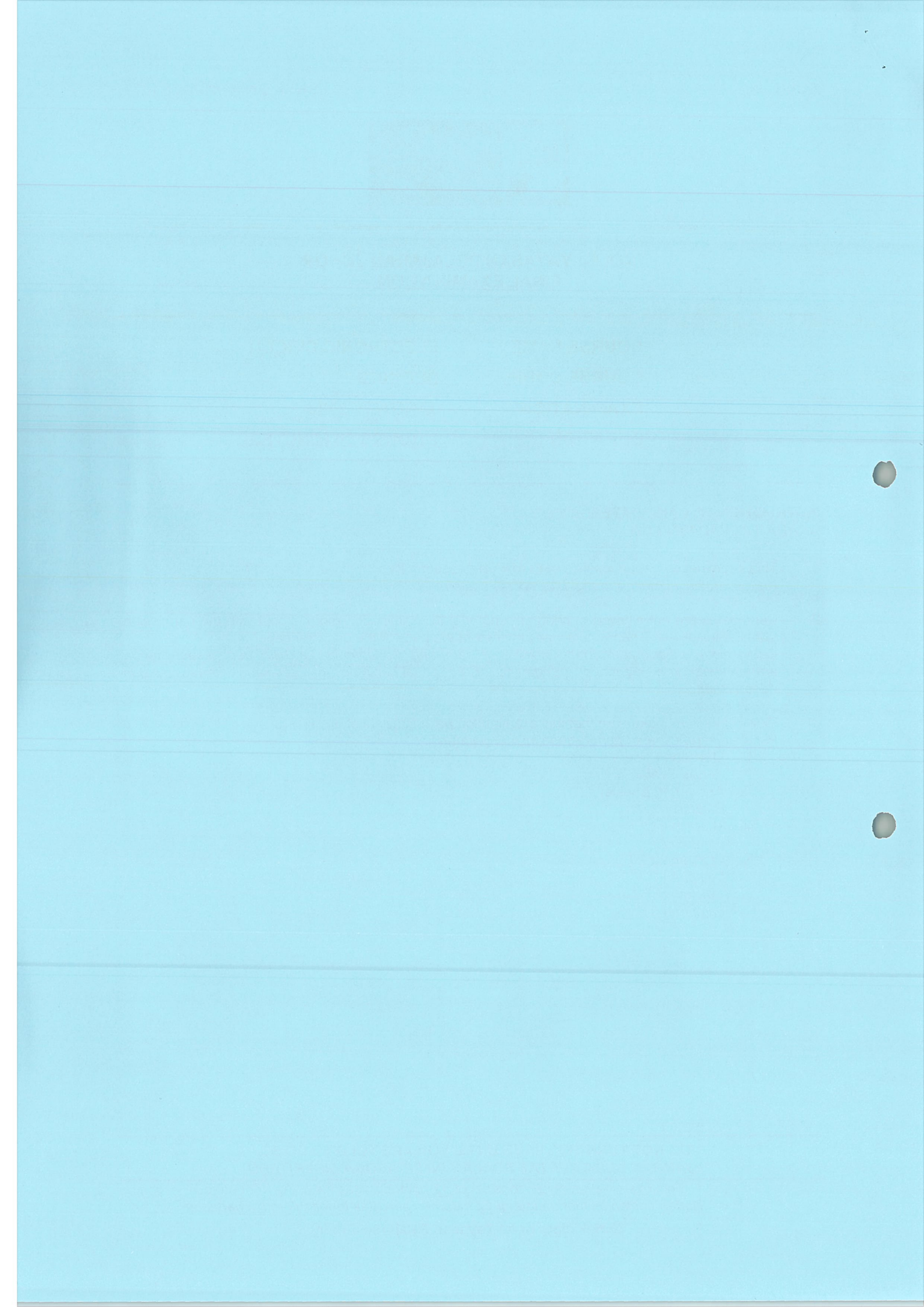This examination paper consists of **12** printed pages including front page  
*Kertas soalan ini mengandungi 12 halaman bercetak termasuk muka hadapan*



This examination paper consists of **FOUR (4)** questions. Answer **ALL** the questions in the Answer booklet.

*Kertas soalan ini mengandungi **EMPAT (4)** soalan. Jawab **SEMUA** soalan dalam buku jawapan.*

**QUESTION 1/ SOALAN 1**

a) Draw the transfer curve using shorthand method for **Figure 1(a)**. The graph is given in the **Attachment 1**.

(10 marks/ markah)

b) Solve the value of  $I_{DQ}$  and  $V_{GSQ}$  using the universal curve given in the **Attachment 2**.

(5 marks/ markah)

c) Using answer in question (b), solve value of  $V_{DS}$ ,  $V_S$ ,  $V_G$  and  $V_D$ .

(9 marks/ markah)

d) If the value of  $R_s$  increased, what happen to Q-point?

(1 marks/ markah)

a) Lukiskan lengkung pindah menggunakan kaedah terengkas bagi **Rajah 1(a)**. Graf diberikan di **Lampiran 1**.

b) Selesaikan nilai  $I_{DQ}$  and  $V_{GSQ}$  menggunakan lengkung universal yang diberikan dalam **Lampiran 2**.

c) Selesaikan nilai  $V_{DS}$ ,  $V_S$ ,  $V_G$  and  $V_D$  dengan menggunakan jawapan pada soalan b.

d) Jika jumlah  $R_s$  meningkat, apakah akan terjadi terhadap titik - Q?

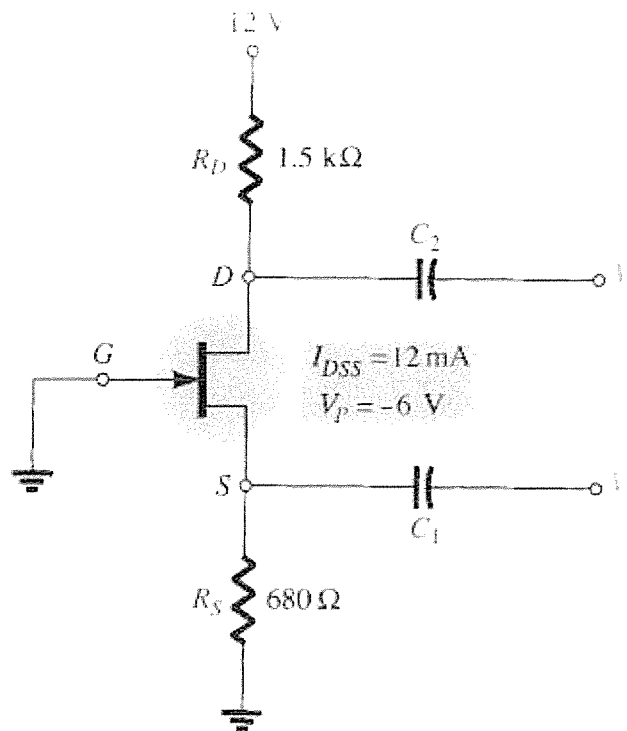


Figure 1(a) / Rajah 1(a)

## QUESTION 2/ SOALAN 2

- a) Solve the value of transconductance,  $g_{m0}$  for a JFET having device parameters  $I_{DSS} = 12$  mA and  $V_p = -4$  V.

(5 marks/ markah)

- b) Solve the value of  $Z_i$ ,  $Z_o$  and  $A_v$  for circuit in **Figure 2(b)**. Given,  $I_{DSS} = 10$  mA,  $V_p = -6$  V, and  $r_d = 40$  kΩ.

(20 marks/ markah)

- a) Selesaikan nilai bagi kealiran pindah,  $g_{m0}$  untuk JFET yang mempunyai parameter  $I_{DSS} = 12$  mA dan  $V_p = -4$  V.
- b) Selesaikan nilai bagi of  $Z_i$ ,  $Z_o$  dan  $A_v$  untuk litar dalam **Rajah 2(b)**. Diberikan  $I_{DSS} = 10$  mA,  $V_p = -6$  V, and  $r_d = 40$  kΩ.

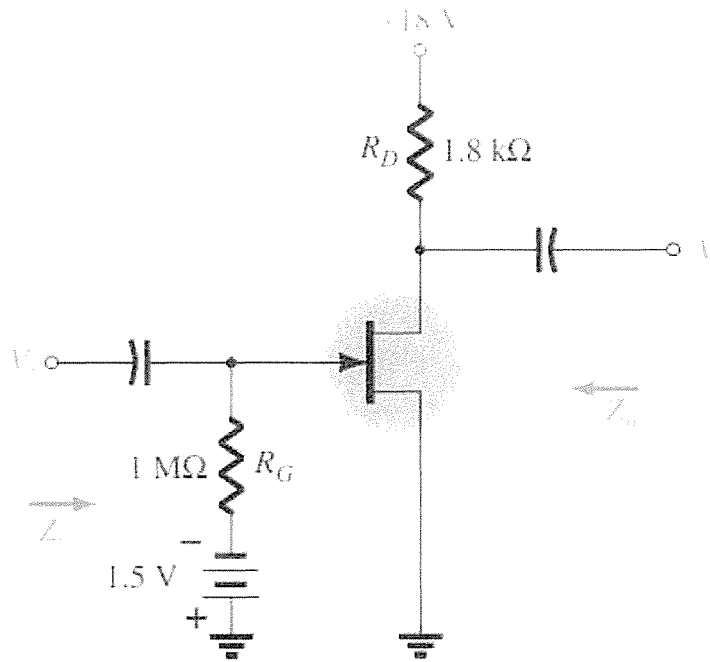


Figure 2(b) / Rajah 2(b)

**QUESTION 3/ SOALAN 3**

Differential operation involves the use of opposite-polarity inputs. Common-mode operation involves the use of the same-polarity inputs. Common-mode rejection ratio (CMRR) compares the gain for differential inputs to that for common inputs.

- a) Solve the CMRR (in dB) for the circuit measurements of  $V_d = 1 \text{ mV}$ ,  $V_o = 120 \text{ mV}$ ,  $V_C = 1 \text{ mV}$ , and  $V_o = 20 \text{ } \mu\text{V}$ .

(8 marks/ markah)

- b) Solve the output voltage for **Figure 3(b)**. Given  $V_1 = 50 \sin(1000t) \text{ mV}$  and  $V_2 = 10 \sin(3000t) \text{ mV}$ .

(5 marks/ markah)

- c) Solve the output voltage,  $V_o$  for the op-amp circuit in **Figure 3(c)**. Given  $V_1 = 12 \text{ mV}$  and  $V_2 = 18 \text{ mV}$ .

(12 marks/ markah)

Operasi pembezaan melibatkan penggunaan masukan kutub berlawanan. Operasi mod biasa melibatkan penggunaan masukan kutub sama. Nisbah penolakan mod biasa (CMRR) membandingkan gandaan bagi masukan pembezaan terhadap masukan biasa.

- a) Selesaikan nilai CMRR (dalam dB) bagi ukuran litar  $V_d = 1 \text{ mV}$ ,  $V_o = 120 \text{ mV}$ ,  $V_C = 1 \text{ mV}$ , dan  $V_o = 20 \text{ } \mu\text{V}$ .
- b) Selesaikan voltan keluaran bagi **Rajah 3(b)**. Diberi  $V_1 = 50 \sin(1000t) \text{ mV}$  dan  $V_2 = 10 \sin(3000t) \text{ mV}$ .
- c) Merujuk kepada litar penguat kendalian dalam **Rajah 3(c)**, kirakan voltan keluaran,  $V_o$ . Diberi  $V_1 = 12 \text{ mV}$  dan  $V_2 = 18 \text{ mV}$ .

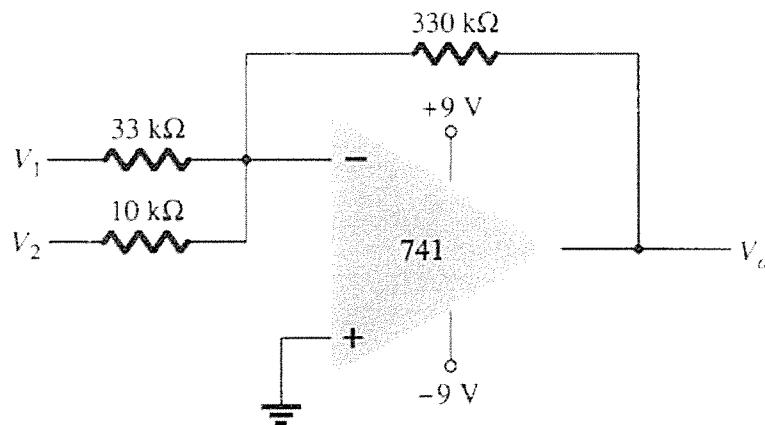


Figure 3(b) / Rajah 3(b)

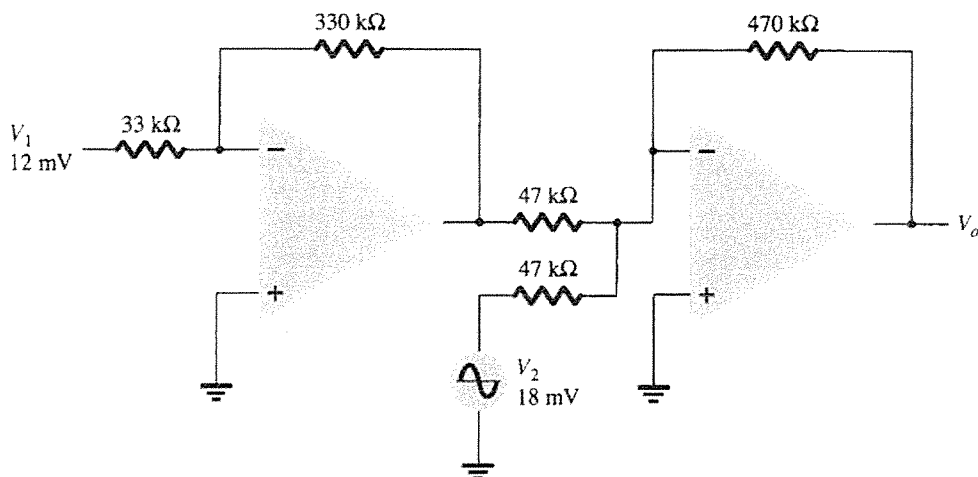


Figure 3(c) / Rajah 3(c)

## QUESTION 4/ SOALAN 4

Power Amplifier can be categorized into several classes. Each class will be different in their operating cycle and efficiency. Based on Class B Power Amplifier circuit in **Figure 4**, solve the value of:

- a) the peak input voltage,  $V_{i(p)}$ . (3 marks/ *markah*)
- b) the peak voltage across the load,  $V_{L(p)}$ . (1 marks/ *markah*)
- c) the peak load current,  $I_{L(p)}$ . (3 marks/ *markah*)
- d) the direct current,  $I_{DC}$ . (3 marks/ *markah*)
- e) the input power,  $P_{in(dc)}$ . (3 marks/ *markah*)
- f) the output power,  $P_{o(ac)}$ . (2 marks/ *markah*)
- g) the power dissipated by each output transistor,  $P_Q$ . (4 marks/ *markah*)
- h) the circuit efficiency,  $\% \eta$ . (3 marks/ *markah*)
- i) the maximum input power,  $P_{in(max)}$ . (1.5 marks/ *markah*)
- j) the maximum output power,  $P_{o(max)}$ . (1.5 marks/ *markah*)

*Penguat Kuasa boleh dikategorikan kepada beberapa kelas. Setiap kelas akan berbeza dari segi kitaran operasi dan kecekapan Berdasarkan litar Penguat Kuasa Kelas B dalam **Rajah 4**, kirakan:*

- a) *voltan puncak merentasi masukan,  $V_{i(p)}$ .*
- b) *voltan puncak merentasi beban,  $V_{L(p)}$ .*
- c) *arus puncak pada beban,  $I_{L(p)}$ .*
- d) *arus terus,  $I_{DC}$ .*
- e) *kuasa masukan,  $P_{in(dc)}$ .*
- f) *kuasa keluaran,  $P_{o(ac)}$ .*
- g) *kuasa yang dilesapkan oleh setiap keluaran transistor,  $P_Q$ .*
- h) *kecekapan litar,  $\% \eta$ .*
- i) *kuasa masukan maksimum  $P_{in(max)}$ .*

j) kuasa keluaran maksimum  $P_{o(max)}$ .

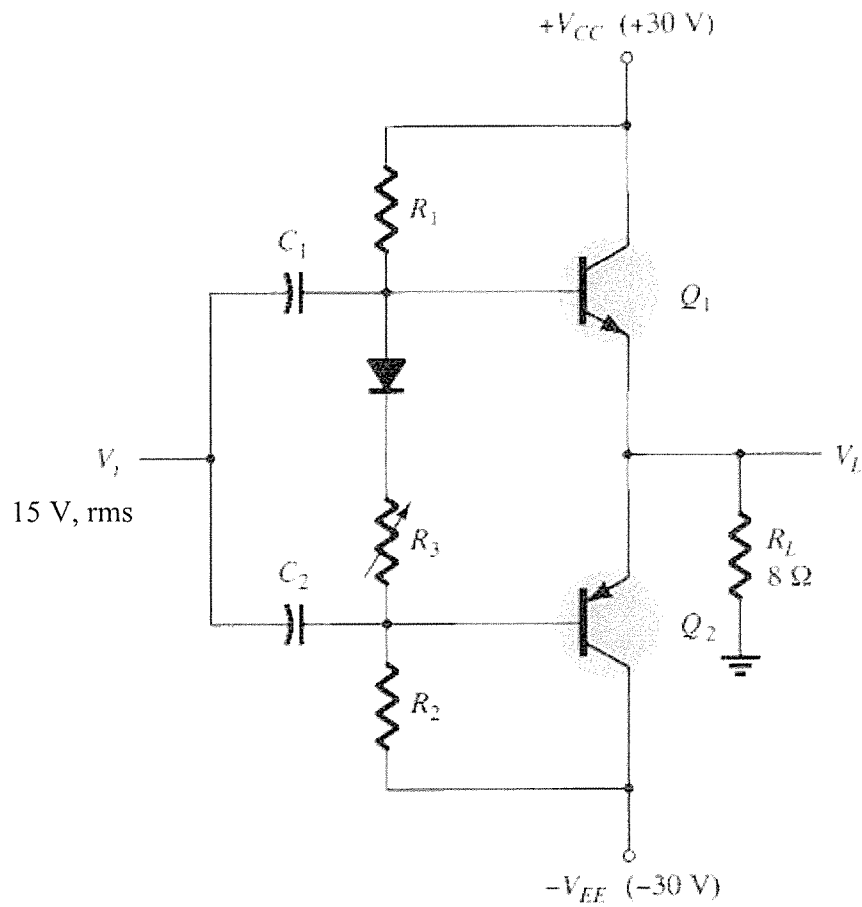


Figure 4 / Rajah 4

[100 MARKS/ MARKAH]

END OF QUESTION PAPER/ KERTAS SOALAN TAMAT



**Attachment 1 / Lampiran 1**

**Name / Nama** : .....


**Lecturer / Pensyarah** : .....

The image shows a large grid of graph paper. The grid consists of 10 columns and 20 rows of squares. A vertical line runs down the center of the grid, dividing it into two equal halves of 5 columns each. The grid is intended for drawing or plotting a graph.

Attachment 2 / Lampiran 2

Name / Nama : .....

Lecturer / Pensyarah : .....

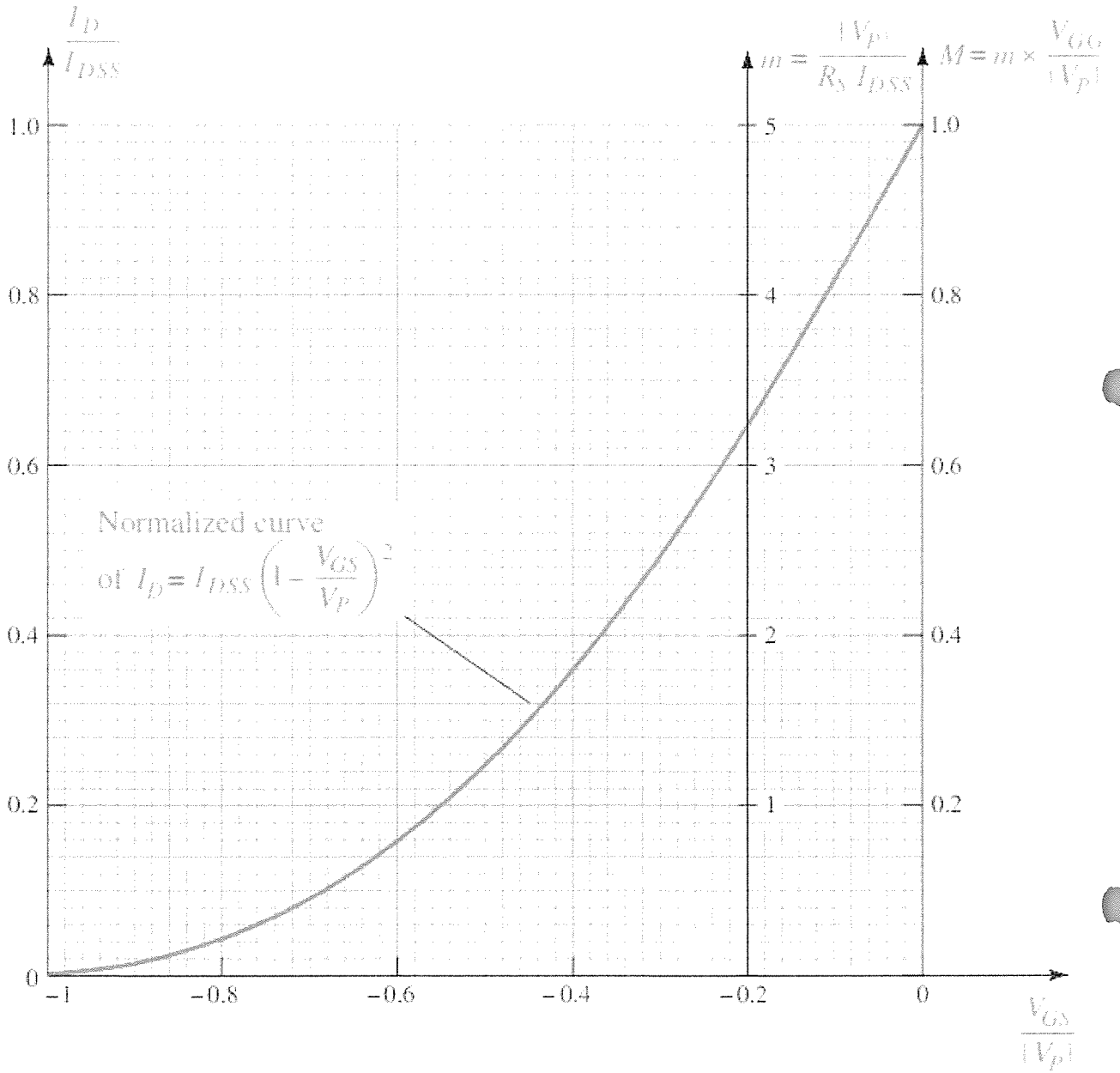

## Attachment 3 / Lampiran 3

## Formula / Rumus

JFET:

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = I_{DSS} |_{V_{GS}=0} \quad I_D = 0 \text{ mA} |_{V_{GS}=V_P} \quad I_D = \frac{I_{DSS}}{4} |_{V_{GS}=V_P/2} \quad V_{GS} \cong 0.3V_P |_{I_D=I_{DSS}/2}$$

$$V_{GS} = V_P \left( 1 - \sqrt{\frac{I_D}{I_{DSS}}} \right)$$

$$P_D = V_{DS} I_D$$

$$r_d = \frac{r_o}{(1 - V_{GS}/V_P)^2}$$

MOSFET (enhancement):

$$I_D = k(V_{GS} - V_T)^2$$

$$k = \frac{I_{D(on)}}{(V_{GS(on)} - V_T)^2}$$

JFETs/depletion-type MOSFETs:

$$\text{Fixed-bias configuration: } V_{GS} = -V_{GG} = V_G$$

$$\text{Self-bias configuration: } V_{GS} = -I_D R_S$$

$$\text{Voltage-divider biasing: } V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$V_{GS} = V_G - I_D R_S$$

Enhancement-type MOSFETs:

$$\text{Feedback biasing: } V_{DS} = V_{GS}$$

$$V_{GS} = V_{DD} - I_D R_D$$

$$\text{Voltage-divider biasing: } V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$V_{GS} = V_G - I_D R_S$$

$$g_m = y_{fs} = \frac{\Delta I_D}{\Delta V_{GS}}$$

$$g_{m0} = \frac{2I_{DSS}}{|V_P|}$$

$$g_m = g_{m0} \left[ 1 - \frac{V_{GS}}{V_P} \right]$$

$$g_m = g_{m0} \sqrt{\frac{I_D}{I_{DSS}}}$$

$$r_d = \frac{1}{y_{ov}} = \frac{\Delta V_{DS}}{\Delta I_D} \Big|_{V_{GS}=\text{constant}}$$

$$\text{CMRR} = 20 \log_{10} \frac{A_v}{A_{cl}}$$

Inverting amplifier:

$$\frac{V_o}{V_i} = -\frac{R_f}{R_1}$$

Noninverting amplifier:

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R_1}$$

Unity follower:

$$V_o = V_i$$

Summing amplifier:

$$V_o = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3\right)$$

Integrator amplifier:

$$v_o(t) = -\frac{1}{RC} \int v_i(t) dt$$

$$\text{Slew rate (SR)} = \frac{\Delta V_o}{\Delta t} \quad \text{V}/\mu\text{s}$$

Constant-gain multiplier:

$$A = -\frac{R_f}{R_1}$$

Noninverting constant-gain multiplier:

$$A = 1 + \frac{R_f}{R_1}$$

Voltage-summing amplifier:

$$A = -\left[\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3\right]$$

Voltage buffer:

$$V_o = V_i$$

Low-pass active filter cutoff frequency:

$$f_{OH} = \frac{1}{2\pi R_1 C_1}$$

High-pass active filter cutoff frequency:

$$f_{OL} = \frac{1}{2\pi R_1 C_1}$$

$$I_C(\text{dc}) = \frac{V_{CE}(\text{p-p})}{8R_C}$$

$$P_o(\text{ac}) = V_{CE}(\text{rms}) I_C(\text{rms})$$

$$= I_C^2(\text{rms}) R_C$$

$$= \frac{V_{CE}^2(\text{rms})}{R_C}$$

$$P_o(\text{ac}) = \frac{V_{CE}(\text{p}) I_C(\text{p})}{2}$$

$$= \frac{I_C^2(\text{p})}{2R_C}$$

$$= \frac{V_{CE}^2(\text{p})}{2R_C}$$

$$P_o(\text{ac}) = \frac{V_{CE}(\text{p-p}) I_C(\text{p-p})}{8}$$

$$= \frac{I_C^2(\text{p-p})}{8} R_C$$

$$= \frac{V_{CE}^2(\text{p-p})}{8R_C}$$

$$\% \eta = \frac{P_o(\text{ac})}{P_i(\text{dc})} \times 100\%$$

Transformer action:

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

$$\frac{I_2}{I_1} = \frac{N_1}{N_2}$$

$$I_{\text{dc}} = \frac{2}{\pi} I(\text{p})$$

$$P_i(\text{dc}) = V_{CC} \left( \frac{2}{\pi} I(\text{p}) \right)$$

$$P_o(\text{ac}) = \frac{V_L^2(\text{rms})}{R_L}$$

$$\text{maximum } P_o(\text{ac}) = \frac{V_{CC}^2}{2R_L}$$

$$\text{maximum } P_i(\text{dc}) = V_{CC}(\text{maximum } I_{\text{dc}}) = V_{CC} \left( \frac{2V_{CC}}{\pi R_L} \right) = \frac{2V_{CC}^2}{\pi R_L}$$

$$\text{maximum } P_{2Q} = \frac{2V_{CC}^2}{\pi^2 R_L}$$

Harmonic distortion:

$$\% \text{ nth harmonic distortion} = \% D_n = \frac{|A_n|}{|A_1|} \times 100\%$$

Heat sink:

$$\theta_{JA} = \theta_{JC} + \theta_{CS} + \theta_{SA}$$

