



**KOLEJ YAYASAN PELAJARAN JOHOR
ONLINE FINAL EXAMINATION**

COURSE NAME : POWER ELECTRONICS
COURSE CODE : DKE 3063
SESSION : DECEMBER 2021
DURATION : 2 HOURS 30 MINUTES

**INSTRUCTION TO CANDIDATES /
ARAHAH KEPADA CALON**

1. This examination paper consists of **FIVE (5)** questions. Answer **ALL** questions. /
*Kertas soalan ini mengandungi **LIMA (5)** soalan. Jawab **SEMUA** soalan.*
2. Students are allowed to refer to resources such as lecture notes, books, internet or any other relevant resources. /
Pelajar dibenarkan merujuk kepada sumber seperti nota kuliah, buku, internet atau mana - mana sumber yang berkaitan.
3. Answer ALL questions in the answer sheet which is A4 size paper (or other paper with the consent of the relevant lecturer). /
*Jawab **SEMUA** soalan di dalam kertas jawapan iaitu kertas bersaiz A4 (atau lain-lain kertas dengan persetujuan pensyarah berkaitan).*
4. Write your details as follows in the upper left corner for each answer sheet: /
Tulis butiran anda seperti mana berikut di penjuru atas kiri bagi setiap kertas jawapan:
 - i. Student Full Name / Nama Penuh Pelajar
 - ii. Identification Card (I/C) No. / No. Kad Pengenalan
 - iii. Class Section / Seksyen Kelas
 - iv. Course Code / Kod Kursus
 - v. Course Name / Nama Kursus
 - vi. Lecturer Name / Nama Pensyarah
5. Each answer sheet must have a page number written at the bottom right corner. /
Setiap helai kertas jawapan mesti ditulis nombor muka surat di penjuru bawah kanan.
6. Answers should be handwritten, neat and clear. /
Jawapan hendaklah ditulis tangan, kemas dan jelas.

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIBERITAHU**

This examination paper consists of **9** printed pages including front page
*Kertas soalan ini mengandungi **9** halaman bercetak termasuk muka hadapan*

This paper contains of **FIVE (5)** questions. Answer **ALL** questions.

Answer the questions in an answer sheet.

*Kertas soalan ini mengandungi **LIMA (5)** soalan. Jawab **SEMUA** soalan.*

Sila jawab dalam kertas jawapan.

QUESTION 1 / SOALAN 1

- a) Define power electronic. **(2 marks / markah)**
- b) List **three (3)** of power semiconductor devices. **(3 marks / markah)**
- c) For half-wave rectifier with R-L load, $R=100\Omega$, $L=0.1H$, $\omega=377\text{rad/s}$, and $V_s=100V$. Determine:
- An expression for the current in this circuit.
 - The point where diode turns off.
 - The average current.
 - The rms current.
 - The power absorbed by the R-L load.
 - The power factor.
- (15 marks / markah)**
- a) Berikan definisi elektronik kuasa.
- b) Senaraikan **tiga (3)** peranti semikonduktor kuasa.
- c) Bagi penerus separuh gelombang dengan beban $R-L$, $R = 100\Omega$, $L = 0.1H$, $\omega = 377\text{rad / s}$, dan $V_s = 100V$. Tentukan:
- Satu ungkapan untuk arus dalam litar ini.
 - Titik di mana diod dimatikan.
 - Arus purata.
 - Arus pmkd.
 - Kuasa yang diserap oleh beban $R-L$.
 - Faktor kuasa

QUESTION 2 / SOALAN 2

- a) Give **two (2)** applications of controlled rectifier.
(2 marks / markah)
- b) Sketch and label the I-V characteristic curve for a SCR.
(3 marks / markah)
- c) The full wave controlled bridge rectifier has an AC input of $120 \text{ V}_{\text{rms}}$ at 60 Hz and a 20Ω load resistor. The delay angle is 30° . Draw the circuit diagram and sketch the output voltage waveform. Determine:
- Average and rms current in the load.
 - Power absorbed by load in watt.
 - Power source in volt-ampere.
 - Power factor.
- (15 marks / markah)**
- a) *Berikan dua (2) aplikasi bagi penerus terkawal.*
- b) *Lakar dan labelkan lengkung ciri I-V bagi SCR.*
- c) *Penerus terkawal titi gelombang penuh mempunyai masukan AU, $120 \text{ V}_{\text{pmkd}}$ pada 60 Hz dan beban rentangan, 20Ω . Sudut lengah adalah 30° . Lukiskan gambar rajah litar dan lakarkan gelombang voltan keluaran. Tentukan:*
- Arus purata dan pmkd beban.*
 - Kuasa diserap oleh beban dalam watt.*
 - Kuasa bekalan dalam volt-ampere.*
 - Faktor kuasa.*

QUESTION 3 / SOALAN 3

- a) Define the AC voltage controller.

(2 marks / markah)

- b) List down **three (3)** applications of AC voltage controllers.

(3 marks / markah)

- c) Single phase AC voltage controller in **Figure Q3(c)** has a resistive load of $R = 10 \Omega$ and input voltage is $V_s = 120 V$, 60 Hz. The delay angle of thyristor T_1 is $\alpha = \pi/2$. Determine:

- $V_{o(rms)}$
- Input power factor.
- Average input current.

(15 marks / markah)

- a) Berikan definisi pengawal voltan AU.

- b) Senaraikan **tiga (3)** aplikasi pengawal voltan AU.

- c) Fasa pengawal AU voltan dalam **Rajah Q3(c)** mempunyai rintangan beban, $R = 10 \Omega$ dan voltan masukan adalah $V_s = 120 V$, 60 Hz. Sudut lengah thyristor T_1 adalah $\alpha = \pi/2$. Tentukan:

- $V_{o (pmkd)}$
- Faktor kuasa masukan.
- Arus masukan purata.

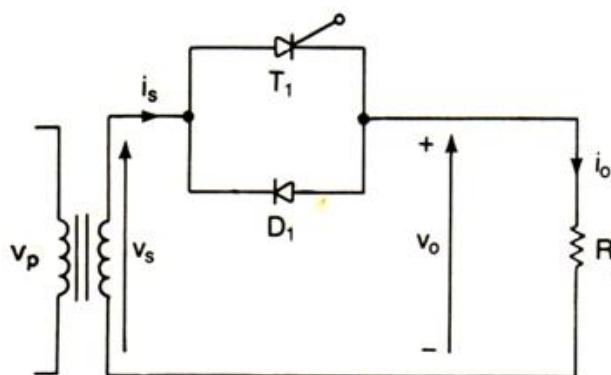


Figure Q3(c) / Rajah Q3(c)

QUESTION 4 / SOALAN 4

- a) State **two (2)** applications of DC chopper. **(2 marks / markah)**
- b) List **three (3)** advantages of a DC chopper circuit. **(3 marks / markah)**
- c) The Step-down DC Chopper in **Figure Q4(c)** has a resistive load, $R = 10 \Omega$ and input voltage, $V_s = 220 \text{ V}$. When the chopper switch (SW) remains ON, its voltage drop is $V_{ch} = 2 \text{ V}$ and chopping frequency is $f = 10 \text{ kHz}$. If the duty cycle is 50%, determine:
- The average output voltage, $V_{o,dc}$.
 - The rms output voltage, $V_{o,rms}$.
 - The chopper efficiency, η .
- (15 marks / markah)**
- a) Nyatakan **dua (2)** aplikasi pemenggal AT.
- b) Senaraikan **tiga (3)** kelebihan litar pemenggal AT.
- c) Sebuah pemenggal AT Langkah-turun seperti dalam **Rajah Q4(c)** berbeban perintang tulen, $R = 10 \Omega$ dan voltan masukan, $V_s = 220 \text{ V}$. Semasa suis pemenggal (SW) kekal TUTUP, voltan kejatuhannya, $V_{ch} = 2 \text{ V}$ dan frekuensi pemenggal $f = 10 \text{ kHz}$. Jika kitar kerja, adalah 50%, tentukan:
- Voltan keluaran purata, $V_{o,dc}$.
 - Voltan keluaran pmkd, $V_{o,pmkd}$.
 - Kecekapan pemenggal, η .

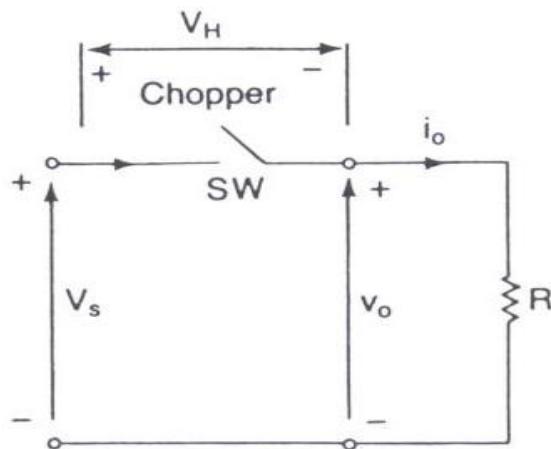


Figure Q4(c) / Rajah Q4(c)

QUESTION 5 / SOALAN 5

- a) Define an inverter.
(2 marks / markah)
- b) State **three (3)** applications of inverter in industrial application.
(3 marks / markah)
- c) Referring to **Figure Q5(c)**. Given $V_s = 220 \text{ V}$ and $R = 10 \Omega$, determine:
 - i. The rms output voltage at the fundamental frequency, V_1 .
 - ii. The output power, P_o .
 - iii. The average current of each transistor, I_Q .
 - iv. The rms current of each transistor, I_1 .
 - v. The peak current of each transistor, I_p .

(15 marks / markah)

- a) Berikan definisi penyongsang.
- b) Nyatakan **tiga (3)** aplikasi penyongsang dalam aplikasi industri.
- c) Merujuk kepada **Rajah Q5(c)**. Diberi $V_s = 220\text{ V}$ and $R = 10\Omega$, tentukan
- Voltan keluaran pmkd pada frekuensi asas, V_1 .
 - Kuasa keluaran, P_o .
 - Arus purata bagi setiap transistor, I_Q .
 - Arus pmkd bagi setiap transistor, I_1 .
 - Arus puncak bagi setiap transistor, I_p .

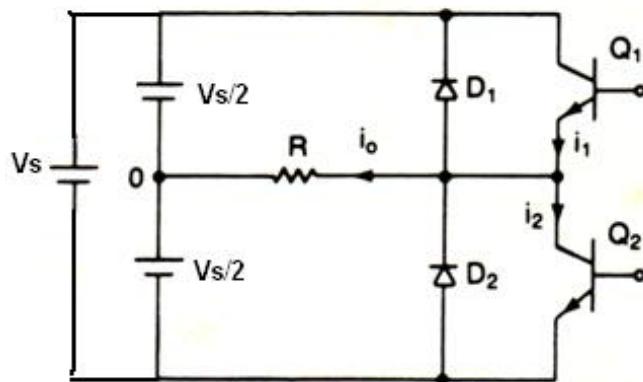


Figure Q5(c) / Rajah Q5(c)

[100 MARKS / MARKAH]

END OF QUESTION PAPER / KERTAS SOALAN TAMAT

Attachment 1 / Lampiran 1

Uncontrolled rectifier

$$V_{o(dc)} = 0.318 V_m \quad V_{o(rms)} = 0.5 V_m$$

$$V_{o(dc)} = \frac{V_m}{2\pi} [1 - \cos(\beta)] \quad V_{o(rms)} = \frac{V_m}{2} \sqrt{\frac{\beta}{\pi} - \frac{\sin(2\beta)}{2\pi}}$$

$$V_{o(dc)} = 0.6366 V_m \quad V_{o(rms)} = 0.707 V_m$$

$$V_{o(dc)} = 1.654 V_m \quad V_{o(rms)} = 1.6554 V_m$$

$$V_{o(dc)} = 0.827 V_m \quad V_{o(rms)} = 0.8407 V_m$$

Controlled rectifier

$$V_{o(dc)} = \frac{V_m}{2\pi} (1 + \cos \alpha) \quad V_{o(rms)} = \frac{V_m}{2} \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}$$

$$V_{o(dc)} = \frac{2V_m}{\pi} \cos \alpha \quad V_{o(rms)} = V_m \left[\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi} \right]^{1/2}$$

Principle of AC Voltage controller

$$Vs = \sqrt{2} Vs \sin \alpha t \quad Vo = Vs \sqrt{\frac{n}{m+n}} = Vs \sqrt{k}$$

$$Vo(rms) = Vs \left[\frac{1}{2\pi} \left(2\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}$$

$$Vo(dc) = \frac{\sqrt{2} Vs}{2\pi} (\cos \alpha - 1)$$

AC Voltage controller : Single Phase

$$Vo(rms) = Vs \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{\alpha} \right) \right]^{1/2} \quad Vo(rms) = Vs \left[\frac{1}{\pi} \left(\beta - \alpha + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right) \right]^{1/2}$$

AC Voltage controller : Three Phase Half wave**For $0^\circ \leq \alpha < 90^\circ$:**

$$V_o(\text{rms}) = \sqrt{3}Vs \left[\frac{1}{\pi} \left(\frac{\pi}{3} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{8} \right) \right]^{1/2}$$

For $90^\circ \leq \alpha < 120^\circ$:

$$V_o(\text{rms}) = \sqrt{3}Vs \left[\frac{1}{\pi} \left(\frac{11\pi}{24} - \frac{\alpha}{2} \right) \right]^{1/2}$$

For $120^\circ \leq \alpha < 210^\circ$:

$$V_o(\text{rms}) = \sqrt{3}Vs \left[\frac{1}{\pi} \left(\frac{7\pi}{24} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{16} - \frac{\sqrt{3} \cos 2\alpha}{16} \right) \right]^{1/2}$$

AC Voltage controller : Three Phase Full wave**For $0^\circ \leq \alpha < 60^\circ$:**

$$V_o(\text{rms}) = \sqrt{6}Vs \left[\frac{1}{\pi} \left(\frac{\pi}{6} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{8} \right) \right]^{1/2}$$

For $60^\circ \leq \alpha < 90^\circ$:

$$V_o(\text{rms}) = \sqrt{6}Vs \left[\frac{1}{\pi} \left(\frac{\pi}{12} + \frac{3\sin 2\alpha}{16} + \frac{\sqrt{3} \cos 2\alpha}{16} \right) \right]^{1/2}$$

For $120^\circ \leq \alpha < 210^\circ$:

$$V_o(\text{rms}) = \sqrt{6}Vs \left[\frac{1}{\pi} \left(\frac{5\pi}{24} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{16} + \frac{\sqrt{3} \cos 2\alpha}{16} \right) \right]^{1/2}$$