



---

**KOLEJ YAYASAN PELAJARAN JOHOR  
ONLINE FINAL EXAMINATION**

---

**COURSE NAME : CIRCUIT ANALYZE**  
**COURSE CODE : DKE 2093**  
**SESSION : JUNE 2022**  
**DURATION : 2 HOURS 30 MINUTES**

---

**INSTRUCTION TO CANDIDATES/  
ARAHAN KEPADA CALON**

1. This examination paper consists of **SIX (6)** questions. /  
*Kertas soalan ini mengandungi **ENAM (6)** soalan.*
2. Students are allowed to refer to resources such as lecture notes, books, internet or any other relevant resources. /  
*Pelajar dibenarkan merujuk kepada sumber seperti nota kuliah, buku, internet atau mana-mana sumber yang berkaitan.*
3. Answer **ALL** questions in the answer sheet which is **A4** size paper (or other paper with the consent of the relevant lecturer). /  
*Jawab **SEMUA** soalan di dalam kertas jawapan iaitu kertas bersaiz **A4** (atau lain-lain kertas dengan persetujuan pensyarah berkaitan).*
4. Write your details as follows in the upper left conner for each answer sheet: /  
*Tulis butiran anda sepertimana berikut di penjuru atas kiri bagi setiap kertas jawapan:*
  - i. Student Full Name / Nama Penuh Pelajar
  - ii. Identification Card (I/C) No. / No. Kad Pengenalan
  - iii. Class Section / Seksyen Kelas
  - iv. Course Code / Kod Kursus
  - v. Course Name / Nama Kursus
  - vi. Lecturer Name / Nama Pensyarah
5. Each answer sheet must have a page number written at the bottom right corner. /  
*Setiap helai kertas jawapan mesti ditulis nombor muka surat di penjuru bawah kanan.*
6. Answers should be **neat and clear in handwritten form.** /  
*Jawapan hendaklah ditulis tangan, kemas dan jelas.*

---

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /  
JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIBERITAHU**

---

This examination paper consists of **10** printed pages including front page  
*Kertas soalan ini mengandungi **10** halaman bercetak termasuk muka hadapan*

This examination paper consists of **SIX (6)** questions. Answer **ALL** the questions in an Answering Booklet.


*Kertas soalan ini mengandungi ENAM (6) soalan. Jawab SEMUA soalan dalam Buku Jawapan.*

### QUESTION 1/ SOALAN 1

Referring to **Figure 1**, find the equivalent capacitance,  $C_{eq}$  view from terminal A-B and the energy stored in equivalent capacitance,  $C_{eq}$  for the circuit under direct current condition.

**(15 marks / markah)**

*Merujuk kepada **Rajah 1**, dapatkan kemuatan setara,  $C_{eq}$  dilihat dari terminal A-B dan tenaga yang disimpan dalam kemuatan setara,  $C_{eq}$  untuk litar di bawah keadaan arus terus.*

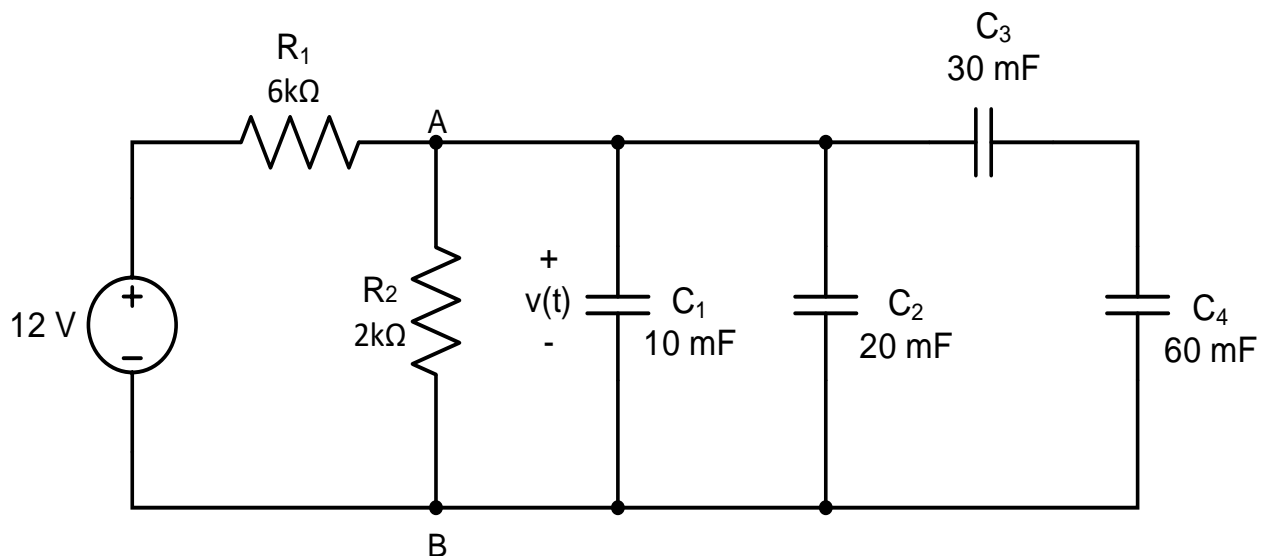

**Figure 1/ Rajah 1**

## QUESTION 2/ SOALAN 2

The switch in **Figure 2** has been in position X for a long time. At  $t = 0$ , the switch is moved to position Y. Find  $i(t)$  for  $t > 0$  using transient analysis method.

**(20 marks / markah)**

Suis dalam **Rajah 2** telah berada pada posisi X untuk jangka masa yang panjang. Pada  $t = 0$ , suis diubah ke posisi Y. Dapatkan  $i(t)$  untuk  $t > 0$  dengan menggunakan analisis ubah-tika.

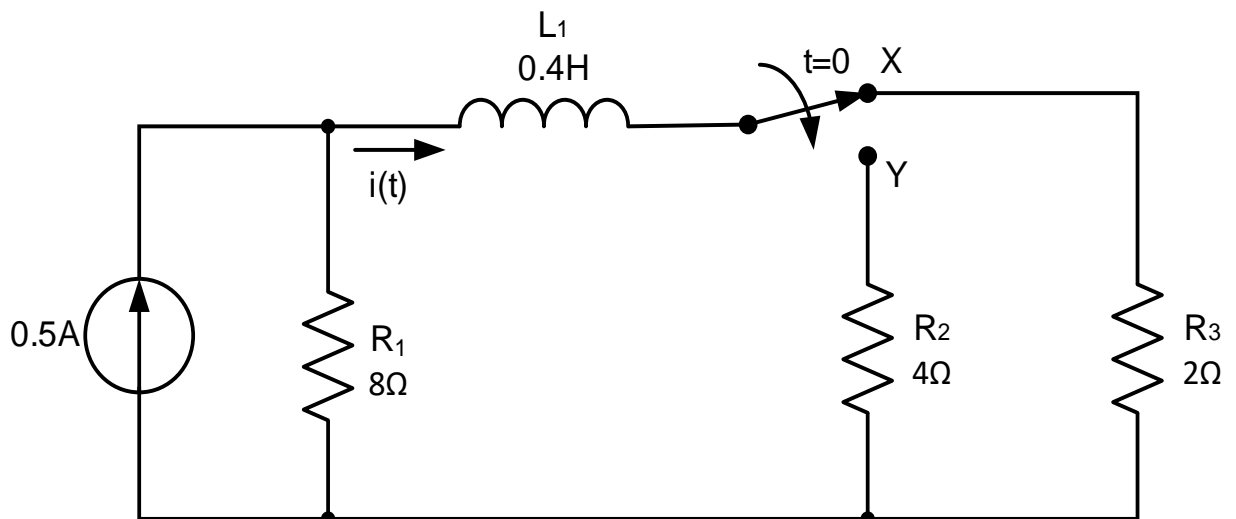


Figure 2/ Rajah 2

## QUESTION 3/ SOALAN 3

The differential equation of the current flowing through an inductor,  $i(t)$  in a second order circuit is given as:

$$\frac{d^2i(t)}{dt^2} + 5 \frac{di(t)}{dt} + 4i(t) = 4A$$

Given that the initial current flowing through an inductor,  $i(0^-) = 1A$  and

$$\frac{di(0^+)}{dt} = -6 \frac{A}{s}$$

. Find the current,  $i(t)$  using transient analysis method.

**(20 marks / markah)**

*Persamaan kebezaan bagi arus mengalir melalui pearuh,  $i(t)$  dalam satu litar tertib kedua diberi sebagai:*

$$\frac{d^2i(t)}{dt^2} + 5 \frac{di(t)}{dt} + 4i(t) = 4A$$

*Diberi arus awal melalui mengalir pearuh,  $i(0^-) = 1A$  dan  $\frac{di(0^+)}{dt} = -6 \frac{A}{s}$ .*

*Dapatkan arus,  $i(t)$  menggunakan kaedah analisis ubahtika.*

## QUESTION 4/ SOALAN 4

The circuit in **Figure 4** has been in position A for a long time. At  $t = 0$ , the switch is moved to position B. Given the initial current flowing through an inductor,  $i(0^-) = 4\text{A}$  and the initial voltage across capacitor,  $v(0^-) = 8\text{V}$ . Find the Laplace function of the voltage across capacitor,  $V(s)$  for  $t \geq 0$ .

(15 marks / markah)

Litar dalam **Rajah 4** telah berada pada posisi A untuk jangka masa yang panjang. Pada  $t = 0$ , suis diubah ke posisi B. Diberi arus awalan mengalir melalui pearuh,  $i(0^-) = 4\text{A}$  dan voltan awalan merintang pemuat,  $v(0^-) = 8\text{V}$ . Dapatkan fungsi Laplace bagi voltan merintang pemuat,  $V(s)$  untuk  $t \geq 0$ .

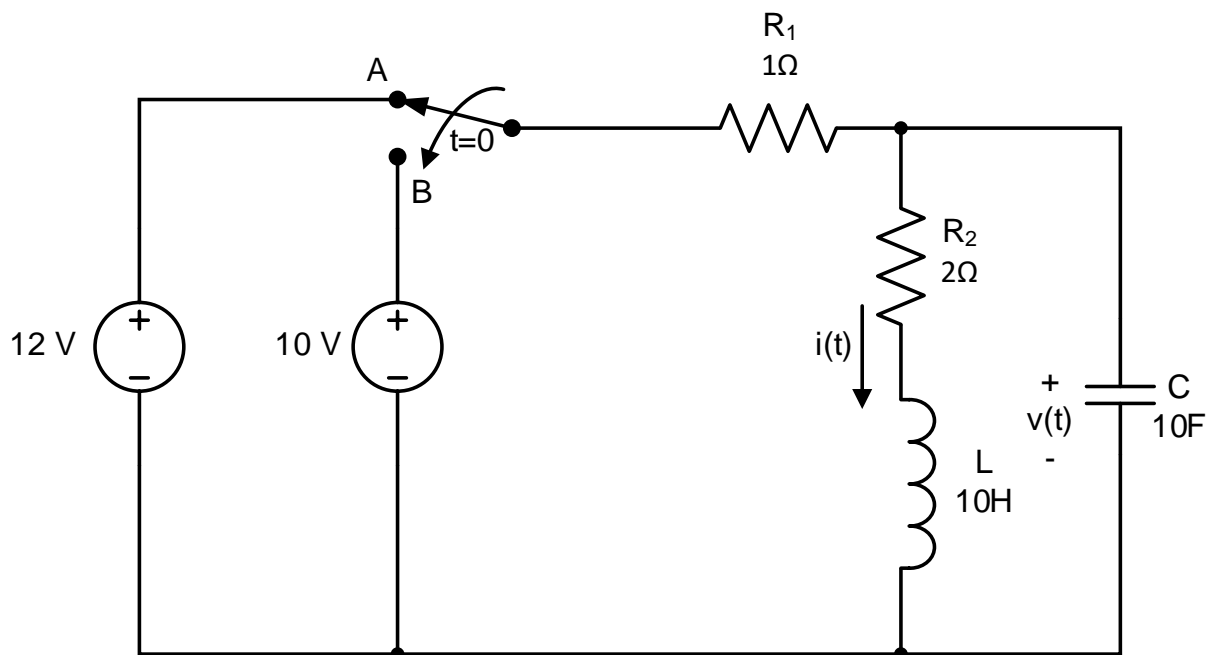


Figure 4/ Rajah 4

**QUESTION 5/ SOALAN 5**

Draw the magnitude Bode Plot for the following transfer function:

$$H(s) = \frac{200(s^2 + 10s + 900)(s + 2000)}{s^2(s + 400)^2}$$

Use minimum frequency,  $\omega = 1$  rad/s and maximum frequency,  $\omega = 100,000$  rad/s.

**(15 marks / markah)**

*Lukiskan Plot Bode Magnitud untuk rangkap pindah berikut:*

$$H(s) = \frac{200(s^2 + 10s + 900)(s + 2000)}{s^2(s + 400)^2}$$


*Guna frekuensi minima,  $\omega = 1$  rad/s dan frekuensi maksima,  $\omega = 100,000$  rad/s.*

**QUESTION 6/ SOALAN 6**

Referring to **Figure 6**, find the y-parameter for the two-port network given.

**(15 marks / markah)**

Merujuk kepada **Rajah 6**, dapatkan parameter-y bagi rangkaian dua-liang yang diberi.

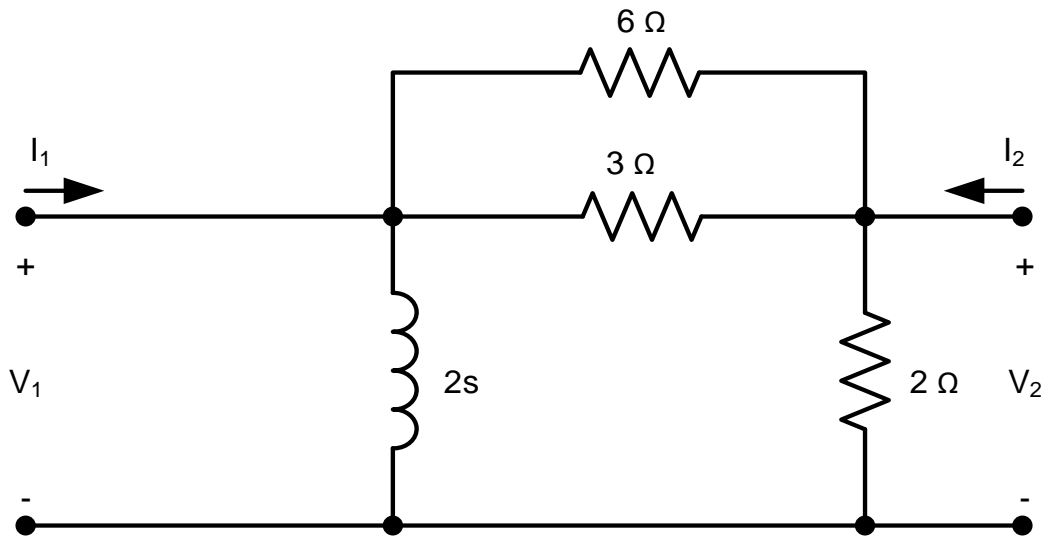

**Figure 6/ Rajah 6**

**[100 MARKS/ 100 MARKAH]**

**END OF QUESTION PAPER/ KERTAS SOALAN TAMAT**

Forcing Functions and Their Assumed Solutions  
(Fungsi Berdaya dan Penyelesaian Anggapan)

<i>Forcing functions (Fungsi Berdaya)</i>		<i>Assumed Solutions (Penyelesaian Anggapan)</i>
Constan ( <i>Malar</i> )		$f(t) = A$ $x_f(t) = K_2$
Exponential ( <i>Eksponen</i> )		$f(t) = M e^{-st}$ $x_f(t) = K_2 e^{-st}$
Variable ( <i>Pembolehubah</i> )	Ramp ( <i>Tanjak</i> )	$f(t) = mt$ $x_f(t) = K_2 t + K_3$
	Parabolic ( <i>Parabola</i> )	$f(t) = t^2$ $x_f(t) = K_2 t^2 + K_3 t + K_4$
Sinusoidal ( <i>Sinus</i> )		$f(t) = M \sin(\omega t + \theta)$ $f(t) = M \cos(\omega t + \theta)$ $x_f(t) = K_2 \sin \omega t + K_3 \cos \omega t$
Exponential Sinusoidal ( <i>Sinus Eksponen</i> )		$f(t) = M e^{-st} \sin(\omega t + \theta)$ $x_f(t) = e^{-st} (K_2 \sin \omega t + K_3 \cos \omega t)$



Table of Laplace Transform Pairs  
(Jadual Penukaran Pasangan Penjelmaan Laplace)

Functions ( <i>Fungsi</i> )	$f(t)$	$F(s)$
Unit Impulse ( <i>Dedenyut</i> )	$\delta(t)$	1
Unit Step ( <i>Unit langkah</i> ) Constant ( <i>Malar</i> )	$u(t)$ 1	$\frac{1}{s}$
Unit Ramp ( <i>Unit Tanjak</i> ) $t$ function ( <i>Rangkap <math>t</math></i> )	$t u(t)$	$\frac{1}{s^2}$
Unit Parabolic ( <i>Unit Parabola</i> )	$\frac{1}{2} t^2 u(t)$	$\frac{1}{s^3}$
$n^{\text{th}}$ integral of impulse ( <i>Kamiran ke-<math>n</math> dedenyut</i> )	$\delta^{-n}(t)$	$\frac{1}{s^n}$
$n^{\text{th}}$ derivative of impulse ( <i>Kerbezaan ke-<math>n</math> dedenyut</i> )	$\delta^n(t)$	$s^n$
Power of $t$ ( <i>Kuasa <math>t</math></i> )	$\frac{t^{n-1}}{(n-1)!}$	$\frac{1}{s^n}$
Exponential ( <i>Eksponen</i> )	$e^{-at}$	$\frac{1}{s+a}$
$t$ -multiplication exponential ( <i>Pendaraban <math>t</math> bagi eksponen</i> )	$te^{-at}$	$\frac{1}{(s+a)^2}$
Repeated $t$ -multiplication exponential ( <i>Pendaraban <math>t</math> berulang bagi eksponen</i> )	$\frac{1}{(n-1)!} t^{n-1} e^{-at}$	$\frac{1}{(s+a)^n}$
Sine ( <i>Sinus</i> )	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
Cosine ( <i>Kosinus</i> )	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
Damped sine ( <i>Sinus teredam</i> )	$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
Damped cosine ( <i>Kosinus teredam</i> )	$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$
$t$ -multiplied sine ( <i>Pendaraban <math>t</math> bagi sinus</i> )	$t \sin \omega t$	$\frac{2\omega s}{(s^2 + \omega^2)^2}$
$t$ -multiplied cosine ( <i>Pendaraban <math>t</math> bagi kosinus</i> )	$t \cos \omega t$	$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$

Two-Port Network Parameters  
(Parameter Rangkaian Dua Liang)

Impedance parameters

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

Admittance parameters

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

Hybrid parameters

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

Transmission parameters

$$V_1 = A V_2 - B I_2$$

$$I_1 = C V_2 - D I_2$$

Jadual Penukaran Untuk Rangkaian Dua Liang  
(Conversion Table for Two-Port Network Parameters)

	z		y		h		ABCD	
z	$z_{11}$	$z_{12}$	$\frac{y_{22}}{\Delta_y}$	$-\frac{y_{12}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$	$\frac{A}{C}$	$\frac{\Delta_T}{C}$
	$z_{21}$	$z_{22}$	$-\frac{y_{21}}{\Delta_y}$	$\frac{y_{11}}{\Delta_y}$	$-\frac{h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$	$\frac{1}{C}$	$\frac{D}{C}$
y	$\frac{z_{22}}{\Delta_z}$	$-\frac{z_{12}}{\Delta_z}$	$y_{11}$	$y_{12}$	$\frac{1}{h_{11}}$	$-\frac{h_{12}}{h_{11}}$	$\frac{D}{B}$	$-\frac{\Delta_T}{B}$
	$-\frac{z_{21}}{\Delta_z}$	$\frac{z_{11}}{\Delta_z}$	$y_{21}$	$y_{22}$	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$	$-\frac{1}{B}$	$\frac{A}{B}$
h	$\frac{\Delta_z}{z_{22}}$	$\frac{z_{12}}{z_{22}}$	$\frac{1}{y_{11}}$	$-\frac{y_{12}}{y_{11}}$	$h_{11}$	$h_{12}$	$\frac{B}{D}$	$\frac{\Delta_T}{D}$
	$-\frac{z_{21}}{z_{22}}$	$\frac{1}{z_{22}}$	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta_y}{y_{11}}$	$h_{21}$	$h_{22}$	$-\frac{1}{D}$	$\frac{C}{D}$
ABCD	$\frac{z_{11}}{z_{21}}$	$\frac{\Delta_z}{z_{21}}$	$-\frac{y_{22}}{y_{21}}$	$-\frac{1}{y_{21}}$	$-\frac{\Delta_h}{h_{21}}$	$-\frac{h_{11}}{h_{21}}$	A	B
	$\frac{1}{z_{21}}$	$\frac{z_{22}}{z_{21}}$	$-\frac{\Delta_y}{y_{21}}$	$-\frac{y_{11}}{y_{21}}$	$-\frac{h_{22}}{h_{21}}$	$-\frac{1}{h_{21}}$	C	D