



**KOLEJ YAYASAN PELAJARAN JOHOR
FINAL EXAMINATION**

COURSE NAME : CIRCUIT ANALYSIS
COURSE CODE : DEE 2113
SESSION : JANUARY 2024
DURATION : 2 HOURS 30 MINUTES

**INSTRUCTION TO CANDIDATES /
ARAHAN KEPADA CALON**


1. This examination paper consists of **SIX (6)** questions. Answer **ALL** questions. /
Kertas soalan ini mengandungi ENAM (6) soalan. Jawab SEMUA soalan.

2. Candidates are not allowed to bring any material/note to the examination hall/room except with the permission from the invigilator. /
Calon tidak dibenarkan untuk membawa sebarang bahan/nota ke dewan/bilik peperiksaan tanpa kebenaran daripada pengawas.

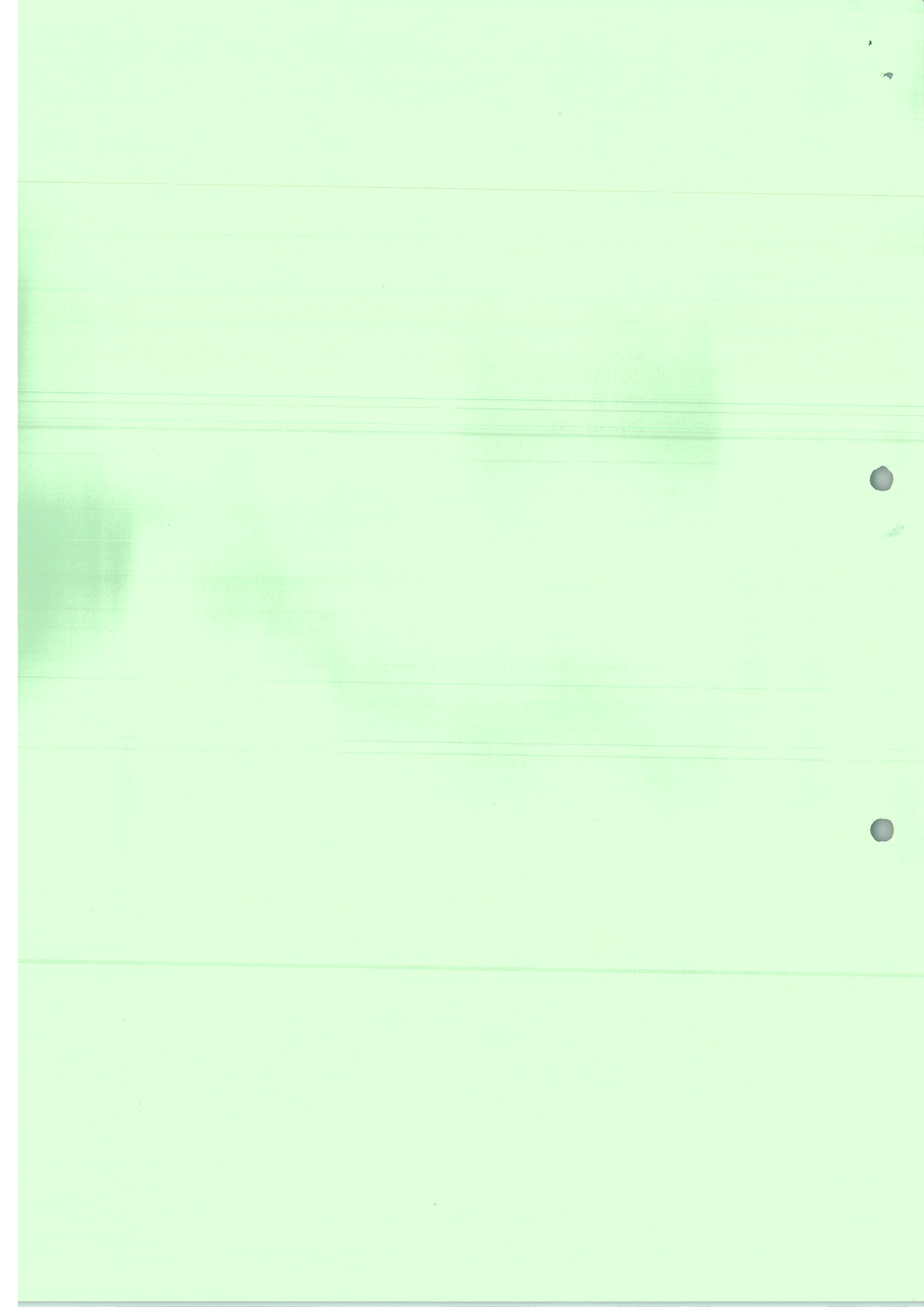3. Please check to make sure that this examination pack consist of: /
Pastikan kertas soalan peperiksaan ini mengandungi:
 - i. The Question Paper /
Kertas Soalan
 - ii. An Answering Booklet /
Buku Jawapan
 - iii. Attachment 1 /
Lampiran 1
 - iv. Semilog Paper/
Kertas Semilog

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIBERITAHU**

This examination paper consists of **14** printed pages including front page
Kertas soalan ini mengandungi 14 halaman bercetak termasuk muka hadapan



This examination paper consists of **SIX (6)** questions. Answer **ALL** the questions in the Answering Booklet.

*Kertas soalan ini mengandungi **ENAM (6)** soalan. Jawab **SEMUA** soalan dalam Buku Jawapan.*

QUESTION 1 / SOALAN 1

Figure 1 shows five (5) interconnected capacitor. The initial voltages for four (4) of the capacitors are also shown in **Figure 1**. Looking from terminal A - B.

- Calculate the equivalent capacitance, C_{eq} .
- Calculate the initial voltage in the capacitive network.
- Find the energy stored in equivalent capacitance, C_{eq} .

(10 marks/ markah)

***Rajah 1** menunjukkan lima (5) pemuat yang saling berkaitan. Voltan awalan bagi empat (4) pemuat juga ditunjukkan dalam **Rajah 1**. Dilihat dari terminal A - B.*

- Kirakan kemuatan setara, C_{eq} .*
- Kirakan voltan awalan dalam rangkaian pemuat.*
- Dapatkan tenaga yang disimpan di dalam kemuatan setara, C_{eq} .*

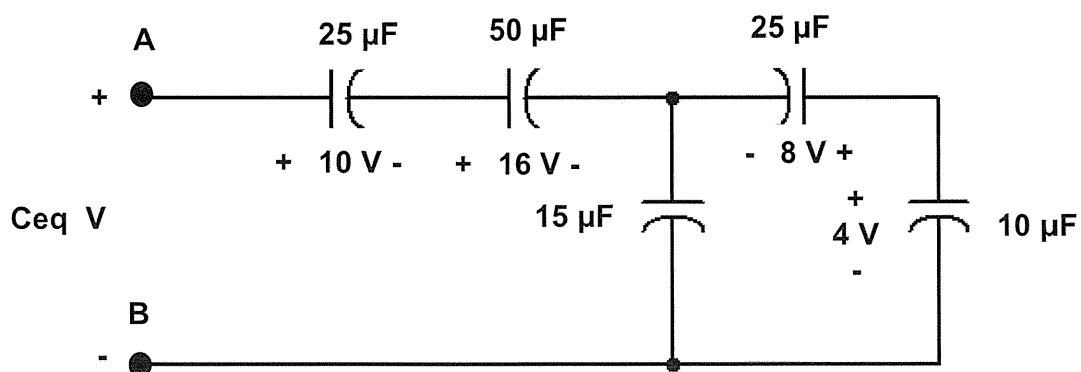


Figure 1/ Rajah 1

QUESTION 2 / SOALAN 2

Refer to **Figure 2**, S_1 at position B and S_2 closed at $t > 0$. Find $i(t)$ for $t \geq 0$ using transient analysis method.

(15 marks/ *markah*)

Merujuk kepada **Rajah 2**, S_1 pada kedudukan B dan S_2 ditutup pada $t > 0$. Cari $i(t)$ untuk $t \geq 0$ menggunakan kaedah analisis ubah-tika.

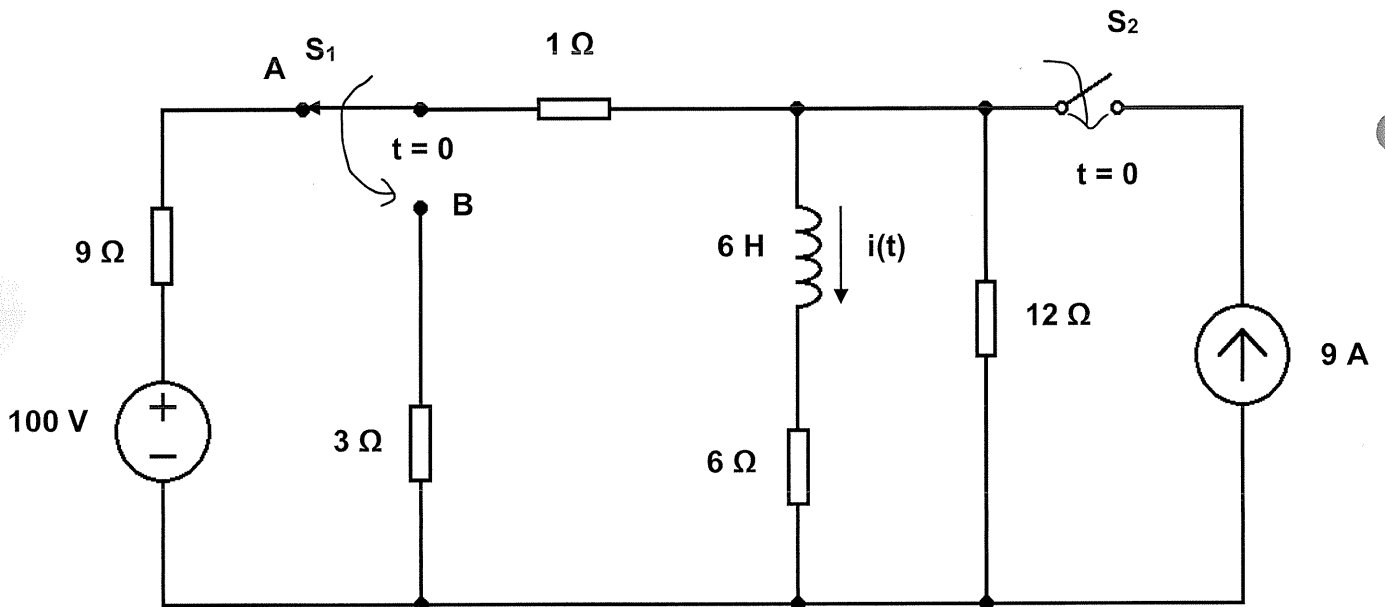


Figure 2 / *Rajah 2*

QUESTION 3 / SOALAN 3

By referring to **Figure 3**. When switch is closed, $t < 0$ and when the switch is opened $t \geq 0$. Find:

- the initial value at $t < 0$.
- the possible behaviour for the natural response by refers to circuit.
- the complete response of the current, $i(t)$. Assumed that the circuit has reached steady state at $t = 0^-$.

(25 marks/ markah)

Dengan merujuk kepada **Rajah 3**. Apabila suis ditutup, $t < 0$ dan apabila suis dibuka, $t \geq 0$. Dapatkan:

- nilai awalan pada $t < 0$.
- kemungkinan kelakuan bagi tindak balas semula jadi dengan merujuk kepada litar.
- tindak balas lengkap bagi arus, $i(t)$. Dianggap bahawa litar telah mencapai keadaan mantap pada $t = 0^-$.

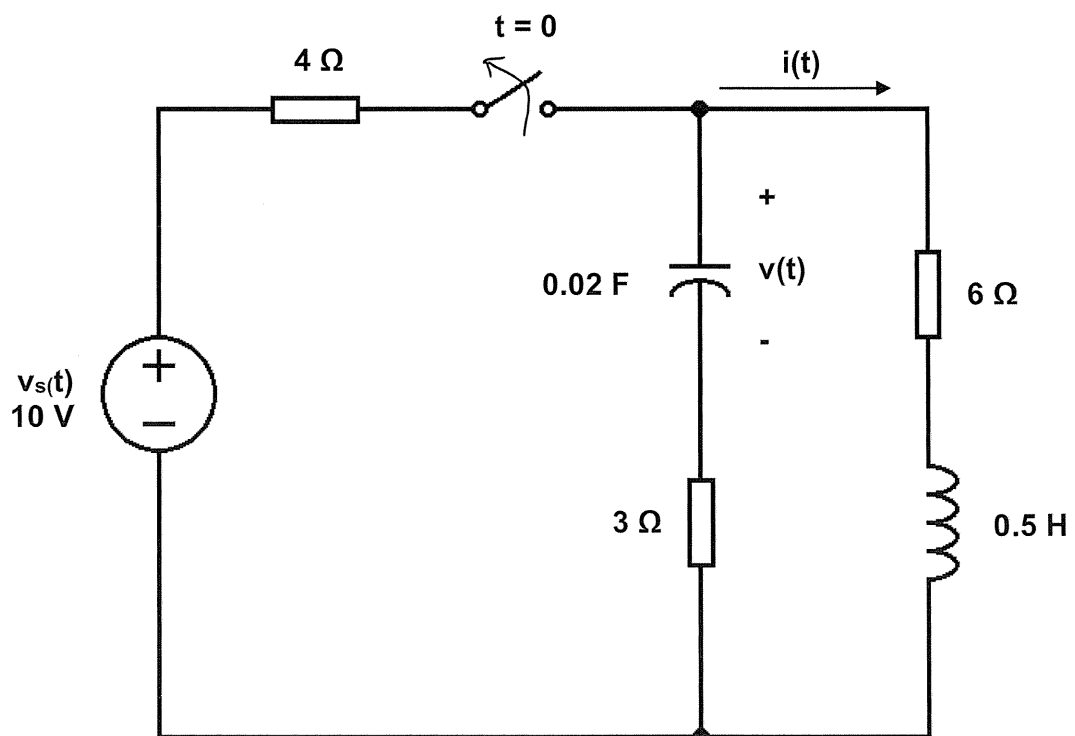


Figure 3 / Rajah 3

QUESTION 4 / SOALAN 4

Referring to **Figure 4**, find the value of the voltage across the capacitor by using Laplace method. Assuming that the value of $v_s(t) = 10$ V. Given initial value of current flow through inductor, $i(0^-) = -1$ A and initial value of voltage at voltage across capacitor, $v(0^-) = 5$ V.

(15 marks/ *markah*)

Merujuk kepada **Rajah 4**, cari nilai voltan merentasi pemuat dengan menggunakan kaedah Laplace. Dengan mengandaikan bahawa nilai $v_s(t) = 10$ V. Diberi nilai awalan arus mengalir pearuh, $i(0^-) = -1$ A dan nilai awalan voltan merentasi pemuat, $v(0^-) = 5$ V.

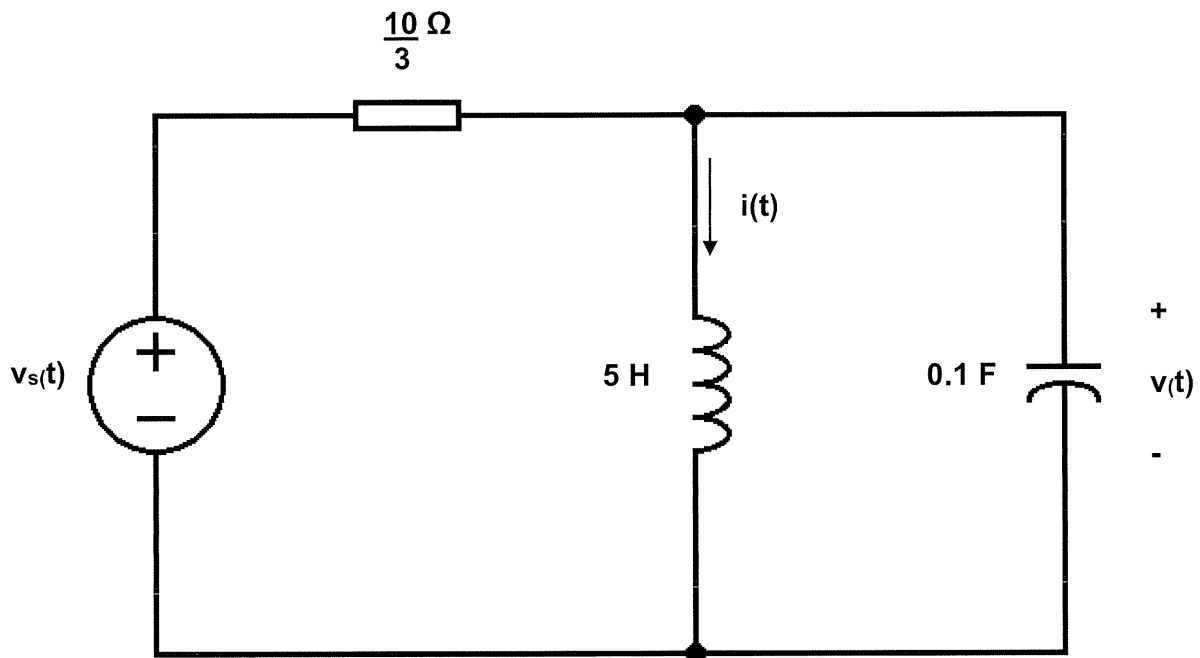


Figure 4/ *Rajah 4*

QUESTION 5 / SOALAN 5

Draw the magnitude Bode Plot for the following transfer function:

$$H(s) = \frac{50s}{(s + 4)(s + 10)^2}$$

Use minimum frequency, $\omega=0.1$ radian/second and maximum frequency, $\omega=10,000$ radian/second.

(15 marks/ markah)

Lukis Plot Bode magnitud untuk rangkap pindah berikut:

$$H(s) = \frac{50s}{(s + 4)(s + 10)^2}$$

Guna frekuensi minima, $\omega=0.1$ radian/saat dan frekuensi maksima, $\omega=10,000$ radian/saat.

QUESTION 6 / SOALAN 6

Referring to the **Figure 5**, obtain the y-parameters for the network as function of s.

(20 marks/ *markah*)

Merujuk kepada **Rajah 5**, dapatkan parameter-y untuk rangkaian sebagai fungsi s.

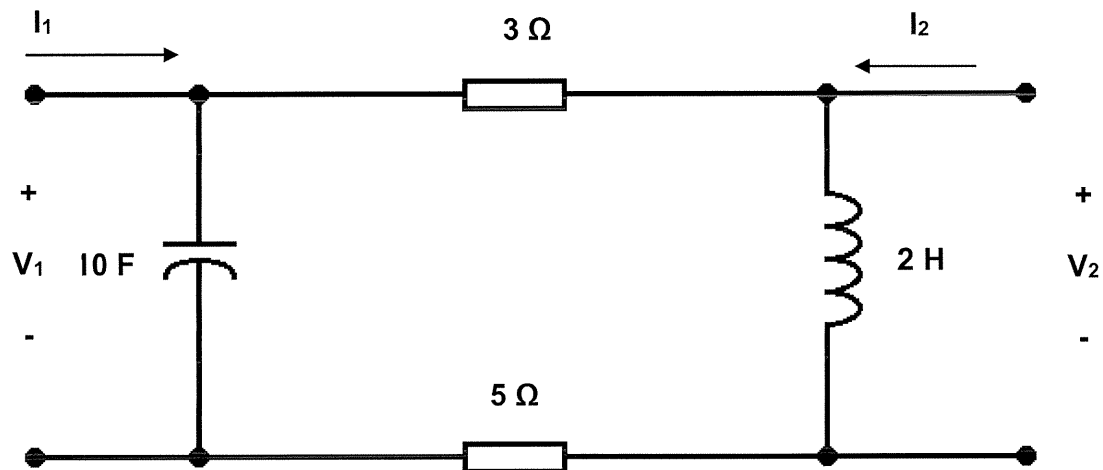


Figure 5 / *Rajah 5*

[100 MARKS/ *MARKAH*]




END OF QUESTION PAPER / KERTAS SOALAN TAMAT

Attachment 1 / Lampiran 1

Series, Parallel for Capacitor and Inductor
Siri, Selari untuk Pemuat dan Pearuh

Series / Siri	Parallel / Selari
Capacitor / Pemuat	
$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$	$C_{eq} = C_1 + C_2 + \dots + C_N$
Inductor / Pearuh	
$L_{eq} = L_1 + L_2 + \dots + L_N$	$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$

Current and Voltage Relationship for R, L, C
Hubungan Arus dan Voltan untuk R, L, C

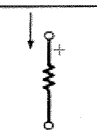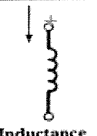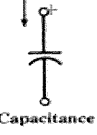Circuit element	Units	Voltage	Current	Power
 Resistance	ohms (Ω)	$v = Ri$ (Ohm's law)	$i = \frac{v}{R}$	$p = vi = i^2R$
 Inductance	henries (H)	$v = L \frac{di}{dt}$	$i = \frac{1}{L} \int v dt + k_1$	$p = vi = Li \frac{di}{dt}$
 Capacitance	farads (F)	$v = \frac{1}{C} \int i dt + k_2$	$i = C \frac{dv}{dt}$	$p = vi = Cv \frac{dv}{dt}$

RL Circuit and RC Circuit
Litar RL dan Litar RC

RL Circuit / Litar RL	RC Circuit / Litar RC
Free Source / Tiada Sumber	
$i(t) = I_0 e^{-t/\tau} \quad \tau = \frac{L}{R}$	$v(t) = V_0 e^{-t/\tau} \quad \tau = RC$
Variety Source / Pelbagai Sumber	
$i(t) = i(\infty) + [i(0+) - i(\infty)] e^{-t/\tau}$	$v(t) = v(\infty) + [v(0+) - v(\infty)] e^{-t/\tau}$

Free Source RLC Circuit
Litar RLC Tiada Sumber

Series RLC Circuit
Litar RLC Siri

1. If $\alpha > \omega_0$, over-damped case

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \text{where } s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

2. If $\alpha = \omega_0$, critical damped case

$$i(t) = (A_2 + A_1 t) e^{-\alpha t} \quad \text{where } s_{1,2} = -\alpha$$

3. If $\alpha < \omega_0$, under-damped case

$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) \quad \text{where } \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

Where:

$$\alpha = \frac{R}{2L} \quad \text{and} \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

Parallel RLC Circuit
Litar RLC Selari

1. If $\alpha > \omega_0$, over-damped case

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \text{where } s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

2. If $\alpha = \omega_0$, critical damped case

$$v(t) = (A_2 + A_1 t) e^{-\alpha t} \quad \text{where } s_{1,2} = -\alpha$$

3. If $\alpha < \omega_0$, under-damped case

$$v(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t) \quad \text{where } \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

Where:

$$\alpha = \frac{1}{2RC} \quad \text{and} \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

Step Response RLC Circuit
Litar RLC Tindak Balas Langkah

Series RLC Circuit
Litar RLC Siri

$$v(t) = v_t(t) + v_{ss}(t)$$

$$v_t(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \text{If } \alpha > \omega_0 \quad (\text{over-damped}) \quad s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$v_t(t) = (A_1 + A_2 t) e^{-\alpha t} \quad \text{If } \alpha = \omega_0 \quad (\text{critically damped}) \quad s_{1,2} = -\alpha$$

$$v_t(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t) \quad (\text{under-damped}) \quad \text{If } \alpha < \omega_0$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$\text{And } v_{ss}(t) = v(\infty)$$

Parallel RLC Circuit
Litar RLC Selari

$$i(t) = i_t(t) + i_{ss}(t)$$

$$i_t(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \text{If } \alpha > \omega_0 \quad (\text{over-damped}) \quad s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$i_t(t) = (A_1 + A_2 t) e^{-\alpha t} \quad \text{If } \alpha = \omega_0 \quad (\text{critical damped}) \quad s_{1,2} = -\alpha$$

$$i_t(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t) \quad (\text{under-damped}) \quad \text{If } \alpha < \omega_0$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$\text{And } i_{ss}(t) = i(\infty)$$

Forcing Functions and Their Assumed Solutions
Fungsi Berdaya dan Penyelesaian Anggapan

Forcing function / Fungsi Berdaya		Assumed Solution / Penyelesaian Anggapan
Constan / Malar		$f(t) = A$ $x_f(t) = K_2$
Exponential/ Eksponen		$f(t) = M e^{-st}$ $x_f(t) = K_2 e^{-st}$
Variable/ Pembolehubah	Ramp/ Tanjak	$f(t) = mt$ $x_f(t) = K_2 t + K_3$
	Parabolic/ Parabola	$f(t) = t^2$ $x_f(t) = K_2 t^2 + K_3 t + K_4$
Sinusoidal/ Sinus		$f(t) = M \sin(\omega t + \theta)$
		$f(t) = M \cos(\omega t + \theta)$ $x_f(t) = K_2 \sin \omega t + K_3 \cos \omega t$
Exponential Sinusoidal/ Sinus Eksponen		$f(t) = M e^{-st} \sin(\omega t + \theta)$ $x_f(t) = e^{-st} (K_2 \sin \omega t + K_3 \cos \omega t)$

Table of Laplace Transform Pairs
Jadual Penukaran Pasangan Jelmaan Laplace

Function/ <i>Rangkap</i>	$f(t)$	$F(s)$
Unit Impulse/ <i>Dedenyut</i>	$\delta(t)$	1
Unit Step/ <i>Unit langkah</i> Constant / <i>Malar</i>	$u(t)$ 1	$\frac{1}{s}$
Unit Ramp/ <i>Unit Tanjak</i> t function / <i>Rangkap t</i>	$t u(t)$	$\frac{1}{s^2}$
Unit Parabolic / <i>Unit Parabola</i>	$\frac{1}{2}t^2 u(t)$	$\frac{1}{s^3}$
n^{th} integral of impulse/ <i>Kamiran ke-n dedenyut</i>	$\delta^{-n}(t)$	$\frac{1}{s^n}$
n^{th} derivative of impulse/ <i>Kerbezaan ke-n dedenyut</i>	$\delta^n(t)$	s^n
Power of t / <i>Kuasa t</i>	$\frac{t^{n-1}}{(n-1)!}$	$\frac{1}{s^n}$
Exponential / <i>Eksponen</i>	e^{-at}	$\frac{1}{s+a}$
t -multiplication exponential/ <i>Pendaraban t bagi eksponen</i>	te^{-at}	$\frac{1}{(s+a)^2}$
Repeated t -multiplication exponential/ <i>Pendaraban t berulang bagi eksponen</i>	$\frac{1}{(n-1)!} t^{n-1} e^{-at}$	$\frac{1}{(s+a)^n}$
Sine/ <i>Sinus</i>	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
Cosine/ <i>Kosinus</i>	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
Damped sine/ <i>Sinus teredam</i>	$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$

Damped cosine/ <i>Kosinus teredam</i>	$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$
<i>t</i> -multiplied sine <i>Pendaraban t bagi sinus</i>	$t \sin \omega t$	$\frac{2\omega s}{(s^2 + \omega^2)^2}$
<i>t</i> -multiplied cosine <i>Pendaraban t bagi kosinus</i>	$t \cos \omega t$	$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$

Two-Port Network Parameters
Parameter Rangkaian Dua Liang

Impedance parameters

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

Hybrid parameters

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

Admittance parameters

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

Transmission parameters

$$V_1 = A V_2 - B I_2$$

$$I_1 = C V_2 - D I_2$$

Conversion Table for Two-Port Network Parameters
Jadual Penukaran Untuk Rangkaian Dua Liang

	Z	Y	h	ABCD
Z	z_{11} z_{12} z_{21} z_{22}	$\frac{y_{22}}{\Delta_y}$ $-\frac{y_{12}}{\Delta_y}$ $-\frac{y_{21}}{\Delta_y}$ $\frac{y_{11}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$ $\frac{h_{12}}{h_{22}}$ $-\frac{h_{21}}{h_{22}}$ $\frac{1}{h_{22}}$	$\frac{A}{C}$ $\frac{\Delta_T}{C}$ $\frac{1}{C}$ $\frac{D}{C}$
Y	$\frac{z_{22}}{\Delta_z}$ $-\frac{z_{12}}{\Delta_z}$ $-\frac{z_{21}}{\Delta_z}$ $\frac{z_{11}}{\Delta_z}$	y_{11} y_{12} y_{21} y_{22}	$\frac{1}{h_{11}}$ $-\frac{h_{12}}{h_{11}}$ $\frac{h_{21}}{h_{11}}$ $\frac{\Delta_h}{h_{11}}$	$\frac{D}{B}$ $-\frac{\Delta_T}{B}$ $-\frac{1}{B}$ $\frac{A}{B}$
h	$\frac{\Delta_z}{z_{22}}$ $\frac{z_{12}}{z_{22}}$ $-\frac{z_{21}}{z_{22}}$ $\frac{1}{z_{22}}$	$\frac{1}{y_{11}}$ $-\frac{y_{12}}{y_{11}}$ $\frac{y_{21}}{y_{11}}$ $\frac{\Delta_y}{y_{11}}$	h_{11} h_{12} h_{21} h_{22}	$\frac{B}{D}$ $\frac{\Delta_T}{D}$ $-\frac{1}{D}$ $\frac{C}{D}$
ABCD	$\frac{z_{11}}{z_{21}}$ $\frac{\Delta_z}{z_{21}}$ $\frac{1}{z_{21}}$ $\frac{z_{22}}{z_{21}}$	$-\frac{y_{22}}{y_{21}}$ $-\frac{1}{y_{21}}$ $-\frac{\Delta_y}{y_{21}}$ $-\frac{y_{11}}{y_{21}}$	$-\frac{\Delta_h}{h_{21}}$ $-\frac{h_{11}}{h_{21}}$ $-\frac{h_{22}}{h_{21}}$ $-\frac{1}{h_{21}}$	A B C D

