



---

KOLEJ YAYASAN PELAJARAN JOHOR  
FINAL EXAMINATION

---

COURSE NAME : CIRCUIT ANALYZE  
COURSE CODE : DKE 2093  
SESSION : DECEMBER 2022  
DURATION : 2 HOURS 30 MINUTES

---

INSTRUCTION TO CANDIDATES/  
ARAHAN KEPADA CALON

1. This examination paper consists of **SIX (6)** questions. /  
*Kertas soalan ini mengandungi ENAM (6) soalan.*
2. Candidates are not allowed to bring any material to examination room except with the permission from the invigilator. /  
*Calon tidak dibenarkan untuk membawa sebarang bahan/nota ke bilik peperiksaan tanpa kebenaran daripada pengawas.*
3. Please check to make sure that this examination pack consists of: /  
*Pastikan kertas soalan peperiksaan ini mengandungi:*
  - i. Question Paper /  
*Kertas Soalan.*
  - ii. Answering Booklet /  
*Buku Jawapan.*
  - iii. Semilog Graph Paper/  
*Kertas Semilog Graf.*

---

DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /  
JANGAN BUKA KERTAS SOALANINI SEHINGGA DIBERITAHU

---

This examination paper consists of **10** printed pages including front page  
*Kertas soalan ini mengandungi 10 halaman bercetak termasuk kulit hadapan*

This examination paper consists of **SIX (6)** questions. Answer **ALL** the questions in an Answering Booklet.

*Kertas soalan ini mengandungi **ENAM (6)** soalan. Jawab **SEMUA** soalan dalam Buku Jawapan.*

### QUESTION 1/ SOALAN 1

Referring to **Figure 1**, find the equivalent inductance,  $L_{eq}$  view from terminal A-B and the energy stored in equivalent inductance,  $L_{eq}$  for the circuit under direct current condition.

(15 marks/ markah)

Berdasarkan **Rajah 1**, dapatkan kearuhan setara,  $L_{eq}$  dilihat dari terminal A-B dan tenaga yang disimpan dalam kearuhan setara,  $L_{eq}$  untuk litar di bawah keadaan arus terus.

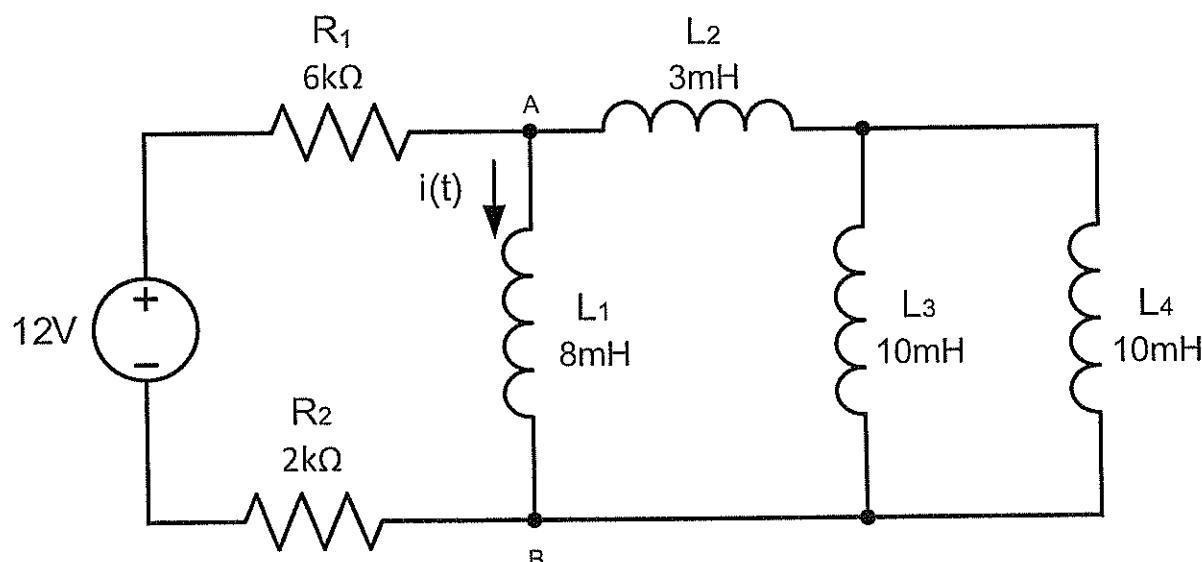


Figure 1/ Rajah 1

## QUESTION 2/ SOALAN 2

Assume that the circuit in **Figure 2** is in its steady state condition at  $t < 0$ . Find  $v(t)$  for  $t > 0$  using transient analysis method.

(20 marks/ markah)

*Anggapkan bahawa litar dalam **Rajah 2** telah berada dalam keadaan mantap pada  $t < 0$ . Dapatkan  $v(t)$  untuk  $t > 0$  dengan menggunakan kaedah analisis ubahtika.*

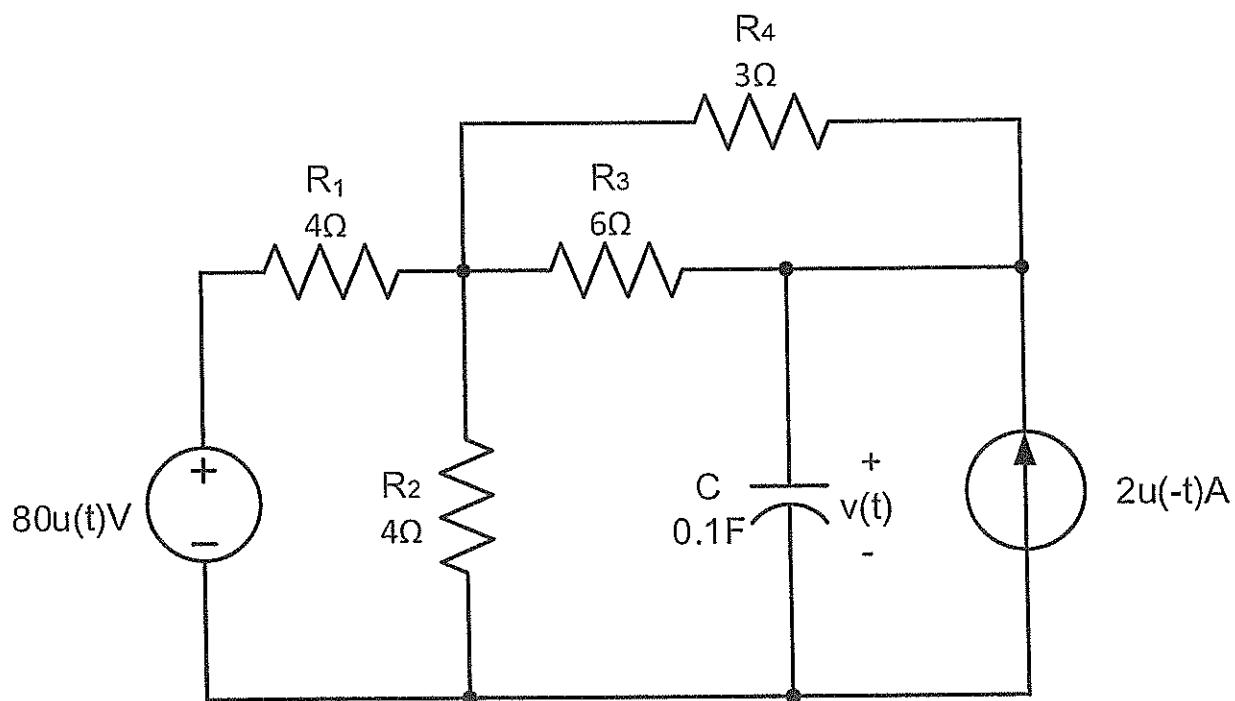


Figure 2/ Rajah 2

**QUESTION 3/ SOALAN 3**

The differential equation of the voltage across capacitor,  $v(t)$  in a second order circuit is given as:

$$\frac{d^2v(t)}{dt^2} + 4 \frac{dv(t)}{dt} + 4v(t) = 12V$$

$$\frac{dv(0^+)}{dt} = 1 \frac{V}{s}$$

Given that the initial voltage across capacitor,  $v(0^-)=6V$  and  $\frac{dv(0^+)}{dt} = 1 \frac{V}{s}$ . Find the voltage,  $v(t)$  using transient analysis method.

(20 marks/ markah)

*Persamaan kebezaan bagi voltan merintangi pemuat,  $v(t)$  dalam satu litar tertib kedua diberi sebagai:*

$$\frac{d^2v(t)}{dt^2} + 4 \frac{dv(t)}{dt} + 4v(t) = 12V$$

$$\frac{dv(0^+)}{dt} = 1 \frac{V}{s}$$

*Diberi voltan awalan merintangi pemuat,  $v(0)=6V$  dan  $\frac{dv(0^+)}{dt} = 1 \frac{V}{s}$ . Dapatkan voltan,  $v(t)$  menggunakan kaedah analisis ubahtika.*

## QUESTION 4/ SOALAN 4

The switches  $S_1$  and  $S_2$  in the circuit of Figure 4 have been opened for a long time at  $t < 0$ . At  $t = 0$ , both switches are closed. Find the Laplace function of the voltage across capacitor,  $V(s)$  for  $t \geq 0$  using Laplace analysis method.

(15 marks/ markah)

Suis  $S_1$  dan  $S_2$  dalam litar Rajah 4 telah dibuka dalam jangka masa yang panjang pada  $t < 0$ . Pada  $t = 0$ , kedua-dua suis ditutup. Dapatkan fungsi Laplace bagi voltan melintangi pemuat,  $V(s)$  untuk  $t \geq 0$  menggunakan kaedah analisis Laplace.

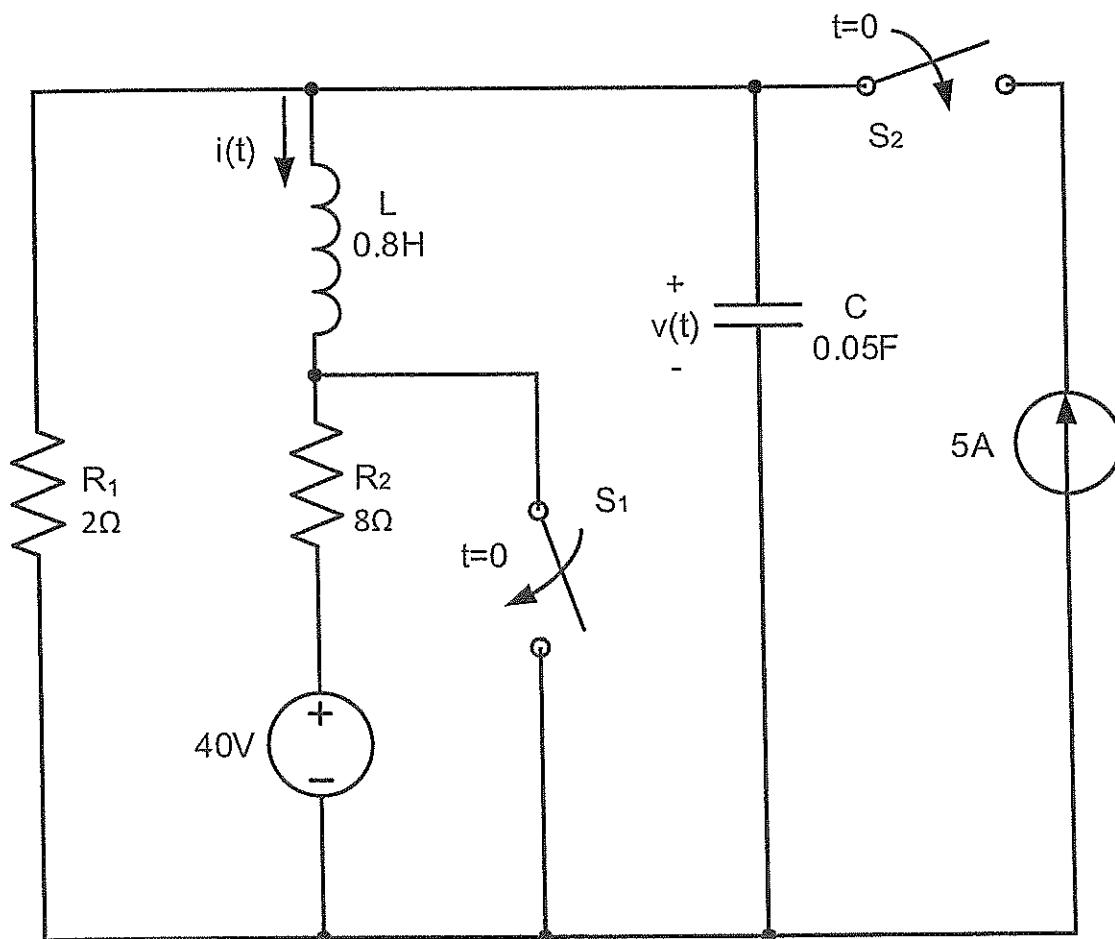


Figure 4/ Rajah 4

**QUESTION 5/ SOALAN 5**

Draw the magnitude Bode Plot for the following transfer function:

$$H(s) = \frac{(s + 20)^2(s^2 + 48s + 360000)}{563s^2(s + 8000)}$$

Use minimum frequency,  $\omega=1$  rad/s and maximum frequency,  $\omega=100,000$  rad/s.

(15 marks/ markah)

Lukiskan magnitud Rajah Bode untuk rangkap pindah berikut:

$$H(s) = \frac{(s + 20)^2(s^2 + 48s + 360000)}{563s^2(s + 8000)}$$

Guna frekuensi minima,  $\omega=1$  rad/s dan frekuensi maksima,  $\omega=100,000$  rad/s.

**QUESTION 6/ SOALAN 6**

The two-port network is terminated as shown in Figure 6. Find the output voltage,  $V_2$  and the output current,  $I_2$ .

$$Z = \begin{pmatrix} s+2 & \frac{1}{s} \\ -2 & 2 + \frac{1}{s} \end{pmatrix}$$

(15 marks/ markah)

Rangkaian dua-liang ditamatkan seperti ditunjukkan dalam Rajah 6. Dapatkan voltan keluaran,  $V_2$  dan arus keluaran,  $I_2$ .

$$Z = \begin{pmatrix} s+2 & \frac{1}{s} \\ -2 & 2 + \frac{1}{s} \end{pmatrix}$$

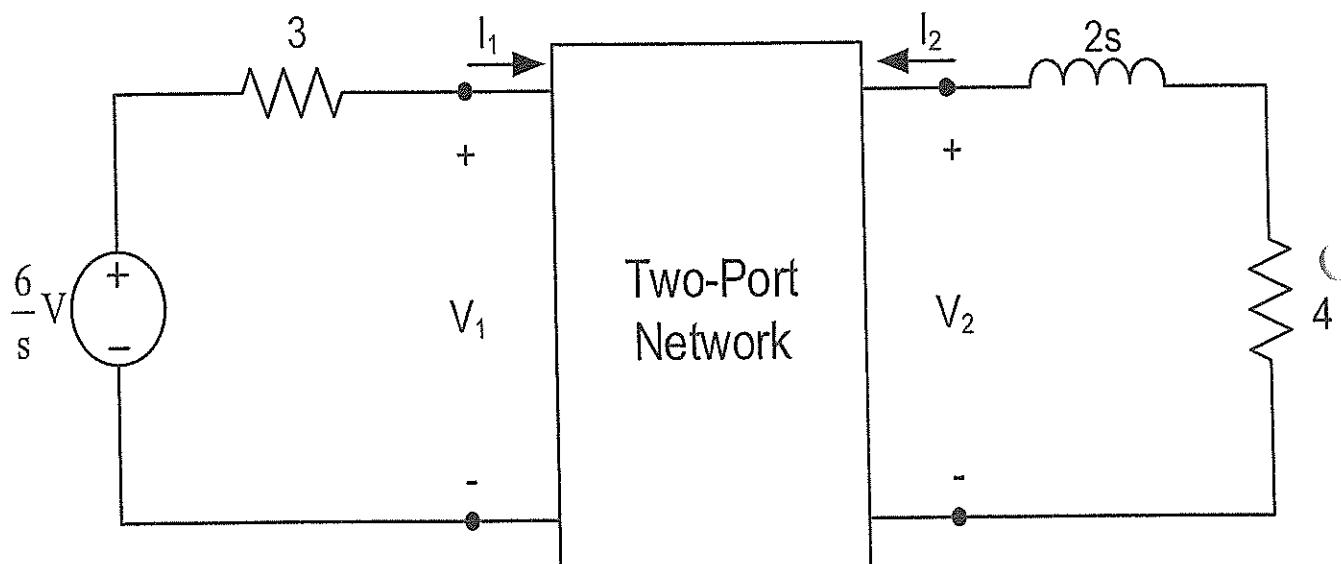


Figure 6/ Rajah 6

[100 MARKS/ 100 MARKAH]

**END OF QUESTION PAPER/ KERTAS SOALAN TAMAT**

Forcing Functions and Their Assumed Solutions  
*(Fungsi Berdaya dan Penyelesaian Anggapan)*

<i>Forcing functions (Fungsi Berdaya)</i>		<i>Assumed Solutions (Penyelesaian Anggapan)</i>	
Constan (Malar)	$f(t) = A$	$x_f(t) = K_2$	
Exponential (Eksponen)	$f(t) = M e^{-st}$	$x_f(t) = K_2 e^{-st}$	
Variable <i>(Pembolehubah)</i>	Ramp <i>(Tanjak)</i>	$f(t) = mt$	$x_f(t) = K_2 t + K_3$
	Parabolic <i>(Parabola)</i>	$f(t) = t^2$	$x_f(t) = K_2 t^2 + K_3 t + K_4$
Sinusoidal <i>(Sinus)</i>	$f(t) = M \sin(\omega t + \theta)$	$x_f(t) = K_2 \sin \omega t + K_3 \cos \omega t$	
	$f(t) = M \cos(\omega t + \theta)$		
Exponential Sinusoidal <i>(Sinus Eksponen)</i>	$f(t) = M e^{-st} \sin(\omega t + \theta)$	$x_f(t) = e^{-st} (K_2 \sin \omega t + K_3 \cos \omega t)$	

Table of Laplace Transform Pairs  
(Jadual Penukaran Pasangan Penjelmaan Laplace)

Functions (Fungsi)	$f(t)$	$F(s)$
Unit Impulse (Dedenyut)	$\delta(t)$	1
Unit Step (Unit langkah)	$u(t)$	$\frac{1}{s}$
Constant (Malar)	1	
Unit Ramp (Unit Tanjak)	$t u(t)$	$\frac{1}{s^2}$
$t$ function (Rangkap $t$ )		
Unit Parabolic (Unit Parabola)	$\frac{1}{2}t^2 u(t)$	$\frac{1}{s^3}$
$n^{th}$ integral of impulse (Kamiran ke- $n$ dedenyut)	$\delta^{-n}(t)$	$\frac{1}{s^n}$
$n^{th}$ derivative of impulse (Kerbezaan ke- $n$ dedenyut)	$\delta^n(t)$	$s^n$
Power of $t$ (Kuasa $t$ )	$\frac{t^{n-1}}{(n-1)!}$	$\frac{1}{s^n}$
Exponential (Eksponen)	$e^{-at}$	$\frac{1}{s+a}$
$t$ -multiplication exponential (Pendaraban $t$ bagi eksponen)	$te^{-at}$	$\frac{1}{(s+a)^2}$
Repeated $t$ -multiplication exponential (Pendaraban $t$ berulang bagi eksponen)	$\frac{1}{(n-1)!} t^{n-1} e^{-at}$	$\frac{1}{(s+a)^n}$
Sine (Sinus)	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
Cosine (Kosinus)	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
Damped sine (Sinus teredam)	$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
Damped cosine (Kosinus teredam)	$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$
$t$ -multiplicated sine (Pendaraban $t$ bagi sinus)	$t \sin \omega t$	$\frac{2\omega s}{(s^2 + \omega^2)^2}$
$t$ -multiplicated cosine (Pendaraban $t$ bagi kosinus)	$t \cos \omega t$	$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$

Two-Port Network Parameters  
(Parameter Rangkaian Dua Liang)

## Impedance parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

## Admittance parameters

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

## Hybrid parameters

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

## Transmission parameters

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

Jadual Penukaran Untuk Rangkaian Dua Liang  
(Conversion Table for Two-Port Network Parameters)

	z		y		h		ABCD	
z	$Z_{11}$	$Z_{12}$	$\frac{y_{22}}{\Delta_y}$	$\frac{-y_{12}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$	$\frac{A}{C}$	$\frac{\Delta_T}{C}$
	$Z_{21}$	$Z_{22}$	$\frac{-y_{21}}{\Delta_y}$	$\frac{y_{11}}{\Delta_y}$	$\frac{-h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$	$\frac{1}{C}$	$\frac{D}{C}$
y	$\frac{Z_{22}}{\Delta_z}$	$\frac{-Z_{12}}{\Delta_z}$	$y_{11}$	$y_{12}$	$\frac{1}{h_{11}}$	$\frac{-h_{12}}{h_{11}}$	$\frac{D}{B}$	$\frac{-\Delta_T}{B}$
	$\frac{-Z_{21}}{\Delta_z}$	$\frac{Z_{11}}{\Delta_z}$	$y_{21}$	$y_{22}$	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$	$\frac{-1}{B}$	$\frac{A}{B}$
h	$\frac{\Delta_z}{Z_{22}}$	$\frac{Z_{12}}{Z_{22}}$	$\frac{1}{y_{11}}$	$\frac{-y_{12}}{y_{11}}$	$h_{11}$	$h_{12}$	$\frac{B}{D}$	$\frac{\Delta_T}{D}$
	$\frac{-Z_{21}}{Z_{22}}$	$\frac{1}{Z_{22}}$	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta_y}{y_{11}}$	$h_{21}$	$h_{22}$	$\frac{-1}{D}$	$\frac{C}{D}$
ABCD	$\frac{Z_{11}}{Z_{21}}$	$\frac{\Delta_z}{Z_{21}}$	$\frac{-y_{22}}{y_{21}}$	$\frac{-1}{y_{21}}$	$\frac{-\Delta_h}{h_{21}}$	$\frac{h_{11}}{h_{21}}$	A	B
	$\frac{1}{Z_{21}}$	$\frac{Z_{22}}{Z_{21}}$	$\frac{-\Delta_y}{y_{21}}$	$\frac{-y_{11}}{y_{21}}$	$\frac{-h_{22}}{h_{21}}$	$\frac{-1}{h_{21}}$	C	D