



---

**KOLEJ YAYASAN PELAJARAN JOHOR  
ONLINE FINAL EXAMINATION**

---

**COURSE NAME** : CIRCUIT THEORY  
**COURSE CODE** : DKE 1053  
**EXAMINATION** : JUNE 2022  
**DURATION** : 2 HOURS 30 MINUTES

---

**INSTRUCTION TO CANDIDATES/  
ARAHAH KEPADA CALON**

1. This examination paper consists of **SIX (6)** questions. /  
*Kertas soalan ini mengandungi ENAM (6) soalan.*
2. Students are allowed to refer to resources such as lecture notes, books, internet or any other relevant resources. /  
*Pelajar dibenarkan merujuk kepada sumber seperti nota kuliah, buku, internet atau mana-mana sumber yang berkaitan.*
3. Answer ALL questions in the answer sheet which is A4 size paper (or other paper with the consent of the relevant lecturer). /  
*Jawab SEMUA soalan di dalam kertas jawapan iaitu kertas bersaiz A4 (atau lain-lain kertas dengan persetujuan pensyarah berkaitan).*
4. Write your details as follows in the upper left corner for each answer sheet: /  
*Tulis butiran anda seperti mana berikut di penjuru atas kiri bagi setiap kertas jawapan:*
  - i. Student Full Name. / Nama Penuh Pelajar.
  - ii. Identification Card (I/C) No. / No. Kad Pengenalan.
  - iii. Class Section. / Seksyen Kelas.
  - iv. Course Code. / Kod Kursus.
  - v. Course Name. / Nama Kursus.
  - vi. Lecturer Name. / Nama Pensyarah.
5. Each answer sheet must have a page number written at the bottom right corner. /  
*Setiap helai kertas jawapan mesti ditulis nombor muka surat di penjuru bawah kanan.*
6. Answer should be handwritten, neat and clear. /  
*Jawapan hendaklah ditulis tangan, kemas dan jelas.*

---

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /  
JANGAN BUKA KERTAS SOALANINI SEHINGGA DIBERITAHU**

---

This examination paper consists of 7 printed pages including front page  
*Kertas soalan ini mengandungi 7 halaman bercetak termasuk muka hadapan*

This examination paper consists of **SIX (6)** questions. Answer **ALL** the questions in an answer booklet.

*Kertas soalan ini mengandungi **ENAM (6)** soalan. Jawab **SEMUA** soalan dalam buku jawapan.*

### QUESTION 1/ SOALAN 1

Given the daily use of energy as follows:

Two (2) 1200 W air conditioners for 10 hours 35 minutes.

Two (2) 250 W LCD television for 8 hours 45 minutes.

One (1) 480 W iron for 20 minutes.

One (1) 680 W washing machines for 2 hours 30 minutes.

Calculate the total cost of electricity for 30 days at RM 0.25 per kilowatthour.

**(12 marks/ markah)**

Diberi penggunaan tenaga harian seperti berikut:

Dua (2) 1200 W penghawa dingin untuk 10 jam 35 minit.

Dua (2) 250 W televisyen LCD untuk 8 jam 45 minit.

Satu (1) 480 W seterika untuk 20 minit.

Satu (1) 680 W mesin basuh untuk 2 jam 30 minit.

Kirakan jumlah kos elektrik untuk 30 hari pada kadar RM 0.25 per kilowattjam.

**QUESTION 2/ SOALAN 2**


Based on **Figure 2**, determine the following values:

- the resistance viewed from the voltage supply.
- supply current,  $I_s$ .
- voltage,  $V_B$  using voltage divider rule.
- voltage,  $V_{AB}$  using Kirchhoff's voltage law.
- current,  $I_3$  using current divider rule.
- current,  $I_1$  using Kirchhoff's current law.

(20 marks / markah)

Berdasarkan kepada **Rajah 2**, tentukan nilai berikut:

- rintangan jumlah dilihat dari bekalan voltan.
- arus bekalan,  $I_s$ .
- voltan,  $V_B$  menggunakan aturan pembahagi voltan.
- voltan,  $V_{AB}$  menggunakan hukum voltan Kirchhoff.
- arus,  $I_3$  menggunakan aturan pembahagi arus.
- arus,  $I_1$  menggunakan hukum arus Kirchhoff.

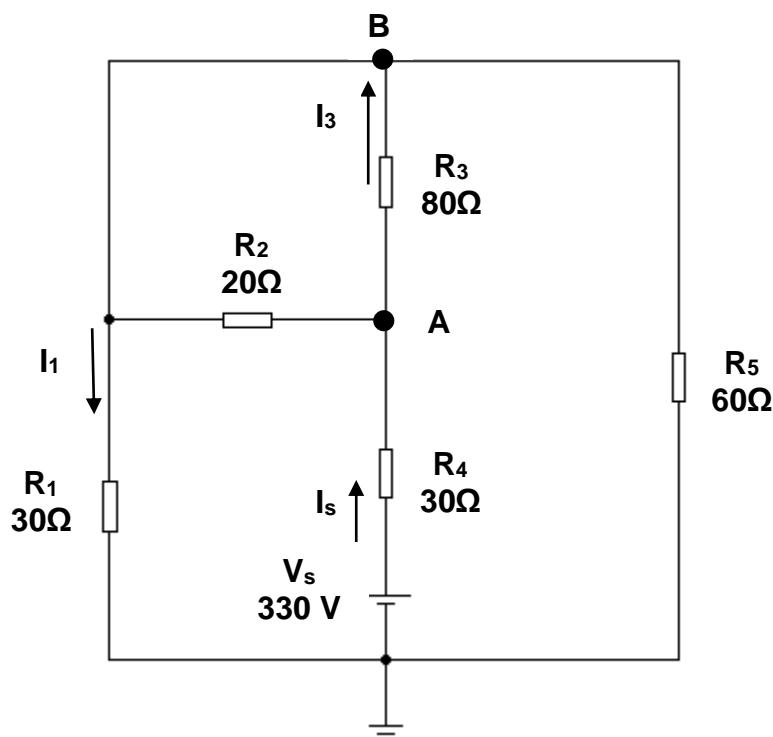

**Figure 2 / Rajah 2**

**QUESTION 3/ SOALAN 3**


Based on **Figure 3**, looking from terminal A-B,

- Calculate the Norton's equivalent resistance,  $R_N$ .
- Determine the Norton's equivalent current,  $I_N$  using superposition theorem.
- Draw the Norton's equivalent circuit.
- Calculate the voltage,  $V_o$  across the load resistor,  $R_L$ .

(18 marks / markah)

Berdasarkan kepada **Rajah 3**, dilihat dari terminal A-B,

- Kirakan rintangan setara Norton,  $R_N$ .
- Tentukan arus setara Norton,  $I_N$  dengan menggunakan teorem tindihan.
- Lukiskan litar setara Norton.
- Kirakan voltan,  $V_o$  melintangi resistor beban  $R_L$ .

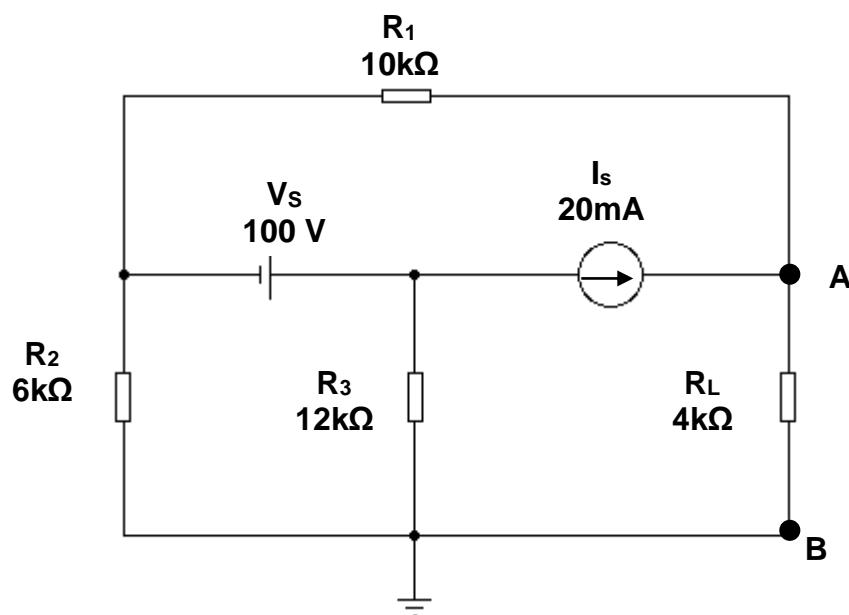

**Figure 3 / Rajah 3**

**QUESTION 4/ SOALAN 4**

Given the following sinusoidal wave equations:

$$v_1(t) = 60 \sin (523t + 70^\circ) \text{ V}$$

$$v_2(t) = 120 \sin (523t - 30^\circ) \text{ V}$$

- a) For  $v_1(t)$ , determine:
  - i) peak value.
  - ii) angular velocity.
  - iii) frequency.
  - iv) period.
  - v) phase angle in radian and millisecond.
  - vi) instantaneous value at  $t = 2.0 \text{ ms}$ .
- b) Sketch the sinusoidal waveform of  $V_1(t)$  and  $V_2(t)$  for one cycle on the same axis.
- c) Sketch the phasor diagram for both waveforms on the same axis.
- d) Determine the phase relationship between  $V_1(t)$  and  $V_2(t)$ .

**(20 marks/ markah)**

Diberi persamaan gelombang sinus berikut:

$$v_1(t) = 60 \sin (523t + 70^\circ) \text{ V}$$

$$v_2(t) = 120 \sin (523t - 30^\circ) \text{ V}$$


- a) Untuk  $v_1(t)$ , tentukan:
  - i) nilai puncak.
  - ii) halaju sudut.
  - iii) frekuensi.
  - iv) tempoh.
  - v) sudut fasa dalam radian dan milisaat.
  - vi) Nilai ketika pada  $t = 2.0 \text{ ms}$ .
- b) Lakarkan gelombang sinus bagi  $V_1(t)$  dan  $V_2(t)$  untuk satu kitar di atas paksi yang sama.
- c) Lakarkan gambar rajah pemfasa bagi kedua-dua gelombang di atas paksi yang sama.
- d) Tentukan hubungan fasa di antara  $V_1(t)$  dan  $V_2(t)$ .

**QUESTION 5/ SOALAN 5**

Determine the voltage  $I_o$  in the circuit of **Figure 5** using nodal analysis.

(18 marks/ markah)

Tentukan voltan  $I_o$  dalam litar **Rajah 5** menggunakan analisis nod.

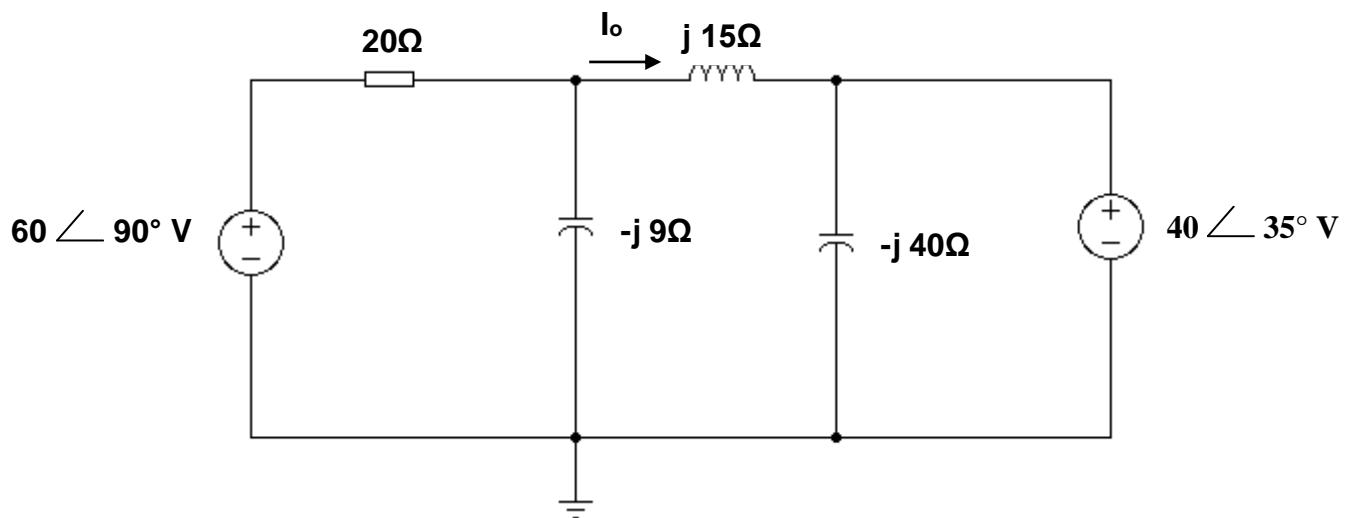

**Figure 5/ Rajah 5**

**QUESTION 6/ SOALAN 6**

For a load,  $v(t) = 120 \cos 377t$  V and  $i(t) = 6 \cos (377t - 60^\circ)$  A. Calculate:

- a) the complex power, S.
- b) the apparent power, |S|.
- c) the real power, P and reactive power, Q.
- d) the power factor, pf.
- e) the load impedance, Z.

**(12 marks/ markah)**

Untuk beban,  $v(t) = 120 \cos 377t$  V and  $i(t) = 6 \cos (377t - 60^\circ)$  A. Kirakan:

- a) kuasa komplek, S.
- b) kuasa ketara, |S|.
- c) kuasa nyata, P dan kuasa reaktif, Q.
- d) faktor kuasa, pf.
- e) galangan beban, Z.

**[100 MARKS/ MARKAH]**

**END OF QUESTION PAPER/ KERTAS SOALAN TAMAT**