



**KOLEJ YAYASAN PELAJARAN JOHOR
ONLINE FINAL EXAMINATION**

COURSE NAME : ELECTRONICS 2
COURSE CODE : DKE 2073
EXAMINATION : NOVEMBER 2020
DURATION : 6 HOURS

**INSTRUCTION TO CANDIDATES/
ARAHAH KEPADA CALON**

1. This examination paper consists of **FOUR (4)** questions. /
*Kertas soalan ini mengandungi **EMPAT (4)** soalan.*
2. Students are allowed to refer to resources such as lecture notes, books, internet or any other relevant resources. /
Pelajar dibenarkan merujuk kepada sumber seperti nota kuliah, buku, internet atau mana-mana sumber yang berkaitan.
3. Answer ALL questions in the answer sheet which is A4 size paper (or other paper with the consent of the relevant lecturer). /
Jawab SEMUA soalan di dalam kertas jawapan iaitu kertas bersaiz A4 (atau lain-lain kertas dengan persetujuan pensyarah berkaitan).
4. Write your details as follows in the upper left corner for each answer sheet: /
Tulis butiran anda seperti mana berikut di penjuru atas kiri bagi setiap kertas jawapan:
 - i. Student Full Name. / Nama Penuh Pelajar.
 - ii. Identification Card (I/C) No. / No. Kad Pengenalan.
 - iii. Class Section. / Seksyen Kelas.
 - iv. Course Code. / Kod Kursus.
 - v. Course Name. / Nama Kursus.
 - vi. Lecturer Name. / Nama Pensyarah.
5. Each answer sheet must have a page number written at the bottom right corner. /
Setiap helai kertas jawapan mesti ditulis nombor muka surat di penjuru bawah kanan.
- 6.. Answer should be handwritten, neat and clear. /
Jawapan hendaklah ditulis tangan, kemas dan jelas.

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALANINI SEHINGGA DIBERITAHU**

This examination paper consists of 7 printed pages including front page
Kertas soalan ini mengandungi 7 halaman bercetak termasuk muka hadapan

This examination paper consists of **FOUR (4)** questions. Answer **ALL** the questions in the answer sheet.

*Kertas soalan ini mengandungi **EMPAT (4)** soalan. Jawab **SEMUA** soalan dalam kertas jawapan.*

QUESTION 1/ SOALAN 1

- a) Referring to **Figure 1(a)**, point out I_{DQ} and V_{GSQ} using transfer curve technique. The graph is given in the **Attachment 1**.

*Merujuk kepada **Rajah 1(a)**, tunjukkan I_{DQ} dan V_{GSQ} menggunakan teknik lengkuk pindah. Graf diberi di **Lampiran 1**.*

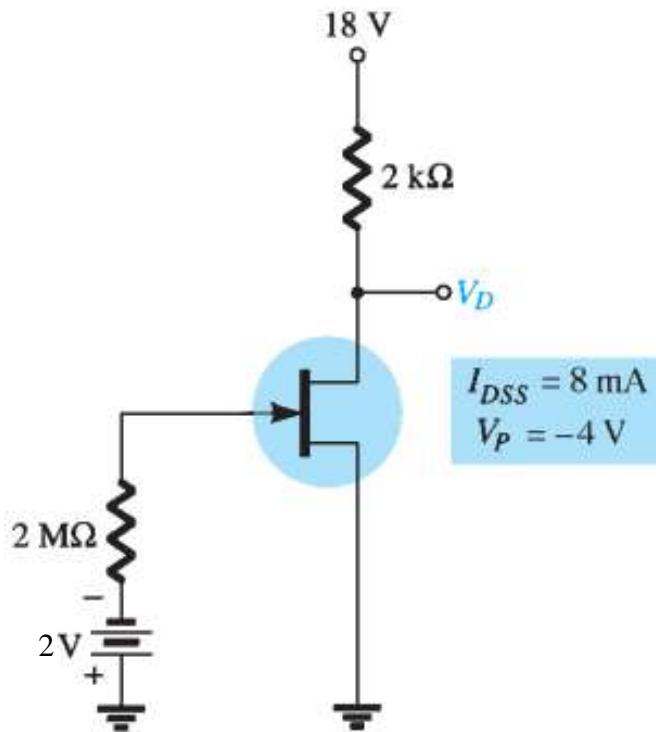


Figure 1(a) / Rajah 1(a)

(15 marks/ markah)

- b) Referring to **Figure 1(a)**, identify the values of V_{DS} , V_S , V_G and V_D .

*Merujuk pada **Rajah 1(a)**, kenal pasti nilai V_{DS} , V_S , V_G dan V_D .*

(10 marks/ markah)

QUESTION 2/ SOALAN 2

- a) Calculate g_{mo} for a JFET having device parameters $I_{DSS} = 12\text{mA}$ and $V_p = -4\text{V}$.

Kirakan g_{mo} untuk JFET yang mempunyai parameter $I_{DSS} = 12\text{mA}$ dan $V_p = -4\text{V}$.

(5 marks/ markah)

- b) Referring to **Figure 2(b)**, determine Z_i , Z_o , and Av . Given $I_{DSS} = 10\text{mA}$, $V_p = -6\text{V}$, and $r_d = 40\text{k}\Omega$.

*Merujuk kepada **Rajah 2(b)**, tentukan Z_i , Z_o , dan Av . Given $I_{DSS} = 10\text{mA}$, $V_p = -6\text{V}$, dan $r_d = 40\text{k}\Omega$.*

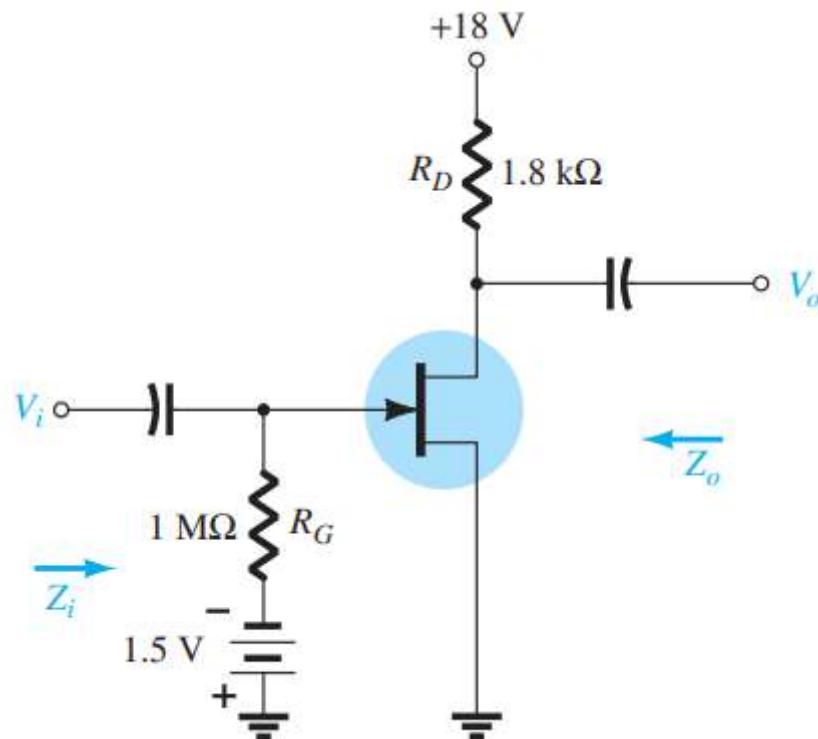


Figure 2(b) / Rajah 2(b)

(20 marks/ markah)

QUESTION 3/ SOALAN 3

- a) Calculate the CMRR (in dB) for the circuit measurements of $V_d = 1\text{mV}$, $V_o = 120 \text{ mV}$, $V_C = 1\text{mV}$, and $V_o = 20\mu\text{V}$.

Kirakan CMRR (dalam dB) bagi ukuran litar $V_d = 1\text{mV}$, $V_o = 120 \text{ mV}$, $V_C = 1\text{mV}$, dan $V_o = 20\mu\text{V}$.

(8 marks/ markah)

- b) Calculate the output voltage for **Figure 3(b)** below. Given $V_1 = 50 \sin(1000t) \text{ mV}$ and $V_2 = 10 \sin(3000t) \text{ mV}$.

*Kirakan voltan keluaran bagi **Rajah 3(b)** di bawah. Diberi $V_1 = 50 \sin(1000t) \text{ mV}$ dan $V_2 = 10 \sin(3000t) \text{ mV}$.*

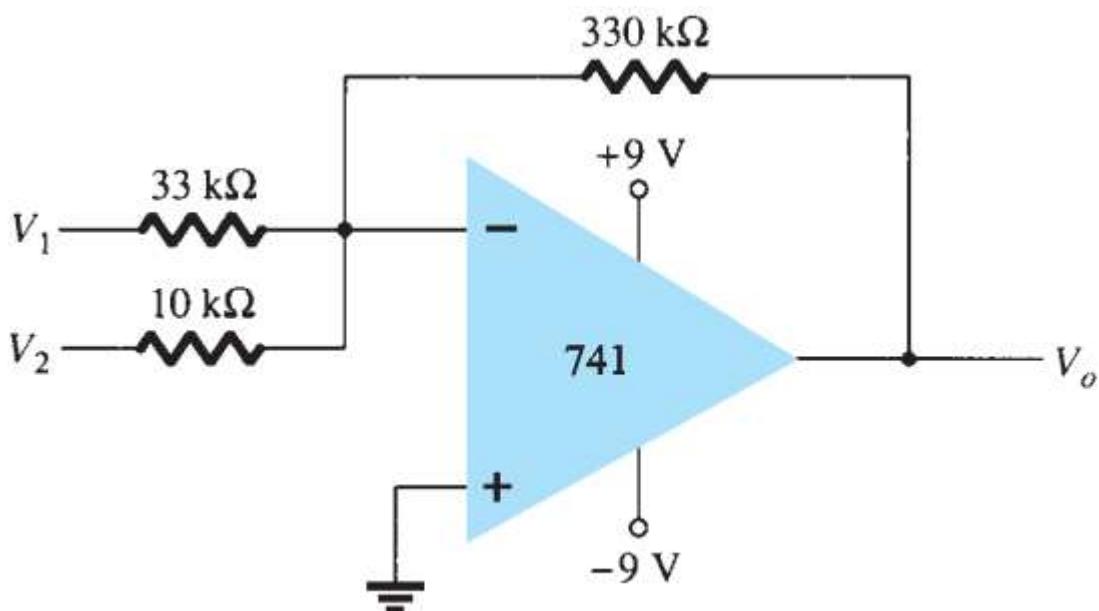


Figure 3(b) / Rajah 3(b)

(5 marks/ markah)

- c) Referring to the op-amp circuit in **Figure 3(c)**, calculate the output voltage, V_o . Given $V_1 = 12 \text{ mV}$ and $V_2 = 18\text{mV}..$

*Merujuk kepada litar penguat kendalian dalam **Rajah 3(c)**, kirakan voltan keluaran, V_o . Diberi $V_1 = 12 \text{ mV}$ dan $V_2 = 18\text{mV}..$*

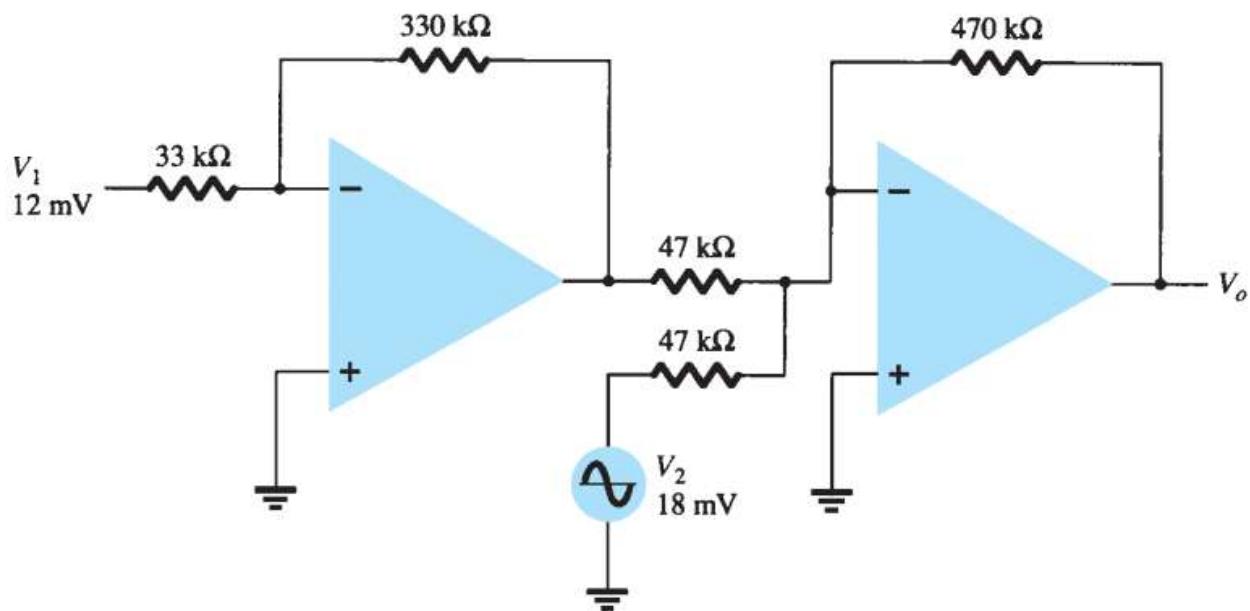


Figure 3(c) / Rajah 3(c)

(12 marks/ markah)

QUESTION 4/ SOALAN 4

Based on Class B Power Amplifier in **Figure 4**, calculate :

- The peak input voltage, $V_{i(p)}$
- The peak voltage across the load, $V_{L(p)}$
- The peak load current, $I_{L(p)}$
- The direct current, I_{DC}
- The input power, $P_{in(dc)}$
- The output power, $P_{o(ac)}$
- The power dissipated by each output transistor, P_Q
- The circuit efficiency, $\% \eta$
- The maximum input power, $P_{in(max)}$
- The maximum output power, $P_{o(max)}$

Berdasarkan litar Penguat Kuasa Kelas B dalam **Rajah 4**. Kirakan:

- Voltan puncak pada masukan, $V_{i(p)}$
- Voltan puncak pada beban, $V_{L(p)}$
- Arus puncak pada beban, $I_{L(p)}$
- Arus terus, I_{DC}
- Kuasa masukan, $P_{in(dc)}$

- f) Kuasa keluaran, $P_{o(ac)}$
- g) Kuasa yang dilesapkan oleh transistor pada keluaran, P_Q
- h) Kecekapan litar, $\% \eta$
- i) Kuasa masukan maksimum $P_{in(max)}$
- j) Kuasa keluaran maksimum $P_{o(max)}$

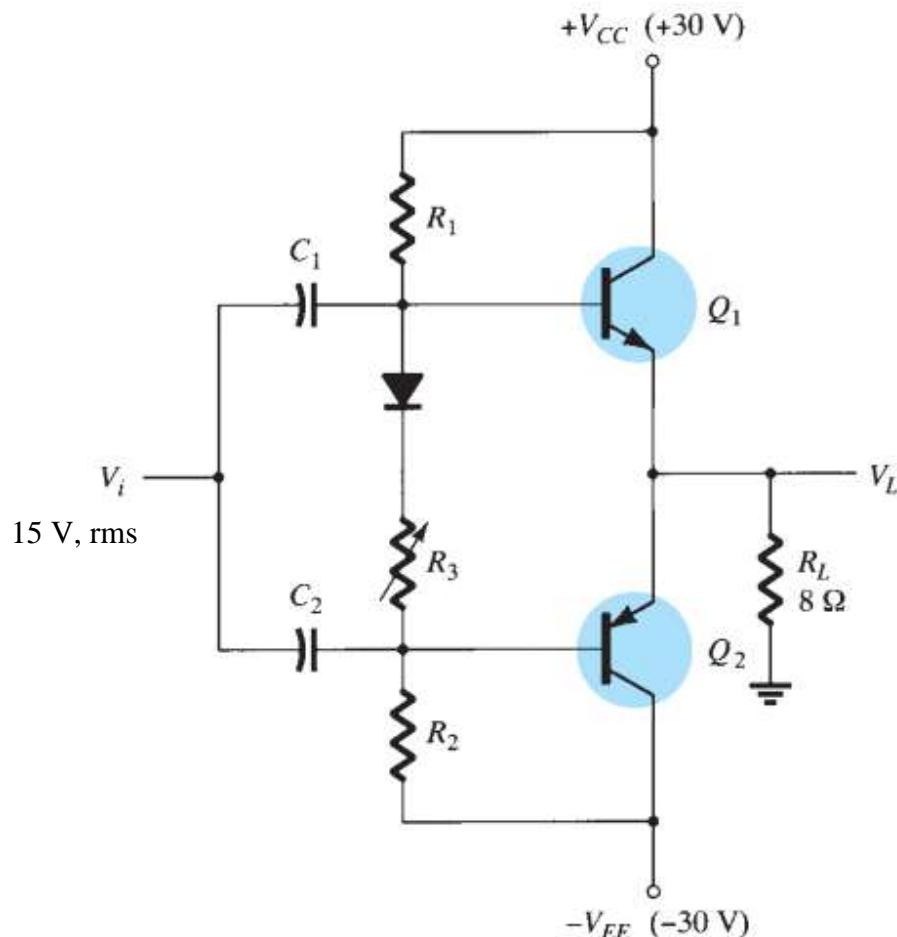
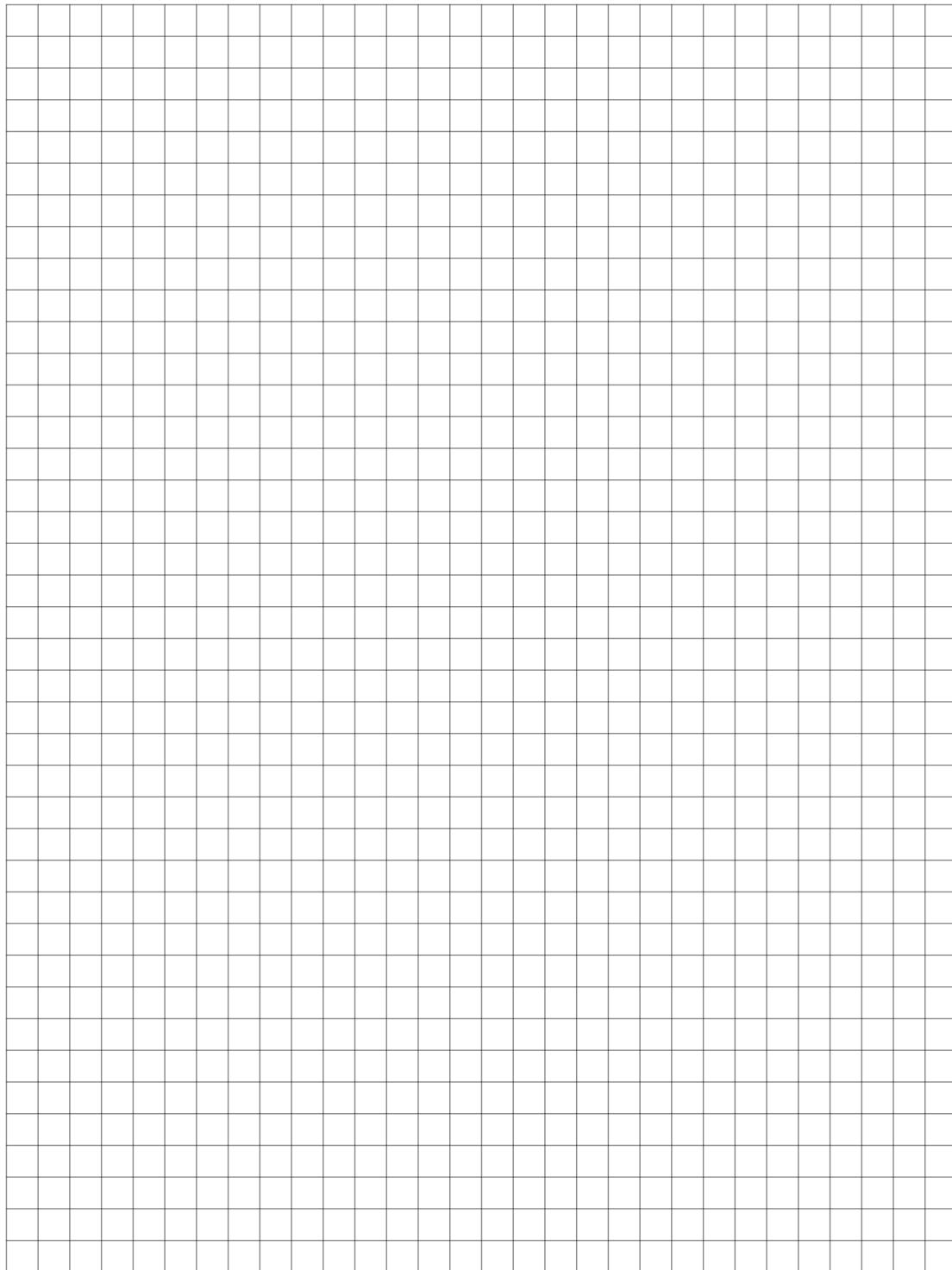


Figure 4 / Rajah 4

(25 marks/ markah)

[100 MARKS/ MARKAH]

END OF QUESTION PAPER/ KERTAS SOALAN TAMAT

Attachment 1 / Lampiran 1**Name / Nama** :**Lecturer / Pensyarah** :

Free Simple Grid Graph Paper from <http://incompetech.com/graphpaper/lite/>