



---

**KOLEJ YAYASAN PELAJARAN JOHOR  
ONLINE FINAL EXAMINATION**

---

**COURSE NAME : ELECTRONICS 2**  
**COURSE CODE : DKE 2073**  
**EXAMINATION : DECEMBER 2021**  
**DURATION : 2 HOURS 30 MINUTES**

---

**INSTRUCTION TO CANDIDATES/  
ARAHAH KEPADA CALON**

1. This examination paper consists of **FOUR (4)** questions. /  
*Kertas soalan ini mengandungi **EMPAT (4)** soalan.*
2. Answer ALL questions in the answer sheet which is A4 size paper (or other paper with the consent of the relevant lecturer). /  
*Jawab SEMUA soalan di dalam kertas jawapan iaitu kertas bersaiz A4 (atau lain-lain kertas dengan persetujuan pensyarah berkaitan).*
3. Write your details as follows in the upper left corner for each answer sheet: /  
*Tulis butiran anda seperti mana berikut di penjuru atas kiri bagi setiap kertas jawapan:*
  - i. Student Full Name / Nama Penuh Pelajar
  - ii. Identification Card (I/C) No. / No. Kad Pengenalan
  - iii. Class Section / Seksyen Kelas
  - iv. Course Code / Kod Kursus
  - v. Course Name / Nama Kursus
  - vi. Lecturer Name / Nama Pensyarah
4. Each answer sheet must have a page number written at the bottom right corner. /  
*Setiap helai kertas jawapan mesti ditulis nombor muka surat di penjuru bawah kanan.*
5. Answer should be **neat and clear in handwritten form.** /  
*Jawapan hendaklah ditulis tangan, kemas dan jelas.*

---

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /  
JANGAN BUKA KERTAS SOALANINI SEHINGGA DIBERITAHU**

---

This examination paper consists of 7 printed pages including front page  
*Kertas soalan ini mengandungi 7 halaman bercetak termasuk muka hadapan*

This examination paper consists of **FOUR (4)** questions. Answer **ALL** the questions in the answer sheet.

*Kertas soalan ini mengandungi **EMPAT (4)** soalan. Jawab **SEMUA** soalan dalam kertas jawapan.*

### QUESTION 1/ SOALAN 1

- a) Referring to **Figure 1(a)**, point out  $I_{DQ}$  and  $V_{GSQ}$  using transfer curve technique. The graph is given in the **Attachment 1**.

(15 marks/ markah)

- b) Referring to **Figure 1(a)**, identify the values of  $V_{DS}$ ,  $V_S$ ,  $V_G$  and  $V_D$ .

(10 marks/ markah)

- a) Merujuk kepada **Rajah 1(a)**, tunjukkan  $I_{DQ}$  dan  $V_{GSQ}$  menggunakan teknik lengkuk pindah. Graf diberi di **Lampiran 1**.

- b) Merujuk pada **Rajah 1(a)**, kenal pasti nilai  $V_{DS}$ ,  $V_S$ ,  $V_G$  dan  $V_D$ .

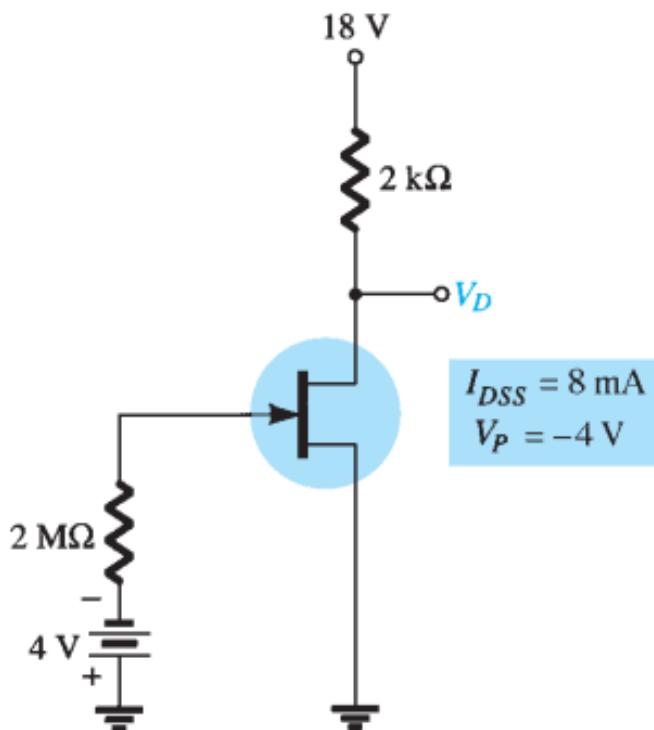


Figure 1 (a) / Rajah 1 (a)

## QUESTION 2/ SOALAN 2

- a) Calculate  $g_{mo}$  for a JFET having device parameters  $I_{DSS} = 12\text{mA}$  and  $V_p = -4\text{V}$ .

(5 marks/ markah)

- b) Referring to **Figure 2(b)**, determine  $Z_i$ ,  $Z_o$ , and  $Av$ . Given  $I_{DSS} = 10\text{mA}$ ,  $V_p = -6\text{V}$ , and  $r_d = 40\text{k}\Omega$ .

(20 marks/ markah)

a) Kirakan  $g_{mo}$  untuk JFET yang mempunyai parameter  $I_{DSS} = 12\text{mA}$  dan  $V_p = -4\text{V}$ .

b) Merujuk kepada **Rajah 2(b)**, tentukan  $Z_i$ ,  $Z_o$ , dan  $Av$ . Given  $I_{DSS} = 10\text{mA}$ ,  $V_p = -6\text{V}$ , dan  $r_d = 40\text{k}\Omega$ .

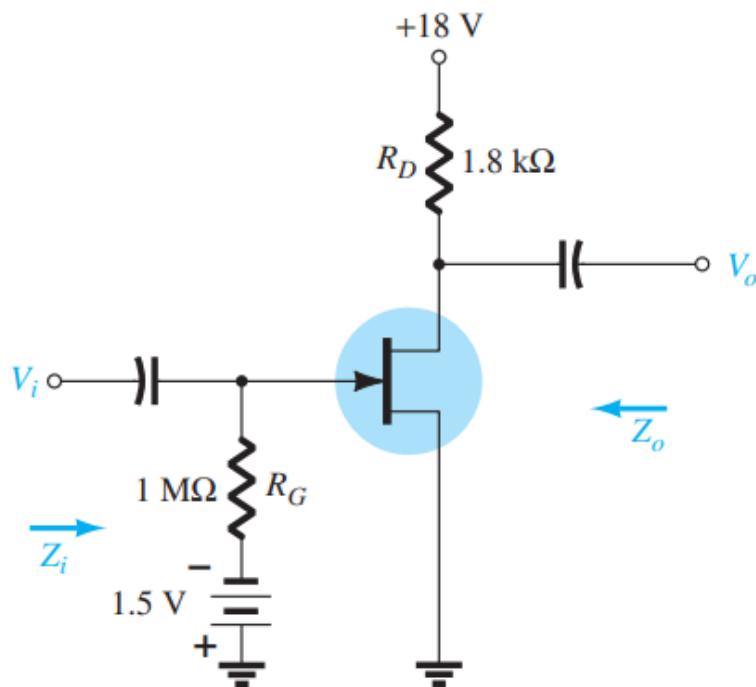


Figure 2 (b) / Rajah 2(b)

## QUESTION 3/ SOALAN 3

- a) Calculate the CMRR (in dB) for the circuit measurements of  $V_d = 1\text{mV}$ ,  $V_o = 120 \text{ mV}$ ,  $V_C = 1\text{mV}$ , and  $V_o = 20\mu\text{V}$ .

(8 marks/ markah)

- b) Calculate the output voltage for **Figure 3(b)** below. Given  $V_1 = 50 \sin(1000t)$  mV and  $V_2 = 10 \sin(3000t)$  mV.

(5 marks/ markah)


- c) Referring to the op-amp circuit in **Figure 3(c)**, calculate the output voltage,  $V_o$ . Given  $V_1 = 12$  mV and  $V_2 = 18$  mV..

(12 marks/ markah)


a) Kirakan CMRR (dalam dB) bagi ukuran litar  $V_d = 1$  mV,  $V_o = 120$  mV,  $V_C = 1$  mV, dan  $V_o = 20\mu$ V.

b) Kirakan voltan keluaran bagi **Rajah 3(b)** di bawah. Diberi  $V_1 = 50 \sin(1000t)$  mV dan  $V_2 = 10 \sin(3000t)$  mV.

c) Merujuk kepada litar penguat kendalian dalam **Rajah 3(c)**, kirakan voltan keluaran,  $V_o$ . Diberi  $V_1 = 12$  mV dan  $V_2 = 18$  mV.

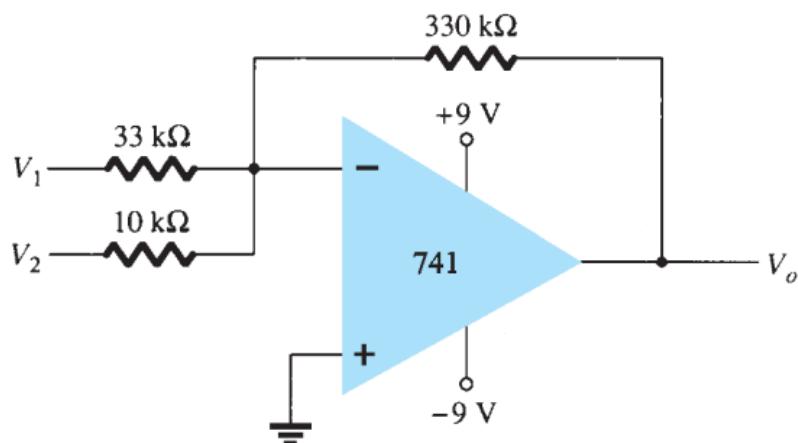

**Figure 3 (b) / Rajah 3(b)**

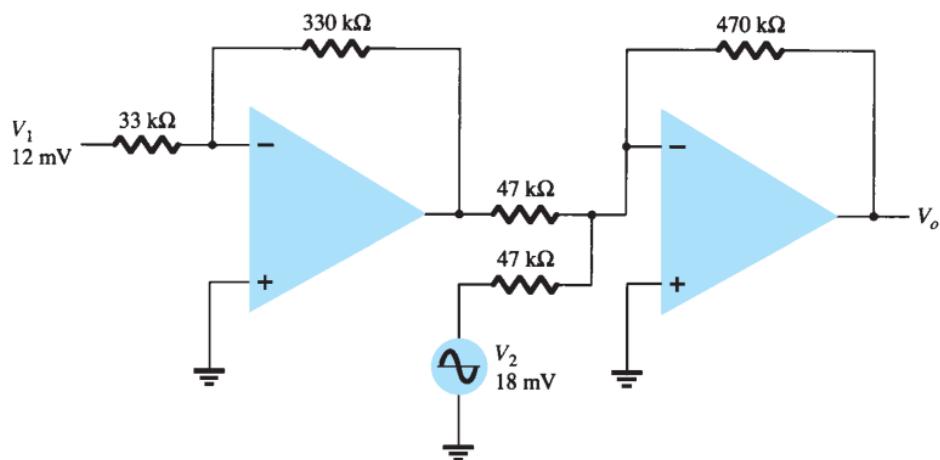

**Figure 3(c) / Rajah 3(c)**

**QUESTION 4/ SOALAN 4**

Based on Class B Power Amplifier in **Figure 4**, calculate:

- a) The peak input voltage,  $V_{i(p)}$
- b) The peak voltage across the load,  $V_L(p)$
- c) The peak load current,  $I_L(p)$
- d) The direct current,  $I_{DC}$
- e) The input power,  $P_{in(dc)}$
- f) The output power,  $P_{o(ac)}$
- g) The power dissipated by each output transistor,  $P_Q$
- h) The circuit efficiency,  $\% \eta$
- i) The maximum input power,  $P_{in(max)}$
- j) The maximum output power,  $P_{o(max)}$

Berdasarkan litar Penguat Kuasa Kelas B dalam **Rajah 4**. Kirakan:

- a) Voltan puncak pada masukan,  $V_{i(p)}$
- b) Voltan puncak pada beban,  $V_{L(p)}$
- c) Arus puncak pada beban,  $I_{L(p)}$
- d) Arus terus,  $I_{DC}$
- e) Kuasa masukan,  $P_{in(dc)}$
- f) Kuasa keluaran,  $P_{o(ac)}$
- g) Kuasa yang dilesapkan oleh transistor pada keluaran,  $P_Q$
- h) Kecekapan litar,  $\% \eta$
- i) Kuasa masukan maksimum  $P_{in(max)}$
- j) Kuasa keluaran maksimum  $P_{o(max)}$

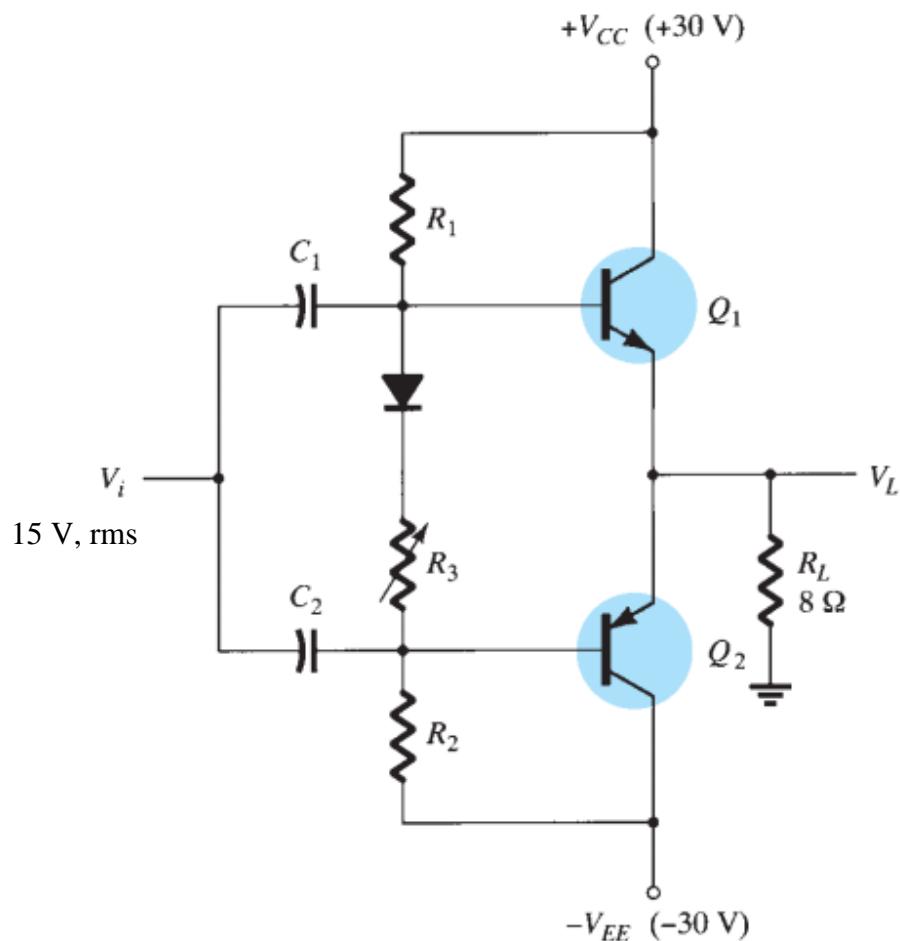
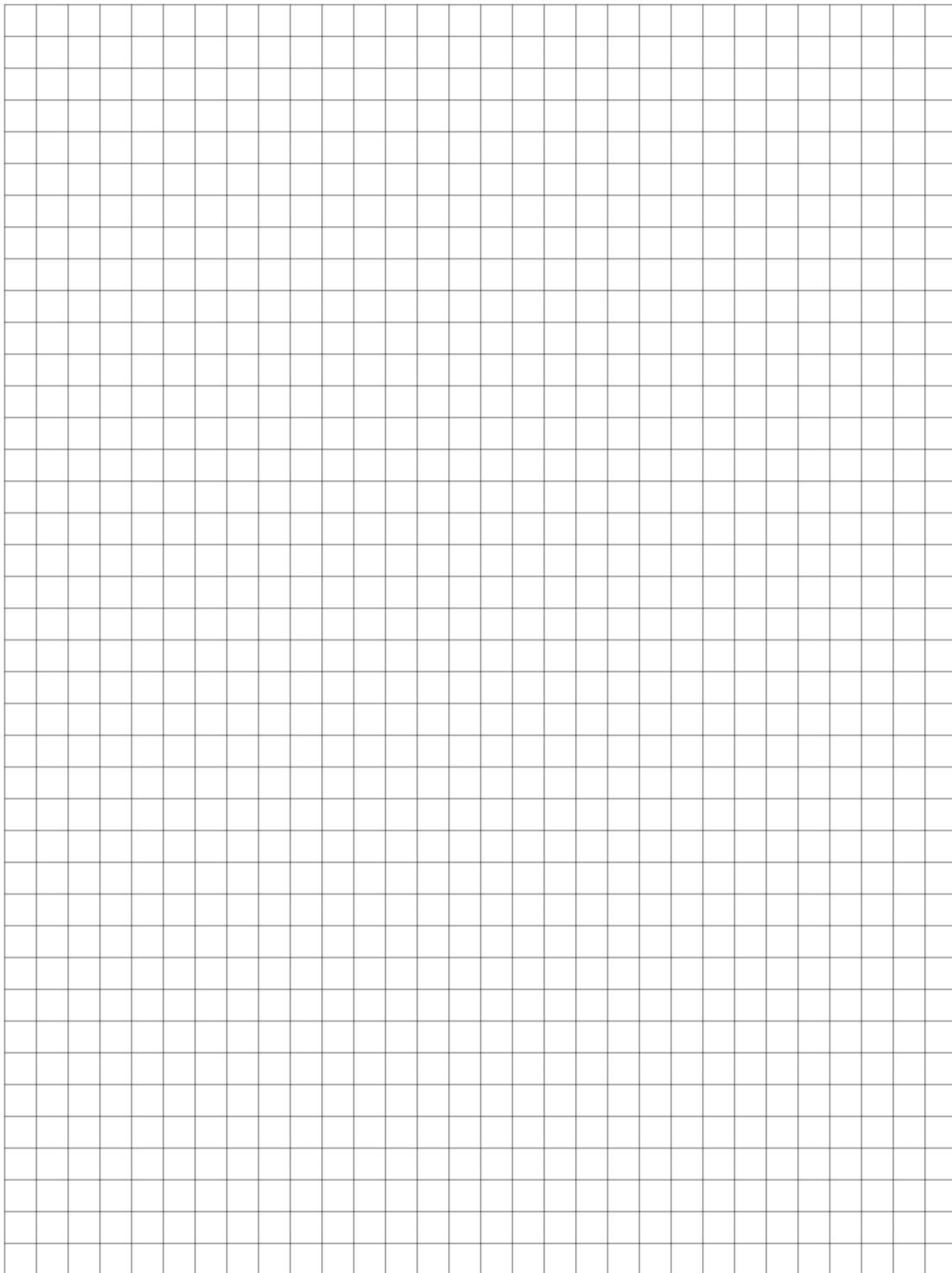


Figure 4 / Rajah 4

(25 marks/ markah)

[100 MARKS/ MARKAH]

END OF QUESTION PAPER/ KERTAS SOALAN TAMAT

**Attachment 1 / Lampiran 1****Name / Nama** : .....**Lecturer / Pensyarah** : .....

Free Simple Grid Graph Paper from <http://incompetech.com/graphpaper/lite/>