



KOLEJ YAYASAN PELAJARAN JOHOR
FINAL EXAMINATION

COURSE NAME : INSTRUMENTATION AND MEASUREMENT
COURSE CODE : DEE 1053
EXAMINATION : JUNE 2023
DURATION : 2 HOURS 30 MINUTES

INSTRUCTION TO CANDIDATES /
ARAHAN KEPADA CALON


1. This examination paper consists of **FIVE (5)** questions. Answer **ALL** questions. /
Kertas soalan ini mengandungi LIMA (5) soalan. Jawab SEMUA soalan.

2. Candidates are not allowed to bring any material/note to the examination hall/room except with the permission from the invigilator. /
Calon tidak dibenarkan untuk membawa sebarang bahan/nota ke dewan/bilik peperiksaan tanpa kebenaran daripada pengawas.

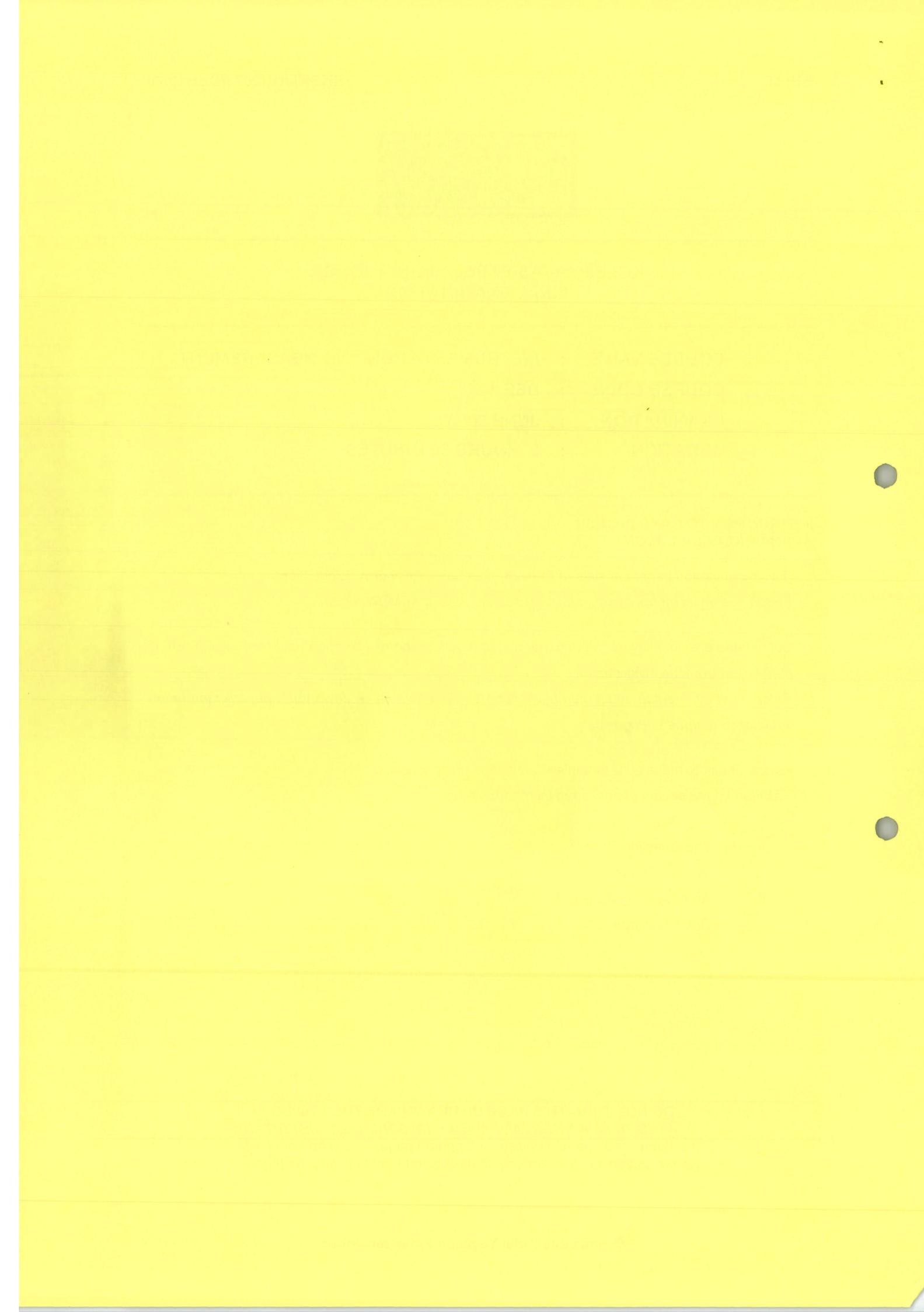3. Please check to make sure that this examination pack consist of: /
Pastikan kertas soalan peperiksaan ini mengandungi:
 - i. The Question Paper /
Kertas Soalan
 - ii. An Answering Booklet /
Buku Jawapan

DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALANINI SEHINGGA DIBERITAHU

This examination paper consists of **8** printed pages including front page
Kertas soalan ini mengandungi 8 muka surat termasuk kulit hadapan



This part contains **FIVE (5)** questions. Answer **ALL** questions in the Answering Booklet.

Kertas soalan ini mengandungi LIMA (5) soalan. Jawab SEMUA soalan di dalam Kertas Jawapan.

QUESTION 1 / SOALAN 1

- a) Explain two (2) suitable times to calibrate the equipment.

(4 marks/ markah)

- b) Systematic error is one of the type that frequently occur in any measurement. Briefly explain two (2) types of errors that are categorized as systematic error.

(4 marks/ markah)

- c) Refer to **Table 1**, calculate:

- i. the average value of the readings.
- ii. the deviation.
- iii. algebraic sum of all deviations.
- iv. the standard deviation.

(12 marks/ markah)

- a) Terangkan dua (2) masa yang sesuai bagi mententukur sesuatu peralatan.

- b) Ralat sistemistik merupakan salah satu jenis ralat yang sering berlaku di dalam sesuatu pengukuran. Terangkan dengan ringkas dua (2) jenis ralat yang dikategorikan sebagai ralat sistemistik.

c) Merujuk pada Jadual 1, kirakan:

- nilai purata bacaan.
- sisihan.
- hasil tambah aljabar kesemua sisihan.
- sisihan piawaian.

Data/ Data	1	2	3	4	5
Readings/ Bacaan	4.5	4.7	5.0	5.2	4.6

Table 1 / Jadual 1

QUESTION 2 / SOALAN 2

a) Briefly explain the operating principle of the d'Arsonval movement with its diagram.

(4 marks/ markah)

b) A 1 mA full scale deflection current meter movement is used in an ohmmeter circuit. The meter movement has an internal resistance, $R_m = 100 \Omega$ and a 3 V battery is used in the circuit. Determine:

- the ohmmeter basic circuit.
- the value of the variable resistance, R_z .
- the value of R_x at 20%, 50% and 70% full-scale reflection.

(8 marks/ markah)

c) Figure 1 shows a half-wave rectifier type AC meter with a range of 50 V. The diodes have a forward resistance of 100Ω while the parameters of the d'Arsonval movement are $50 \mu\text{A}$, 200Ω . It is required that $I_{sh} = I_m$.

- Calculate the shunt resistor, R_{sh} .
- Calculate the multiplier resistor, R_s .
- Calculate the DC sensitivity of the meter, S_{dc} .

(8 marks/ markah)

- a) Terangkan dengan ringkas prinsip pengendalian gerakan d'Arsonval berserta gambar rajahnya.
- b) Gerakan meter arus pesongan skala penuh 1 mA digunakan dalam litar meter ohm. Gerakan meter tersebut mempunyai rintangan dalam, $R_m = 100 \Omega$ dan sebuah bateri 3 V digunakan dalam litar tersebut. Tentukan:
- litar asas meter ohm.
 - nilai rintangan bolehubah, R_z .
 - nilai R_x pada 20% , 50% dan 70% pesongan skala penuh.
- c) Rajah 1 menunjukkan meter AU jenis penerus separuh-gelombang berjulat 50 V . Diod mempunyai rintangan ke depan 100Ω sementara parameter gerakan d'Arsonval ialah $50 \mu\text{A}$, 200Ω . Dikehendaki supaya $I_{sh} = I_m$.
- Kirakan rintangan pirau, R_{sh} .
 - Kirakan rintangan pendarab, R_s .
 - Kirakan kepekaan AT meter, S_{at} .

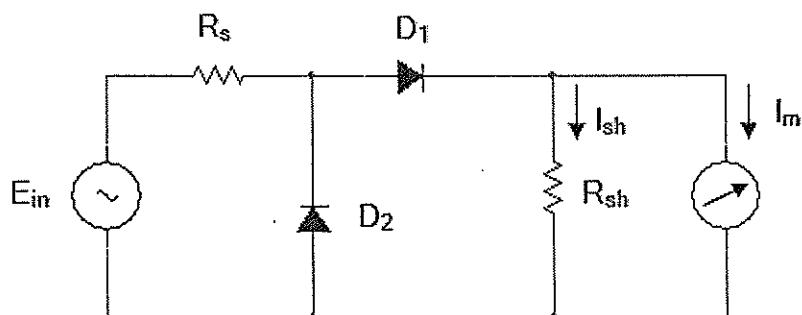


Figure 1 / Rajah 1

QUESTION 3 / SOALAN 3

- a) With the aid of diagrams, explain **three (3)** differences between a digital instrument and a digital display instrument.

(12 marks/ markah)

- b) A digital voltmeter as shown in **Figure 2** utilizes a voltage-to-frequency converter as its analogue-to-digital converter. The relationship between the input voltage V_i and the output frequency f is given as:

$$V_i = \frac{f}{100}$$

If 130 pulses are sent to the AND gate in 0.5 seconds, calculate the amplitude of the input voltage V_i .

(8 marks/ markah)

- a) *Dengan bantuan gambar rajah, terangkan tiga (3) perbezaan di antara alatan digital dan alatan paparan digital.*
- b) *Sebuah meter volt digital seperti dalam Rajah 2 menggunakan penukar voltan-ke-frekuensi sebagai penukar analog-ke-digital. Hubungan antara voltan masukan V_i dan frekuensi keluaran f diberikan sebagai:*

$$V_i = \frac{f}{100}$$

Jika 130 denyutan dihantar ke get DAN dalam masa 0.5 saat, kirakan amplitud voltan masukan V_i .

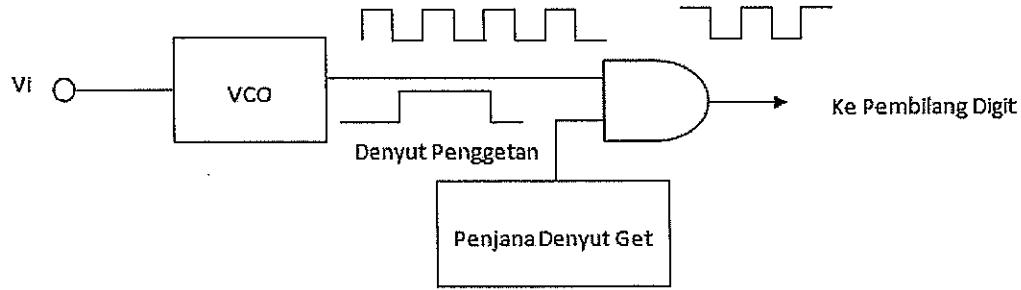


Figure 2 / Rajah 2

QUESTION 4 / SOALAN 4

- a) There are eight (8) main factors to be considered when choosing a suitable transducer. Explain any **three (3)** of these factors.

(6 marks/ markah)

- b) A strain gauge with gauge factor 10 and unstrained resistance 100Ω is attached to a steel beam with Young's modulus $E = 2.0 \times 10^6 \text{ N/m}^2$. The beam changes in length from 100 mm to 100.4 mm.

- i. Explain the relationship between the strain and the resistance of the strain gauge.
- ii. Calculate the strain G experienced by the beam.
- iii. Calculate the resistance of the gauge after the strain has been applied.
- iv. Calculate the magnitude of the stress.
- v. State **two (2)** main problems in the use of strain gauge.

(14 marks/ markah)

- a) Terdapat *lapan (8)* faktor utama yang perlu dipertimbangkan ketika memilih transduser yang sesuai. Terangkan mana-mana **tiga (3)** dari faktor tersebut.

- b) Sebuah tolak terikan dengan faktor tolok 10 dan rintangan tak terterik 100Ω dilekatkan pada alur keluli dengan modulus Young $E = 2.0 \times 10^6 \text{ N/m}^2$. Alur tersebut berubah panjang dari 100 mm ke 100.4 mm.

- i. Terangkan hubungan antara terikan dan rintangan bagi tolak terikan.
- ii. Kirakan terikan G yang dialami oleh alur tersebut.
- iii. Kirakan rintangan tolok setelah terikan dikenakan.
- iv. Kirakan jumlah magnitud bagi tegasan.
- v. Nyatakan **dua (2)** masalah utama di dalam penggunaan tolok terikan.

QUESTION 5 / SOALAN 5

- a) State **three (3)** characteristics of the operational amplifier.
(3 marks/ markah)

b) The Wheatstone Bridge in **Figure 3** is used as quarter-bridge where R_4 is connected to a strain gauge. Given that $R_1 = R_2 = R_3 = R$ where R is the initial resistance of the strain gauge. The strain gauge with gauge factor $K = 2.0$ and initial resistance 350Ω is used. The voltage supply $10 V$. The gauge experiences a strain of $1450 \mu\text{m/m}$.

- i. Prove that the output of the bridge is

$$V_o = \frac{\Delta R}{4R} E$$

- ii. Find the change in resistance of the strain gauge, ΔR .
 iii. Calculate the output voltage.

(14 marks/ markah)

- c) List down **three (3)** advantages of IEEE488 compared to RS232.

(3 marks/ markah)

- a) Nyatakan **tiga (3)** ciri penguat kendalian.

b) Titik Wheatstone dalam **Rajah 3** digunakan sebagai titik suku di mana R_4 disambungkan kepada tolak terikan. Diberi bahawa $R_1 = R_2 = R_3 = R$ dimana R ialah rintangan awal tolak terikan. Tolok terikan dengan faktor $K = 2.0$ dan rintangan awal 350Ω digunakan. Voltan bekalan ialah $10 V$. Tolok tersebut mengalami terikan $1450 \mu\text{m/m}$.

- i. Buktikan bahawa keluaran titi tersebut ialah

$$V_o = \frac{\Delta R}{4R} E$$

- ii. Dapatkan perubahan rintangan tolak terikan, ΔR .
 iii. Kirakan voltan keluaran.

- c) Senaraikan **tiga (3)** kebaikan IEEE488 berbanding dengan RS232.

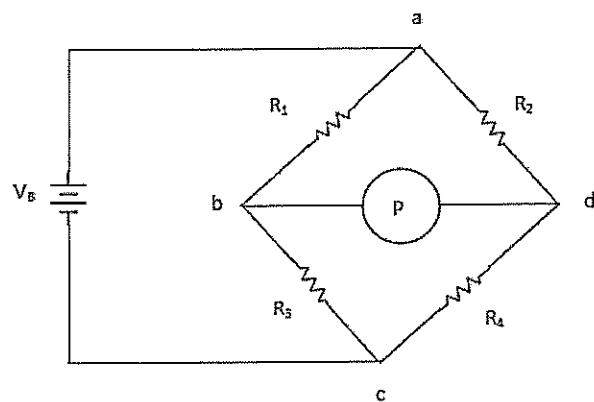


Figure 3 / Rajah 3

[100 MARKS / 100 MARKAH]

END OF QUESTION PAPER / KERTAS SOALAN TAMAT

