



**KOLEJ YAYASAN PELAJARAN JOHOR
FINAL EXAMINATION**

COURSE NAME : CIRCUIT ANALYZE
COURSE CODE : DKE 2093
EXAMINATION : OCTOBER 2019
DURATION : 2 HOURS 30 MINUTES

**INSTRUCTION TO CANDIDATES/
ARAHAN KEPADA CALON**

1. This examination paper consists of **SIX (6)** questions. /
Kertas soalan ini mengandungi ENAM (6) soalan.
2. Answer **ALL** questions in the answer booklet and semilog graph paper provided. Sketch a diagram if necessary to help illustrate your answer. /
Jawab SEMUA soalan di dalam buku jawapan dan kertas semilog graf yang disediakan. Lakarkan gambarajah jika perlu bagi membantu menggambarkan jawapan anda.
3. Candidates are not allowed to bring any material to examination room except with permission from the invigilator. /
Calon tidak dibenarkan membawa masuk sebarang peralatan ke dalam bilik peperiksaan kecuali dengan kebenaran pengawas peperiksaan.
4. Please check to make sure that this examination pack consist of: /
Pastikan kertas soalan peperiksaan ini mengandungi:
 - i. Question Paper /
Kertas Soalan.
 - ii. Kertas Semilog Graf /
Semilog Graph Paper.
 - iii. Answer Booklet /
Buku Jawapan.

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIBERITAHU**

This examination paper consists of 10 printed pages including front page
Kertas soalan ini mengandungi 10 halaman bercetak termasuk muka hadapan



This examination paper consists of **SIX (6)** questions. Answer **ALL** the questions in the answer booklet and semilog graph paper.

*Kertas soalan ini mengandungi **ENAM (6)** soalan. Jawab **SEMUA** soalan dalam buku jawapan dan kertas semilog graf.*

QUESTION 1/ SOALAN 1

Referring to **Figure Q1**. Determine:

- a. the equivalent inductance, L_{eq} . (5 marks)
- b. the total voltage, v_T . (3 marks)
- c. the total energy stored in circuit, ω_T (2 marks)
- d. the voltage across each inductor. (6 marks)

*Merujuk kepada **Rajah Q1**. Tentukan:*

- a. *Kearuhan setara, L_{eq} .* (5 markah)
- b. *Jumlah voltan, v_T .* (3 markah)
- c. *Jumlah tenaga yang disimpan dalam litar, ω_T* (2 markah)
- d. *Voltan melintang setiap pearuh.* (6 markah)

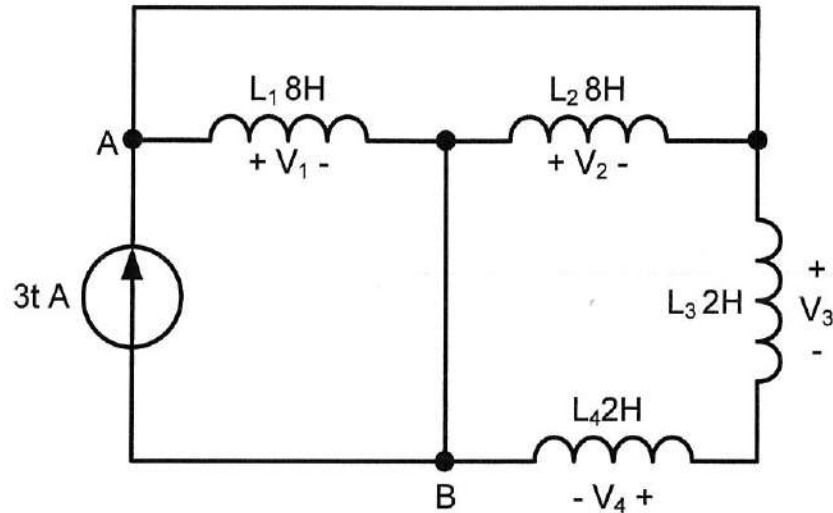


Figure Q1/ Rajah Q1

QUESTION 2/ SOALAN 2

Referring to **Figure Q2**, switch S1 has been opened for a long time until the circuit reaches steady-state. At $t = 0$, switch S1 is close. Find the voltage, $v(t)$ using transient analysis method.

(20 marks)

Merujuk kepada **Rajah Q2**, suis S1 telah dibuka buat sekian lama sehingga litar mencapai keadaan mantap. Pada $t = 0$, suis S1 ditutup. Dapatkan voltan, $v(t)$ menggunakan kaedah analisis ubahtika.

(20 markah)

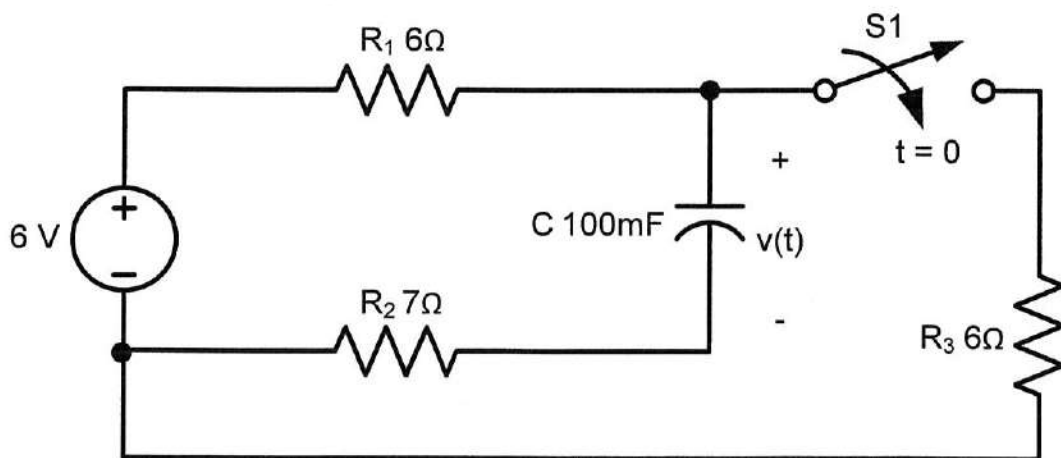


Figure Q2/ Rajah Q2

QUESTION 3/ SOALAN 3

The differential equation of the voltage across capacitor, $v(t)$ in a second order circuit is given as:

$$\frac{d^2v(t)}{dt^2} + 9\frac{dv(t)}{dt} + 20v(t) = 4e^{-2t}V$$

Given that the initial voltage across capacitor, $v(0^-) = 2V$ and $\frac{dv(0^+)}{dt} = -10\frac{V}{s}$.

Find the voltage, $v(t)$ using transient analysis method.

(20 marks)

Persamaan kebezaan bagi voltan melintang kapasitor, $v(t)$ dalam satu litar tertib kedua diberi sebagai:

$$\frac{d^2v(t)}{dt^2} + 9\frac{dv(t)}{dt} + 20v(t) = 4e^{-2t}V$$

Diberi voltan awal melintang kapasitor, $v(0^-) = 2V$ dan $\frac{dv(0^+)}{dt} = -10\frac{V}{s}$. Dapatkan voltan, $v(t)$ menggunakan kaedah analisis ubahtika.

(20 markah)

QUESTION 4/ SOALAN 4

Referring to **Figure Q4**, the switch is at position X and the circuit is in steady state for $t < 0$. At $t = 0$, the switch is moved to position Y. Find:

- a. the initial value of the voltage across the capacitor, $V(0^-)$.

(4 marks)

- b. Laplace functions of the voltage, $V(s)$ for $t > 0$.

(10 marks)

*Merujuk kepada **Rajah Q4**, suis berada pada kedudukan X dan litar berada dalam keadaan mantap untuk $t < 0$. Pada $t = 0$, suis diubah ke kedudukan Y. Dapatkan:*

a. nilai awalan voltan melintang kapasitor, $V(0^-)$.

(4 markah)

b. fungsi Laplace bagi voltan, $V(s)$ untuk $t > 0$.

(10 markah)

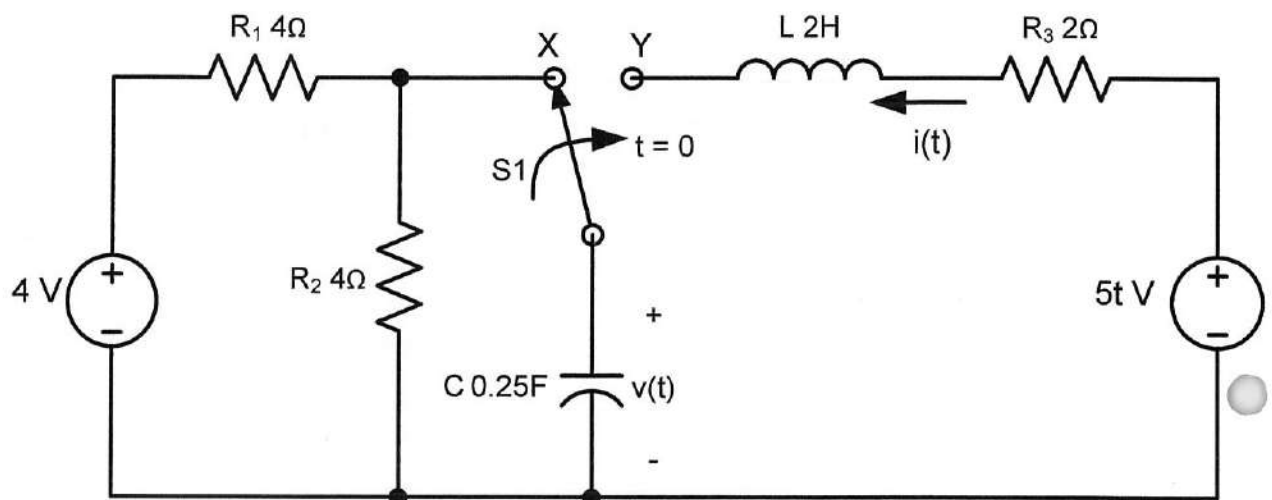


Figure Q4/ Rajah Q4

QUESTION 5/ SOALAN 5

Referring to **Figure Q5**, determine the transfer function, $H(s)$ that relates the output voltage, $V_o(s)$ to input current $I_i(s)$ and draw the magnitude Bode plot. Use minimum frequency, $\omega = 1$ rad/s and maximum frequency, $\omega = 100,000$ rad/s.

(14 marks)

Merujuk kepada **Rajah Q5**, tentukan rangkap pindah, $H(s)$ yang menghubungkan voltan keluaran, $V_o(s)$ kepada arus masukan, $I_i(s)$ dan lukis magnitud rajah Bode. Guna frekuensi minima, $\omega = 1$ rad/s dan frekuensi maksima, $\omega = 100,000$ rad/s.

(14 markah)

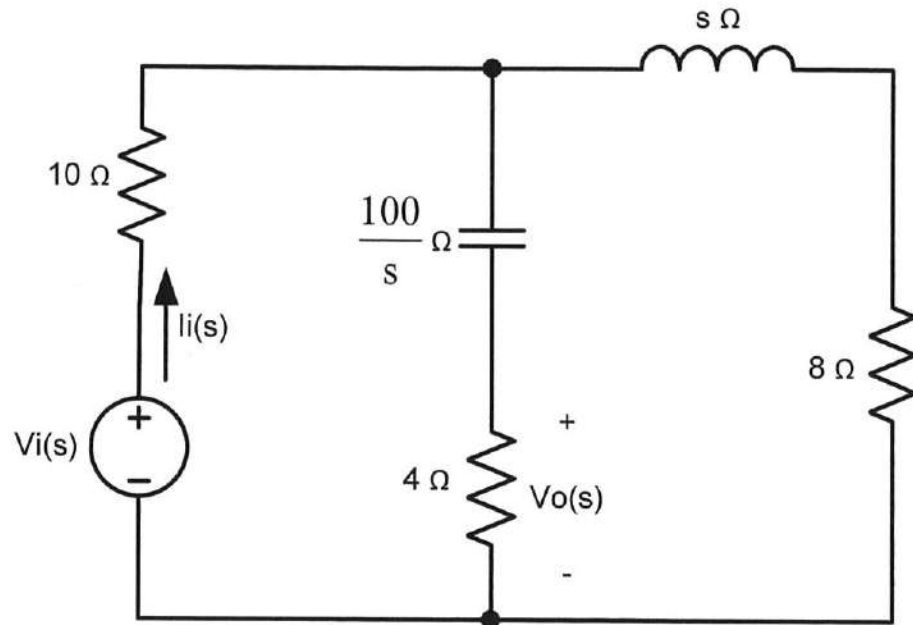


Figure Q5/ Rajah Q5

QUESTION 6/ SOALAN 6

A two-port network is terminated as shown in **Figure Q6**. The two-port network consists of two identical two-port networks interconnected in series where each network has Z-parameters. Determine voltage value, V_1 and current value, I_2 .

(16 marks)

Satu rangkaian dua-liang ditamatkan seperti ditunjukkan dalam **Rajah Q6**. Rangkaian dua-liang ini terdiri daripada dua rangkaian dua-liang yang serupa disaling hubung secara sesiri di mana setiap satu rangkaian mempunyai parameter-Z. Tentukan nilai voltan, V_1 dan nilai arus, I_2 .

(16 markah)

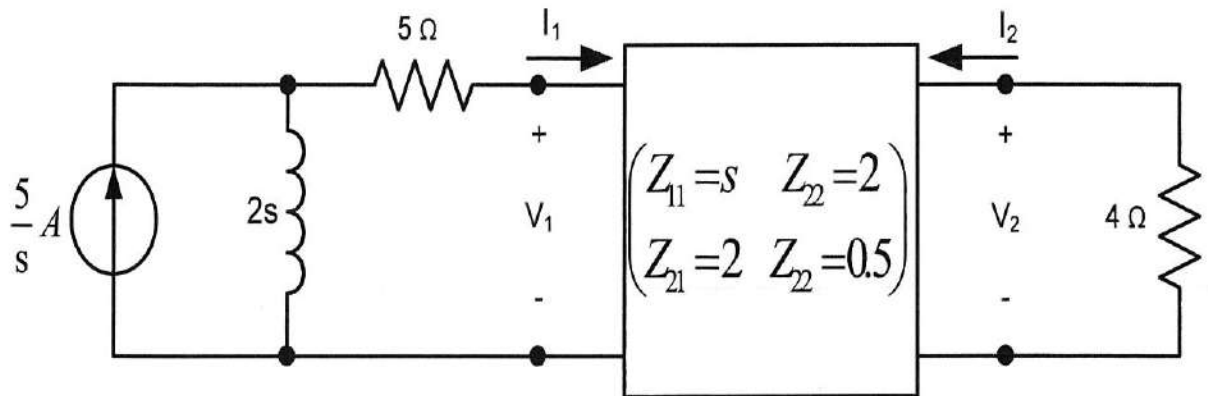


Figure Q6/ Rajah Q6

[100 MARKS/ MARKAH]

END OF QUESTION PAPER/ KERTAS SOALAN TAMAT

Forcing Functions and Their Assumed Solutions
(Fungsi Berdaya dan Penyelesaian Anggapan)

Forcing function (Fungsi Berdaya)		Assumed Solution (Penyelesaian Anggapan)
Constan (Malar)		$x_f(t) = K_2$
Exponential (Eksponen)		$x_f(t) = K_2 e^{-st}$
Variable (Pembolehubah)	Ramp (Tanjak)	$x_f(t) = K_2 t + K_3$
	Parabolic (Parabola)	$x_f(t) = K_2 t^2 + K_3 t + K_4$
Sinusoidal (Sinus)		$x_f(t) = K_2 \sin \omega t + K_3 \cos \omega t$
Exponential Sinusoidal (Sinus Eksponen)		$x_f(t) = e^{-st} (K_2 \sin \omega t + K_3 \cos \omega t)$

Table of Laplace Transform Pairs
(*Jadual Penukaran Pasangan Jelmaan Laplace*)

Functions (<i>Rangkap</i>)	$f(t)$	$F(s)$
Unit Impulse (<i>Dedenyut</i>)	$\delta(t)$	1
Unit Step (<i>Unit langkah</i>) Constant (<i>Malar</i>)	$u(t)$ 1	$\frac{1}{s}$
Unit Ramp (<i>Unit Tanjak</i>) t function (<i>Rangkap t</i>)	$t u(t)$	$\frac{1}{s^2}$
Unit Parabolic (<i>Unit Parabola</i>)	$\frac{1}{2} t^2 u(t)$	$\frac{1}{s^3}$
n^{th} integral of impulse (<i>Kamiran ke-n dedenyut</i>)	$\delta^{-n}(t)$	$\frac{1}{s^n}$
n^{th} derivative of impulse (<i>Kerbezaan ke-n dedenyut</i>)	$\delta^n(t)$	s^n
Power of t (<i>Kuasa t</i>)	$\frac{t^{n-1}}{(n-1)!}$	$\frac{1}{s^n}$
Exponential (<i>Eksponen</i>)	e^{-at}	$\frac{1}{s+a}$
t -multiplication exponential (<i>Pendaraban t bagi eksponen</i>)	te^{-at}	$\frac{1}{(s+a)^2}$
Repeated t -multiplication exponential (<i>Pendaraban t berulang bagi eksponen</i>)	$\frac{1}{(n-1)!} t^{n-1} e^{-at}$	$\frac{1}{(s+a)^n}$
Sine (<i>Sinus</i>)	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
Cosine (<i>Kosinus</i>)	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
Damped sine (<i>Sinus teredam</i>)	$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
Damped cosine (<i>Kosinus teredam</i>)	$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$
t -multiplied sine (<i>Pendaraban t bagi sinus</i>)	$t \sin \omega t$	$\frac{2\omega s}{(s^2 + \omega^2)^2}$
t -multiplied cosine (<i>Pendaraban t bagi kosinus</i>)	$t \cos \omega t$	$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$

Two-Port Network Parameters
(Parameter Rangkaian Dua Liang)

Impedance parameters

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

Admittance parameters

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

Hybrid parameters

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

Transmission parameters

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

Jadual Penukaran Untuk Rangkaian Dua Liang
(Conversion Table for Two-Port Network Parameters)

	Z	Y	h	ABCD
Z	z_{11} z_{12} z_{21} z_{22}	$\frac{y_{22}}{\Delta_y}$ $-\frac{y_{12}}{\Delta_y}$ $-\frac{y_{21}}{\Delta_y}$ $\frac{y_{11}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$ $\frac{h_{12}}{h_{22}}$ $-\frac{h_{21}}{h_{22}}$ $\frac{1}{h_{22}}$	$\frac{A}{C}$ $\frac{\Delta_T}{C}$ $\frac{1}{C}$ $\frac{D}{C}$
Y	$\frac{z_{22}}{\Delta_z}$ $-\frac{z_{12}}{\Delta_z}$ $-\frac{z_{21}}{\Delta_z}$ $\frac{z_{11}}{\Delta_z}$	y_{11} y_{12} y_{21} y_{22}	$\frac{1}{h_{11}}$ $-\frac{h_{12}}{h_{11}}$ $\frac{h_{21}}{h_{11}}$ $\frac{\Delta_h}{h_{11}}$	$\frac{D}{B}$ $-\frac{\Delta_T}{B}$ $-\frac{1}{B}$ $\frac{A}{B}$
h	$\frac{\Delta_z}{z_{22}}$ $\frac{z_{12}}{z_{22}}$ $-\frac{z_{21}}{z_{22}}$ $\frac{1}{z_{22}}$	$\frac{1}{y_{11}}$ $-\frac{y_{12}}{y_{11}}$ $\frac{y_{21}}{y_{11}}$ $\frac{\Delta_y}{y_{11}}$	h_{11} h_{12} h_{21} h_{22}	$\frac{B}{D}$ $\frac{\Delta_T}{D}$ $-\frac{1}{D}$ $\frac{C}{D}$
ABCD	$\frac{z_{11}}{z_{21}}$ $\frac{\Delta_z}{z_{21}}$ $\frac{1}{z_{21}}$ $\frac{z_{22}}{z_{21}}$	$-\frac{y_{22}}{y_{21}}$ $-\frac{1}{y_{21}}$ $-\frac{\Delta_y}{y_{21}}$ $-\frac{y_{11}}{y_{21}}$	$-\frac{\Delta_h}{h_{21}}$ $-\frac{h_{11}}{h_{21}}$ $-\frac{h_{22}}{h_{21}}$ $-\frac{1}{h_{21}}$	A B C D

