



**KOLEJ YAYASAN PELAJARAN JOHOR
ONLINE FINAL EXAMINATION**

COURSE NAME : CIRCUIT ANALYZE
COURSE CODE : DKE 2093
SESSION : NOVEMBER 2020
DURATION : 6 HOURS

**INSTRUCTION TO CANDIDATES/
ARAHAH KEPADA CALON**

1. This examination paper consists of **SIX (6)** questions. /
Kertas soalan ini mengandungi ENAM (6) soalan.
2. Students are allowed to refer to resources such as lecture notes, books, internet or any other relevant resources. /
Pelajar dibenarkan merujuk kepada sumber seperti nota kuliah, buku, internet atau mana-mana sumber yang berkaitan.
3. Answer **ALL** questions in the answer sheet which is **A4** size paper (or other paper with the consent of the relevant lecturer). /
Jawab SEMUA soalan di dalam kertas jawapan iaitu kertas bersaiz A4 (atau lain-lain kertas dengan persetujuan pensyarah berkaitan).
4. Write your details as follows in the upper left corner for each answer sheet: /
Tulis butiran anda sepetimana berikut di penjuru atas kiri bagi setiap kertas jawapan:
 - i. Student Full Name / Nama Penuh Pelajar
 - ii. Identification Card (I/C) No. / No. Kad Pengenalan
 - iii. Class Section / Seksyen Kelas
 - iv. Course Code / Kod Kursus
 - v. Course Name / Nama Kursus
 - vi. Lecturer Name / Nama Pensyarah
5. Each answer sheet must have a page number written at the bottom right corner. /
Setiap helai kertas jawapan mesti ditulis nombor muka surat di penjuru bawah kanan.
6. Answers should be handwritten, neat and clear. /
Jawapan hendaklah ditulis tangan, kemas dan jelas.

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO /
JANGAN BUKA KERTAS SOALANINI SEHINGGA DIBERITAHU**

This examination paper consists of **10** printed pages including front page
Kertas soalan ini mengandungi 10 halaman bercetak termasuk muka hadapan

This examination paper consists of **SIX (6)** questions. Answer **ALL** the questions in an Answering Booklet.

*Kertas soalan ini mengandungi **ENAM (6)** soalan. Jawab **SEMUA** soalan dalam Buku Jawapan.*

QUESTION 1/ SOALAN 1

Referring to **Figure Q1**. Find:

- The equivalent capacitance, C_{eq} .
- The total charge, Q_T .
- The voltage across capacitors C_1 and C_4 .
- The energy stored in capacitor C_4 .

*Merujuk kepada **Rajah Q1**. Dapatkan:*

- Kemuatan setara, C_{eq} .*
- Jumlah cas, Q_T .*
- Voltan merintangi pemuat C_1 dan C_4 .*
- Tenaga yang disimpan dalam pemuat C_4*

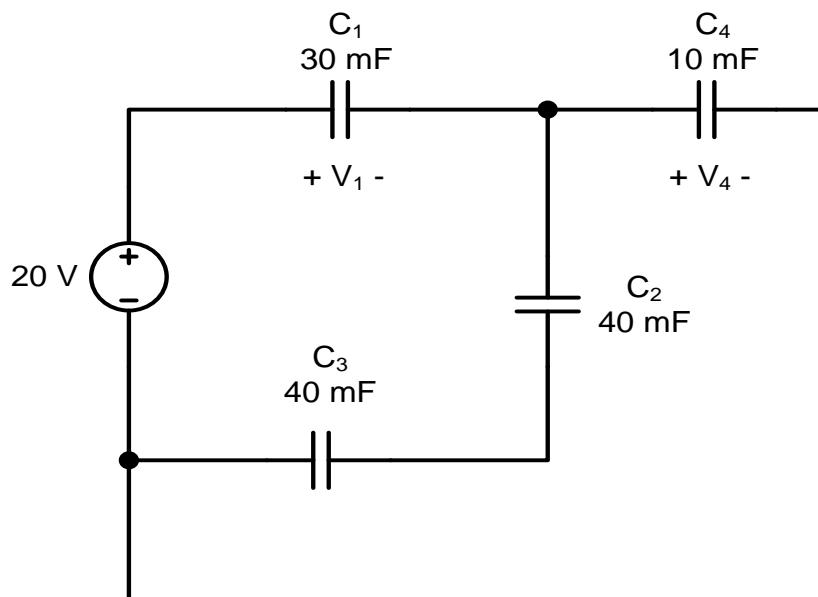


Figure Q1/ Rajah Q1

(15 marks / markah)

QUESTION 2/ SOALAN 2

Referring to **Figure Q2**, the switch S1 has been closed for a long time until the circuit reaches steady-state. At $t = 0$, switch S1 is open. Find the current, $i(t)$ using transient analysis method.

*Merujuk kepada **Rajah Q2**, suis S1 telah ditutup buat sekian lama sehingga litar mencapai keadaan mantap. Pada $t = 0$, suis S1 dibuka. Dapatkan arus, $i(t)$ menggunakan kaedah analisis ubahtika.*

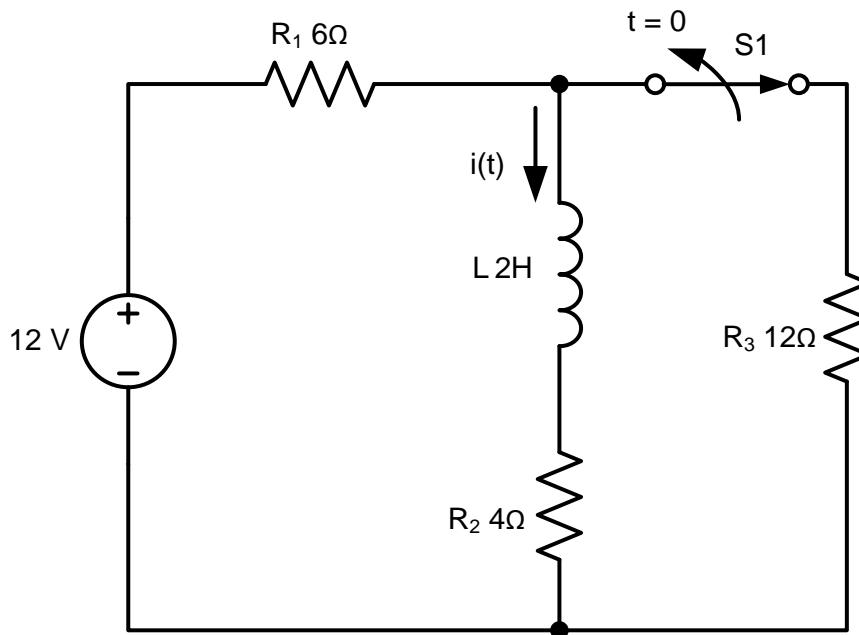


Figure Q2/ Rajah Q2

(20 marks / markah)

QUESTION 3/ SOALAN 3

The differential equation of the current flowing through an inductor, $i(t)$ in a second order circuit is given as:

$$\frac{d^2i(t)}{dt^2} + 5\frac{di(t)}{dt} + 10i(t) = 12A$$

Given that the initial current flowing through an inductor, $i(0^-) = 1A$ and

$\frac{di(0^+)}{dt} = -4 \frac{A}{s}$. Find the current $i(t)$ using transient analysis method.

Persamaan kebezaan bagi arus mengalir melalui induktor, $i(t)$ dalam satu litar tertib kedua diberi sebagai:

$$\frac{d^2i(t)}{dt^2} + 5\frac{di(t)}{dt} + 10i(t) = 12A$$

Diberi arus awal melalui pearuh, $i(0^-) = 1A$ dan $\frac{di(0^+)}{dt} = -4 \frac{A}{s}$. Dapatkan arus


$i(t)$ menggunakan kaedah analisis ubahtika.

(20 marks / markah)

QUESTION 4/ SOALAN 4

The circuit in **Figure Q4** is in steady state at $t < 0$. Find the Laplace function of the voltage across capacitor, $V(s)$ for $t \geq 0$.

*Litar dalam **Rajah Q4** berada dalam keadaan mantap pada $t < 0$. Dapatkan fungsi Laplace bagi voltan merintangi pemuat, $V(s)$ untuk $t \geq 0$.*

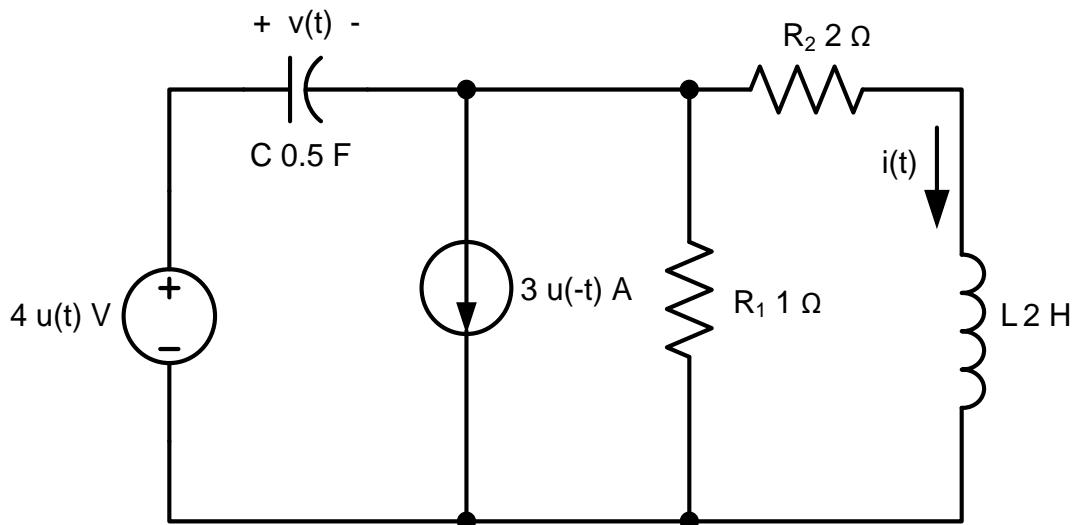
**Figure Q4/ Rajah Q4**

(15 marks / markah)

QUESTION 5/ SOALAN 5

Referring to **Figure Q5**, find the transfer function, $H(s)$ that relates the output voltage, $V_o(s)$ to input voltage, $V_i(s)$ and draw the magnitude Bode plot. Use minimum frequency, $\omega = 1 \text{ rad/s}$ and maximum frequency, $\omega = 100,000 \text{ rad/s}$.

Merujuk kepada **Rajah Q5**, dapatkan rangkap pindah, $H(s)$ yang menghubungkan voltan keluaran, $V_o(s)$ kepada voltan masukan, $V_i(s)$ dan lukis magnitud rajah Bode. Guna frekuensi minima, $\omega = 1 \text{ rad/s}$ dan frekuensi maksima, $\omega = 100,000 \text{ rad/s}$.

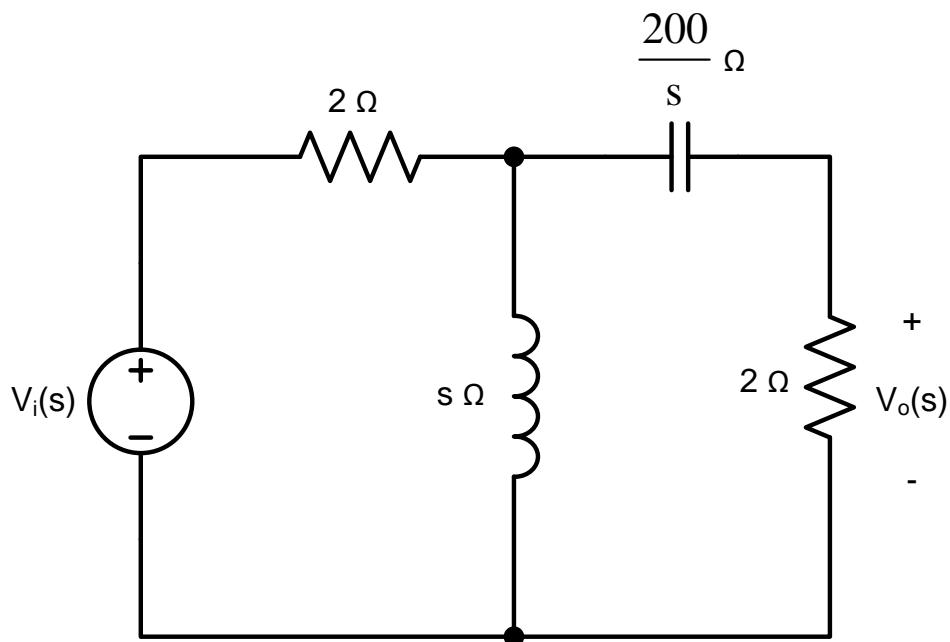**Figure Q5/ Rajah Q5**

(15 marks / markah)

QUESTION 6/ SOALAN 6

Referring to **Figure Q6**, find the y-parameters for the two-port network given.

Merujuk kepada **Rajah Q6**, dapatkan parameter-y untuk rangkaian dua-liang yang diberi.

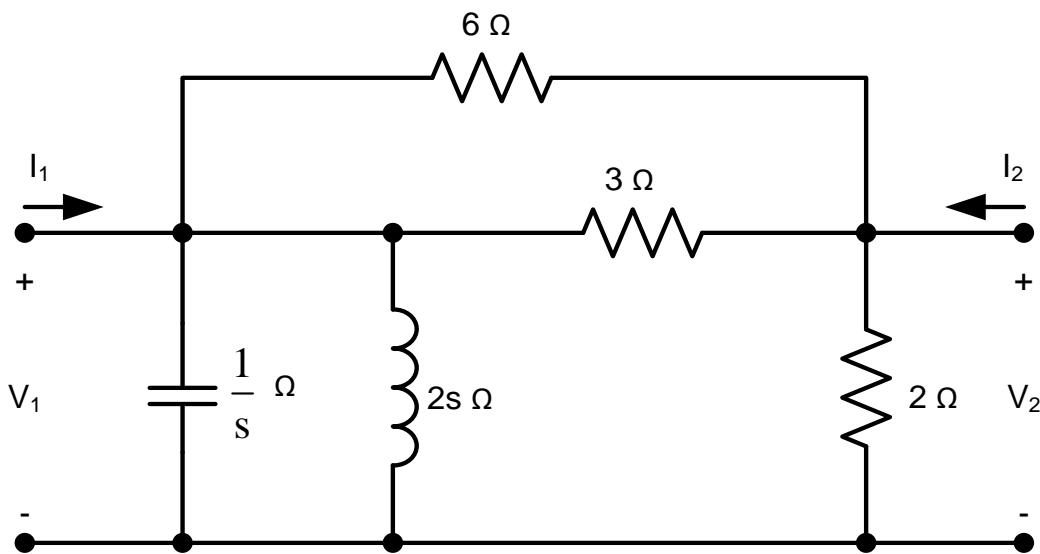


Figure Q6/ Rajah Q6

(15 marks / markah)

[100 MARKS/ 100 MARKAH]

END OF QUESTION PAPER/ KERTAS SOALAN TAMAT

**Forcing Functions and Their Assumed Solutions
(Fungsi Berdaya dan Penyelesaian Anggapan)**

<i>Forcing function (Fungsi Berdaya)</i>		<i>Assumed Solution (Penyelesaian Anggapan)</i>
Constan (<i>Malar</i>)	$f(t) = A$	$x_f(t) = K_2$
Exponential (<i>Eksponen</i>)	$f(t) = M e^{-st}$	$x_f(t) = K_2 e^{-st}$
Variable (Pembolehubah)	Ramp (<i>Tanjak</i>)	$f(t) = mt$
	Parabolic (<i>Parabola</i>)	$f(t) = t^2$
Sinusoidal (<i>Sinus</i>)	$f(t) = M \sin(\omega t + \theta)$	$x_f(t) = K_2 \sin \omega t + K_3 \cos \omega t$
	$f(t) = M \cos(\omega t + \theta)$	
Exponential Sinusoidal (<i>Sinus Eksponen</i>)	$f(t) = M e^{-st} \sin(\omega t + \theta)$	$x_f(t) = e^{-st} (K_2 \sin \omega t + K_3 \cos \omega t)$

Table of Laplace Transform Pairs
(Jadual Penukaran Pasangan Penjelmaan Laplace)

Functions (Rangkap)	$f(t)$	$F(s)$
Unit Impulse (Dedenyut)	$\delta(t)$	1
Unit Step (Unit langkah) Constant (Malar)	$u(t)$ 1	$\frac{1}{s}$
Unit Ramp (Unit Tanjak) t function (Rangkap t)	$t u(t)$	$\frac{1}{s^2}$
Unit Parabolic (Unit Parabola)	$\frac{1}{2} t^2 u(t)$	$\frac{1}{s^3}$
n^{th} integral of impulse (Kamiran ke-n dedenyut)	$\delta^{-n}(t)$	$\frac{1}{s^n}$
n^{th} derivative of impulse (Kerbezaan ke-n dedenyut)	$\delta^n(t)$	s^n
Power of t (Kuasa t)	$\frac{t^{n-1}}{(n-1)!}$	$\frac{1}{s^n}$
Exponential (Eksponen)	e^{-at}	$\frac{1}{s+a}$
t-multiplication exponential (Pendaraban t bagi eksponen)	te^{-at}	$\frac{1}{(s+a)^2}$
Repeated t-multiplication exponential (Pendaraban t berulang bagi eksponen)	$\frac{1}{(n-1)!} t^{n-1} e^{-at}$	$\frac{1}{(s+a)^n}$
Sine (Sinus)	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
Cosine (Kosinus)	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
Damped sine (Sinus teredam)	$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
Damped cosine (Kosinus teredam)	$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$
t-multiplicated sine (Pendaraban t bagi sinus)	$t \sin \omega t$	$\frac{2\omega s}{(s^2 + \omega^2)^2}$
t-multiplicated cosine (Pendaraban t bagi kosinus)	$t \cos \omega t$	$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$

Two–Port Network Parameters
(Parameter Rangkaian Dua Liang)

Impedance parameters

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

Admittance parameters

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

Hybrid parameters

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

Transmission parameters

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

Jadual Penukaran Untuk Rangkaian Dua Liang
(Conversion Table for Two–Port Network Parameters)

	z		y		h		ABCD	
z	z_{11}	z_{12}	$\frac{y_{22}}{\Delta_y}$	$\frac{-y_{12}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$	$\frac{A}{C}$	$\frac{\Delta_T}{C}$
	z_{21}	z_{22}	$\frac{-y_{21}}{\Delta_y}$	$\frac{y_{11}}{\Delta_y}$	$\frac{-h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$	$\frac{1}{C}$	$\frac{D}{C}$
y	$\frac{z_{22}}{\Delta_z}$	$\frac{-z_{12}}{\Delta_z}$	y_{11}	y_{12}	$\frac{1}{h_{11}}$	$\frac{-h_{12}}{h_{11}}$	$\frac{D}{B}$	$\frac{-\Delta_T}{B}$
	$\frac{-z_{21}}{\Delta_z}$	$\frac{z_{11}}{\Delta_z}$	y_{21}	y_{22}	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$	$\frac{-1}{B}$	$\frac{A}{B}$
h	$\frac{\Delta_z}{z_{22}}$	$\frac{z_{12}}{z_{22}}$	$\frac{1}{y_{11}}$	$\frac{-y_{12}}{y_{11}}$	h_{11}	h_{12}	$\frac{B}{D}$	$\frac{\Delta_T}{D}$
	$\frac{-z_{21}}{z_{22}}$	$\frac{1}{z_{22}}$	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta_y}{y_{11}}$	h_{21}	h_{22}	$\frac{-1}{D}$	$\frac{C}{D}$
ABCD	$\frac{z_{11}}{z_{21}}$	$\frac{\Delta_z}{z_{21}}$	$\frac{-y_{22}}{y_{21}}$	$\frac{-1}{y_{21}}$	$\frac{-\Delta_h}{h_{21}}$	$\frac{-h_{11}}{h_{21}}$	A	B
	$\frac{1}{z_{21}}$	$\frac{z_{22}}{z_{21}}$	$\frac{-\Delta_y}{y_{21}}$	$\frac{-y_{11}}{y_{21}}$	$\frac{-h_{22}}{h_{21}}$	$\frac{-1}{h_{21}}$	C	D